

# Achieve Low Loss Rectification Using TI's Diode Bridge Controllers



Shiven Dhir

End equipments such as home security sensors, video doorbells, landscape lighting, thermostats, Power over Ethernet (PoE) powered security cameras use low-voltage AC sources (typically 24Vac) as input but downstream loads require a DC source. For these kinds of applications, full wave rectifiers are used to convert AC to DC. Conventionally, this is achieved by Schottky diodes which have poor performance in terms of power dissipation and thermals. This article highlights how LM74680/1 Ideal Diode Bridge Controller enables lower power dissipation for better thermal management in a space constraint end equipments.

## Low Voltage AC Rectification


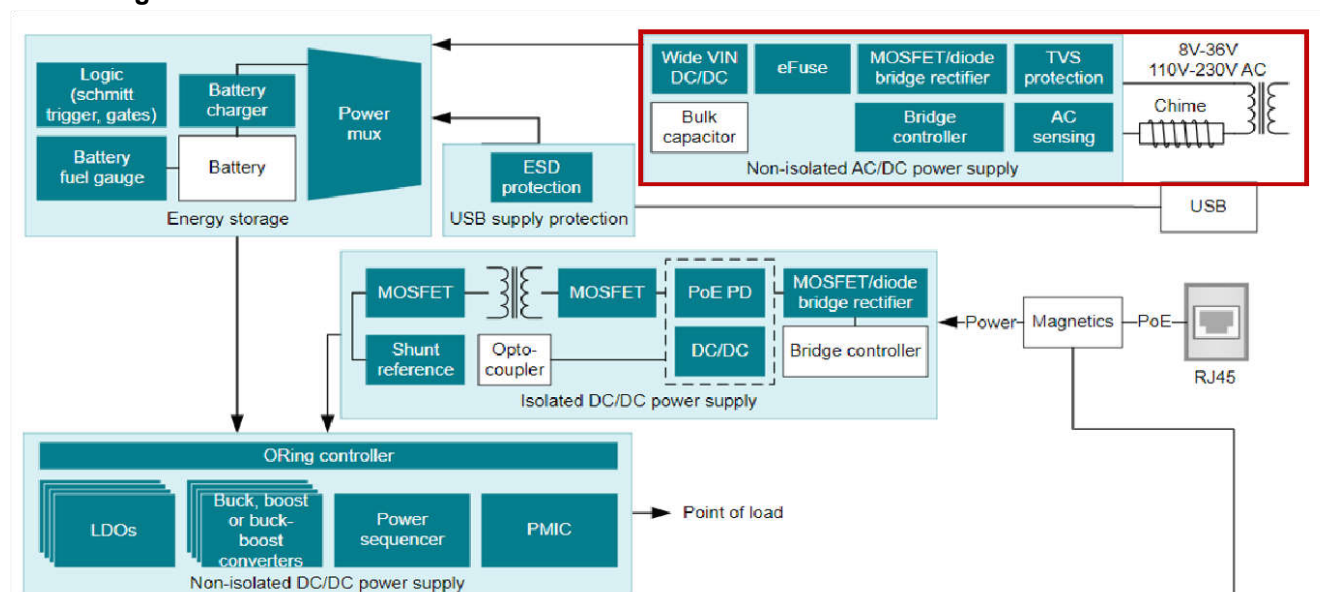


Figure 1. Typical Block Diagram of a Video Doorbell

Many modern-day doorbells even including low-voltage AC powered doorbells, contain circuits that require a DC power supply such as microcontrollers, sensors, or communication modules. Conventionally, a diode bridge is used to convert low-voltage AC to a steady DC voltage for powering these components. These components are particularly sensitive to noise sources such as fluctuations in the power supply, electromagnetic interference, and temperature variations. The most important feature is wide input range to support operating voltage due to different transformer rating ranging from 8V to 36V AC. Video doorbell front end designs must include power-management products that support high efficiency across a wide input range and operating load current.

To design a video doorbell that can be mounted on any door frame and perform best in any temperature, the designer must consider the thermals of the power-management components. Traditionally, diode bridge rectifiers are used at the input to power the downstream loads in the design which offer poor performance due to high drop across each diode in each AC cycle.

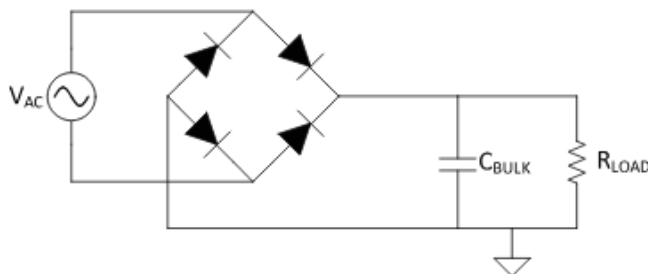

**Figure 2. Conventional Diode Bridge Rectifier**


Considering 0.5V Schottky in a conventional diode bridge, the drop in each cycle is around 1V ( $0.5V \times 2$ ). This dissipates around 1.5W power each cycle for 1.5A load.

### Power over Ethernet (PoE)

Power over Ethernet allows electrical power and data to be transmitted simultaneously over a single Ethernet cable. This eliminates extra wiring for electrical power and simplifies the installation process. PoE mainly consists of three components.

- Power Source Equipment (PSE)
- Powered Device (PD)
- Ethernet Cable

With addition of IEEE 802.3bt in 2018, the power capability of POE has increased which enables a wider range of applications, such as powering devices like high-performance IP cameras, wireless access points, and LED lighting systems. The new standard introduced type 3 (up to 60W) and type 4 (up to 100W) power delivery by using of all four pairs of wires.

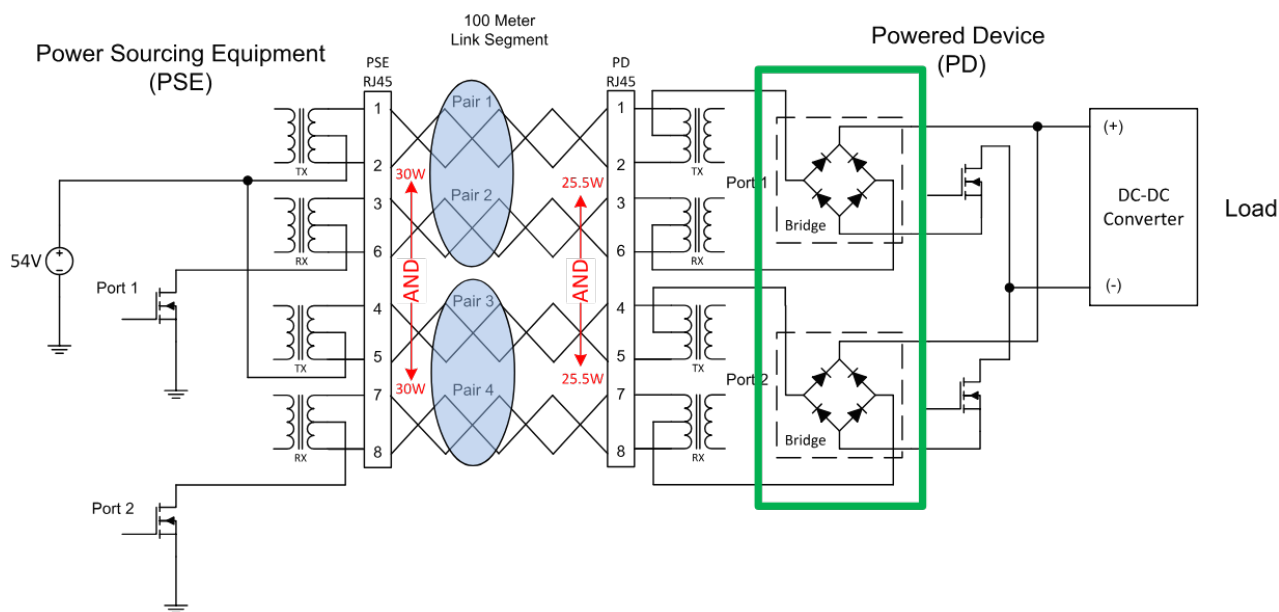


**Figure 3. Power Over Ethernet Input Architecture**

Conventionally, the design uses two diode bridges which results in total voltage drop of  $0.5V \times 4 = 2V$  (considering a 500mV Schottky). To deliver 90W power to downstream load with 48V rail, the required current is about 1.9A if equal current sharing is considered. This dissipates a total of 1.9W power.


## Design with LM7468X Ideal Diode Bridge Controllers

The LM74680 is a diode bridge controller that provides voltage rectification by driving four N-channel MOSFETs in a full-bridge configuration. LM74680 enables lower voltage drop and reduced power dissipation as compared to conventional diode bridge rectifiers. This helps to simplify the power supply design, eliminate heat sinks, and reduce the PCB area. The integrated charge pump allows use of N-channel MOSFETs, which are smaller and more cost-effective than P-channel MOSFETs for the same power level. The charge pump also offers fast response to reverse current conditions for protection against input short events. The LM74680 has an enable pin which allows for the gate driver to be either enabled or disabled by an external signal. The LM74680 supports voltage rectification from DC to 1kHz.

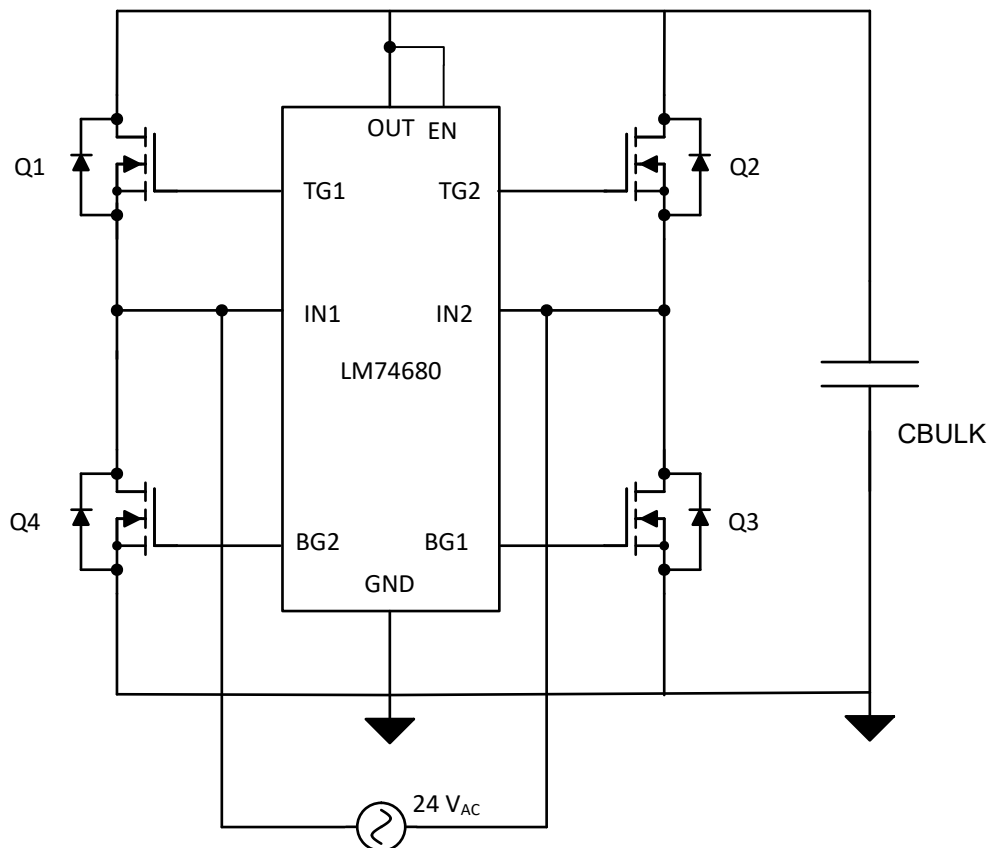

**Figure 4. LM74680 Ideal Diode Bridge Controller**

When compared to the performance of LM74680, the drop in each cycle is only  $2(I_{\text{LOAD}} \times R_{\text{DS, ON}})$  when operating in full conduction mode. For a 1.5A load, when using CSD88537ND FETs from our EVM, LM74680 only dissipates  $2 \times (1.5\text{A}^2 \times 12\text{m}\Omega) = 54\text{mW}$  power in every cycle. A conventional bridge dissipates 27x more power than the smart controller.

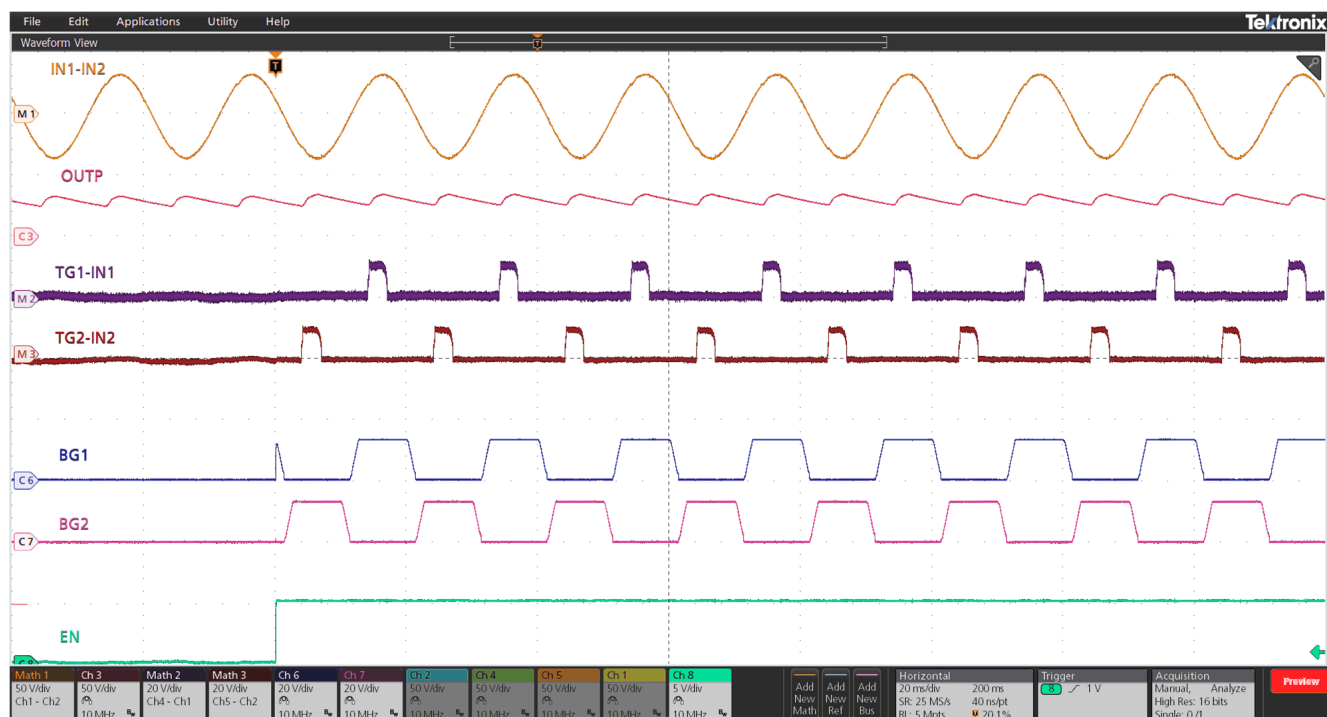


**Figure 5. LM74680 Active Rectification of 24VAC 50Hz Source**

#### Note

Component selection to achieve AC rectification as shown in [Figure 5](#) can be found in the LM74680 data sheet referenced below.


The size, power consumption and thermal management play significant role in designing smaller end equipment such as video doorbell. The LM74680 diode bridge controller is a good fit to address those challenges and design systems which can reliably work across the desired temperature range.

[Figure 6](#) shows the theoretical power dissipation comparison between B360A schottky diode and CSD88537ND MOSFET when paired with LM7468x.

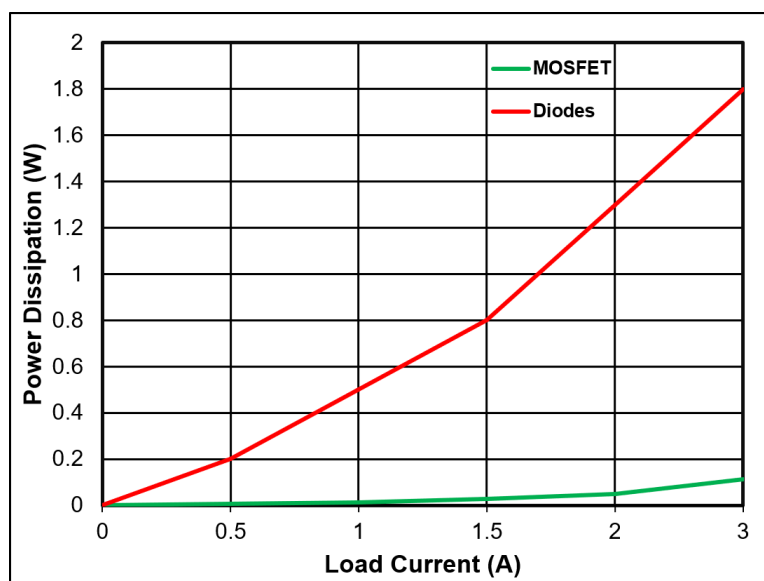


**Figure 6. Power Loss Comparison Between Schottky Diode and LM7468x Design**

Figure 7 and Figure 8 show the difference in temperature rise when each of the design scheme is subjected to 3A DC load at room temperature.

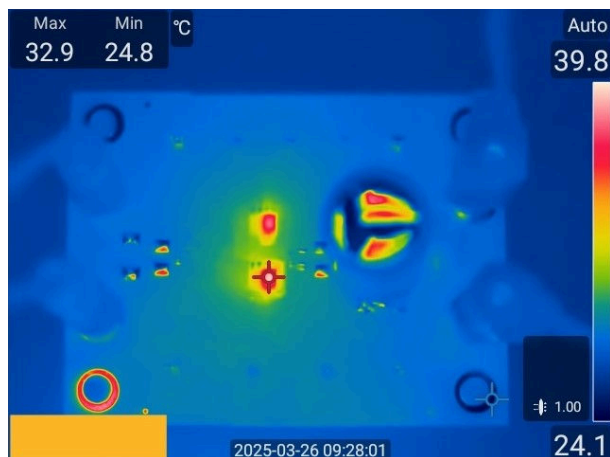

**Figure 7. CSD88537ND FETs Thermal Performance with 3A DC Load**

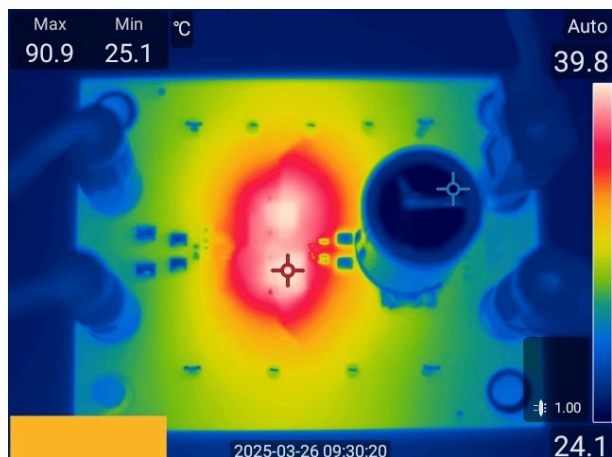

**Figure 8. B360A Diodes Thermal Performance with 3A DC Load**

## Conclusion

Passive diodes are an easy way to design a circuit but are very inefficient to use because of bigger size, high voltage drop, and poor thermals. With miniaturization of new age designs, replacing the passive diodes is critical to increase the performance. Active bridge rectifier controllers like LM74680 and LM74681 offer best in class performance from thermals and efficiency aspect. With help of the controllers, reliability and lifespan of designs can be increased.

## References

- [PoE Lighting Is Coming](#)
- [Enabling the next generation of video doorbells](#)
- [LM74681 100V Ideal Diode Bridge Controller for PoE Powered Applications](#)
- [LM74680 Ideal Diode Bridge Controller for Low Loss Rectification](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2025, Texas Instruments Incorporated