

EFFICIENCY AND POWER LOSSES CALCULATION of SYNCHRONOUS BUCK CONVERTER


Supplemental MathCad file to the paper

"What MOSFET Driver Can Do to Boost the Performance of VRM Design"

presented at Power Electronics Technology Exhibition & Conference, October 25, 2006, Long Beach, California

The author, and/or Texas Instruments Inc are not responsible for any issue as the result of use of this software!

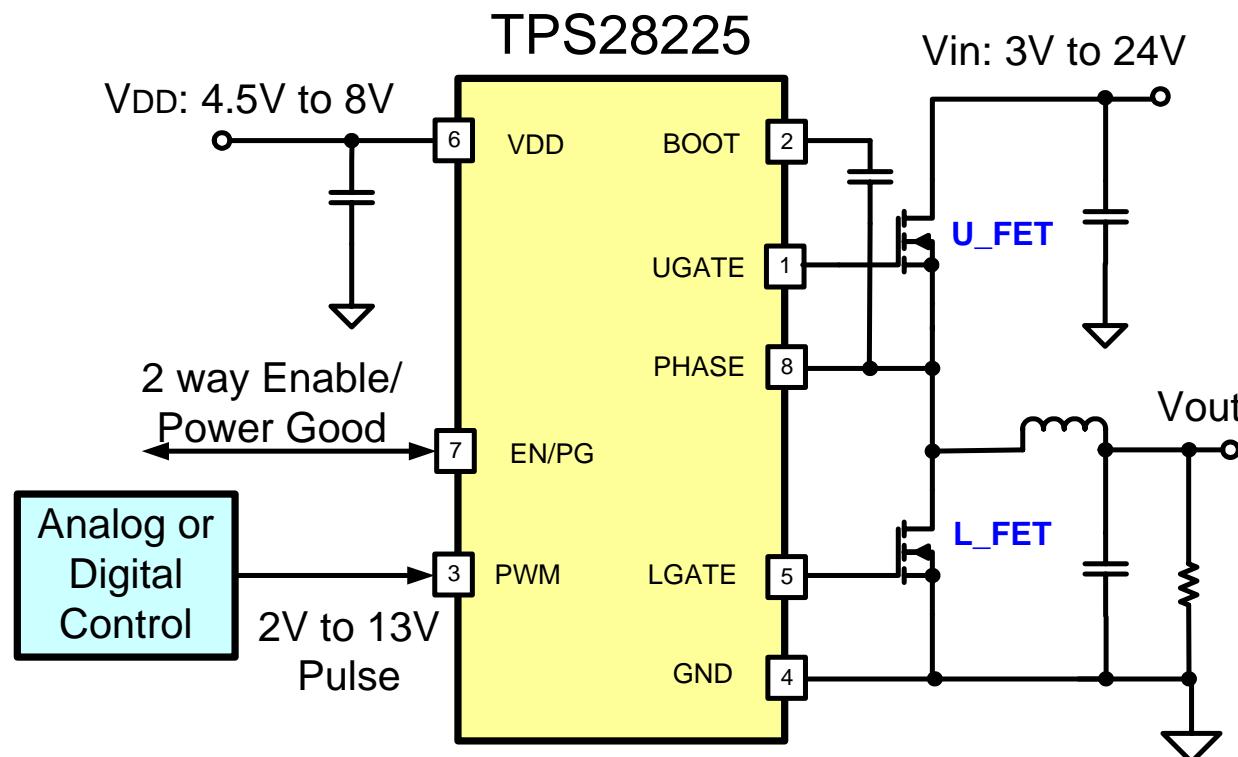One Phase of Synchronous Buck Converter used as an Example in this File



Control FET (U_FET): HAT2168N: Parameters taken from Data Sheet

$$gU := \frac{0.5 \cdot V}{35 \cdot A} \quad gU = 0.014 \frac{V}{A} \quad \frac{1}{gU} = 70 S$$

- Forward Transconductance

$$V_{thU} := 2.0 \cdot V \quad \text{- Threshold Voltage}$$

$$Qgs1t := 2.5 \cdot ncoul \quad \text{- Charge from 0 to } V_{th}$$

$$Qgs2t := 2.5 \cdot ncoul \quad \text{- Charge from } V_{th} \text{ to } V_{Miller}$$

$$Qgst := Qgs1t + Qgs2t$$

$$Qgst = 5 \text{ ncoul}$$

$$Qgdः := 2.4 \cdot ncoul$$

$$Vgs := 2.3 \cdot V, 2.4 \cdot V .. 12 \cdot V$$

$$Qtt(Vgs) := Qgst + Qgdः + \frac{27 \cdot ncoul}{10 \cdot V} \cdot (Vgs - 0.4 \cdot V - 3 \cdot V) \quad \text{- Charge at } Vgs$$

$$Qtt(4.5 \cdot V) = 10.37 \text{ ncoul}$$


$$Qtt(5 \cdot V) = 11.72 \text{ ncoul}$$

$$Qtt(7 \cdot V) = 17.12 \text{ ncoul}$$

$$Qtt(10 \cdot V) = 25.22 \text{ ncoul}$$

$$Qtt(12 \cdot V) = 30.62 \text{ ncoul}$$
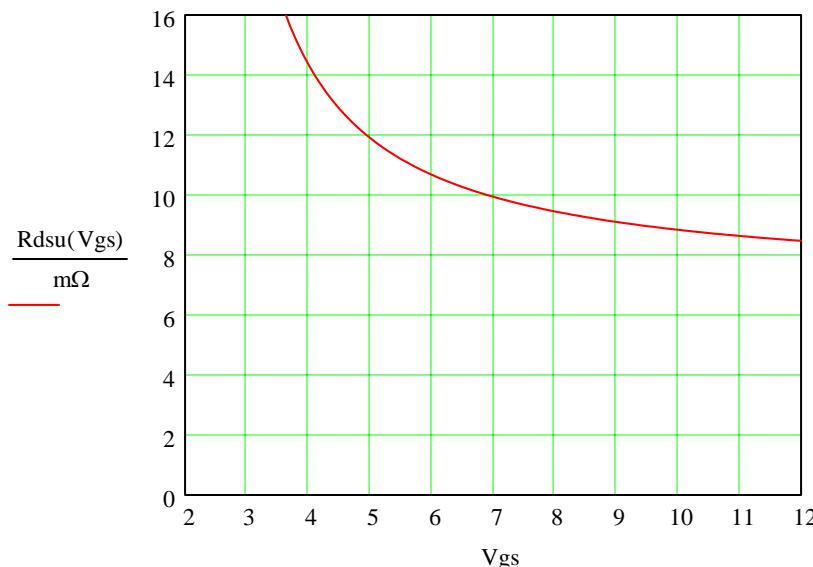
$$Rdsu(Vgs) := \left[5 \cdot m\Omega + \frac{10.5 \cdot V \cdot m\Omega}{(Vgs - V_{thU})} \right] \cdot 1.4 \quad \text{- Rdson at 125 C}$$



Synchronous FET (L_FET): HAT2166N: Parameters taken from Data Sheet

$$gL := \frac{0.5 \cdot V}{35 \cdot A} \quad gL = 0.014 \frac{V}{A}$$

$$\frac{1}{gL} = 70 S$$

- Forward Transconductance

$$V_{thL} := 2.2 \cdot V$$

$$Q_{gs1b} := 6 \cdot nCoul$$

$$Q_{gs2b} := 6 \cdot nCoul$$

$$Q_{gsb} := Q_{gs1b} + Q_{gs2b}$$

$$Q_{gsb} = 12 \text{ nCoul}$$

$$Q_{gdb} := 5.9 \cdot nCoul$$

$$Q_{tb}(V_{gs}) := Q_{gsb} + Q_{gdb} + \frac{30 \cdot nCoul}{4 \cdot V} \cdot (V_{gs} - 3.2 \cdot V)$$

- Charge at V_{gs}

$$Q_{tb}(4.5 \cdot V) = 27.65 \text{ nCoul}$$

$$Q_{tb}(5 \cdot V) = 31.4 \text{ nCoul}$$


$$Q_{tb}(7 \cdot V) = 46.4 \text{ nCoul}$$

$$Q_{tb}(10 \cdot V) = 68.9 \text{ nCoul}$$

$$Q_{tb}(12 \cdot V) = 83.9 \text{ nCoul}$$

$$R_{dsL}(V_{gs}) := \left[2.55 \cdot m\Omega + \frac{4 \cdot V \cdot m\Omega}{(V_{gs} - V_{thL})} \right] \cdot 1.4$$

- R_{dson} at 125 C

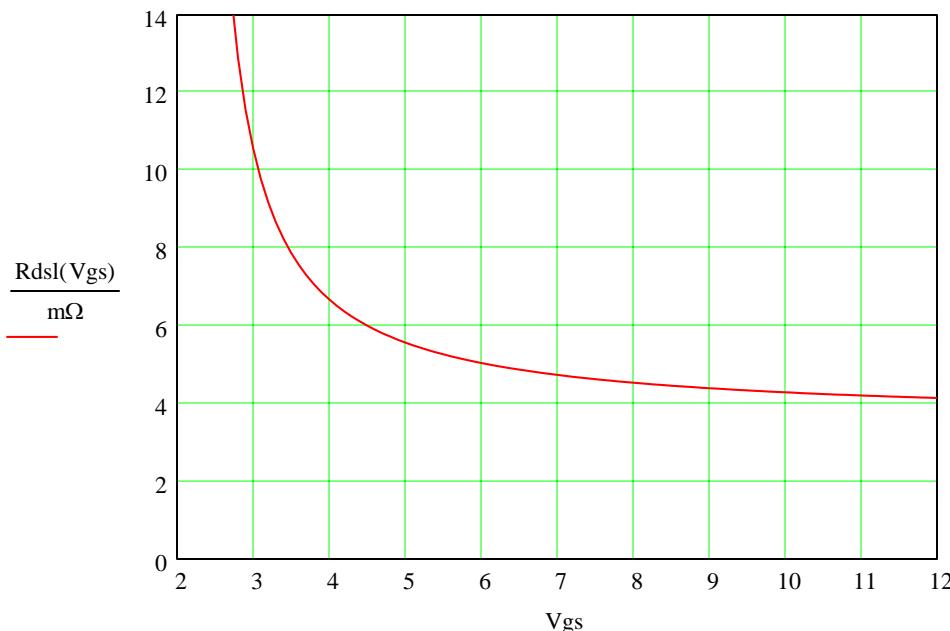

EFFICIENCY AND POWER LOSSES BUDGET

INPUT DATA

$$\begin{array}{llllll}
 V_s := 12 \cdot V & V_o := 1.3 \cdot V & I_{omax} := 32.5 \cdot A & f_s := 400 \cdot kHz & T_s := \frac{1}{f_s} & N_{ph} := 4 \\
 \\
 V_{gs} := 7 \cdot V & L_o := 0.12 \cdot \mu H & R_i := 0.36 \cdot m\Omega & \text{- Output Inductor} & R_{pcb} := 0 \cdot m\Omega & \text{number of phases}
 \end{array}$$

$$N_u := 1 \quad \text{- number of top FETs} \quad N_l := 2 \quad \text{- number of low FETs}$$

$$\begin{array}{lllll}
 R_{dsU}(V_{gs}) := \frac{R_{dsU}(V_{gs})}{N_u} & R_{dsU}(5 \cdot V) = 11.9 \, m\Omega & R_{dsU}(7 \cdot V) = 9.94 \, m\Omega & R_{dsU}(12 \cdot V) = 8.47 \, m\Omega & R_{dsU_25}(V_{gs}) := \frac{R_{dsU}(V_{gs})}{1.4} \\
 \\
 R_{dsL}(V_{gs}) := \frac{R_{dsL}(V_{gs})}{N_l} & R_{dsL}(5 \cdot V) = 2.785 \, m\Omega & R_{dsL}(7 \cdot V) = 2.368 \, m\Omega & R_{dsL}(12 \cdot V) = 2.071 \, m\Omega & R_{dsL_25}(V_{gs}) := \frac{R_{dsL}(V_{gs})}{1.4} \\
 \end{array}$$

- Rdson at 25 C

STATIC POWER LOSSES PER PHASE

$$I_o := 0 \cdot A, 1 \cdot A..I_{omax}$$

$$K_t(I_o) := 1 + 0.4 \cdot \frac{I_o}{I_{omax}} \quad 0.57 \cdot 120 \cdot 13 = 889.2$$

$$D(V_s, I_o, V_{gs}) := \frac{V_o + I_o \cdot \left(R_{dsL}(V_{gs}) \cdot \frac{K_t(I_o)}{1.4} + R_i \cdot K_t(I_o) \right)}{V_s - I_o \cdot (R_{dsU}(V_{gs}) - R_{dsL}(V_{gs})) \cdot \frac{K_t(I_o)}{1.4}}$$

$$D(V_s, I_{omax}, V_{gs}) = 0.119$$

$$\delta I_o(V_s, I_o, V_{gs}) := \frac{[V_s - I_o \cdot (R_{dsU}(V_{gs}) + R_i) - V_o] \cdot D(V_s, I_o, V_{gs})}{L_o \cdot f_s}$$

$$\delta I_o(V_s, 40 \cdot A, V_{gs}) = 26.109 \, A \quad \text{- inductor ripple current}$$

$$I_{Q1rms}(V_s, I_o, V_{gs}) := \left[D(V_s, I_o, V_{gs}) \cdot \left(I_o^2 + \frac{1}{12} \cdot \delta I_o(V_s, I_o, V_{gs})^2 \right) \right]^{0.5} \quad \text{- high-side FET RMS current}$$

$$P_{Q1}(V_s, I_o, V_{gs}) := I_{Q1rms}(V_s, I_o, V_{gs})^2 \cdot R_{dsU}(V_{gs}) \cdot \frac{K_t(I_o)}{1.4} \quad \text{- high-side FET static losses}$$

$$I_{Q2rms}(V_s, I_o, V_{gs}) := \left[(1 - D(V_s, I_o, V_{gs})) \cdot \left(I_o^2 + \frac{1}{12} \cdot \delta I_o(V_s, I_o, V_{gs})^2 \right) \right]^{0.5} \quad \text{- low-side FET RMS current}$$

$$PQ2(V_s, I_o, V_{gs}) := IQ2rms(V_s, I_o, V_{gs})^2 \cdot R_{dsL}(V_{gs}) \cdot \frac{K_t(I_o)}{1.4}$$

- low-side FET static losses

$$IQ1p(V_s, I_o, V_{gs}) := I_o + \frac{\delta I_o(V_s, I_o, V_{gs})}{2}$$

- high-side FET peak current

$$IQ1m(V_s, I_o, V_{gs}) := I_o - \frac{\delta I_o(V_s, I_o, V_{gs})}{2}$$

- high-side FET minimum current

$$I_{rms}(V_s, I_o, V_{gs}) := \left(I_o^2 + \frac{1}{12} \cdot \delta I_o(V_s, I_o, V_{gs})^2 \right)^{0.5}$$

- inductor RMS current

$$I_{rms}(V_s, I_{omax}, V_{gs}) = 33.33 \text{ A}$$

$$ICorms(V_s, I_o, V_{gs}) := \frac{1}{2 \cdot \sqrt{3}} \cdot \delta I_o(V_s, I_o, V_{gs})$$

- output capacitor RMS current (for 1-phase buck)

$$ICorms(V_s, I_{omax}, V_{gs}) = 7.39 \text{ A} \quad ICorms(V_s, 0 \cdot A, V_{gs}) = 6.971 \text{ A}$$

$$ICinrms(V_s, I_o, V_{gs}) := \left[D(V_s, I_o, V_{gs}) \cdot (1 - D(V_s, I_o, V_{gs})) \cdot I_o^2 + \frac{D(V_s, I_o, V_{gs})}{12} \cdot \delta I_o(V_s, I_o, V_{gs})^2 \right]^{0.5}$$

input capacitor RMS current

$$PLo(V_s, I_o, V_{gs}) := I_{rms}(V_s, I_o, V_{gs})^2 \cdot R_i \cdot K_t(I_o)$$

- output inductor power losses

$$Ppcb(V_s, I_o, V_{gs}) := I_{rms}(V_s, I_o, V_{gs})^2 \cdot R_{pcb} \cdot K_t(I_o)$$

- PCB traces power losses

$$I_{in}(V_s, I_o, V_{gs}) := I_o \cdot D(V_s, I_o, V_{gs})$$

- input current

$$PQ(V_s, I_o, V_{gs}) := PQ1(V_s, I_o, V_{gs}) + PQ2(V_s, I_o, V_{gs})$$

- conduction losses in FETs

Total Conduction Power Losses

$$Ploss(V_s, I_o, V_{gs}) := PQ1(V_s, I_o, V_{gs}) + PQ2(V_s, I_o, V_{gs}) + PLo(V_s, I_o, V_{gs}) + Ppcb(V_s, I_o, V_{gs})$$

$$PQ1(V_s, I_{omax}, V_{gs}) = 1.309 \text{ W} \quad PQ1(V_s, 0 \cdot A, V_{gs}) = 0.037 \text{ W}$$

$$PQ2(V_s, I_{omax}, V_{gs}) = 2.319 \text{ W} \quad PQ2(V_s, 0 \cdot A, V_{gs}) = 0.073 \text{ W}$$

Conduction losses per FET

$$PQ11(V_s, I_o, V_{gs}) := \frac{1}{N_u} \cdot PQ1(V_s, I_o, V_{gs})$$

$$PQ11(V_s, I_{omax}, V_{gs}) = 1.309 \text{ W}$$

$$PQ21(V_s, I_o, V_{gs}) := \frac{1}{N_l} \cdot PQ2(V_s, I_o, V_{gs})$$

$$PQ21(V_s, I_{omax}, V_{gs}) = 1.16 \text{ W}$$

$$PLo(V_s, I_{omax}, V_{gs}) = 0.56 \text{ W}$$

- inductor conduction losses

$$P_{pcb}(V_s, I_{omax}, V_{gs}) = 0 \text{ W}$$

- PCB conduction losses

$$P_{loss}(V_s, I_{omax}, V_{gs}) = 4.188 \text{ W}$$

- Total Conduction Power Losses

DYNAMIC POWER LOSSES

$$R_{gU} := 0.5 \cdot \text{ohm}$$

- internal gate resistor of FET

$$R_{geU} := 0 \cdot \text{ohm}$$

- external gate resistor

$$R_{dp} := 1 \cdot \text{ohm}$$

- source output resistor of driver

$$R_{dn} := 1 \cdot \text{ohm}$$

- sink output resistor of driver

$$IgU1(V_s, I_o, V_{gs}, R_{dp}) := \frac{V_{gs} - 0.4 \cdot V - \left(V_{thU} + \frac{gU}{N_u} \cdot IQ1m(V_s, I_o, V_{gs}) \right)}{\frac{R_{gU}}{N_u} + R_{geU} + R_{dp}}$$

- source gate current of high-side FET

$$IgU1(V_s, I_{omax}, 5 \cdot V, R_{dp}) = 1.547 \text{ A}$$

$$IgU1(V_s, I_{omax}, 7 \cdot V, R_{dp}) = 2.879 \text{ A}$$

$$IgU1(V_s, I_{omax}, 12 \cdot V, 1.8 \cdot \text{ohm}) = 4.051 \text{ A}$$

$$IgU2(V_s, I_o, V_{gs}, R_{dn}) := \frac{V_{thU} + \frac{gU}{N_u} \cdot IQ1p(V_s, I_o, V_{gs})}{\frac{R_{gU}}{N_u} + R_{geU} + R_{dn}}$$

- sink gate current of high-side FET

$$IgU2(V_s, I_{omax}, 5 \cdot V, R_{dp}) = 1.766 \text{ A}$$

$$IgU2(V_s, I_{omax}, 7 \cdot V, R_{dp}) = 1.765 \text{ A}$$

$$IgU2(V_s, I_{omax}, 12 \cdot V, 1.0 \cdot \text{ohm}) = 1.764 \text{ A}$$

- high-side FET switching losses

$$P_{swt}(V_s, I_o, V_{gs}, R_{dp}, R_{dn}) := IQ1m(V_s, I_o, V_{gs}) \cdot V_s \cdot \frac{f_s}{2} \cdot N_u \cdot \frac{Q_{gs2t} + Q_{gdlt}}{IgU1(V_s, I_o, V_{gs}, R_{dp})} + IQ1p(V_s, I_o, V_{gs}) \cdot V_s \cdot \frac{f_s}{2} \cdot N_u \cdot \frac{Q_{gs2t} + Q_{gdlt}}{IgU2(V_s, I_o, V_{gs}, R_{dn})}$$

$$P_{swt}(V_s, I_{omax}, V_{gs}, R_{dn}, R_{dn}) = 0.382 \text{ W}$$

$$P_{swbd}(V_{gs}) := 0.5 \cdot Q_{tt}(V_{gs}) \cdot (V_{gs} - 0.4 \cdot V) \cdot f_s \cdot N_u$$

- losses in bootstrap diode

$$P_{swbd}(V_{gs}) = 0.023 \text{ W}$$

$$P_{swdt}(V_{gs}) := Q_{tt}(V_{gs}) \cdot (V_{gs} - 0.4 \cdot V) \cdot f_s \cdot N_u$$

$$P_{swdt}(V_{gs}) = 0.045 \text{ W}$$

- high-side FET drive losses

$$P_{swdb}(V_{gs}) := Q_{tb}(V_{gs}) \cdot V_{gs} \cdot f_s \cdot N_l$$

$$P_{swdb}(V_{gs}) = 0.26 \text{ W}$$

- low-side FET driver losses

$$I_{dd}(V_{gs}) := \frac{V_{gs}}{7 \cdot V} \cdot 3 \cdot \text{mA}$$

$$P_{bias}(V_{gs}) := V_{gs} \cdot I_{dd}(V_{gs})$$

$$P_{swdr}(V_{gs}) := P_{swdt}(V_{gs}) + P_{swdb}(V_{gs}) + P_{bias}(V_{gs}) \quad P_{swdr}(V_{gs}) = 0.326 \text{ W} \quad \text{- drive power losses without bootstrap diode}$$

$$P_{swd}(V_{gs}) := P_{swdt}(V_{gs}) + P_{swdb}(V_{gs}) + P_{swbd}(V_{gs}) + P_{bias}(V_{gs})$$

$$P_{swd}(V_{gs}) = 0.349 \text{ W}$$

- drive power losses

$$I_{dr}(V_{gs}) := \frac{P_{swd}(V_{gs})}{V_{gs}}$$

$$P_{ldo}(V_{gs}) := (V_s - V_{gs}) \cdot I_{dr}(V_{gs})$$

- LDO power losses

Driver input current

$$I_{dr}(5 \cdot V) = 33.732 \text{ mA}$$

$$N_{ph} \cdot I_{dr}(5 \cdot V) = 134.929 \text{ mA}$$

$$P_{swd}(5 \cdot V) = 0.169 \text{ W}$$

$$P_{swdr}(5 \cdot V) = 0.158 \text{ W}$$

$$I_{dr}(6 \cdot V) = 41.767 \text{ mA}$$

$$N_{ph} \cdot I_{dr}(6 \cdot V) = 167.067 \text{ mA}$$

$$P_{swd}(6 \cdot V) = 0.251 \text{ W}$$

$$P_{swdr}(6 \cdot V) = 0.234 \text{ W}$$

$$I_{dr}(7 \cdot V) = 49.805 \text{ mA}$$

$$N_{ph} \cdot I_{dr}(7 \cdot V) = 199.22 \text{ mA}$$

$$P_{swd}(7 \cdot V) = 0.349 \text{ W}$$

$$P_{swdr}(7 \cdot V) = 0.326 \text{ W}$$

$$I_{dr}(8 \cdot V) = 57.846 \text{ mA}$$

$$N_{ph} \cdot I_{dr}(8 \cdot V) = 231.384 \text{ mA}$$

$$P_{swd}(8 \cdot V) = 0.463 \text{ W}$$

$$P_{swdr}(8 \cdot V) = 0.433 \text{ W}$$

$$I_{dr}(12 \cdot V) = 90.022 \text{ mA}$$

$$N_{ph} \cdot I_{dr}(12 \cdot V) = 360.09 \text{ mA}$$

$$P_{swd}(12 \cdot V) = 1.08 \text{ W}$$

$$P_{swdr}(12 \cdot V) = 1.009 \text{ W}$$

$$(Vs - 6 \cdot V) \cdot Nph \cdot Idr(6 \cdot V) = 1.002 \text{ W}$$

$$Nph \cdot Pswd(5 \cdot V) = 0.675 \text{ W}$$

$$(Vs - 7 \cdot V) \cdot Nph \cdot Idr(7 \cdot V) = 0.996 \text{ W}$$

$$Nph \cdot Pswd(6 \cdot V) = 1.002 \text{ W}$$

$$(Vs - 8 \cdot V) \cdot Nph \cdot Idr(8 \cdot V) = 0.926 \text{ W}$$

$$Nph \cdot Pswd(7 \cdot V) = 1.395 \text{ W}$$

- overall LDO power losses

- overall drive losses without LDO

$$Nph \cdot Pswd(8 \cdot V) = 1.851 \text{ W}$$

$$Nph \cdot Pswd(12 \cdot V) = 4.321 \text{ W}$$

Diode losses: HAT2166N at 125C

$$Tdt := 20 \cdot \text{nS} \quad Rdi := 0.006 \cdot \text{ohm} \quad Vf := 0.5 \cdot \text{V}$$

$$Pd(Vs, Io, Vgs) := IQ1m(Vs, Io, Vgs) \cdot \left(Vf + \frac{Rdi}{Nl} \cdot IQ1m(Vs, Io, Vgs) \right) \cdot \frac{Tdt}{Ts} + IQ1p(Vs, Io, Vgs) \cdot \left(Vf + \frac{Rdi}{Nl} \cdot IQ1p(Vs, Io, Vgs) \right) \cdot \frac{Tdt}{Ts}$$

$$Pd(Vs, Iomax, Vgs) = 0.319 \text{ W} \quad Pd(Vs, 0 \cdot A, Vgs) = 6.998 \times 10^{-3} \text{ W}$$

Diode recovery losses (HAT2166N for If = 45A, di/dt=100A/us. Trr = 37ns):

$$Qrr(Vs, Io, Vgs) := 46 \cdot \text{ncoul}$$

$$PQ1rr(Vs, Io, Vgs) := \text{if} \left(IQ1m(Vs, Io, Vgs) < 0, 0 \cdot \text{W}, fs \cdot Qrr(Vs, Io, Vgs) \cdot \frac{IQ1m(Vs, Io, Vgs)}{45 \cdot A} \cdot Vs \right)$$

$$PQ1rr(Vs, Iomax, Vgs) = 0.097 \text{ W} \quad PQ1rr(Vs, 0 \cdot A, Vgs) = 0 \text{ W}$$

Total switching losses proportional to current

$$PswIo(Vs, Io, Vgs, Rdp, Rdn) := Pd(Vs, Io, Vgs) + PQ1rr(Vs, Io, Vgs) + Pswt(Vs, Io, Vgs, Rdp, Rdn)$$

$$PswIo(Vs, Iomax, Vgs, Rdp, Rdn) = 0.798 \text{ W} \quad PswIo(Vs, 0 \cdot A, Vgs, Rdp, Rdn) = 0.06 \text{ W}$$

Coss related losses:

Cossu10 := 400 · pF	Cossl10 := 1000 · pF
---------------------	----------------------

$$\text{Cossu}(Vs) := \text{Cossu10} \cdot \frac{\sqrt{10 \cdot V}}{\sqrt{Vs}} \quad \text{Cossl}(Vs) := \text{Cossl10} \cdot \frac{\sqrt{10 \cdot V}}{\sqrt{Vs}}$$

$$Crssu10 := 130 \cdot \text{pF} \quad Crssl10 := 330 \cdot \text{pF}$$

$$Crssu(Vs) := Crssu10 \cdot \frac{\sqrt{10 \cdot V}}{\sqrt{Vs}} \quad Crssl(Vs) := Crssl10 \cdot \frac{\sqrt{10 \cdot V}}{\sqrt{Vs}}$$

$$\text{Possint(Vs)} := \text{fs} \cdot \frac{2}{3} \cdot [(\text{Cossu(Vs)} + \text{Crssu(Vs)}) \cdot \text{Nu} + (\text{CossI(Vs)} + \text{Crssl(Vs)}) \cdot \text{NI}] \cdot \text{Vs}^2$$

$$\text{Poss(Vs, Io)} := \text{if} \left[\text{Io} < \frac{1}{2} \cdot \frac{\text{Vo} \cdot (\text{Vs} - \text{Vo})}{\text{Vs} \cdot \text{Lo} \cdot \text{fs}}, \frac{\text{Io} \cdot 2 \cdot (\text{Vs} \cdot \text{Lo} \cdot \text{fs})}{\text{Vo} \cdot (\text{Vs} - \text{Vo})} \cdot (\text{Possint(Vs)}), \text{Possint(Vs)} \right]$$

$$\text{Poss(Vs, Iomax)} = 0.112 \text{ W}$$

Snubber losses:

$$C_{sn} := 2000 \cdot \text{pF}$$

$$P_{sn}(Vs) := C_{sn} \cdot V_{s}^2 \cdot fs$$

$$P_{sn}(Vs) = 0.115 \text{ W}$$

$$P_{swconst}(Vs, Io, Vgs) := \text{Poss(Vs, Io)} + P_{sn}(Vs) + P_{swd}(Vgs) \quad \text{-total constant switching losses without LDO but with bootstrap diode}$$

$$P_{swtt}(Vs, Io, Vgs, Rdp, Rdn) := P_{swt}(Vs, Io, Vgs, Rdp, Rdn) + PQ1rr(Vs, Io, Vgs) + Poss(Vs, Io) \quad \text{-upper FET switching losses}$$

$$P_{sw}(Vs, Io, Vgs, Rdp, Rdn) := P_{swtt}(Vs, Io, Vgs, Rdp, Rdn) + Pd(Vs, Io, Vgs) + P_{sn}(Vs) + P_{swd}(Vgs) \quad \text{-total switching losses}$$

$$P_{sw}(Vs, Iomax, Vgs, Rdp, Rdn) = 1.373 \text{ W} \quad P_{swtt}(Vs, Iomax, Vgs, Rdp, Rdn) = 0.591 \text{ W} \quad P_{swt}(Vs, Iomax, Vgs, Rdp, Rdn) = 0.382 \text{ W}$$

$$P_{ufet}(Vs, Io, Vgs, Rdp, Rdn) := PQ1(Vs, Io, Vgs) + P_{swt}(Vs, Io, Vgs, Rdp, Rdn) + PQ1rr(Vs, Io, Vgs) + Poss(Vs, Io) \quad \text{-total upper FET losses}$$

$$P_{ufet}(Vs, Iomax, Vgs, Rdp, Rdn) = 1.9 \text{ W}$$

$$Pu(Vs, Io, Vgs, Rdp, Rdn) := \frac{1}{Nu} \cdot P_{ufet}(Vs, Io, Vgs, Rdp, Rdn) \quad Pu(Vs, Iomax, Vgs, Rdp, Rdn) = 1.9 \text{ W} \quad \text{Upper FET power losses (per one FET):}$$

$$Plfet(Vs, Io, Vgs) := (PQ2(Vs, Io, Vgs) + Pd(Vs, Io, Vgs)) \quad \text{-total lower FET losses}$$

$$Plfet(Vs, Iomax, Vgs) = 2.638 \text{ W}$$

$$Pl(Vs, Io, Vgs) := \frac{1}{NI} \cdot Plfet(Vs, Io, Vgs) \quad Pl(Vs, Iomax, Vgs) = 1.319 \text{ W} \quad \text{Lower FET power losses (per one FET):}$$

$$Pfet(Vs, Io, Vgs, Rdp, Rdn) := Pufet(Vs, Io, Vgs, Rdp, Rdn) + Plfet(Vs, Io, Vgs)$$

-overall FET losses

$$Pp(Vs, Io, Vgs, Rdp, Rdn) := Psw(Vs, Io, Vgs, Rdp, Rdn) + Ploss(Vs, Io, Vgs)$$

-total power losses per phase without LDO and input inductor

$$Pp(Vs, Iomax, Vgs, Rdp, Rdn) = 5.561 \text{ W}$$

Input Inductor:

Not present

$$Riin := 0.0 \cdot m\Omega$$

$$Riin = 0 \text{ m}\Omega$$

$$Iin(Vs, Io, Rdp, Rdn) := \frac{Nph \cdot (Vo \cdot Io + Pp(Vs, Io, Vgs, Rdp, Rdn))}{Vs} \quad Iin(Vs, Iomax, Rdp, Rdn) = 15.937 \text{ A}$$

$$Piin(Vs, Io, Rdp, Rdn) := Iin(Vs, Io, Rdp, Rdn)^2 \cdot Riin \cdot Kt(Io) \quad Piin(Vs, Iomax, Rdp, Rdn) = 0 \text{ W}$$

$$Ppl(Vs, Io, Vgs, Rdp, Rdn) := Pp(Vs, Io, Vgs, Rdp, Rdn) + Piin(Vs, Io, Rdp, Rdn) \quad \text{-total power losses}$$

$$Ppl2(Vs, Io, Vgs, Rdp, Rdn) := Ppl(Vs, Io, Vgs, Rdp, Rdn) + (Vs - Vgs) \cdot Idr(Vgs)$$

- counts losses in LDO

$$Ppl(Vs, Iomax, Vgs, Rdp, Rdn) = 5.561 \text{ W} \quad \text{- total power losses}$$

$$Ppl(Vs, Iomax, 5 \cdot V, Rdp, Rdn) = 6.136 \text{ W} \quad Nph \cdot [(Ppl(Vs, Iomax, 4.5 \cdot V, Rdp, Rdn)) - (Ppl(Vs, Iomax, 7 \cdot V, Rdp, Rdn))] = 3.744 \text{ W}$$

$$Ppl(Vs, Iomax, 7 \cdot V, Rdp, Rdn) = 5.561 \text{ W} \quad Nph \cdot [(Ppl(Vs, Iomax, 5 \cdot V, Rdp, Rdn)) - (Ppl(Vs, Iomax, 7 \cdot V, Rdp, Rdn))] = 2.302 \text{ W}$$

$$Ppl(Vs, Iomax, 12 \cdot V, Rdp, Rdn) = 5.754 \text{ W} \quad Nph \cdot [(Ppl(Vs, 0 \cdot A, 12 \cdot V, Rdp, Rdn)) - (Ppl(Vs, 0 \cdot A, 7 \cdot V, Rdp, Rdn))] = 2.959 \text{ W}$$

$$Vgs := 2.6 \cdot V, 2.7 \cdot V .. 12 \cdot V$$

$$Imph(Io) := Nph \cdot Io$$

$$Eff(Vs, Io, Vgs, Rdp, Rdn) := \frac{Io \cdot Vo \cdot 100}{Io \cdot Vo + Ppl(Vs, Io, Vgs, Rdp, Rdn)}$$

$$Eff2(Vs, Io, Vgs, Rdp, Rdn) := \frac{Io \cdot Vo \cdot 100}{Io \cdot Vo + Ppl2(Vs, Io, Vgs, Rdp, Rdn)}$$

$$Eff(12 \cdot V, 32.5 \cdot A, 7 \cdot V, 1 \cdot \text{ohm}, 1 \cdot \text{ohm}) = 88.369$$

$$Io := 32.5 \cdot A \quad Itot := Nph \cdot Io$$

Power Losses Summary

$V_s = 12 \text{ V}$ $V_o = 1.3 \text{ V}$ $I_o = 32.5 \text{ A}$ $N_{ph} = 4$ $I_{tot} = 130 \text{ A}$ $f_s = 400 \text{ kHz}$ $N_u = 1$ **HAT2168N** $N_l = 2$ **HAT2166N**

$L_o = 0.12 \mu\text{H}$ $R_i = 0.36 \text{ m}\Omega$ **Inductor at 25C**

$R_{pcb} = 0 \text{ m}\Omega$ **PCB and traces at 25C**

Power Losses per Phase

Conduction Losses

$$\delta I_o(V_s, I_o, 5 \cdot V) = 25.799 \text{ A}$$

$$\delta I_o(V_s, I_o, 7 \cdot V) = 25.599 \text{ A}$$

$$\delta I_o(V_s, I_o, 12 \cdot V) = 25.456 \text{ A}$$

P-P Inductor current

$$P_{Lo}(V_s, I_o, 5 \cdot V) = 0.56 \text{ W}$$

$$P_{Lo}(V_s, I_o, 7 \cdot V) = 0.56 \text{ W}$$

$$P_{Lo}(V_s, I_o, 12 \cdot V) = 0.56 \text{ W}$$

Inductor losses

$$P_{pcb}(V_s, I_o, 5 \cdot V) = 0 \text{ W}$$

$$P_{pcb}(V_s, I_o, 7 \cdot V) = 0 \text{ W}$$

$$P_{pcb}(V_s, I_o, 12 \cdot V) = 0 \text{ W}$$

- PCB traces power losses

$$PQ1(V_s, I_o, 5 \cdot V) = 1.59 \text{ W}$$

$$PQ1(V_s, I_o, 7 \cdot V) = 1.309 \text{ W}$$

$$PQ1(V_s, I_o, 12 \cdot V) = 1.103 \text{ W}$$

-Conduction losses for U_FET

$$PQ2(V_s, I_o, 5 \cdot V) = 2.724 \text{ W}$$

$$PQ2(V_s, I_o, 7 \cdot V) = 2.319 \text{ W}$$

$$PQ2(V_s, I_o, 12 \cdot V) = 2.029 \text{ W}$$

-Conduction losses for L_FET

$$PQ(V_s, I_o, 5 \cdot V) = 4.314 \text{ W}$$

$$PQ(V_s, I_o, 7 \cdot V) = 3.628 \text{ W}$$

$$PQ(V_s, I_o, 12 \cdot V) = 3.133 \text{ W}$$

-Cond. losses for FETs

$$P_{loss}(V_s, I_o, 5 \cdot V) = 4.875 \text{ W}$$

$$P_{loss}(V_s, I_o, 7 \cdot V) = 4.188 \text{ W}$$

$$P_{loss}(V_s, I_o, 12 \cdot V) = 3.692 \text{ W}$$

-total conduction losses

Switching losses proportional to current

$$IgU1(V_s, I_o, 5 \cdot V, 1 \cdot \text{ohm}) = 1.547 \text{ A}$$

$$IgU1(V_s, I_o, 7 \cdot V, 1 \cdot \text{ohm}) = 2.879 \text{ A}$$

$$IgU1(V_s, I_o, 12 \cdot V, 1.8 \cdot \text{ohm}) = 4.051 \text{ A}$$

$$IgU2(V_s, I_o, 5 \cdot V, 1 \cdot \text{ohm}) = 1.766 \text{ A}$$

$$IgU2(V_s, I_o, 7 \cdot V, 1 \cdot \text{ohm}) = 1.765 \text{ A}$$

$$IgU2(V_s, I_o, 12 \cdot V, 1.0 \cdot \text{ohm}) = 1.764 \text{ A}$$

$$P_{swt}(V_s, I_o, 5 \cdot V, 1 \cdot \text{ohm}, 1 \cdot \text{ohm}) = 0.451 \text{ W}$$

$$P_{swt}(V_s, I_o, 7 \cdot V, 1 \cdot \text{ohm}, 1 \cdot \text{ohm}) = 0.382 \text{ W}$$

$$P_{swt}(V_s, I_o, 12 \cdot V, 1.8 \cdot \text{ohm}, 1 \cdot \text{ohm}) = 0.359 \text{ W} \quad \text{-U_FET}$$

$$P_d(V_s, I_o, 5 \cdot V) = 0.319 \text{ W}$$

$$P_d(V_s, I_o, 7 \cdot V) = 0.319 \text{ W}$$

$$P_d(V_s, I_o, 12 \cdot V) = 0.318 \text{ W} \quad \text{-L_FET_Body_Diode}$$

$$PQ1rr(V_s, I_o, 5 \cdot V) = 0.096 \text{ W}$$

$$PQ1rr(V_s, I_o, 7 \cdot V) = 0.097 \text{ W}$$

$$PQ1rr(V_s, I_o, 12 \cdot V) = 0.097 \text{ W} \quad \text{-U_FET_Diode_Recov}$$

$$P_{swIo}(V_s, I_o, 5 \cdot V, 1 \cdot \text{ohm}, 1 \cdot \text{ohm}) = 0.866 \text{ W}$$

$$P_{swIo}(V_s, I_o, 7 \cdot V, 1 \cdot \text{ohm}, 1 \cdot \text{ohm}) = 0.798 \text{ W}$$

$$P_{swIo}(V_s, I_o, 12 \cdot V, 1.8 \cdot \text{ohm}, 1 \cdot \text{ohm}) = 0.774 \text{ W}$$

-total proportional to current switching losses

Constant switching losses

Poss(Vs, Io) = 0.112 W	Poss(Vs, Io) = 0.112 W	Poss(Vs, Io) = 0.112 W	-U_FET
Psn(Vs) = 0.115 W	Psn(Vs) = 0.115 W	Psn(Vs) = 0.115 W	-snubber
Pswbd(5 · V) = 0.011 W	Pswbd(7 · V) = 0.023 W	Pswbd(12 · V) = 0.071 W	-bootstrap diode
Pswdt(5 · V) = 0.022 W	Pswdt(7 · V) = 0.045 W	Pswdt(12 · V) = 0.142 W	- high-side FET drive losses
Pswdb(5 · V) = 0.126 W	Pswdb(7 · V) = 0.26 W	Pswdb(12 · V) = 0.805 W	- low-side FET drive losses
Pbias(5 · V) = 0.011 W	Pbias(7 · V) = 0.021 W	Pbias(12 · V) = 0.062 W	- drive bias losses
Pswdr(5 · V) = 0.158 W	Pswdr(7 · V) = 0.326 W	Pswdr(12 · V) = 1.009 W	- drive losses without bootstrap diode
Pswd(5 · V) = 0.169 W	Pswd(7 · V) = 0.349 W	Pswd(12 · V) = 1.08 W	- drive losses with bootstrap diode
Idr(5 · V) = 33.732 mA	Idr(7 · V) = 49.805 mA	Idr(12 · V) = 90.022 mA	-driver input current
	Pldo(7 · V) = 0.249 W	-LDO losses if necessary	





Pswconst(Vs, Io, 5 · V) = 0.396 W Pswconst(Vs, Io, 7 · V) = 0.576 W Pswconst(Vs, Io, 12 · V) = 1.307 W **-total const switching losses without LDO**


Total switching losses without LDO

Pswtt(Vs, Io, 5 · V, 1 · ohm, 1 · ohm) = 0.659 W	Pswtt(Vs, Io, 7 · V, 1 · ohm, 1 · ohm) = 0.591 W	Pswtt(Vs, Io, 12 · V, 1.8 · ohm, 1 · ohm) = 0.568 W	-U_FET switching losses
Psw(Vs, Io, 5 · V, 1 · ohm, 1 · ohm) = 1.262 W	Psw(Vs, Io, 7 · V, 1 · ohm, 1 · ohm) = 1.373 W	Psw(Vs, Io, 12 · V, 1.8 · ohm, 1 · ohm) = 2.082 W	- total switching losses
Total losses			
Pufet(Vs, Io, 5 · V, 1 · ohm, 1 · ohm) = 2.25 W	Pufet(Vs, Io, 7 · V, 1 · ohm, 1 · ohm) = 1.9 W	Pufet(Vs, Io, 12 · V, 1.8 · ohm, 1 · ohm) = 1.671 W	-total U_FET losses
Pu(Vs, Io, 5 · V, 1 · ohm, 1 · ohm) = 2.25 W	Pu(Vs, Io, 7 · V, 1 · ohm, 1 · ohm) = 1.9 W	Pu(Vs, Io, 12 · V, 1.8 · ohm, 1 · ohm) = 1.671 W	-total U_FET losses (per one FET)

Plfet(Vs, Io, 5 · V) = 3.043 W	Plfet(Vs, Io, 7 · V) = 2.638 W	Plfet(Vs, Io, 12 · V) = 2.348 W	-total L_FET losses
Pl(Vs, Io, 5 · V) = 1.521 W	Pl(Vs, Io, 7 · V) = 1.319 W	Pl(Vs, Io, 12 · V) = 1.174 W	-total L_FET losses (per one FET)
Pfet(Vs, Io, 5 · V, 1 · ohm, 1 · ohm) = 5.292 W	Pfet(Vs, Io, 7 · V, 1 · ohm, 1 · ohm) = 4.537 W	Pfet(Vs, Io, 12 · V, 1.8 · ohm, 1 · ohm) = 4.019 W	-total FET losses
Ppl(Vs, Io, 5 · V, 1 · ohm, 1 · ohm) = 6.136 W	Ppl(Vs, Io, 7 · V, 1 · ohm, 1 · ohm) = 5.561 W	Ppl(Vs, Io, 12 · V, 1.8 · ohm, 1 · ohm) = 5.774 W	-total losses without LDO

Io := 0 .. A..0.5 .. A..Iomax

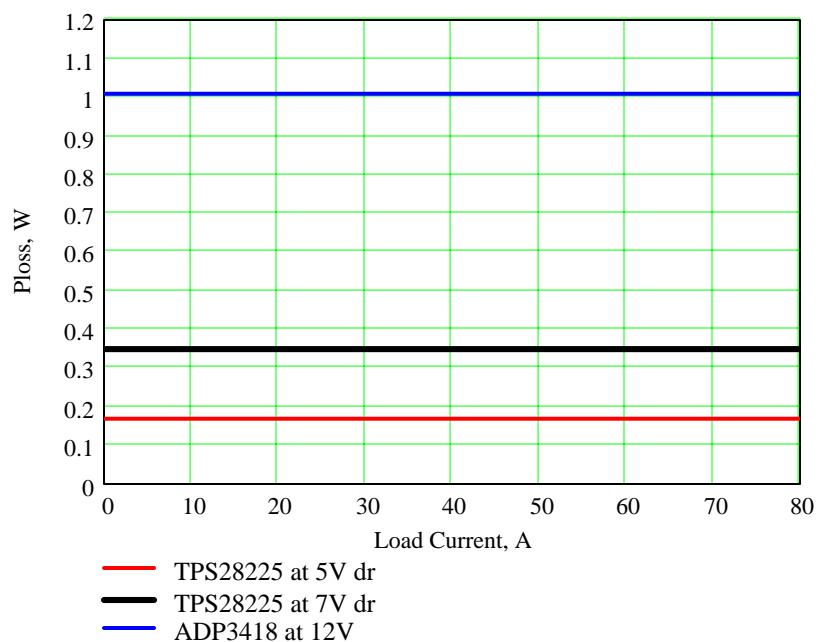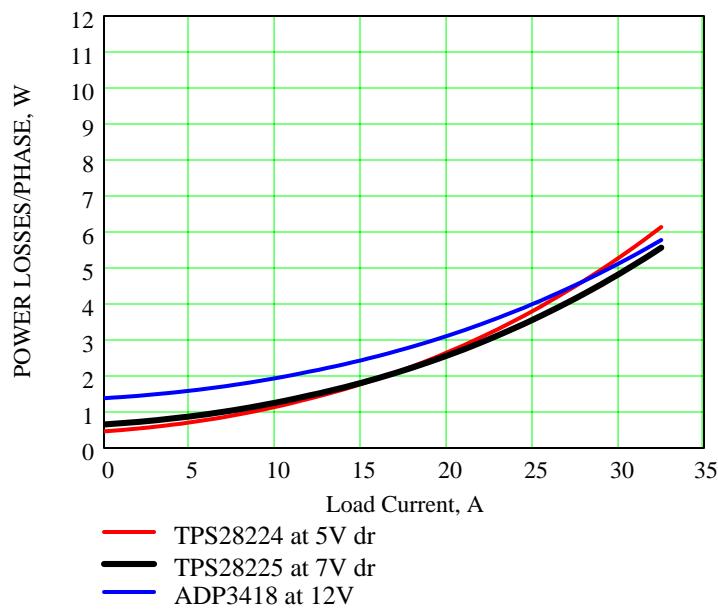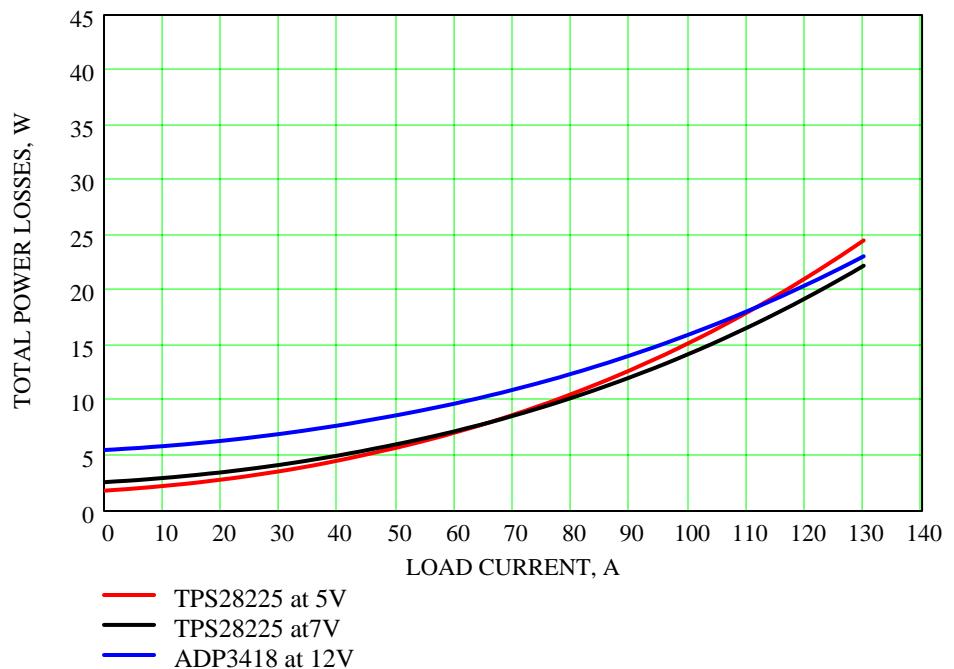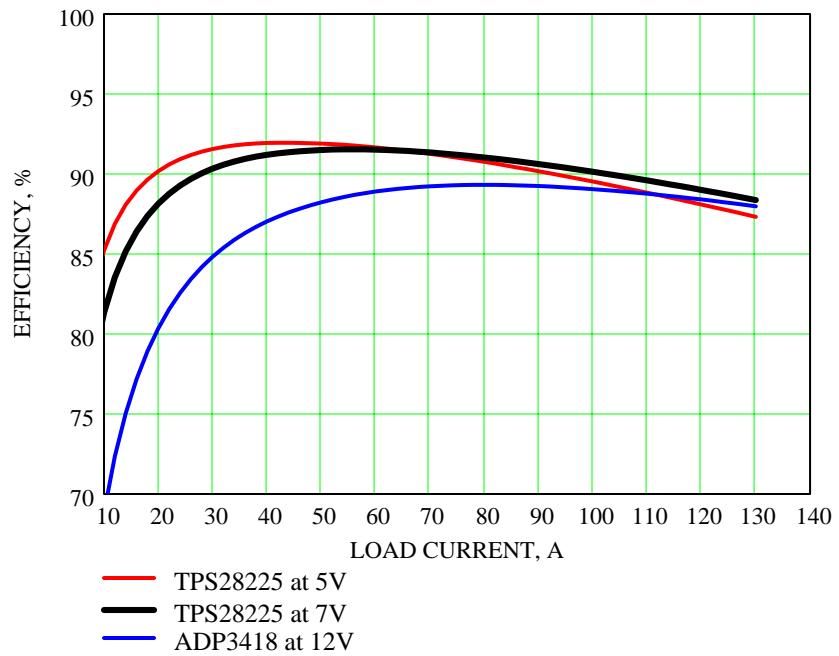

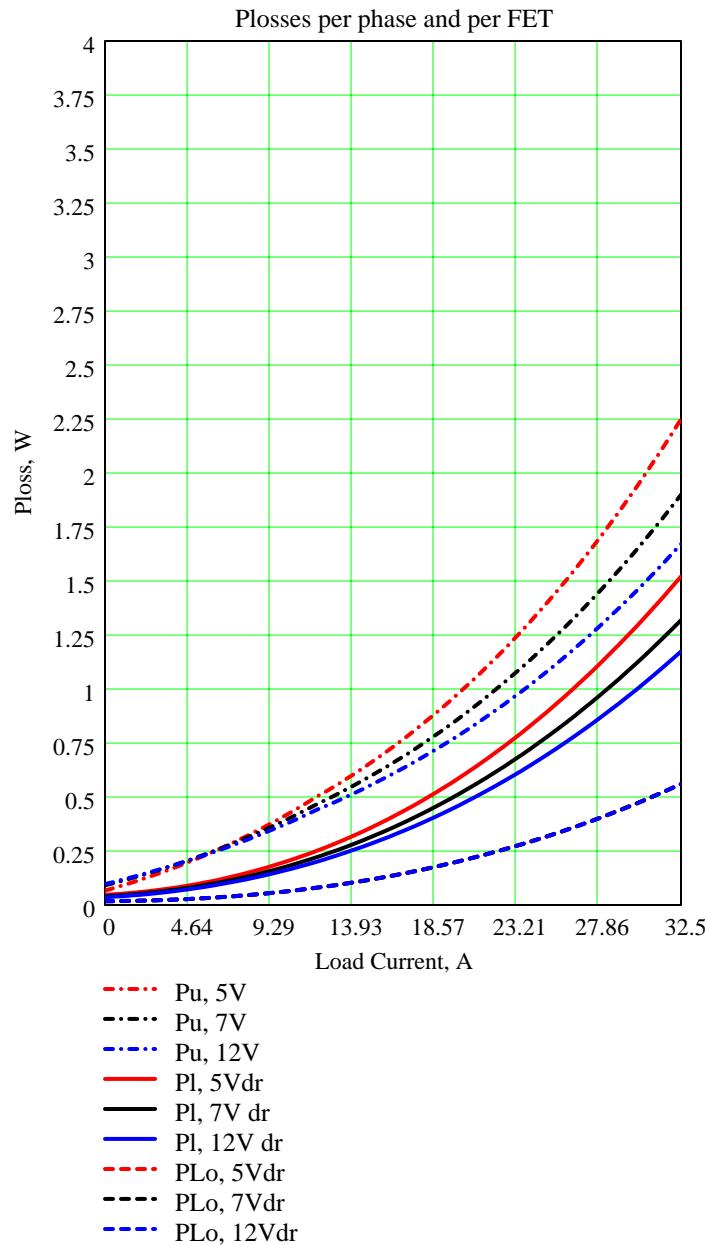

$$Q_{tt}(5 \cdot V) = 11.72 \text{ ncoul}$$

$$Q_{tb}(5 \cdot V) = 31.4 \text{ ncoul}$$

$$Q_{tt}(7 \cdot V) = 17.12 \text{ ncoul}$$

$$Q_{tb}(7 \cdot V) = 46.4 \text{ ncoul}$$

$$Q_{tt}(12 \cdot V) = 30.62 \text{ ncoul}$$

$$Q_{tb}(12 \cdot V) = 83.9 \text{ ncoul}$$

- Overall R_{dson} at 125 C

$$R_{dsU}(5 \cdot V) = 11.9 \text{ m}\Omega$$

$$R_{dsL}(5 \cdot V) = 2.785 \text{ m}\Omega$$

$$R_{dsU}(7 \cdot V) = 9.94 \text{ m}\Omega$$

$$R_{dsL}(7 \cdot V) = 2.368 \text{ m}\Omega$$

$$R_{dsU}(12 \cdot V) = 8.47 \text{ m}\Omega$$

$$R_{dsL}(12 \cdot V) = 2.071 \text{ m}\Omega$$

- R_{dson} of each FET at 25 C

$$R_{dsU_25}(4.5 \cdot V) = 9.2 \text{ m}\Omega$$

$$R_{dsL_25}(4.5 \cdot V) = 4.289 \text{ m}\Omega$$

$$R_{dsU_25}(7 \cdot V) = 7.1 \text{ m}\Omega$$

$$R_{dsL_25}(7 \cdot V) = 3.383 \text{ m}\Omega$$

$$R_{dsU_25}(10 \cdot V) = 6.313 \text{ m}\Omega$$

$$R_{dsL_25}(10 \cdot V) = 3.063 \text{ m}\Omega$$

- R_{dson} at 25 C from DS

HAT2168N


HAT2166N

$$FM_U(V_{gs}) := R_{dsu}(V_{gs}) \cdot Q_{tt}(V_{gs})$$

$$FM_U(7 \cdot V) = 170.173 \text{ ncoul} \cdot \text{m}\Omega$$

$$FM_I(V_{gs}) := R_{dsI}(V_{gs}) \cdot Q_{tb}(V_{gs})$$
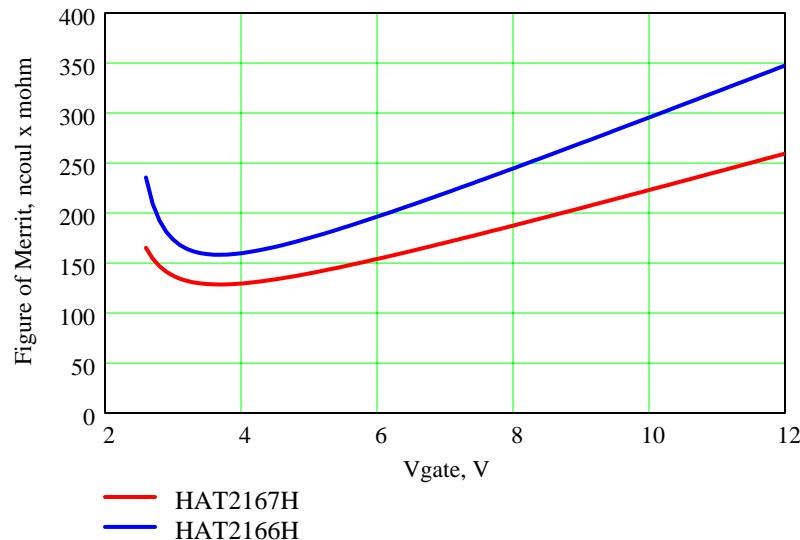
$$FM_I(7 \cdot V) = 219.781 \text{ ncoul} \cdot \text{m}\Omega$$



$fs := 100 \cdot kHz, 150 \cdot kHz .. 1000 \cdot kHz$

$Vgs := 12 \cdot V$

$Pswbd(Vgs, fs) := 0.5 \cdot Qtt(Vgs) \cdot (Vgs - 0.4 \cdot V) \cdot fs \cdot Nu$ - losses in bootstrap diode

$Pswbd(Vgs, 250 \cdot kHz) = 0.044 W$

$Pswdt(Vgs, fs) := Qtt(Vgs) \cdot (Vgs - 0.4 \cdot V) \cdot fs \cdot Nu$

$Pswdt(Vgs, 250 \cdot kHz) = 0.089 W$

- high-side FET drive losses

$Pswdb(Vgs, fs) := Qtb(Vgs) \cdot Vgs \cdot fs \cdot Nl$

$Pswdb(Vgs, 250 \cdot kHz) = 0.503 W$

- low-side FET driver losses

$Idd(Vgs) := \frac{Vgs}{7 \cdot V} \cdot 3 \cdot mA$

$Pbias(Vgs) := Vgs \cdot Idd(Vgs)$

$Pswdr(Vgs, fs) := Pswdt(Vgs, fs) + Pswdb(Vgs, fs) + Pbias(Vgs)$ $Pswdr(Vgs, 250 \cdot kHz) = 0.654 W$

$Pswd(Vgs, fs) := Pswdt(Vgs, fs) + Pswdb(Vgs, fs) + Pswbd(Vgs, fs) + Pbias(Vgs)$



$Pswd(Vgs, 250 \cdot kHz) = 0.698 W$ - drive power losses

Derating Power for SO-8

$T_a := 25, 30..150$

$$P_{diss}(T_a) := 1.25W - 0.01 \cdot W \cdot (T_a - 25)$$

$$P_{diss}(45) = 1.05 \text{ W}$$

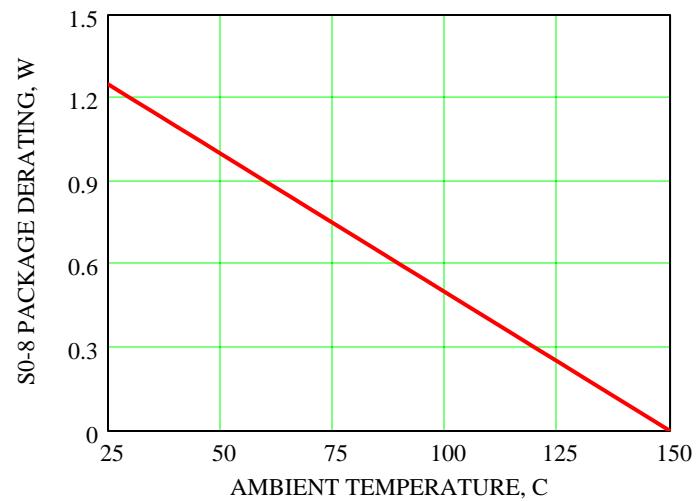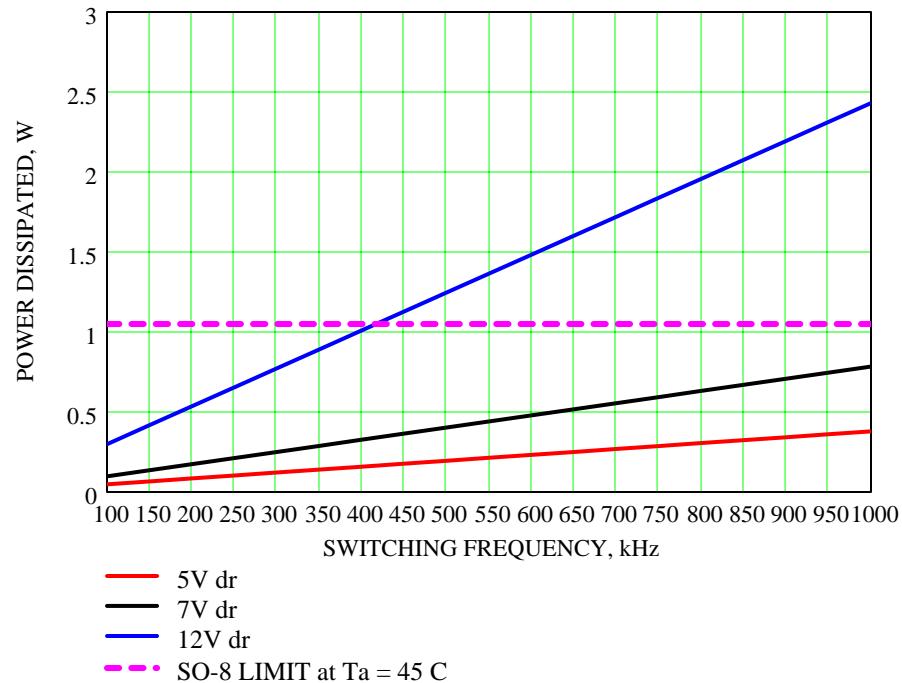

UNIT DEFINITIONS

MKS (SI) unit system

Base units

$$\text{m} \equiv 1\text{L}$$

$$\text{kg} \equiv 1\text{M}$$

$$\text{sec} \equiv 1\text{T}$$

$$\text{coul} \equiv 1\text{Q}$$

Derived units: Electrical

$$\text{cm} \equiv 10^{-2} \cdot \text{m}$$

$$\mu\text{S} \equiv 10^{-6} \cdot \text{sec} \quad \text{nS} \equiv 10^{-9} \cdot \text{sec} \quad \text{mS} \equiv 10^{-3} \cdot \text{sec}$$

$$\text{newton} \equiv \text{kg} \cdot \frac{\text{m}}{\text{sec}^2}$$

$$\text{joule} \equiv \text{newton} \cdot \text{m}$$

$$\mu\text{J} \equiv 10^{-6} \cdot \text{joule} \quad \text{W} \equiv \frac{\text{joule}}{\text{sec}}$$

$$\text{A} \equiv \frac{\text{coul}}{\text{sec}}$$

$$\text{V} \equiv \frac{\text{W}}{\text{A}}$$

$$\text{ohm} \equiv \frac{\text{V}}{\text{A}}$$

$$\text{weber} \equiv \text{V} \cdot \text{sec}$$

$$\text{siemens} \equiv \frac{1}{\text{ohm}}$$

$$\text{farad} \equiv \frac{\text{coul}}{\text{V}}$$

$$\text{oersted} \equiv \frac{1000}{4 \cdot \pi} \cdot \frac{\text{A}}{\text{m}}$$

$$\text{H} \equiv \frac{\text{weber}}{\text{A}}$$

$$\text{T} \equiv \frac{\text{weber}}{\text{m}^2}$$

$$\text{gauss} \equiv 10^{-4} \cdot \text{T}$$

$$\text{MHz} \equiv \frac{10^6}{\text{sec}}$$

$$\text{nH} \equiv 10^{-9} \cdot \text{H}$$

$$\mu\text{H} \equiv 10^{-6} \cdot \text{H}$$

$$\text{pF} \equiv 10^{-12} \cdot \text{farad}$$

$$\text{ncoul} \equiv 10^{-9} \cdot \text{coul}$$

$$\text{m}\Omega \equiv 10^{-3} \cdot \text{ohm}$$

$$\text{nF} \equiv 10^{-9} \cdot \text{farad}$$

$$\text{mA} \equiv 10^{-3} \cdot \text{A}$$

$$\text{S} \equiv \frac{\text{A}}{\text{V}}$$

$$\mu\text{F} \equiv 10^{-6} \cdot \text{farad}$$