

TMS320F28xx and TMS320F28xxx DSP Power Reference Design

This reference design takes into account the voltage, current, and start-up requirements of the TMS320F280x Digital Signal Processor (DSP) families. The operating input voltage ranges from 3.4 V to 6 V. This design is a high-efficiency solution that provides two voltage rails (1.8-V core supply and 3.3-V I/O supply) and an active-low reset signal to the DSP. This design can be easily adapted to fit requirements for the TMS320F28xxx and TMS320F281x, which have a 1.9-V core supply and 3.3-V I/O supply.

Features

- Provides core and I/O voltages from 3.4-V to 6-V input voltages
- High-efficiency solution
- Small solution size using dual converter
- Optional power-save mode, watchdog timer, and power-fail comparator

Related Documentation

For detailed information about operating conditions and component characteristics, click links in [Table 1](#):

Table 1. Related Documentation Links

DEVICE	DATA SHEET
TMS320F28xxx	TMS320F28335, F28334, F28332 F28235, F28234, F28232 DSCs (SPRS439)
TMS320F281x	TMS320F2810, F2811, F2812, C2810, C2811, C2812 DSPs (SPRS174)
TMS320F280x	TMS320F2809, F2808, F2806, F2802, F2801, C2802, C2801, F2801x DSPs (SPRS230)
TPS62400	Adjustable Dual Step-Down Converter (SLVS681)
TPS62402	TPS62402 Dual Step-Down Converter (SLVS681)
TPS3306-18	Dual Processor Supervisor (SLVS290)

Requirements

The TMS320F280x requires two input rails: 1.8 V for the core and 3.3 V for input/output (I/O). To avoid glitches on power up, the 1.8-V rail must be powered prior to or simultaneously with the 3.3-V rail, ensuring that the 1.8-V rail reaches 0.7 V before the 3.3-V rail reaches 0.7 V. See the Power Sequencing section of the relevant DSP data sheet for further details.

Implementation

This design uses the TPS62402 dual-output, step-down converter and the TPS3306-18 dual-supply voltage supervisor (SVS) as shown in [Figure 1](#).

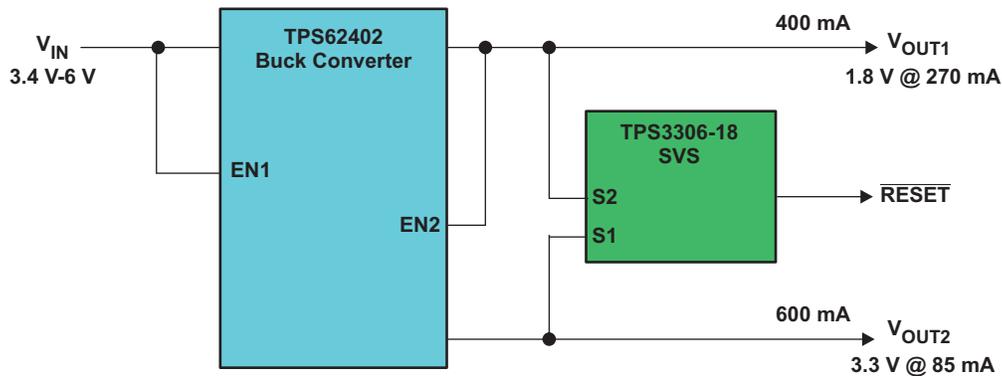


Figure 1. Block Diagram of Power Design

Start-Up

The TPS62402 is a dual step-down converter, with an enable (EN) pin for each output. In this design, the EN1 pin is connected to the input voltage (V_{IN}), so that the 1.8-V rail voltage rises first. The EN2 pin is connected to the 1.8-V rail. Once the voltage reaches the enable threshold of 1.2 V, the 3.3-V rail voltage rises. The 1.8-V rail voltage rises before the 3.3-V rail, so that the start-up requirements are met.

[Figure 2](#) and [Figure 3](#) show the start-up waveforms using a V_{IN} of 5 V and a standard Spectrum Digital EVM board for the F2808 (part number 761132) as the load. The power chip on the board and related circuitry (output capacitors, feedback resistors) are removed, and this design is used to power the board. The TPS62401EVM-167 (HPA167-002) board with the TPS62402DRC instead of the TPS62401DRC is connected to the TPS3305-18D SVS. Then, the voltage rails and reset signal are attached to the F2808 EVM. The TPS62402 is set to forced-PWM mode.

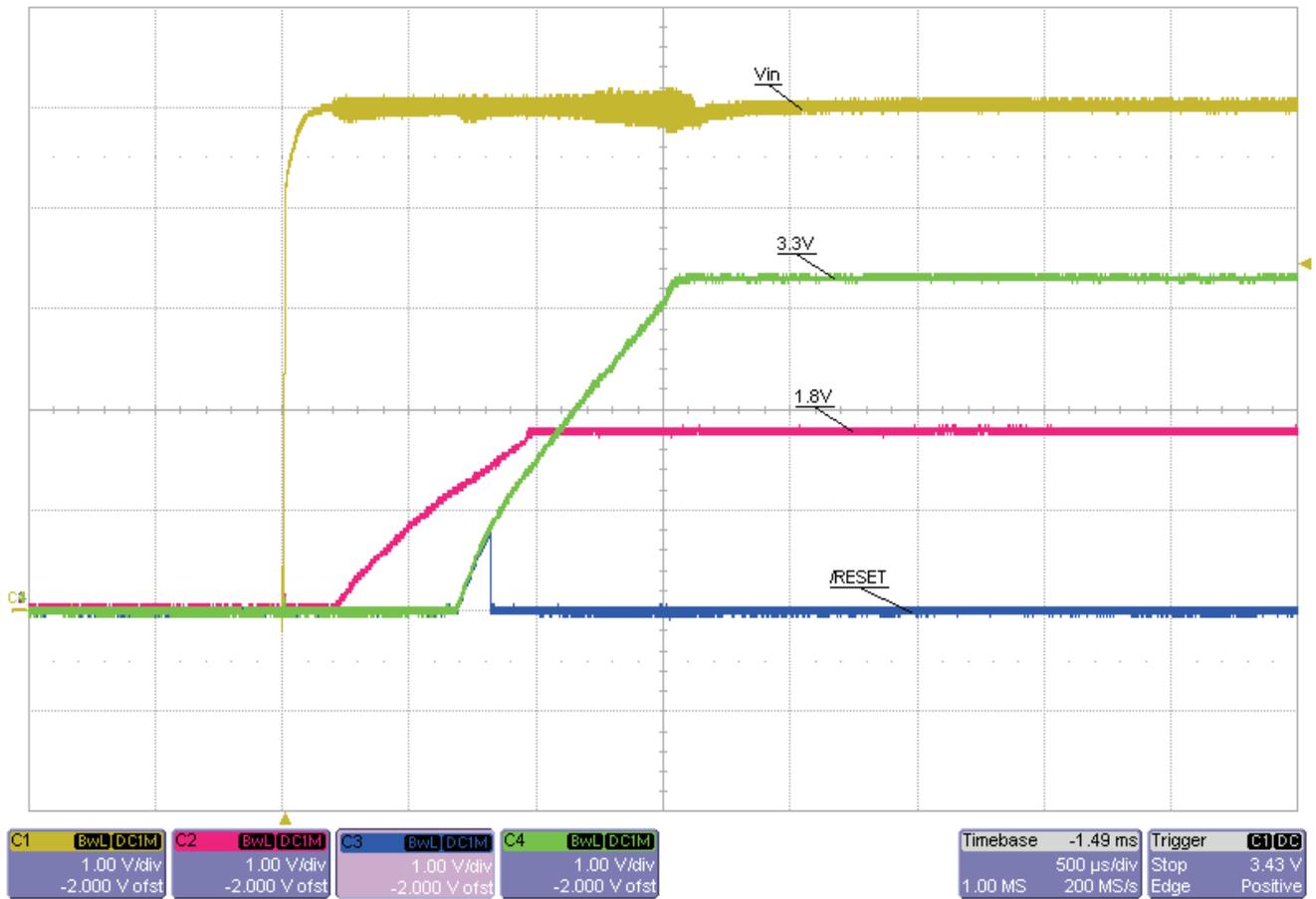


Figure 2. The 1.8-V Rail Voltage Rises Before the 3.3-V Rail

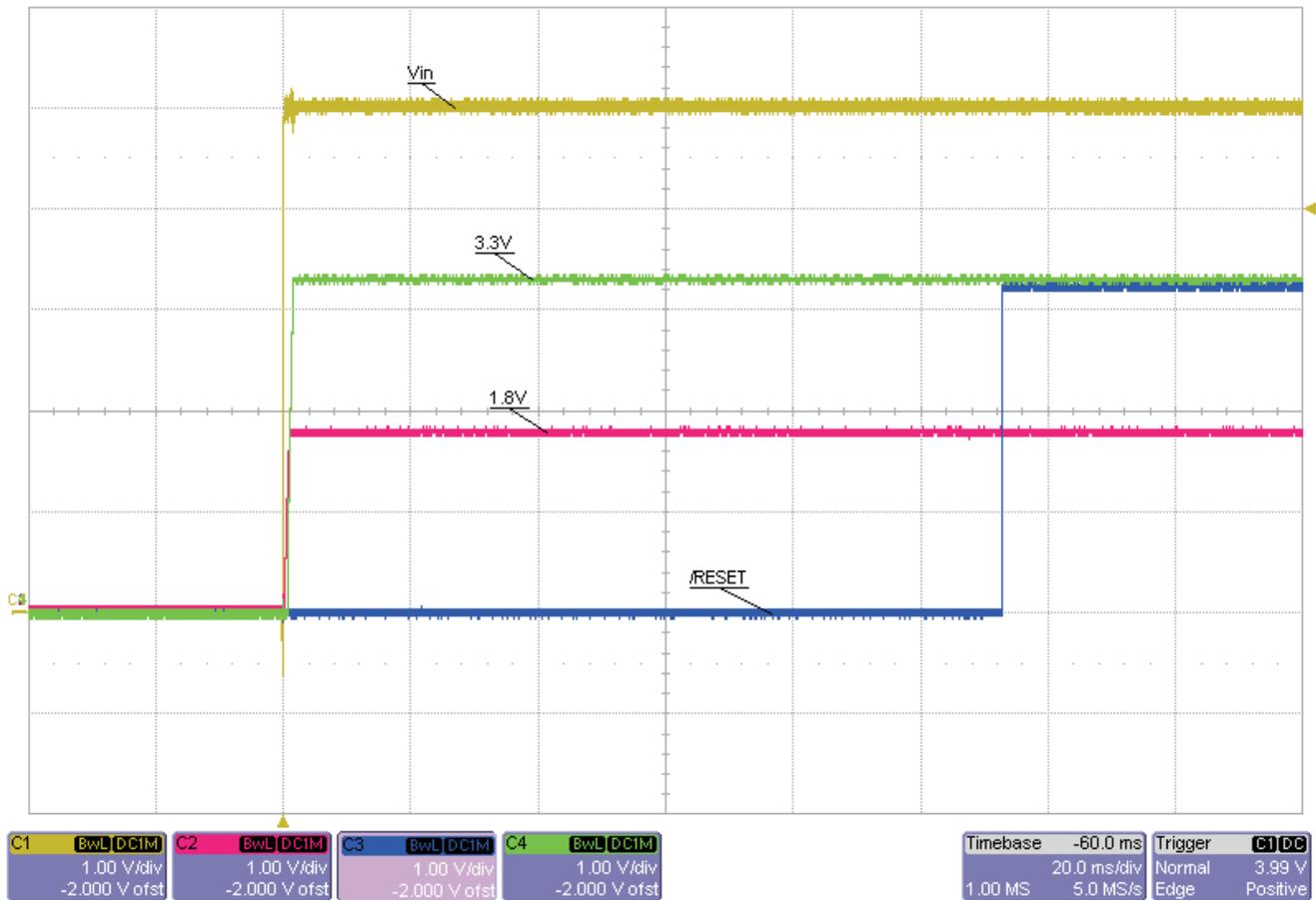


Figure 3. The RESET Signal Held Low for a 100-ms Typical Fixed Delay

Voltage Ripple

For precise measurements on the analog-to-digital converter (ADC) of the DSP, power supply noise and ripple needs to be low. The peak-to-peak voltage ripple values of this design at a V_{in} of 5 V are shown in Table 2. Switching power supplies inherently have more noise and ripple than linear regulators; so, if low noise and ripple is required, consider using a linear regulator like the TPS767D301. For more information on the TPS767D301, see the TPS767D3xx data sheet ([SLVS209](#)) or go to the [TPS767D301 TI Product Page](#). For more detail on the DSP noise and ripple requirements, see the *Total Power Requirement and Selecting Voltage Regulators* section of the *Hardware Design Guidelines for TMS320F28xx and TMS320F28xxx DSCs* application report ([SPRAAS1](#)).

Table 2. Voltage Rail Ripple Voltage Values

OUTPUT CURRENT (mA)	1.8-V RAIL VOLTAGE RIPPLE (mV)	3.3-V RAIL VOLTAGE RIPPLE (mV)
1	5	10
5	5	12
10	5	11
50	6	14
100	6	17
200	6	23
300	9	35
400	10	41

Table 2. Voltage Rail Ripple Voltage Values (continued)

OUTPUT CURRENT (mA)	1.8-V RAIL VOLTAGE RIPPLE (mV)	3.3-V RAIL VOLTAGE RIPPLE (mV)
500	-	53

Output Current

Because the overall requirements depend on the specific application, the maximum output current for the power design is higher than the estimated DSP current consumption at full operation (see [Table 3](#)). For full details on output currents, see the appropriate DSP data sheet.

Table 3. Maximum Output Current


DSP FAMILY	VOLTAGE RAIL (V)	MAXIMUM CONSTANT CURRENT (mA)	CURRENT USED DURING FLASH ERASE(Er)/Write(Wr)
TMS320F28xxx	1.8	328	See data sheet
	3.3	67	
TMS320F281x	1.8	230	140 mA
	3.3	125	95 mA (Er) / 55 mA (Wr)
TMS320F280x	1.8	268	140 mA
	3.3	69	95 mA (Er) / 55 mA (Wr)
TMS320F28044	1.8	268	140 mA
	3.3	57	95 mA (Er) / 55 mA (Wr)

Optional Features

Power-Save Mode—The TPS62402 can be set to constant-PWM mode or Power-Save mode by connecting the MODE/DATA pin to V_{IN} or GND, respectively. See the TPS62402 data sheet ([SLVS681](#)) for more details.

Watchdog Timer—The TPS3306-18 has a Watchdog Timer Input (WTI) that can be connected to the DSP. The Watchdog Timer is deactivated if the WTI pin is left open. See the TPS3306-18 data sheet ([SLVS290](#)) for additional information.

Power-Fail Comparator — The TPS3306-18 has a Power-Fail Comparator that can be used to monitor voltages other than the nominal supply voltages. The threshold can be set using the power-fail input (PFI), which controls the open-drain, power-fail output (PFO). See the TPS3306-18 data sheet ([SLVS290](#)) for more detail.

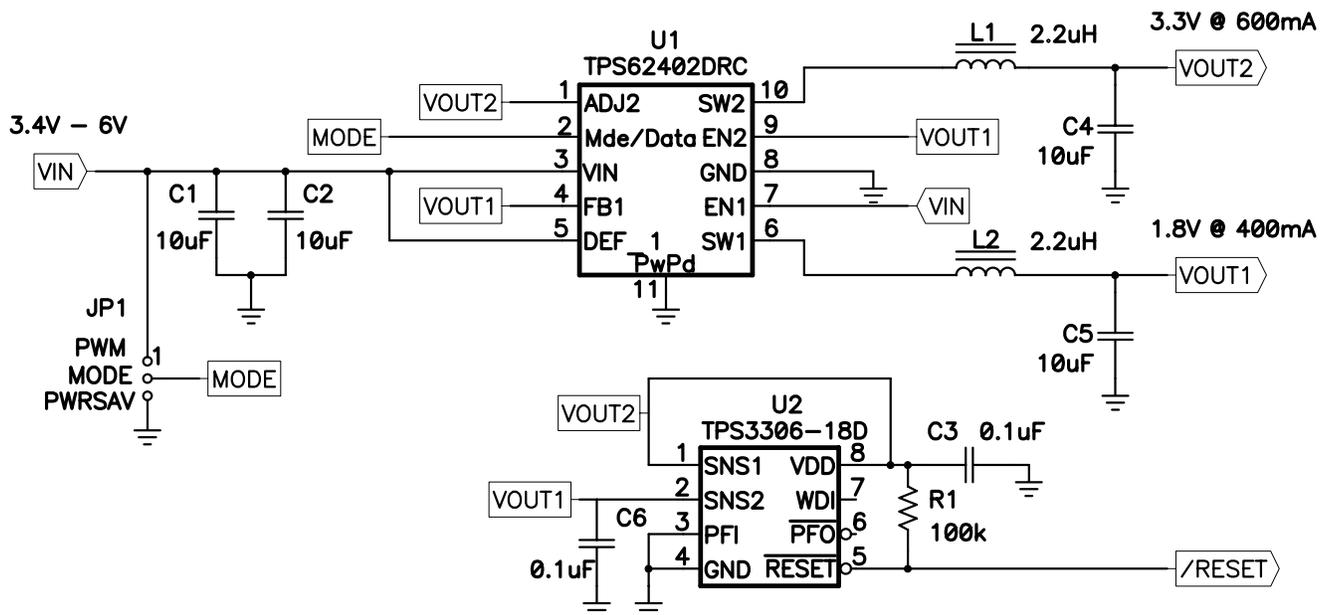Schematic

Bill of Materials

Count	RefDes	Value	Description	Size	Part Number	MFR
4	C1, C2, C4, C5	10 μ F	Capacitor, Ceramic, 10V, X5R, 10%	0805	C2012X5R1A106K	TDK
2	C3, C6	0.1 μ F	Capacitor, Ceramic, 25V, X5R, 10%	0603	C1608X5R1E104K	TDK
2	L1, L2	2.2 μ H	Inductor, SMT, 1.2A, 90 m Ω	0.118 \times 0.118 in	LPS3010-222ML	Coilcraft
1	R1	100k	Resistor, Chip, 1/16W, 1%	0603	Std	
1	U1	TPS62402DRC	IC, 2.25 MHz Dual Step Down Converter	QFN10	TPS62402DRC	TI
1	U2	TPS3306-18D	IC, Dual Processor Supervisory Circuit with Power-fail	SO8	TPS3306-18D	TI

Modifications for the TMS320F281x and TMS320F28xxx

This design can be modified to fit the requirements for the TMS320F281x and TMS320F28xxx. The TPS62402 can be replaced with the TPS62400, which is the adjustable version of the same dual step-down converter. Sequencing requirements can be changed by connecting the enable pin of each converter to the preceding voltage rail. For example, to bring up the 3.3-V rail first, attach the EN2 pin to VIN and the EN1 pin to the 3.3-V rail. The same TPS3306-18 SVS can be used because its voltage threshold is 1.68 V or another SVS can be used as long as the RESET signal is open drain.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2008, Texas Instruments Incorporated