

Simple Power Good Circuit Using the TPS61175 FREQ Pin as Reference

Jeff Falin

PMP - DC/DC Low-Power Converters

ABSTRACT

The TPS61175 FREQ pin can provide a 1.229V reference for use in other circuits, including a power good circuit.

Some systems require a power good signal when a specific power rail reaches regulation. In cost sensitive, low precision applications, where an external supervisory IC, like the TPS38xx family, is not practical, the power supply designer can create a simple supervisory circuit using a low-cost comparator and reference. While the TPS61175 does not specifically provide an external reference, its FREQ pin, which requires a resistor to ground in order to set the switching frequency, tracks the internal reference voltage, 1.229V, through the internal current mirror that is powered by the reference voltage. Mismatches in the current mirror increase the FREQ pin voltage tolerance to approximately $1.229V \pm 5\%$. [Figure 1](#) shows the FREQ pin used as a reference for the power good (PG) circuit created by the TL331 comparator, R4, R5, R2 and C4.

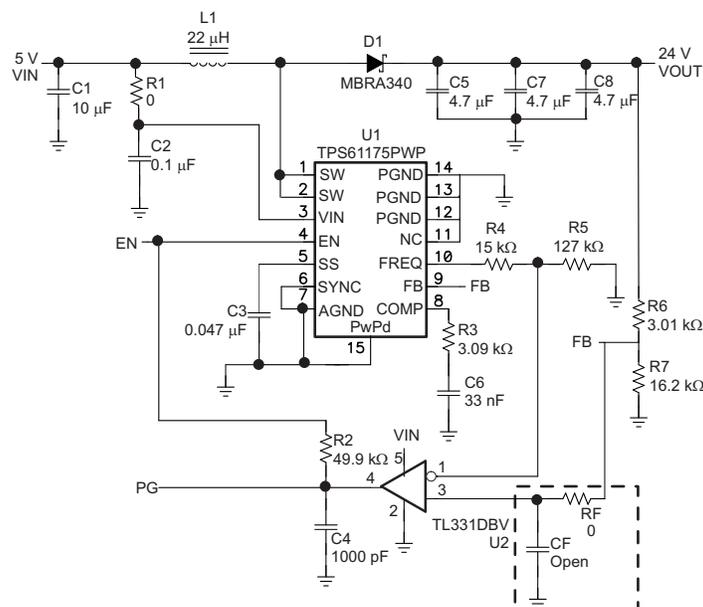


Figure 1. TPS61175 With PG Circuit Using the TL331

The TL331 wide input range and open collector output makes it an excellent choice because the IC itself can be powered by the same input supply as the TPS61175 while the open drain collector is pulled up to a separate logic-level rail. In this application, the FREQ pin resistors, R4 and R5, are sized to meet two criteria. First, their sum must give the desired switching frequency (f_{SW}) per Figure 13 or Table 1 in the data sheet ([SLVS892](#)). Second, they are sized so that the comparator output goes high impedance when the TPS61175 output, and therefore, the FB pin, reaches 90% of its regulated voltage, per [Equation 1](#):

$$\frac{R5}{R4 + R5} = 0.90 \quad (1)$$

As long as the additional load current into the comparator is significantly (e.g., $\ll 1/10$) less than the current sunk by the frequency setting resistors, the switching frequency will not significantly deviate from the expected value. The TL331 has maximum I_{BIAS} current of 250nA, which is more than 1/30 of the $1.229V/(15k + 127k) = 8.6\mu A$ needed through R4 and R5 for the designed switching frequency. Note that the TL331 output is pulled high to EN instead of VIN through resistor R2 not only to keep the PG signal within logic levels of the system, but also because the FREQ pin voltage goes to zero when EN is low. Capacitor C4, was sized with R2 to provide a 50 μs delay so that the PG pull-up voltage is not present before the FREQ pin voltage can rise to 1.229V. RF and CF can be used to create an optional low pass filter to reduce the likelihood false power good failures during a load transient. [Figure 2](#) shows the output voltage and PG signal from a modified TPS61175EVM-326.

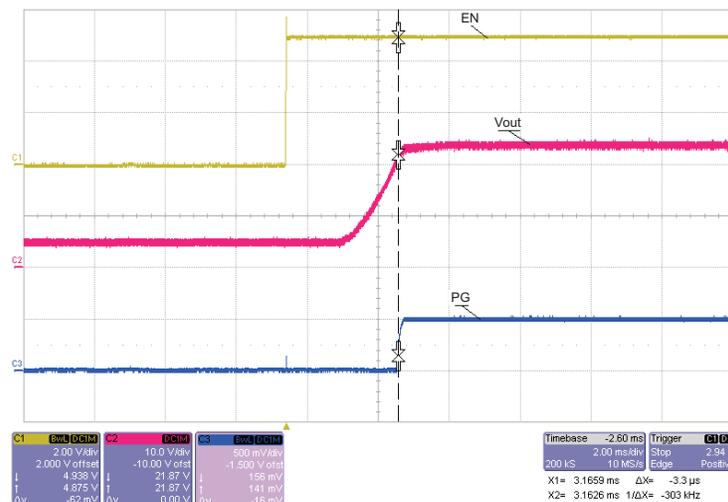


Figure 2.

In this application, there was no noticeable difference in switching frequency with and without the PG circuit installed.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated