

# **Power Reference Design for the TMS320C6472 5-Vin, DC/DC Converters (1x C6472)**

This reference design is intended for designers who wish to design a TMS320C6472 Digital Signal Processor (DSP) into a system using a nominal input voltage of 5 V, DC/DC converters with integrated FETs, and allowing for ease-of-design and a smaller solution size.

### Contents

1	Introduction .....	1
2	Power Requirements .....	2
3	Device Features .....	3
4	Schematic .....	4
5	Bill of Materials .....	5
6	Power-Up Waveforms .....	8

### List of Figures

1	Schematic .....	4
2	Power-Up Waveform, Part 1 .....	8
3	Power-Up Waveform, Part 2 .....	8

### List of Tables

1	TMS320C6472 Power Requirements .....	2
2	Reference Design Parameters .....	2
3	PMP5176 Bill of Materials .....	5

## 1 Introduction

This reference design is for powering one TMS320C6472 DSP and accounts for voltage and current requirements, which are given in [Table 2](#). The core voltage has been optimized for 1-V operation. This design also includes enough margin on the 1.8-V rail to account for typical amounts of memory (2 x 667MHz DDR SDRAM), which comes to just over 600 mA.

The TMS320C6472 requires a 3.3-V, 1.8-V, 1.2-V, and 1-V/1.1-V/1.2-V input. Power-up sequencing is required and is shown in [Table 1](#). In multivoltage architectures, coordinated management of power supplies is necessary to avoid potential problems and ensure reliable performance. Power supply designers must consider the timing and voltage differences between core and I/O voltage supplies during power-up and power-down operations.

Sequencing refers to the order, timing, and differential in which the two voltage rails are powered up and down. A system designed without proper sequencing may be at risk for two types of failures. The first failure represents a threat to the long-term reliability of the dual-voltage device, whereas the second failure is more immediate, with the possibility of damaging interface circuits in the processor or system devices such as memory, logic or data converter integrated circuits (IC).

Another potential problem with improper supply sequencing is bus contention. Bus contention is a condition when the processor and another device both attempt to control a bidirectional bus during power up. Bus contention also may affect I/O reliability. Power supply designers must check the requirements regarding bus contention for individual devices.

## 2 Power Requirements

The power requirements for each TMS320C6472 follow. For more information and other reference designs, visit [www.ti.com/processorpower](http://www.ti.com/processorpower).

**Table 1. TMS320C6472<sup>(1)</sup> Power Requirements**

Core, I/O	Pin Name	Voltage (V)	I <sub>max</sub> (mA)	Tolerance	Sequencing Order	Timing Delay
Core	CVDD, CVDD2 <sup>(2)</sup>	1 / 1.1 / 1.2	9500	±5	2	<200 ms
	CVDD1	1.2	260	±5		
IO	DVDD33	3.3	100	±5	1	<200 ms
	DVDD18 <sup>(3)</sup> , DVDD15	1.8 <sup>(4)</sup>	150	±5		
Analog	AVDDA1, AVDDA2, AVDDA3, DVDDD	1.8 <sup>(4)</sup>	190	±5	3	<200 ms
	AVDDA, DVDDD, AVDDT, AVDDA4, DVDDR	1.2	170	±5		

<sup>(1)</sup> Consult the TMS320C6472 power spreadsheet for your exact power requirements.

<sup>(2)</sup> CVDD and CVDD2 are 1 V @ 500 MHz, 1.1 V @ 625 MHz (I<sub>max</sub> = 4900 mA), and 1.2 V @ 700 MHz (I<sub>max</sub> = 9500 mA).

<sup>(3)</sup> DVDD18 voltage rail includes power required for external DDR2 memory.

<sup>(4)</sup> All 1.8-V rails may be combined and all 1.1-V rails may be combined; however, follow the filtering recommendations for each voltage rail in the *TMS320C6472 Hardware Design Guide* ([SPRAAQ4](#)).

**Table 2. Reference Design Parameters**

V <sub>in</sub>	5 V ± 10%
V <sub>out1</sub>	1 V ± 5% at 5 A
V <sub>out2</sub>	1.2 V ± 5% at 300 mA
V <sub>out3</sub>	3.3 V ± 5% at 1 A
V <sub>out4</sub>	1.8 V ± 5% at 1 A
V <sub>out5</sub>	1.2 V ± 5% at 1.6 A
DDR Termination	0.9 V at 3 A

### 3 Device Features

#### TPS54880

- Input Operating Voltage Range: 4.5 V to 18 V
- Up to 20-A Output Currents
- Supports Pre-Biased Outputs
- 0.5% 0.591-V Reference
- Three Selectable Thermally Compensated Short-Circuit Protection Levels
- Hiccup Restart From Faults
- Internal 5-V Regulator
- High- and Low-Side FET RDSON Current Sensing

#### TPS62200

- 350-mA, High-Performance LDO
- Low Quiescent Current: 38  $\mu$ A
- Excellent Load Transient Response

#### TPS62040

- 350-mA, High-Performance LDO
- Low Quiescent Current: 38  $\mu$ A
- Excellent Load Transient Response

#### TPS51200

- 3-A DDR Termination LDO
- VLDOIN Voltage Range: 1.1 V to 3.5 V
- Sink/Source Termination Regulator Includes Droop Compensation
- Requires Minimum Output Capacitance of 20- $\mu$ F (Typically 3  $\times$  10- $\mu$ F MLCCs) for Memory Termination Applications (DDR)
- PGOOD to Monitor Output Regulation and Remote Sensing (VOSNS)
- $\pm$ 10-mA Buffered Reference (REFOUT)
- Meets DDR, DDR2 JEDEC Specifications; Supports DDR3 and Low-Power DDR3/DDR4 VTT Applications

4 Schematic

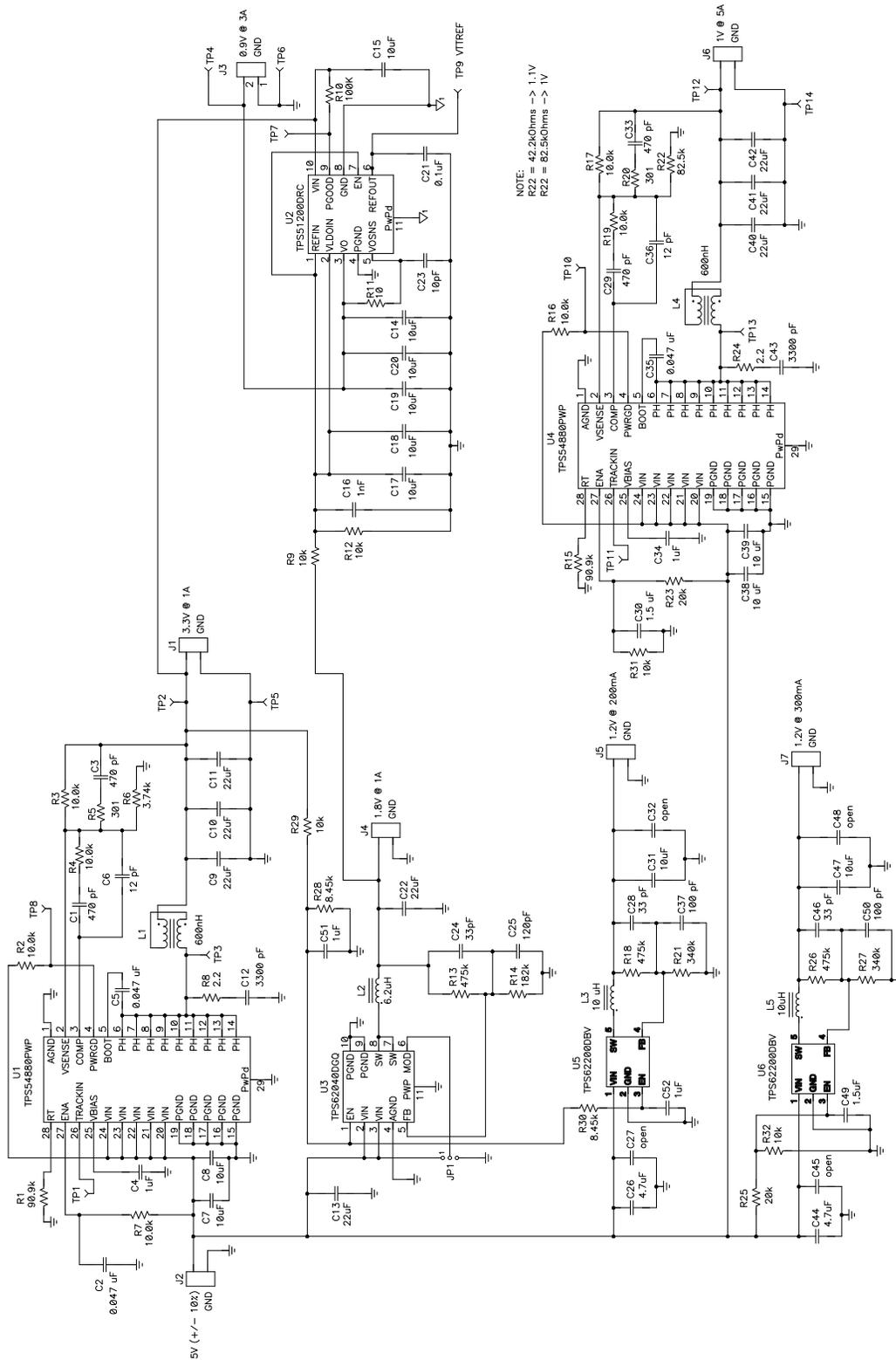


Figure 1. Schematic

## 5 Bill of Materials

**Table 3. PMP5176 Bill of Materials**

Count	RefDes	Value	Description	Size	Part Number	MFR
4	C1	470 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
3	C2	0.047 $\mu$ F	Capacitor, Ceramic, 50V, X7R, 10%	0603	Std	Std
	C3	470 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
1	C4	1.0 $\mu$ F	Capacitor, Ceramic, 25V, X5R, 20%	0603	Std	Std
	C5	0.047 $\mu$ F	Capacitor, Ceramic, 50V, X7R, 10%	0603	Std	Std
2	C6	12 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
4	C7	10 $\mu$ F	Capacitor, Ceramic, 25V, X5R, 20%	1210	Std	Std
	C8	10 $\mu$ F	Capacitor, Ceramic, 25V, X5R, 20%	1210	Std	Std
6	C9	22 $\mu$ F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
	C10	22 F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
	C11	22 F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
2	C12	3300 pF	Capacitor, Ceramic, 50V, X7R, 10%	0603	Std	Std
2	C13	22 F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
	C14	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
	C15	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
1	C16	1 NF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
	C17	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
	C18	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
	C19	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
	C20	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
1	C21	0.1 F	Capacitor, Ceramic, 25V, X7R, 10%	0603	Std	Std
	C22	22 F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
1	C23	10 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
1	C24	33 pF	Capacitor, Ceramic, 50V, C0G, 5%	0805	Std	Std
1	C25	120 pF	Capacitor, Ceramic, 50V, C0G, 5%	0805	Std	Std
2	C26	4.7 F	Capacitor, Ceramic, 10V, X5R, 20%	0805	Std	Std
2	C27	open	Capacitor, Ceramic	0805	Std	Std
2	C28	33 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
	C29	470 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
2	C30	1.5 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0603	Std	Std
7	C31	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
2	C32	open	Capacitor, Ceramic	1210	Std	Std
	C33	470 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
1	C34	1 F	Capacitor, Ceramic, 25V, X5R, 10%	0603	Std	Std
	C35	0.047 F	Capacitor, Ceramic, 50V, X7R, 10%	0603	Std	Std
	C36	12 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
2	C37	100 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
	C38	10 F	Capacitor, Ceramic, 25V, X5R, 20%	1210	Std	Std
	C39	10 F	Capacitor, Ceramic, 25V, X5R, 20%	1210	Std	Std
	C40	22 F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
	C41	22 F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
	C42	22 F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std
	C43	3300 pF	Capacitor, Ceramic, 50V, X7R, 10%	0603	Std	Std
	C44	4.7 F	Capacitor, Ceramic, 10V, X5R, 20%	0805	Std	Std
	C45	open	Capacitor, Ceramic	0805	Std	Std
	C46	33 pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
1	C47	10 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0805	Std	Std
	C48	open	Capacitor, Ceramic	1210	Std	Std
	C49	1.5 F	Capacitor, Ceramic, 6.3V, X5R, 20%	0603	Std	Std

**Table 3. PMP5176 Bill of Materials (continued)**

Count	RefDes	Value	Description	Size	Part Number	MFR
	C50	100 pF	Capacitor, Ceramic, 50V, COG, 5%	0603	Std	Std
2	C51	1 F	Capacitor, Ceramic, 25V, X5R, 20%	0805	Std	Std
	C52	1 F	Capacitor, Ceramic, 25V, X5R, 20%	0805	Std	Std
6	J1	ED1609-ND	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35 inch	ED1609	OT
	J2	ED1609-ND	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35 inch	ED1609	OT
1	J3	ED555/2DS	Terminal Block, 2-pin, 6-A, 3.5mm	0.27 x 0.25 inch	ED555/2DS	OT
	J4	ED1609-ND	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35 inch	ED1609	OT
	J5	ED1609-ND	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35 inch	ED1609	OT
	J6	ED1609-ND	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35 inch	ED1609	OT
	J7	ED1609-ND	Terminal Block, 2-pin, 15-A, 5.1mm	0.40 x 0.35 inch	ED1609	OT
1	JP1		Header, 3-pin, 100mil spacing, (36-pin strip)	0.100 x 3"	PTC36SAAN	Sullies
2	L1	600 NH	Inductor, SMT, 2.53mΩ, 12.6A sat,10.7A rms	0.340 x 0.250	PA0277	Pulse
1	L2	6.2 μH	Inductor, SMT, 45mΩ, 1.8A rms	0.224",CDRH5D28-6R2"	Sumida	
2	L3	10 μH	Inductor, SMD, 128mΩ, 1A rms	0.185 x 0.185	CDRH4D28-100	Sumida
	L4	600 nH	Inductor, SMT, 2.53mΩ, 12.6A sat,10.7A rms	0.340 x 0.250	PA0277	Pulse
	L5	10 μH	Inductor, SMD, 128mΩ, 1A rms	0.185 x 0.185	CDRH4D28-100	Sumida
1	R1	90.9k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
4	R2	10.0k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
	R3	10.0k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
	R4	10.0k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
2	R5	301	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R6	3.74k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
	R7	10.0k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
2	R8	2.2	Resistor, Chip, 2.2-Ω, 1/4-W, 1%	1206	ERJ-8RQF2R2	Panasonic
1	R9	10k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R10	100K	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R11	10	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R12	10k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R13	475k	Resistor, Chip, 1/10W, 1%	0805	Std	Std
1	R14	182k	Resistor, Chip, 1/10W, 1%	0805	Std	Std
1	R15	90.9k	Resistor, Chip, 90.9 kΩ, 1/16-W, 1%	0603	Std	Std
1	R16	10.0k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R17	10.0k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
2	R18	475k	Resistor, Chip, 1/16-W, 1%	0603	Std	Std
1	R19	10.0k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
	R20	301	Resistor, Chip, 1/16W, 1%	0603	Std	Std
2	R21	340k	Resistor, Chip, 1/16-W, 1%	0603	Std	Std
1	R22	82.5k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R23	20k	Resistor, Chip, 10.0 kΩ, 1/16-W, 1%	0603	Std	Std
	R24	2.2	Resistor, Chip, 2.2-Ω, 1/4-W, 1%	1206	ERJ-8RQF2R2	Panasonic
1	R25	20k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
	R26	475k	Resistor, Chip, 1/16-W, 1%	0603	Std	Std
	R27	340k	Resistor, Chip, 1/16-W, 1%	0603	Std	Std
2	R28	8.45k	Resistor, Chip, 1/10W, 1%	0805	Std	Std
1	R29	10k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
	R30	8.45k	Resistor, Chip, 1/10W, 1%	0805	Std	Std
1	R31	10k	Resistor, Chip, 10.0 kΩ, 1/16W, 1%	0603	Std	Std
1	R32	10k	Resistor, Chip, 1/10W, 1%	0805	Std	Std
1	SH1		Short jumper			
8	TP1		Test Point, Red, 1mm	0.038", 240–345"	Farnell	
	TP2		Test Point, Red, 1mm	0.038", 240–345"	Farnell	

**Table 3. PMP5176 Bill of Materials (continued)**

Count	RefDes	Value	Description	Size	Part Number	MFR
	TP3		Test Point, Red, 1mm	0.038", 240–345"	Farnell	
2	TP4	5010	Test Point, Red, Thru Hole	0.125 x 0.125 inch	5010	Keystone
2	TP5		Test Point, Black, 1mm	0.038", 240–333"	Farnell	
1	TP6	5011	Test Point, Black, Thru Hole	0.125 x 0.125 inch	5011	Keystone
1	TP7	5012	Test Point, White, Thru Hole	0.125 x 0.125 inch	5012	Keystone
	TP8		Test Point, Red, 1mm	0.038", 240–345"	Farnell	
	TP9	5010	Test Point, Red, Thru Hole	0.125 x 0.125 inch	5010	Keystone
	TP10		Test Point, Red, 1mm	0.038", 240–345"	Farnell	
	TP11		Test Point, Red, 1mm	0.038", 240–345"	Farnell	
	TP12		Test Point, Red, 1mm	0.038", 240–345"	Farnell	
	TP13		Test Point, Red, 1mm	0.038", 240–345"	Farnell	
	TP14		Test Point, Black, 1mm	0.038", 240–333"	Farnell	
2	U1	TPS54880PWP	IC, 4-6V Input, 8-A Output Tracking Sync. Buck PWM Switcher w/Integrated FETs	HTSSOP-28	TPS54880PWP	TI
1	U2	TPS51200DRC	IC, Sink/Source DDR Termination Regulator	DRC	TPS51200DRC	TI
1	U3	TPS62040DGQ	IC, High-Efficiency Step-Down Low Power DC-DC Converter, Adj V	DGS10	TPS62040DGQ	TI
	U4	TPS54880PWP	IC, 4-6V Input, 8-A Output Tracking Sync. Buck PWM Switcher w/Integrated FETs	HTSSOP-28	TPS54880PWP	TI
2	U5	TPS62200DBV	IC, Switching Buck Converter, 1.8-V, 300-mA	SOT23-5		TI
	U6	TPS62200DBV	IC, Switching Buck Converter, 1.8-V, 300-mA	SOT23-5		TI
<p>Notes: These assemblies are ESD sensitive, ESD precautions shall be observed.</p> <ol style="list-style-type: none"> <li>1. These assemblies must be clean and free from flux and all contaminants. Use of unclean flux is unacceptable.</li> <li>2. These assemblies must comply with workmanship standards IPC-A-610 Class 2.</li> <li>3. Reference designators marked with an asterisk (***) cannot be substituted. All other components can be substituted with equivalent MFG's components.</li> </ol>						

## 6 Power-Up Waveforms

CH1 – Vout 4, CH2 – DDR termination, CH3 – Vout 5, CH4 – Vout 3  
 (2 V/div, 1 V/div, 1 V/div, 2 V/div, 4 ms/div)

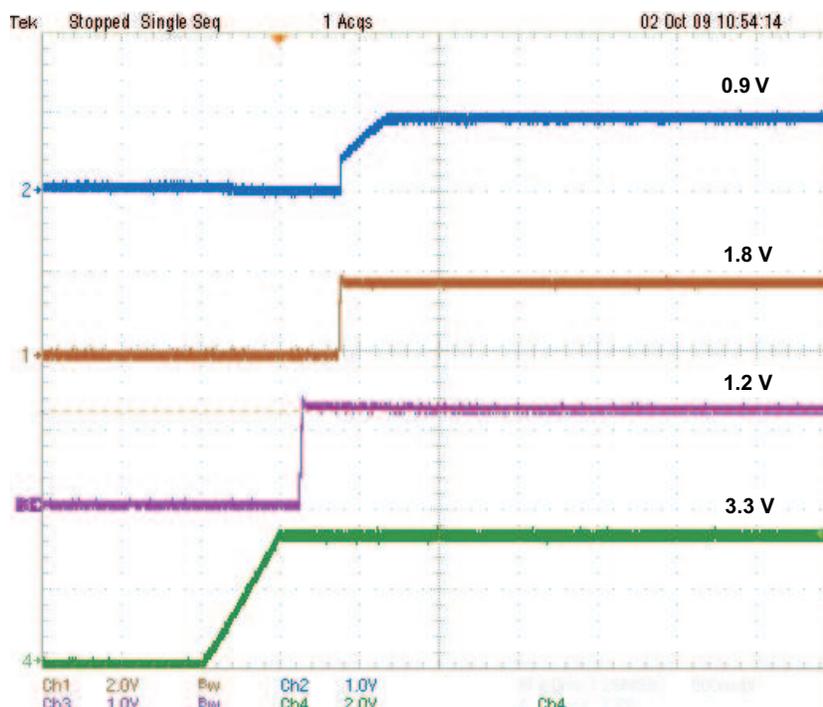


Figure 2. Power-Up Waveform, Part 1

CH1 – Vout 2, CH2 – Vout 1, CH3 – Vout 5, CH4 – Vout 3  
 (1 V/div, 1 V/div, 1 V/div, 1 V/div 4 ms/div)

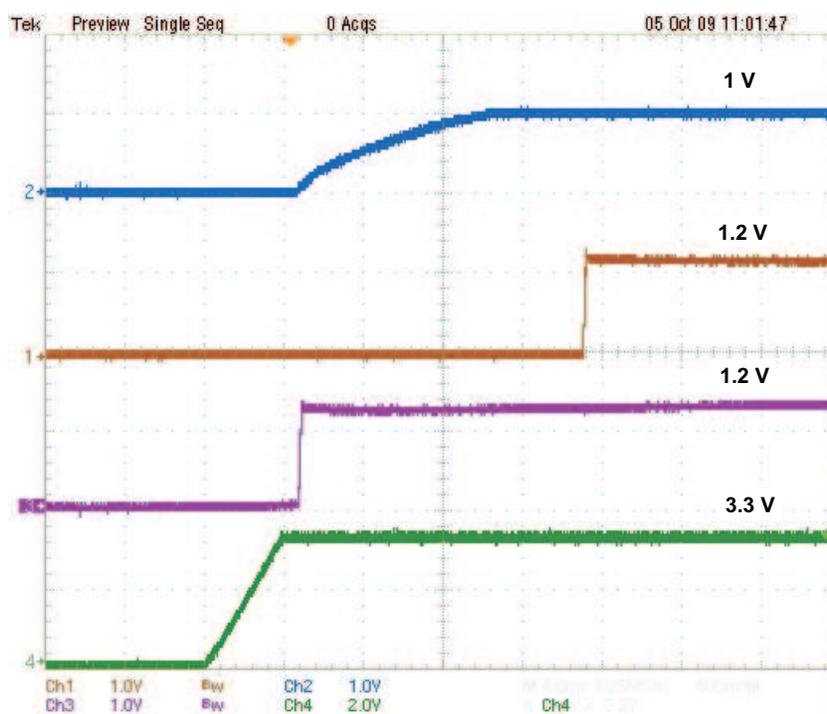


Figure 3. Power-Up Waveform, Part 2

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>	Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>	Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Energy	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Space, Avionics & Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>	Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2010, Texas Instruments Incorporated