

Feedforward Capacitor Makes TPS61021A Boost Converter Fast and Stable

Helen Chen

Low-Power DC/DC Converters

ABSTRACT

A common method to improve the stability and bandwidth of an internally-compensated boost converter is to add a feedforward capacitor (C_{ff}) to the circuit. This capacitor is placed across the high-side feedback resistor. It introduces a zero f_z and a pole f_p into the control loop and helps improve the phase margin and the load transient. This application note describes how to choose this feedforward capacitor for the internally-compensated TPS61021A boost converter.

Contents

1	Introduction	2
2	Feedback Network With the Feedforward Capacitor	2
3	Design Example With the TPS61021A Boost Converter	3
4	Conclusion	8

List of Figures

1	Feedback Network With Feedforward Capacitor C_{ff}	2
2	TPS61021A Boost Converter Without the C_{ff}	3
3	Loop Bode Plot of the TPS61021A Boost Converter Without C_{ff}	3
4	Loop Bode Plot of the TPS61021A Boost Converter with $C_{ff} = 10$ pF	4
5	Load Transient Comparison With and Without $C_{ff} = 10$ pF ($V_{IN} = 2.4$ V, $I_O = 1$ A to 2 A)	5
6	TPS61021A Boost Converter With $C_6 = 100$ μ F (no C_{ff})	5
7	Loop Bode Plot of the TPS61021A Boost Converter in Figure 6 ($V_{IN} = 2.4$ V, $I_O = 2$ A)	6
8	Load Transient Response in Figure 6 ($V_{IN} = 2.4$ V, $I_O = 0$ A to 2 A)	6
9	Loop Bode Plot of the TPS61021A Boost Converter With $C_{ff} = 68$ pF ($V_{IN} = 2.4$ V, $I_O = 2$ A)	7
10	Load Transient Response in Figure 6 With $C_{ff} = 68$ pF ($V_{IN} = 2.4$ V, $I_O = 0$ A to 2 A)	8
11	Output Load Step Response vs Loop Phase Margin	8

List of Tables

1	Phase Boost of a Single Real Zero f_z	4
---	---	---

1 Introduction

An internally-compensated dc-dc converter simplifies the design process while minimizing the number of the external components at the same time. But this simplification narrows the ability of a designer to optimize the stability and the load transient of the converter. Adding a feedback capacitor in the feedback network is a good way to make up for the deficiencies. Using the measured load transient or bode plot of a boost converter, a feedforward capacitor can be chosen such that the load transient can be significantly improved while still maintaining an adequate phase margin.

2 Feedback Network With the Feedforward Capacitor

Figure 1 shows the feedback network with the feedforward capacitor C_{ff} . C_{ff} introduces a zero and a pole into the control loop. The zero f_z and the pole f_p can be calculated using Equation 1:

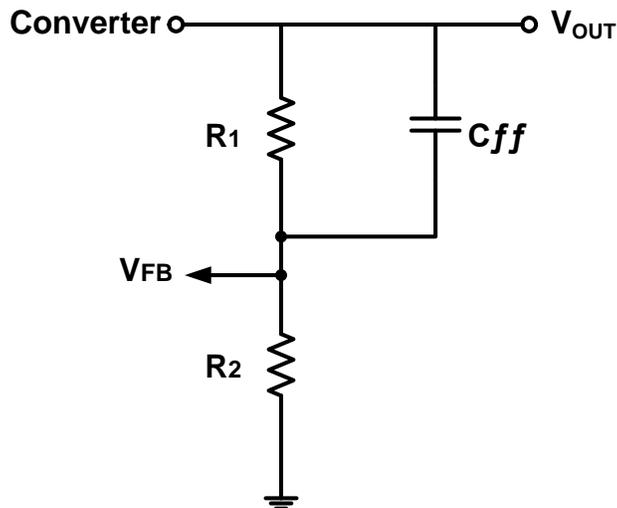


Figure 1. Feedback Network With Feedforward Capacitor C_{ff}

$$f_z = \frac{1}{2\pi \times R1 \times C_{ff}} \quad (1)$$

$$f_p = \frac{1}{2\pi \times C_{ff}} \left(\frac{1}{R1} + \frac{1}{R2} \right) \quad (2)$$

Equation 2 shows the frequency of f_z is lower than the frequency of f_p . Increasing the value of C_{ff} shifts the zero and the pole to lower frequencies, while decreasing the value of C_{ff} shifts the zero and the pole to higher frequencies. C_{ff} shifts the crossover frequency of the converter to a higher frequency. If the value of the C_{ff} is too large, it will make the new crossover frequency very high and results in insufficient phase margin and stability problems. Calculate C_{ff} properly according to the different application conditions. If the phase margin is low while the loop response is fast enough for the application, then a relatively smaller C_{ff} can be chosen to boost the phase margin while making the bandwidth increase a little. If the loop response is too slow while the phase margin is high enough for the application, then a higher C_{ff} can be chosen to boost the bandwidth while keeping enough phase margin.

3 Design Example With the TPS61021A Boost Converter

3.1 Calculating the Feedforward Capacitor for Higher Phase Margin

Figure 2 shows the schematic of the TPS61021A boost converter without the feedforward capacitor.

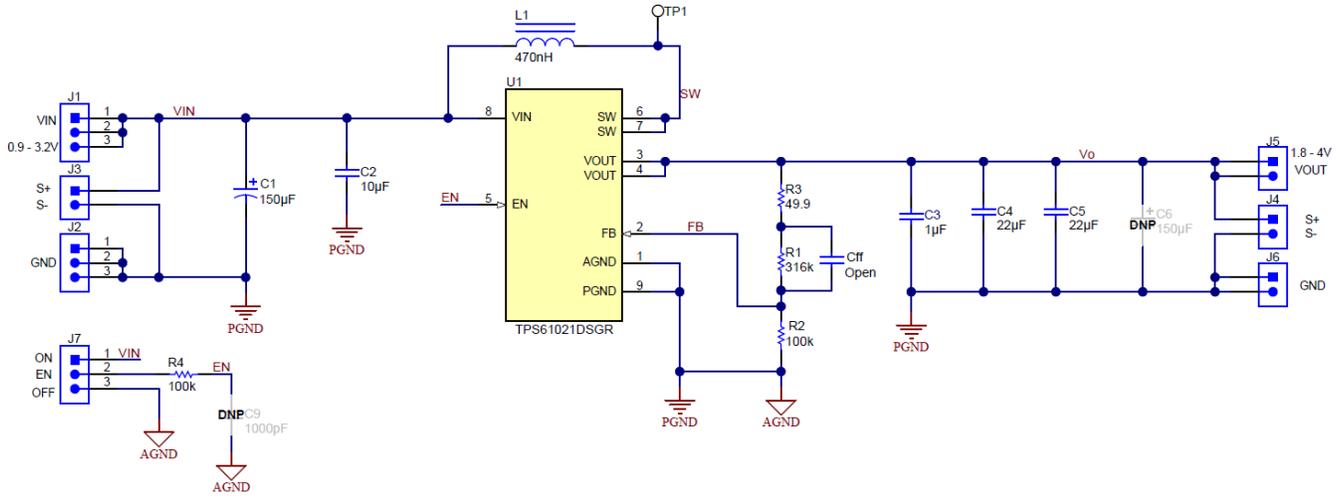


Figure 2. TPS61021A Boost Converter Without the C_{ff}

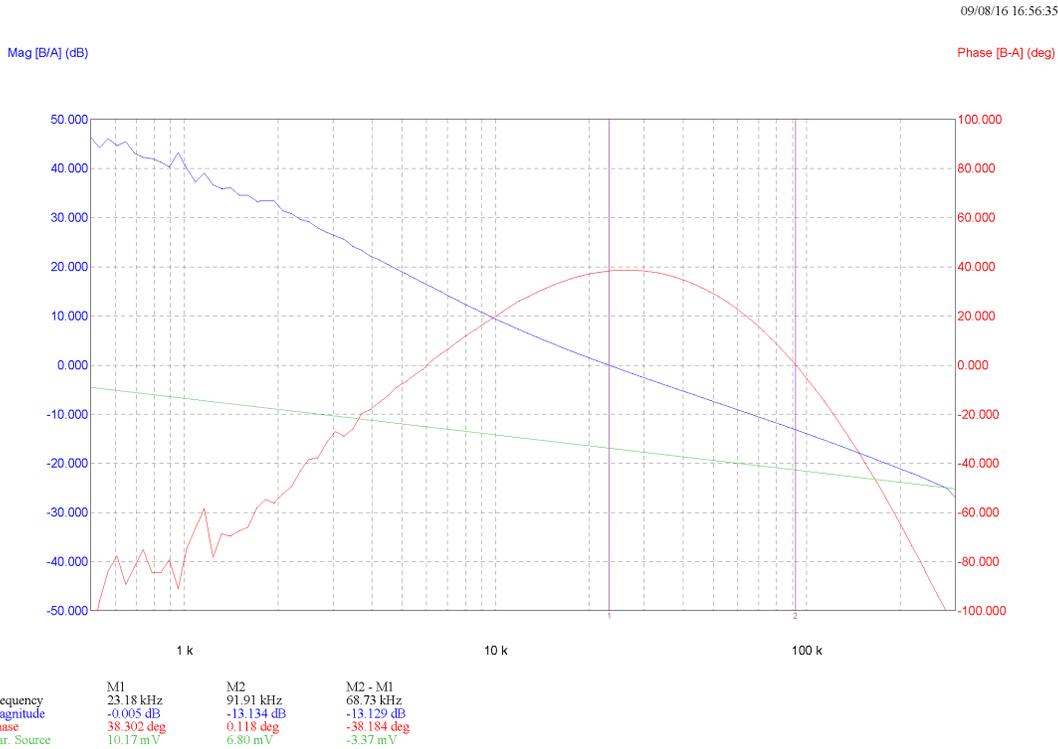


Figure 3. Loop Bode Plot of the TPS61021A Boost Converter Without C_{ff}

The most accurate way to measure the crossover frequency of a dc-dc converter is by using the network analyzer. When such an equipment is available, the crossover frequency can be quickly measured. Figure 3 shows the loop bode plot of the TPS61021A boost converter in Figure 2 using the network analyzer AP300. The phase margin of the boost converter is 38°, the crossover frequency f_{c_noCff} is around 23 kHz without the feedforward capacitor.

If the target phase margin is 60°, then there is a 22° gap between the tested value and the target value. Putting a zero at around $2 \times f_{c_noCff}$ (refer to Table 1) can meet this design target. So we can get:

$$f_z = \frac{1}{2\pi \times R1 \times C_{ff}} = 2 \times f_{c_noCff} \quad (3)$$

$$C_{ff} = \frac{1}{2\pi \times R1 \times 2f_{c_noCff}} \approx 10 \text{ pF}$$

where

- $f_{c_noCff} = 23.18 \text{ kHz}$
 - $R1 = 316 \text{ k}\Omega$
- (4)

Table 1. Phase Boost of a Single Real Zero f_z

Frequency	$(1/10) \times f_z$	$(1/8) \times f_z$	$(1/4) \times f_z$	$(1/2) \times f_z$	f_z	$2 \times f_z$	$4 \times f_z$	$8 \times f_z$	$10 \times f_z$
Phase Boost	5.7°	7.1°	14°	26.5°	45°	63.4°	75.9°	82.8°	84.3°

Figure 4 shows the loop bode plot of the TPS61021A boost converter with 10-pF feedforward capacitor. The new crossover frequency is 28.8 kHz, close to the original crossover frequency. The new phase margin is 61°, about 23° higher than the original value, which is the same as previously estimated.

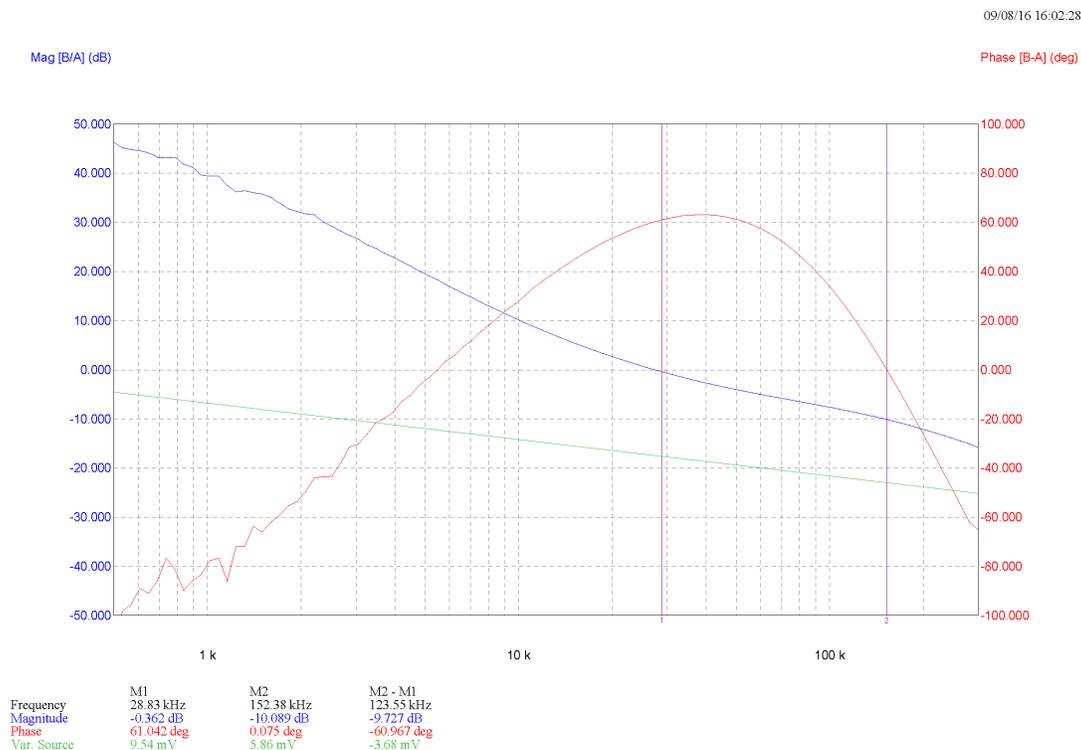


Figure 4. Loop Bode Plot of the TPS61021A Boost Converter with $C_{ff} = 10 \text{ pF}$

Figure 5 shows the load transient comparison with and without the 10-pF feedforward capacitor. The output voltage deviation during the load transient is 240 mV without the feedforward capacitor. With a 10-pF feedforward capacitor, the output voltage deviation can be reduced to 195 mV.

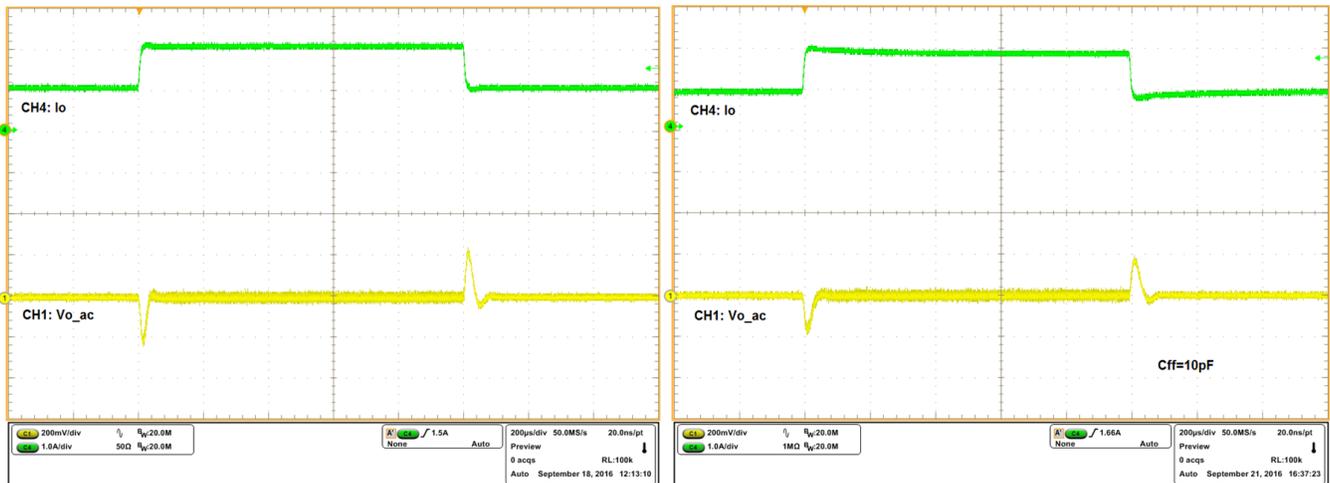


Figure 5. Load Transient Comparison With and Without $C_{ff} = 10 \text{ pF}$ ($V_{IN} = 2.4 \text{ V}$, $I_O = 1 \text{ A to } 2 \text{ A}$)

3.2 Calculating the Feedforward Capacitor for Faster Loop Response With $C_6 = 100 \mu\text{F}$

In some applications, the customer will add electrolytic capacitors or tantalum capacitors at the output side to sustain the big pulsed load current and avoid the output voltage from dropping too much. Figure 6 shows the schematic of the TPS61021A boost converter with an extra 100- μF tantalum capacitor (C_6) at the output side.

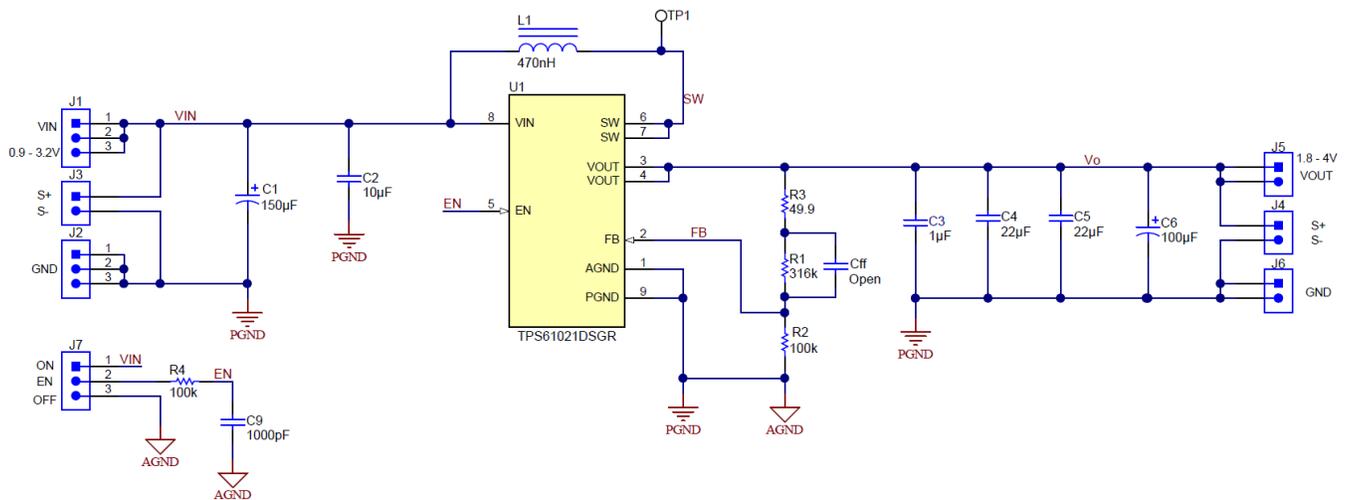


Figure 6. TPS61021A Boost Converter With $C_6 = 100 \mu\text{F}$ (no C_{ff})

Figure 7 shows the loop bode plot of the TPS61021A boost converter in Figure 6. With an extra 100- μ F tantalum capacitor C6 at the output side, the crossover frequency f_{c_noCff} decreases to 9 kHz.

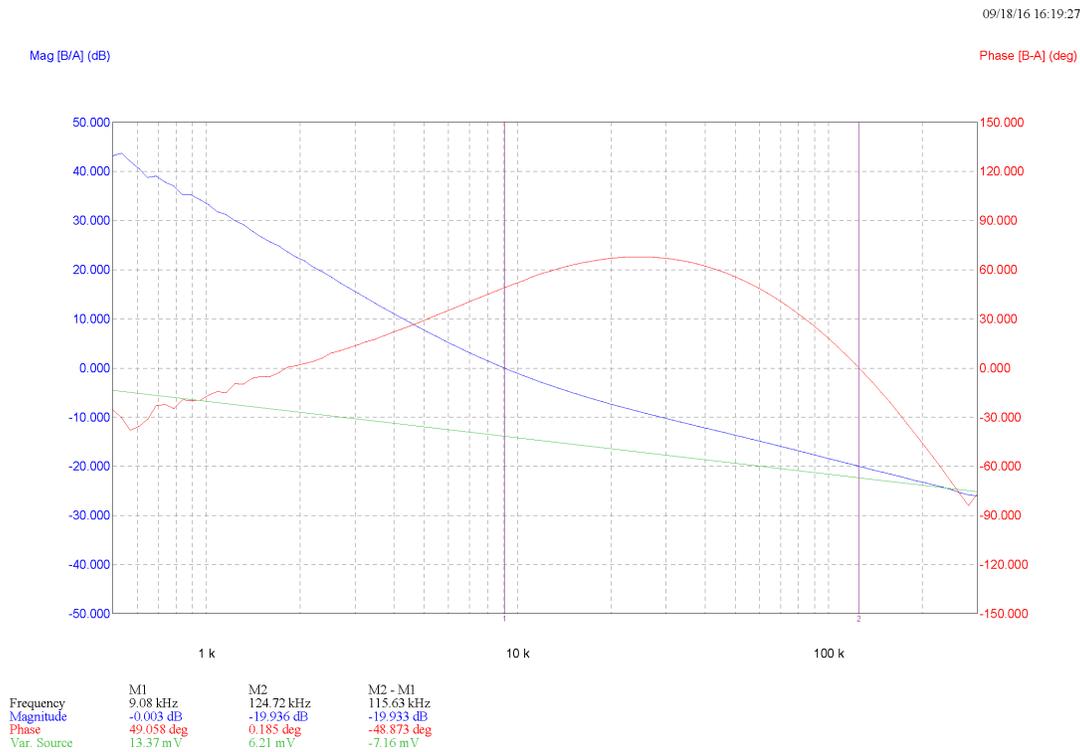


Figure 7. Loop Bode Plot of the TPS61021A Boost Converter in Figure 6 ($V_{IN} = 2.4$ V, $I_O = 2$ A)

Figure 8 shows the load transient response of the TPS61021A boost converter in Figure 6. The output voltage deviation during the load transient is 400 mV.

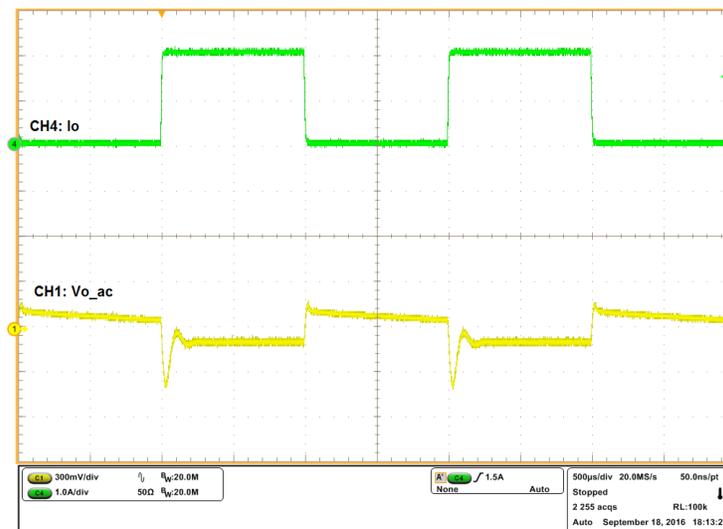


Figure 8. Load Transient Response in Figure 6 ($V_{IN} = 2.4$ V, $I_O = 0$ A to 2 A)

To further reduce the output voltage deviation, a feedforward capacitor can be added to increase the crossover frequency. An effective way of increasing the bandwidth is to put the zero f_z at a frequency equal to or lower than the crossover frequency f_{c_noCff} . So we can get:

$$f_z = \frac{1}{2\pi \times R1 \times C_{ff}} \leq f_{c_noCff} \tag{5}$$

$$C_{ff} = \frac{1}{2\pi \times R1 \times f_{c_noCff}} \geq 56 \text{ pF}$$

where

- $f_{c_noCff} = 9.08 \text{ kHz}$ (6)

A large C_{ff} will shift the crossover frequency to a very high frequency while moving the maximum phase boost point to a lower frequency. So there is an upper limit for the C_{ff} selection. If the minimum phase margin requirement is 45° , then the value of the feedforward capacitor should be lower than the value corresponding to the 45° phase margin. This corresponding C_{ff} value can be determined by testing. Generally, it is not recommended to increase the C_{ff} to a value which is much greater than the value calculated using Equation 6. So $C_{ff} = 68 \text{ pF}$ is chosen in this design example.

Figure 9 shows the loop bode plot of the TPS61021A boost converter with a 68-pF feedforward capacitor. The new crossover frequency is 20.9 kHz, more than twice the original bandwidth. The new phase margin is 104° , also much greater than the original phase margin.

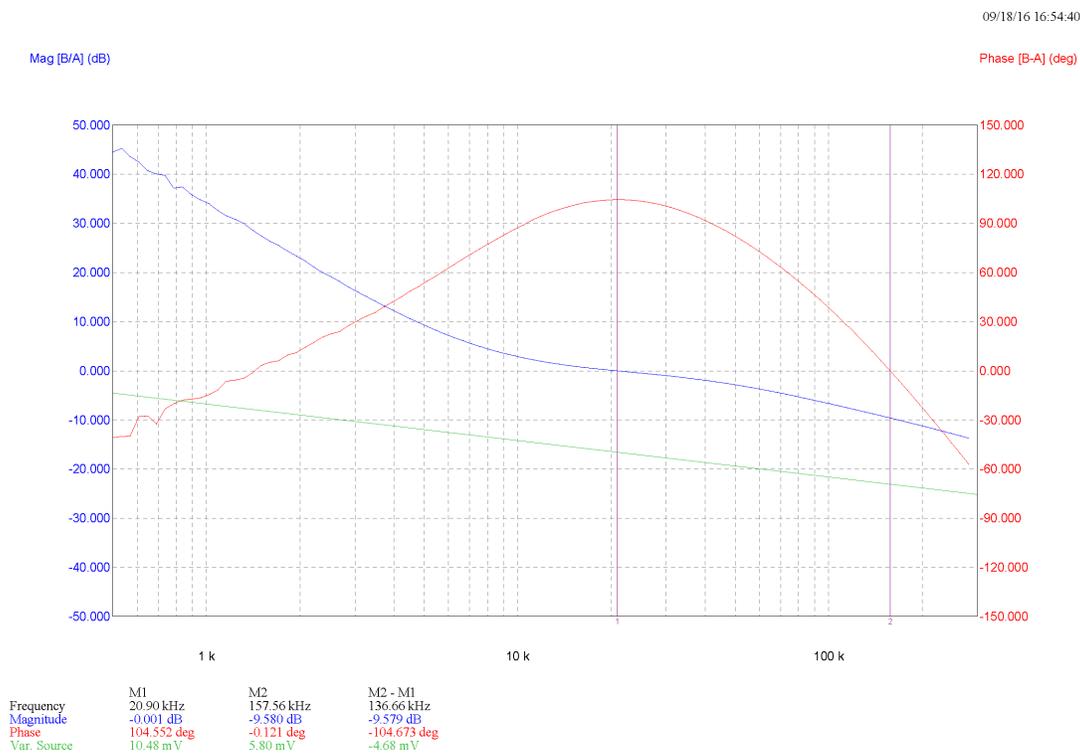


Figure 9. Loop Bode Plot of the TPS61021A Boost Converter With $C_{ff} = 68 \text{ pF}$ ($V_{IN} = 2.4 \text{ V}$, $I_O = 2 \text{ A}$)

Figure 10 shows the load transient response of the TPS61021A boost converter with a 68-pF feedforward capacitor. The output voltage deviation during the load transient is reduced to 250 mV, which is about 150 mV lower than that of the no C_{ff} condition.

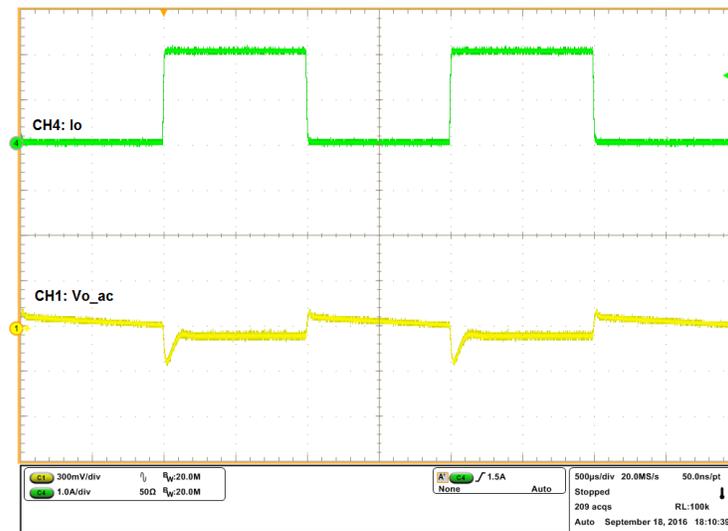


Figure 10. Load Transient Response in Figure 6 With $C_{ff} = 68 \text{ pF}$ ($V_{IN} = 2.4 \text{ V}$, $I_O = 0 \text{ A to } 2 \text{ A}$)

3.3 Determining the Crossover Frequency and Phase Margin by Oscilloscope

In the lack of a network analyzer condition, the crossover frequency and phase margin of the converter can be estimated through the load step waveforms tested by the oscilloscope. The article *Evaluation and Performance Optimization of Fully Integrated DC/DC Converters* (Topic 7 of the 2006 Portable Power Design Seminar) described the relationship of the load step waveform with the crossover frequency and the phase margin. The output voltage load step response of the converter gives the information of the loop stability (refer to Figure 11).

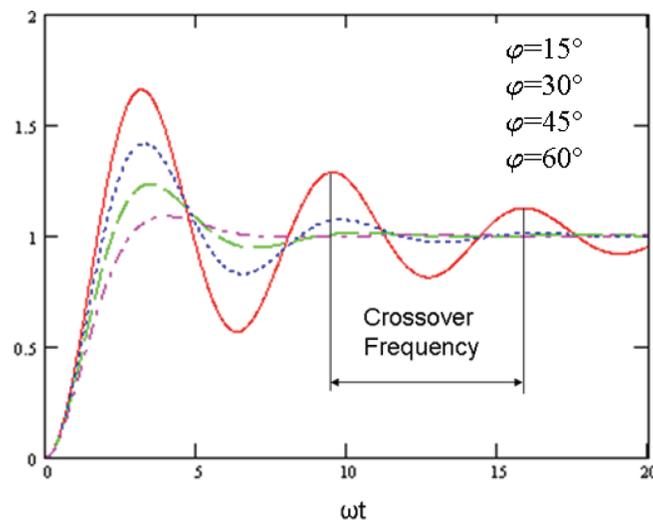


Figure 11. Output Load Step Response vs Loop Phase Margin

4 Conclusion

The feedforward capacitor used in the feedback network improves the performance of the internally-compensated boost converters. With the measured loop bode plot by the network analyzer, the value of the feedforward capacitor can be properly calculated to improve the phase margin or increase the bandwidth. In the lack of the network analyzer condition, the crossover frequency and phase margin of the converter can be determined by the load step waveforms.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com