

# Achieve 20-A Circuit Protection and Space Efficiency Using Paralleled eFuses

Rakesh Panguloori, Venkat Nandam

## ABSTRACT

Today Texas Instrument's eFuse devices are sought-after to replace discrete frontend protection circuits in many applications. These eFuses are available in the current range from 0.1 A to 12 A. However, certain applications like servers and communication equipment demand currents in the range of several tens of amperes. In general, device paralleling is seen as the first option by the system designers to scale the system for higher current requirements and better thermal management. While these devices are operated in parallel, it is essential that individual e-fuse share equal or near to equal load current for proper system operation and dynamic response. This application note describes the design considerations and performance characteristics of using eFuses in parallel configuration. An example of paralleling four eFuse devices to support 20-A load current is considered here to demonstrate load current sharing performance and to illustrate device behavior during transient overload, short-circuit events.

## Contents


1	Introduction .....	2
2	Parallel Operation of eFuse .....	3
3	Application Circuit Schematic for 20-A Load Support.....	6
4	Performance Results .....	7
5	Comparison with External FET Solution .....	12
6	Conclusion .....	13

## List of Figures

1	TPS259241 Block Diagram.....	2
2	Number of "N" eFuse Devices Connected in Parallel Configuration .....	3
3	Equivalent Circuit of 'N' Devices in Steady-State Operation .....	4
4	Equivalent Circuit of Parallel-Connected eFuses When One Device Reaches Current Limit .....	5
5	TPS259241 Devices Connected in Parallel to Support 20-A Load Current.....	6
6	Steady-State Current Sharing of Four-Phase eFuse Parallel Configuration .....	7
7	Current Sharing Among Two Devices During Output Voltage Ramp .....	8
8	Current Profile of Two Devices During Shut-Off .....	8
9	Load Turn-On Behavior of 20-A eFuse With Enable-On .....	9
10	Load Turn-Off Behavior of 20-A eFuse With Enable-Off .....	9
11	20-A Load Step-Up Response of Four-Phase eFuse Parallel Configuration.....	10
12	20-A Load Step-Down Response of Four-Phase eFuse Parallel Configuration .....	10
13	Transient Overload Response of 20-A eFuse .....	11
14	Output Short-Circuit Response of 20-A eFuse .....	11
15	Recovery From Output Short Circuit.....	12

## 1 Introduction

In this application, the TPS259241 device from the TPS2592xx family is considered for parallel operation. The TPS259241 device has an integrated power switch which is controlled to manage current, voltage, and the output voltage ramp profile to a connected load. [Figure 1](#) shows the block diagram of the TPS259241 device. The basic operation of eFuse is as follows. Once the eFuse is enabled, the integrated power switch is controlled in linear-mode to match the desired output voltage ramp. After a successful start-up sequence, integrated power switch is fully turned-on just like a power switch to minimize voltage drop in the power path. If at any point the load current reaches the set current-limit level  $I_{LIM}$ , the gate control transits the integrated power switch into linear mode. This increases ON resistance and corresponding voltage drop across the eFuse to provide constant output current. The inherent current source characteristic of eFuse helps to a great extent for successful parallel operation.

 

**Figure 1. TPS259241 Block Diagram**

The ramp time ( $T_{dVdT}$ ) of output voltage can be adjusted by configuring the external capacitor ( $C_{dVdT}$ ) at dVdT pin using [Equation 1](#). Similarly, the current limit ( $I_{LIM}$ ) which the device needs to restrict under fault/over load conditions can be configured by setting the current-limit resistor ( $R_{ILIM}$ ) as per [Equation 2](#).

$$T_{dVdT} = 10^6 \times V_{IN} \times (C_{dVdT} + 70 \text{ pF}) \quad (1)$$

$$R_{ILIM} = \frac{I_{LIM} - 0.7}{3 \times 10^{-5}} \quad (2)$$

## 2 Parallel Operation of eFuse

When eFuses are operated in a parallel configuration, load sharing among the eFuses is a major challenge. A successful parallel operation ensures equal current sharing among the parallel-connected devices both under steady-state and dynamic conditions. Figure 2 shows the number of “N” eFuse devices connected in parallel configuration. The input and the output terminals are connected together. The following subsections explain how the parallel-connected eFuse devices work in steady state, current limit, and startup modes.

 



Figure 2. Number of “N” eFuse Devices Connected in Parallel Configuration

### 2.1 Operation in Steady-State

When none of the eFuse hits the current limit, the ON-resistance  $R_{DS(on)}$  of the eFuse becomes the equivalent circuit as shown in Figure 3. During steady-state operation, the current sharing is decided by the  $R_{DS(on)}$  mismatch among the parallel-connected eFuse devices. The device having the lowest  $R_{DS(on)}$  ( $R_{DS(on)_min}$ ) shares the highest current ( $I_{MAX}$ ) than the rest of the devices. For example, one device in the parallel configuration has the lowest  $R_{DS(on)_min}$  and the rest of the devices have the highest  $R_{DS(on)_max}$ . The maximum current ( $I_{MAX}$ ) shared by a device from overall load current ( $I_{LOAD}$ ) can be obtained using Equation 3.

$$I_{MAX} = \frac{\left( \frac{R_{DS(on)_max}}{(N-1)} \right)}{R_{DS(on)_min} + \left( \frac{R_{DS(on)_max}}{(N-1)} \right)} \times I_{LOAD} \quad (3)$$

The  $R_{DS(on)}$  variation for a particular device can be found from the datasheet to calculate the current sharing imbalance. However, the self-heating effect due to positive temperature characteristics of the MOSFET helps to a certain extent towards equal load current distribution in parallel applications. The device with the lowest  $R_{DS(on)}$  conducts slightly more load current which leads to a higher junction temperature. This increases ON resistance and slightly reduces its current. A stable operating point is achieved with near to equal current sharing among the parallel-connected eFuses.

 

**Figure 3. Equivalent Circuit of 'N' Devices in Steady-State Operation**

## 2.2 Operation When One or More Devices Reach the Current Limit

As discussed in [Section 2.1](#), due to the mismatch in the device parameters, one or more eFuses in a parallel configuration may enter current-limit mode. In such a scenario, the internal closed current loop aids in proper system operation. [Figure 4](#) shows the equivalent circuit of N parallel-connected eFuses with one or more devices hitting the current-limit. When device #1 reaches the current-limit level, its control circuitry regulates current to the programmed  $I_{LIM}$  value. To facilitate this, the gate drive to its internal integrated power switch is reduced; causing its ON resistance and corresponding voltage drop to increase. This causes the load current to steer towards the other device in parallel, forcing load sharing. In order to achieve this accurately to a larger extent, it becomes necessary to have same programmed current limit for all the devices in parallel configuration. One way to do that is to connect the  $I_{LIM}$  pins of all the parallel-connected eFuses and use a single equivalent current programming resistor ( $R_{ILIM,eq}$ ). This avoids any mismatch in current-limit setting among the devices that could arise due to tolerances in the current-limit resistors. The equivalent current-limit resistor in 'N' array parallel configuration can be calculated using [Equation 4](#).

$$R_{ILIM,eq} = \frac{I_{LIM} - 0.7}{N \times 3 \times 10^{-5}}$$

where

- $R_{ILIM,eq}$  is the equivalent current-limit programming resistor
- $I_{LIM}$  is the individual eFuse current limit

(4)

 


Figure 4. Equivalent Circuit of Parallel-Connected eFuses When One Device Reaches Current Limit

### 2.3 Operation During Startup

It is important to have equal current sharing among the parallel-connected eFuses during startup to ensure successful startup. Current sharing during startup is dependent on the threshold voltage mismatch among the integrated power switches of eFuses. However, eFuses are generally used for output slew control to limit the inrush current and hence these are slow turn-on devices. The gate drive of eFuse controls the integrated power switch to match the output ramp rate set at the dVdT pin. To have synchronized operation, you must connect “EN/UVLO” pins of all the parallel-connected eFuses. Similarly dVdT pins of all the eFuses should be connected together to ensure uniform output ramp rate and equal dynamic power stress. The equivalent dVdT capacitor in ‘N’ array parallel configuration to achieve output voltage ramp time  $T_{dVdT}$  as that of a single device is calculated using Equation 5.

$$C_{dVdT\_eq} = \left( \frac{N \times I_{dVdT} \times GAIN_{dVdT} \times T_{dVdT}}{V_{IN}} \right) - (N \times C_{INT})$$

where

- $C_{dVdT\_eq}$  is the equivalent capacitor at the dVdT pin
- $I_{dVdT} = 220 \text{ nA}$  (typ)
- $GAIN_{dVdT} = 4.85$
- $C_{INT} = 70 \text{ pF}$  (typ)
- $V_{IN}$  is the input voltage

(5)

### 3 Application Circuit Schematic for 20-A Load Support

Figure 5 illustrates the TPS259241 circuit schematic.

 



Figure 5. TPS259241 Devices Connected in Parallel to Support 20-A Load Current

## 4 Performance Results

In this section, test results are presented to demonstrate eFuse performance in a parallel configuration. [Figure 6](#) shows the current sharing performance of four-phase eFuse parallel configuration in steady-state operation. The difference between the average load current and the current of any phase is within  $\pm 70$  mA in the whole load range. The maximum current sharing error at full load is less than 3%.

**Table 1. Design Parameters**

Design Parameter	Example Value
Input voltage range, $V_{IN}$	12 V
Undervoltage lockout set point, $V_{(UV)}$	10.8 V
Overvoltage protection set point, $V_{(OV)}$	Default: $V_{OVC} = 15$ V
Current limit, $I_{OL} = I_{ILIM}$	20 A
Load capacitance, $C_{OUT}$	10 $\mu$ F
Load, $R_L$	0.6 $\Omega$

 

**Figure 6. Steady-State Current Sharing of Four-Phase eFuse Parallel Configuration**

 


Figure 7. Current Sharing Among Two Devices During Output Voltage Ramp

 


Figure 8. Current Profile of Two Devices During Shut-Off

 


Figure 9. Load Turn-On Behavior of 20-A eFuse With Enable-On

 


Figure 10. Load Turn-Off Behavior of 20-A eFuse With Enable-Off

 


Figure 11. 20-A Load Step-Up Response of Four-Phase eFuse Parallel Configuration

 


Figure 12. 20-A Load Step-Down Response of Four-Phase eFuse Parallel Configuration

 


Figure 13. Transient Overload Response of 20-A eFuse

 
 


Figure 14. Output Short-Circuit Response of 20-A eFuse


**Figure 15. Recovery From Output Short Circuit**

## 5 Comparison with External FET Solution

In this section, the basic space-efficiency comparison between the eFuse solution and the external FET solution is carried out for a 20-A load circuit protection. Only the critical space occupying components are considered and are shown in Table 2. The eFuse solution uses four TPS259241 devices, each are 3 mm × 3 mm and occupies a space of 36 mm<sup>2</sup> on the board. The external FET solution, for example, a TPS24720 hot-swap controller with two external FETs (CSD16401Q5, SON package, and 5 mm × 6mm) and a current sense resistor (1 W, 1210 package, and 3.2 mm × 2.5 mm) occupies 77 mm<sup>2</sup> on the board.

**Table 2. Area of Critical Space Occupying Components**

Component	eFuse Solution		External FET Solution	
	Part Count	Area (mm <sup>2</sup> )	Part Count	Area (mm <sup>2</sup> )
Controller IC	4	3 × 3	1	3 × 3
External FET	0	0	2	5 × 6
Current Sense Resistor	0	0	1	3.2 × 2.5
<b>Total Area (mm<sup>2</sup>)</b>	<b>36</b>		<b>77</b>	

## 6 Conclusion

In this application note, four TPS259241 devices are used in parallel to meet 20-A circuit protection, but the approach can be easily extended for other current levels. Parallel eFuse configuration also helps the system designers for better thermal management as the power loss is spread across multiple devices. For more information on the TPS259241 eFuse, see <http://www.ti.com/product/TPS25924>.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)