

How to Estimate the Output Voltage Ranges of the Charge Pumps in the TPS6510x and TPS6514x Devices

Ilona Weiss

ABSTRACT

This application report details how to estimate the output voltage range of the charge pumps in the TPS65100, TPS65101, and TPS65105 (TPS6510x) series but also in the TPS65140, TPS65141, and TPS65145 (TPS6514x) series. It assumes the output current from each charge pump is 50 mA, or less.

Trademarks

All trademarks are the property of their respective owners.

1 Introduction


The TPS6510x and TPS6514x devices contain driver circuitry for a positive and a negative charge pump. For the positive charge pump, these devices also include the diodes which usually need to be connected externally. The device regulates the output voltage of the charge pumps, if the output voltage is in the available range. The application circuit and the operating conditions set the available range of output voltages.

The mathematics used in the estimation is not complicated; however, see [Figure 2](#) and [Figure 5](#) for quick answers.

This application report is based on the standard application circuits from the data sheet of the TPS6510x ([SLVS496](#)) and TPS6514x ([SLVS277](#)) devices.

2 Negative Charge Pump

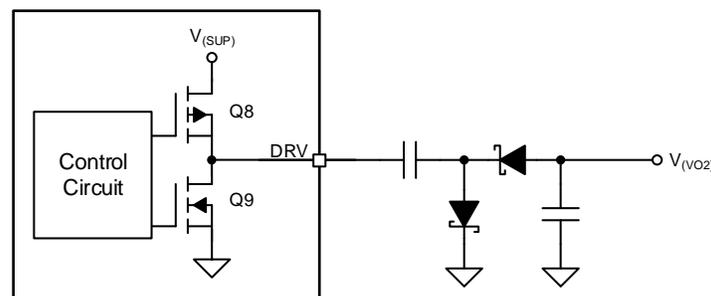Most application circuits use the one-stage negative charge-pump circuit shown in [Figure 1](#). More than one stage can be used to generate more negative voltages, but few LCDs need such negative voltages and therefore they are not discussed here.



Copyright © 2017, Texas Instruments Incorporated

Figure 1. One-Stage Negative Charge-Pump Circuit

The minimum (that is, most negative) output voltage that this circuit can generate is given by:

$$V_{O2} = -(V_{O1} - 2 \times V_F - I_{O2} \times (2 \times r_{DS(on)Q8} + 2 \times r_{DS(on)Q9})) \quad (1)$$

where

- V_{O1} is the output voltage of the boost converter (shown as $V_{(SUP)}$ in Figure 1)
- V_F is the forward voltage of the diodes
- I_{O2} is the output current of the negative charge-pump
- $r_{DS(ON)Q8}$ and $r_{DS(ON)Q9}$ are the on-resistances of the supply circuit

- $V_F = 0.5\text{ V}$ (taken from the data sheet of the BAT54 diode) ⁽¹⁾ diode)
- $r_{DS(ON)Q8} = 4.3\ \Omega$ at $I_{DS} = 20\text{ mA}$
- $r_{DS(ON)Q9} = 2.9\ \Omega$ at $I_{DS} = 20\text{ mA}$

The values of V_F , $r_{DS(ON)Q8}$, and $r_{DS(ON)Q9}$ increase as the output current increases. The negative charge pump in these devices operate with a 50% duty cycle, so the peak current in the diodes and the current sink is two times the output current. Thus, for output currents up to 25 mA, the peak current is 50 mA and

The maximum (that is, least negative) output voltage of the negative charge pump is -2 V .

Figure 2 is a graphic representation of the range of output voltages the negative charge pump in the TPS6510x and TPS6514x devices can generate as a function of the supply voltage V_{O1} .

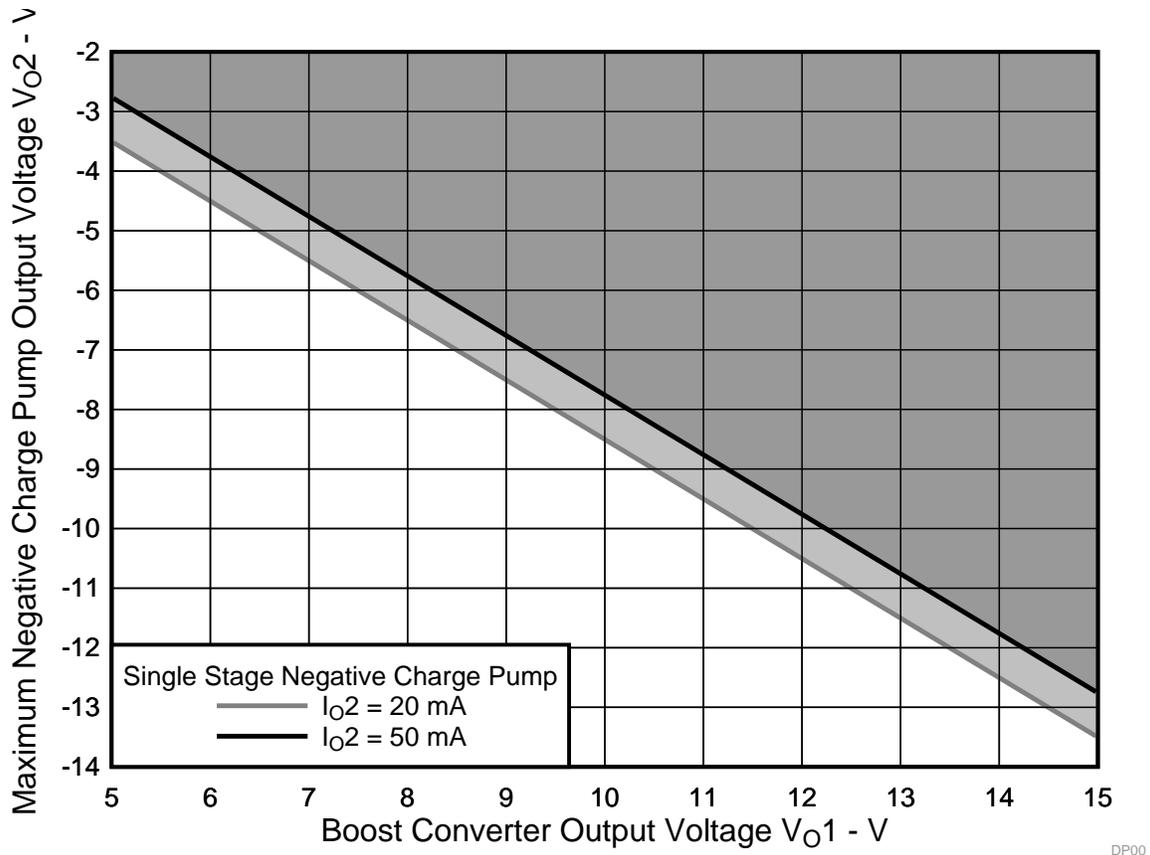


Figure 2. Negative Charge-Pump Output Voltage Range

Ensure that the output voltage of the negative charge pump in the application is in the gray area of Figure 2. The light gray filling shows the additional level the charge pump can provide if the load is only up to 20 mA.

⁽¹⁾ The BAT54 diode is commonly used in charge-pump circuits, but other diodes are available. If using a different diode, use the correct value for V_F .

The bottom boundary of the gray area also shows the output if you try to generate an output voltage below the available range.

For example, if $V_{O1} = 11\text{ V}$ and you try to generate $V_{O2} = -12\text{ V}$, approximately -9.7 V is obtained (found by following the $V_{O1} = 11\text{ V}$ grid line up until it hits the bottom boundary of the gray area).

3 Positive Charge Pump

Many LCD applications can use the positive charge pump in a doubler configuration. Applications that need a higher V_{O3} voltage (that is roughly $2 \times V_{O1}$) than a doubler can generate must use a tripler configuration.

3.1 Positive Charge Pump Doubler

To correctly use the doubler configuration of the positive charge pump connect the flying capacitor across the pins $C1-$ and $C1+$. Leave pins $C2+$ open and connect pin $C2-$ /Mode to ground, as shown in Figure 3

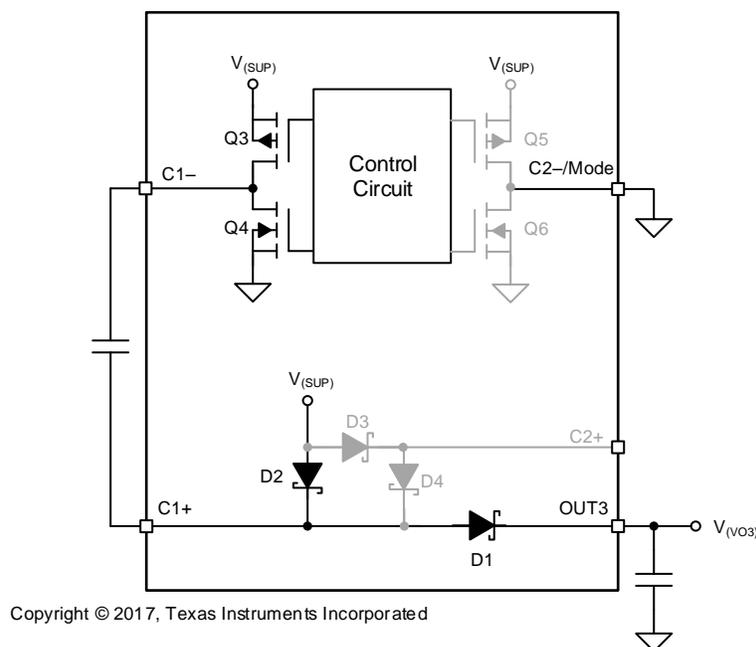


Figure 3. Positive Charge-Pump Circuit in Doubler Mode

The maximum output voltage the doubler can generate is given by:

$$V_{O3(\text{dbl})} = 2 \times V_{O1} - 2 \times V_F - 2 \times I_{O3} \times (2 \times r_{DS(\text{on})Q5} + r_{DS(\text{on})Q4} + r_{DS(\text{on})Q3}) \quad (2)$$

where

- V_{O1} is the output voltage of the boost converter (shown as $V_{(\text{SUP})}$ in Figure 3)
- V_F is the forward voltage of the diodes
- I_{O3} is the output current of the charge pump
- $r_{DS(\text{on})Q3} = 9.9\ \Omega$ at $I_{DS} = 20\text{ mA}$
- $r_{DS(\text{on})Q4} = 1.1\ \Omega$ at $I_{DS} = 20\text{ mA}$
- $r_{DS(\text{on})Q5} = 4.6\ \Omega$ at $I_{DS} = 20\text{ mA}$

The minimum output voltage for a doubler is given by:

$$V_{O3(\text{dbl})(\text{min})} = V_{O1} - 2 \times V_F \quad (3)$$

3.2 Positive Charge Pump Tripler

If the application needs a higher voltage for V_{O3} than a doubler charge pump can generate, use the tripler configuration shown in Figure 4. Connect an additional flying capacitor between pins C2–/Mode and C2+.

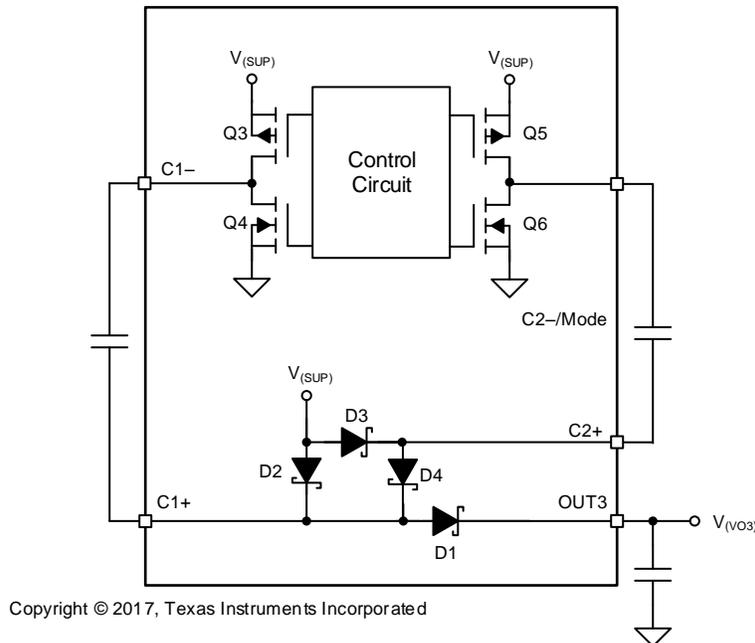


Figure 4. Tripler Positive Charge-Pump Circuit

The maximum output voltage of the tripler circuit is given by:

$$V_{O3(\text{trp})} = 3 \times V_{O1} - 4 \times V_F - 2 \times I_{O3} \times (3 \times r_{DS(\text{on})Q5} + r_{DS(\text{on})Q4} + r_{DS(\text{on})Q3}) \quad (4)$$


Where,

- V_{O1} is the output voltage of the boost converter (shown as $V_{(\text{SUP})}$ in Figure 4)
- $V_F = 0.5 \text{ V}$ (taken from the data sheet of the BAT54 diode)
- I_{O3} is the output current of the positive charge pump
- $r_{DS(\text{on})Q3} = 9.9 \ \Omega$ at $I_{DS} = 20 \text{ mA}$
- $r_{DS(\text{on})Q4} = 1.1 \ \Omega$ at $I_{DS} = 20 \text{ mA}$
- $r_{DS(\text{on})Q5} = 4.6 \ \Omega$ at $I_{DS} = 20 \text{ mA}$


NOTE: The data sheets of the TPS6510x and TPS6514x devices specify a maximum value for V_{O3} of 30 V. Even if the tripler charge pump indicates higher output voltages can be generated in the application, the maximum output voltage is limited to 30 V.

The minimum output voltage for a tripler is given by Equation 2.

Figure 5 shows a graphical representation of the output voltages that these devices can generate doubler and tripler configurations. The light gray area between indicates the additional headroom gained if the output current is only up to 20 mA. In the second figure it is also indicated the area (red filling) that is not available if you are using a tripler configuration.

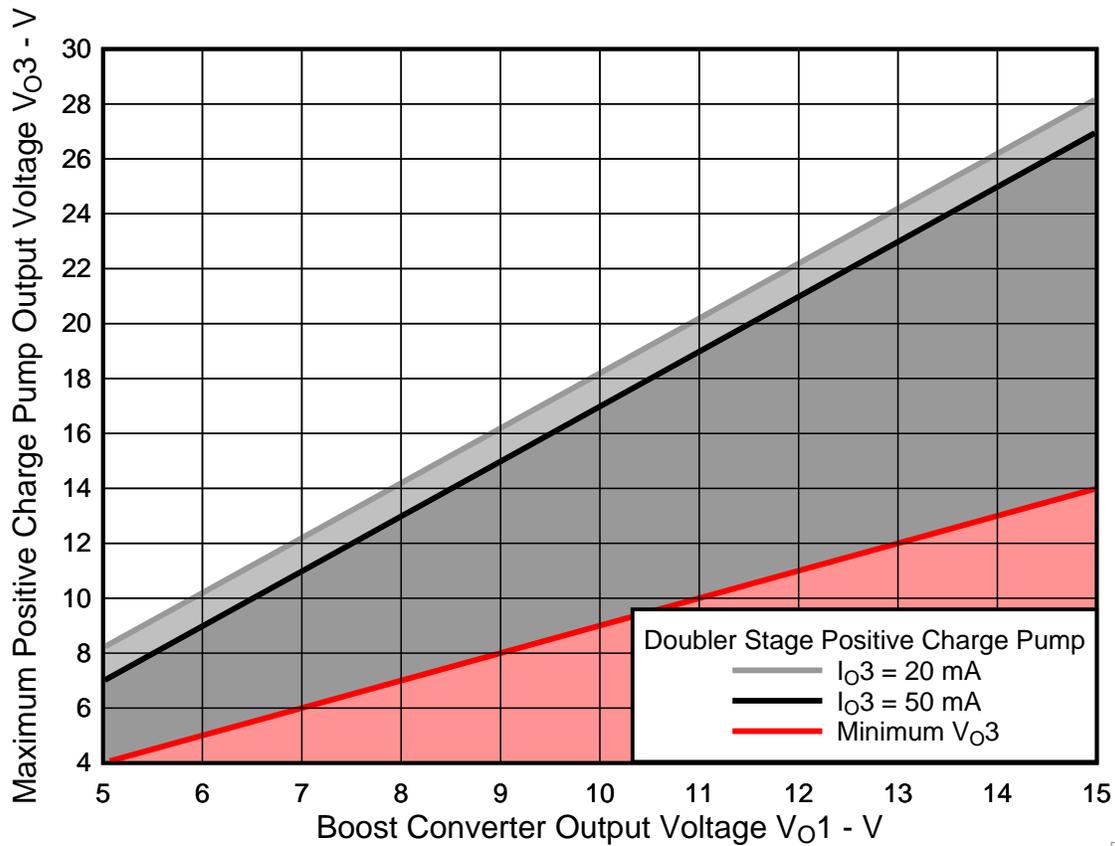

DP00

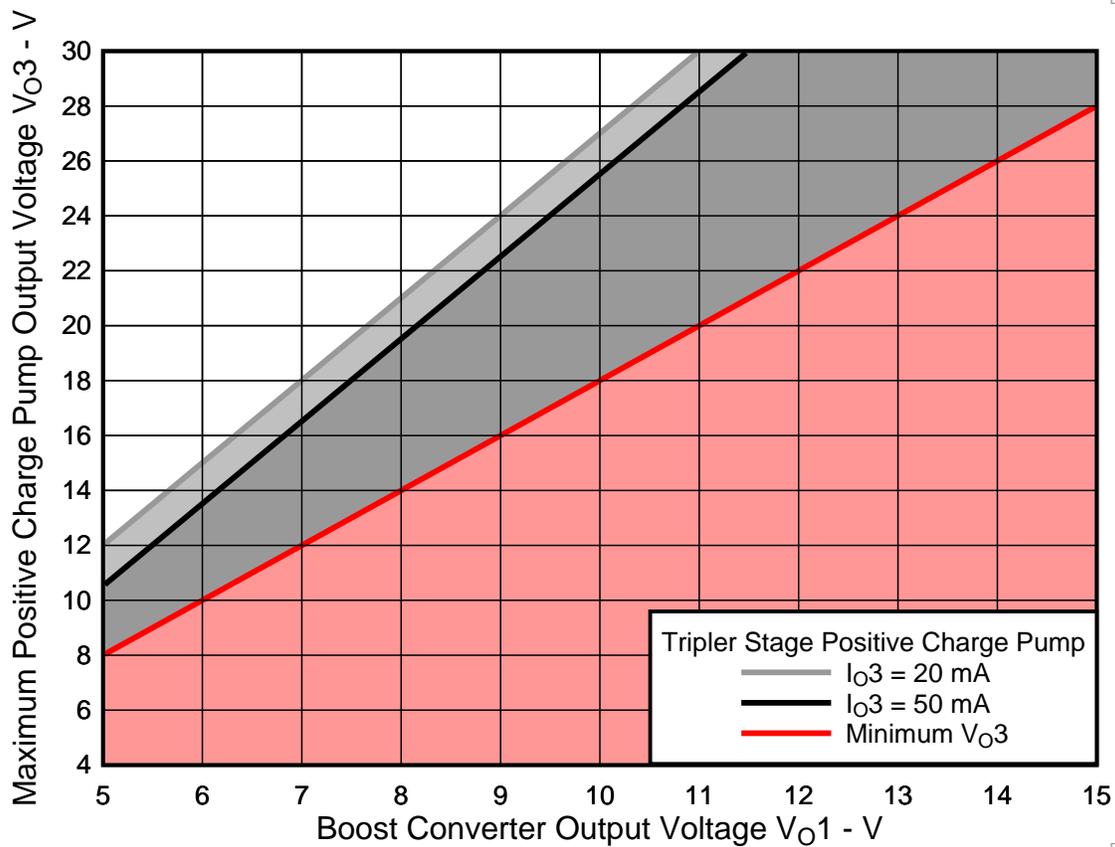

DP00

Figure 5. Positive Charge Pump Output Voltage Ranges

Ensure that the output voltage is in the gray area of [Figure 5](#). The light gray filling shows the additional level the charge pump can provide if the load is only up to 20 mA. The red areas are not available in the according configuration.

The boundaries of each area also indicate what output results if an output voltage outside the available range is generated. For example:

- If $V_{O1} = 11\text{ V}$ and you try to generate $V_{O3} = 24\text{ V}$ with a doubler stage charge pump, approximately 20.6 V is achieved (found by following the $V_{O1} = 11\text{ V}$ grid line up until it hits the top boundary of the gray area).
- If $V_{O1} = 11\text{ V}$ and you try to generate $V_{O3} = 16\text{ V}$ with a tripler charge pump, you will find that this is in the red filled area. As a result, the device will regulate up to its minimum which is at about 20 V (found by following the $V_{O1} = 11\text{ V}$ grid line up to the red line).

4 Summary

The charge pumps in the TPS6510x and the TPS6514x devices can regulate the output voltage if it is in the available range. Use [Figure 2](#) and [Figure 5](#) in this document to see the available output voltage range of the application. If the application operates close to the edge of the permitted range, ensure the design has enough margin to operate correctly under all conditions.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated