

Expand Buck Converter Minimum Input Voltage with External VCC Bias

Vincent Zhang

ABSTRACT

A typical step down (buck) converter has an internal linear low-drop-out (LDO) power supply for internal logic control and circuit drive capability. Integrating the output pin and capacitor of the LDO can help save IC pin count as well as reduce solution size; however, taking the approach of utilizing an external bias cap can provide stronger capability to drive the circuit. Additionally, using an external VCC bias allows the use of a device in lower input voltage applications while also increasing efficiency.

TPS56C215 is a monolithic 12-A synchronous buck converter with an adaptive on-time D-CAP3™ control mode. Using TPS56C215 as an example, this application note introduces a method of using an external VCC bias to support lower input voltage (V_{IN}) applications. First, this report will describe the features of the TPS56C215 device before an example of a low input voltage application is introduced. Then, a detailed schematic with the external VCC bias configuration is presented, followed by the confirmation of this theory via bench testing and an efficiency comparison.

Contents

| | | |
|---|--|----|
| 1 | TPS56C215 Introduction..... | 2 |
| 2 | 12 V / 5 V O-ring supply for DDR application | 2 |
| 3 | Schematic and Bench Results | 3 |
| 4 | Conclusion | 10 |
| 5 | References | 10 |

List of Figures

| | | |
|----|--|---|
| 1 | TPS56C215 Typical Application Diagram | 2 |
| 2 | Simplified Schematic of DDR Vpp Supply | 2 |
| 3 | Configuration Schematic Based on TPS56C215 | 3 |
| 4 | External VREG5 Biased TPS56C215 Schematic | 4 |
| 5 | Efficiency Comparison Between Internal and External VREG5 Power Supply..... | 5 |
| 6 | Steady State, $V_{IN}= 4\text{ V}$, $I_{OUT}= 0\text{ A}$ | 6 |
| 7 | Steady State, $V_{IN}= 4\text{ V}$, $I_{OUT}= 12\text{ A}$ | 6 |
| 8 | Start Up, $V_{IN}= 4\text{ V}$, $I_{OUT}= 0\text{ A}$ | 7 |
| 9 | Shut Down, $V_{IN}= 4\text{ V}$, $I_{OUT}= 0\text{ A}$ | 7 |
| 10 | Start Up, $V_{IN}= 4\text{ V}$, $I_{OUT}= 2\text{ A}$ | 8 |
| 11 | Shut Down, $V_{IN}= 4\text{ V}$, $I_{OUT}= 2\text{ A}$ | 8 |
| 12 | O-ring Switch, $V_{IN}\ 5\text{ V to }12\text{ V}$, $I_{OUT}= 2\text{ A}$ | 9 |
| 13 | O-ring Switch, $V_{IN}\ 12\text{ V to }5\text{ V}$, $I_{OUT}= 2\text{ A}$ | 9 |

List of Tables

| | | |
|---|------------------------|---|
| 1 | System Parameters..... | 5 |
|---|------------------------|---|

Trademarks

All trademarks are the property of their respective owners.

1 TPS56C215 Introduction

TPS56C215 is a monolithic 12-A synchronous buck converter with an adaptive on-time D-CAP3™ control mode. The device integrates low RDS(on) power MOSFETs that enable high efficiency and offer ease-of-use with minimum external component count, handy for space-conscious power systems.

The TPS56C215 has a 4.7 V internal LDO that generates a bias for all internal circuitry. There is a feature to overdrive this internal LDO with an external voltage on the VREG5 pin which improves the converter’s efficiency. [Figure 1](#) is the Typical Application Diagram of TPS56C215.

 


Figure 1. TPS56C215 Typical Application Diagram

2 12 V / 5 V O-ring supply for DDR application

In workstation DDR applications, customers can use 12 V to convert 2.5 V for Vpp supply. When 12 V fails, customers can have another 5 V rail as backup source to supply the Vpp rail. So customers typically want to use their ORing topology summing together 5 V and 12 V inputs to Vin through diodes. Considering the margin, usually a 4 V–13.2 V input range voltage buck converter is employed here. A simplified schematic is shown in [Figure 2](#)

 


Figure 2. Simplified Schematic of DDR Vpp Supply

In the current market, devices with 17 V max-VIN ratings typically have a minimum input voltage in the range of 4.5 V. If the VIN_min goes lower, the internal logic circuit power supply would be difficult to realize or the cost of device will increase significantly, especially for a high-current device. For this DDR application, there is already 5 V rail in the system. When connecting this 5 V to VREG5 for internal circuit supply, the buck converter could support input voltages lower than 4.5 V, meaning the customer could use the current solution to realize 5 V / 12 V ORing topology. The configuration schematic based on TPS56C215 is shown in [Figure 3](#).

 


Figure 3. Configuration Schematic Based on TPS56C215

3 Schematic and Bench Results

The detail schematic of external VREG5 Biased TPS56C215 schematic is shown in [Figure 4](#).

 


Figure 4. External VREG5 Biased TPS56C215 Schematic

The system level parameters are shown in [Table 1](#).

Table 1. System Parameters

| Parameter | Example Value |
|--|---------------|
| 12 V Input Voltage Rail, V ₁₂ | 12 VDC |
| 5 V Input Voltage Rail, V ₅ | 5 VDC |
| VREG5 Supply, V _{DD} | 5 VDC |
| Output V _{PP} Voltage, V _{OUT} | 2.5 VDC |
| Maximum Output Current, I _{O_MAX} | 12 A |
| Switching Frequency, F _{SW} | 800 kHz |
| Output Inductor, L _f | 470 nH |
| Output Capacitor, C _{OUT} | 47uFx4 |

3.1 Efficiency Comparison

With external VREG5 supplied, the internal LDO is disabled. The analog circuitry and driver power supply will come from the external VREG5 supply. While monitoring 12 V normal input rail efficiency, it could be observed that the external VREG5 supply efficiency is slightly higher than internal VREG5 supply. The comparison curve is shown in Figure 5.

 


Figure 5. Efficiency Comparison Between Internal and External VREG5 Power Supply

3.2 Bench Waveforms

Figure 6 through Figure 13 show TPS56C215 steady state, start up, shut down and ORing switch waveforms. It indicates that with external VREG5 power supply, TPS56C215 could support applications with input voltages as low as 4 V. 5 V and 12 V rails switches can be realized smoothly

 


Figure 6. Steady State, $V_{IN} = 4\text{ V}$, $I_{OUT} = 0\text{ A}$

 


Figure 7. Steady State, $V_{IN} = 4\text{ V}$, $I_{OUT} = 12\text{ A}$

 


Figure 8. Start Up, V_{IN} = 4 V, I_{OUT} = 0 A

 


Figure 9. Shut Down, V_{IN} = 4 V, I_{OUT} = 0 A

 


Figure 10. Start Up, V_{IN} = 4 V, I_{OUT} = 2 A

 


Figure 11. Shut Down, V_{IN} = 4 V, I_{OUT} = 2 A

 


Figure 12. O-ring Switch, V_{IN} 5 V to 12 V, $I_{OUT}=2$ A

 


Figure 13. O-ring Switch, V_{IN} 12 V to 5 V, $I_{OUT}=2$ A

4 Conclusion

5 V and 12 V ORing supply rails are common in server applications. Using the system 5 V rail as an external VCC bias supply could extend the minimum input voltage while also improving 12 V rail efficiency. The detailed schematic based on TPS56C215, along with bench testing, both verify the theory.

5 References

1. Texas Instruments, [TPS56C215 3.8-V to 17-V Input , 12-A Synchronous Step-Down SWIFT™ Converter](#)
2. Texas Instruments, [TPS56C215 EVM User Guide](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated