

High-Side MOSFET Driver Power Supply Using the TPS61041-Q1



Zack Liu

Boost and Multi-Channel Phase DC/DC

Introduction

Designing a MOSFET driver supply for a 12-V car supply is quite challenging. The 12-V battery supply voltage is normally in the range of 9 V to 16 V under normal operating conditions depending on charge and load variation. The TPS61041-Q1 is a high-frequency, low-cost boost converter dedicated for a small to medium supply. The device allows the use of small external components, which gives a very small overall solution size. However, its input voltage range is from 1.8 V and 6 V. This application brief proposes an external circuit that can generate an output voltage following the input voltage adjustment and change.

For automotive applications that require a high-side MOSFET driver, the MOSFET gate needs a stable stepped-up voltage to ensure the MOSFET is fully turned on. The 12-V battery supply voltage is normally in the range of 9 V to 16 V under normal operating conditions depending on charge and load variation. Therefore, the driver voltage should follow the input voltage adjustment and change. [Figure 1](#) shows the block diagram.

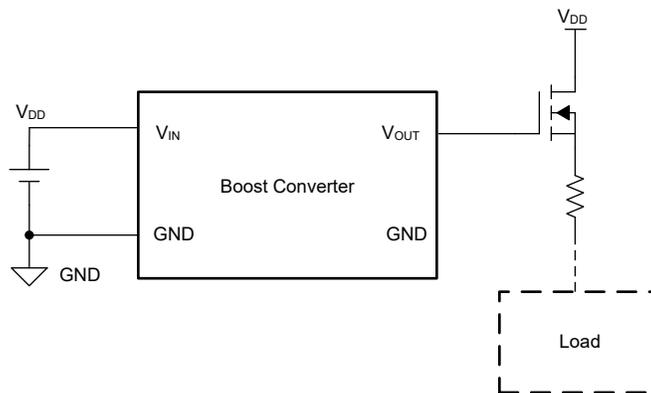


Figure 1. Block Diagram

Table 1. High-Side MOSFET Driver Circuit Specification

V_{DD}/V	V_{OUT}/V	I_{OUT}/mA
9 V to 16 V	$V_{DD} + 10 V$	5 V

The TPS61041-Q1 is a high-frequency boost converter dedicated for low-power applications. The device is ideal to generate output voltages up to 28 V from 1.8-V to 6-V input voltage range. The TPS61041-Q1 operates with a switching frequency up to 1 MHz.

This document introduces a circuit to generate the high-side MOSFET driver voltage using the TPS61041-Q1. Theoretical analysis and bench test results are presented to verify the proposed circuit. [Table 1](#) shows the circuit specification.

Proposed Circuit Principle

Figure 2 shows the schematic of a boost converter using the TPS61041-Q1. Because the TPS61041-Q1 recommended input voltage maximum value is 6 V, the device VIN and GND pin cannot be connected to 12-V car battery directly. A level-shift circuit composed of D3, D2, and Q1 pulls up the IC GND pin voltage potential.

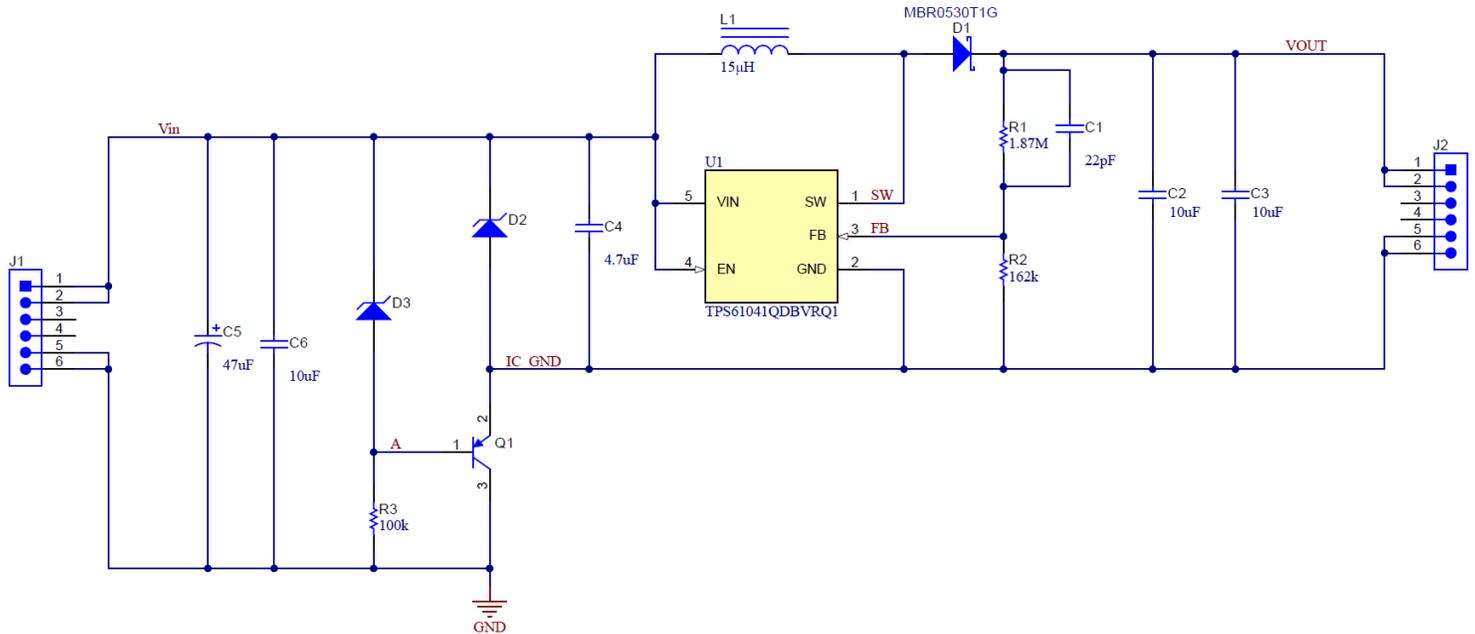


Figure 2. Proposed Schematic

D3 is a Zener diode that clamps the PNP transistor Q1 base voltage V_A to:

$$V_A = V_{in} - V_Z \quad (1)$$

The PNP transistor Q1 turns on, IC_GND voltage follows the calculation in Equation 2:

$$V_{IC_GND} = V_A + V_{BE} \quad (2)$$

In this application, a 6-V Zener diode is selected for D3. So, the TPS61041 VIN pin to GND pin voltage is clamped to below 6 V to protect the IC. Set the TPS61041 output voltage to 10 V higher than V_{in} as in Equation 3:

$$V_{OUT} = V_{IC_GND} + V_{ref} \times \left(1 + \frac{R_1}{R_2}\right) = V_{in} - V_Z + V_{ref} \times \left(1 + \frac{R_1}{R_2}\right) \quad (3)$$

Where V_{ref} is 1.233 V.

Set R_1 at 1.87 M Ω and R_2 at 167 k Ω . Assume the PNP transistor V_{BE} is 0.3 V, the $V_{OUT} - V_{in}$ equals 9.63 V.

Bench Test Result

Using the setup shown in Figure 2, the V_{in} line transient waveform is shown in Figure 3. When V_{in} is 9 V, the TPS61041-Q1 device output voltage is 19 V. When V_{in} is 16 V, the TPS61041-Q1 device output voltage is 26 V. The device V_{OUT} is always 10 V higher than input voltage.

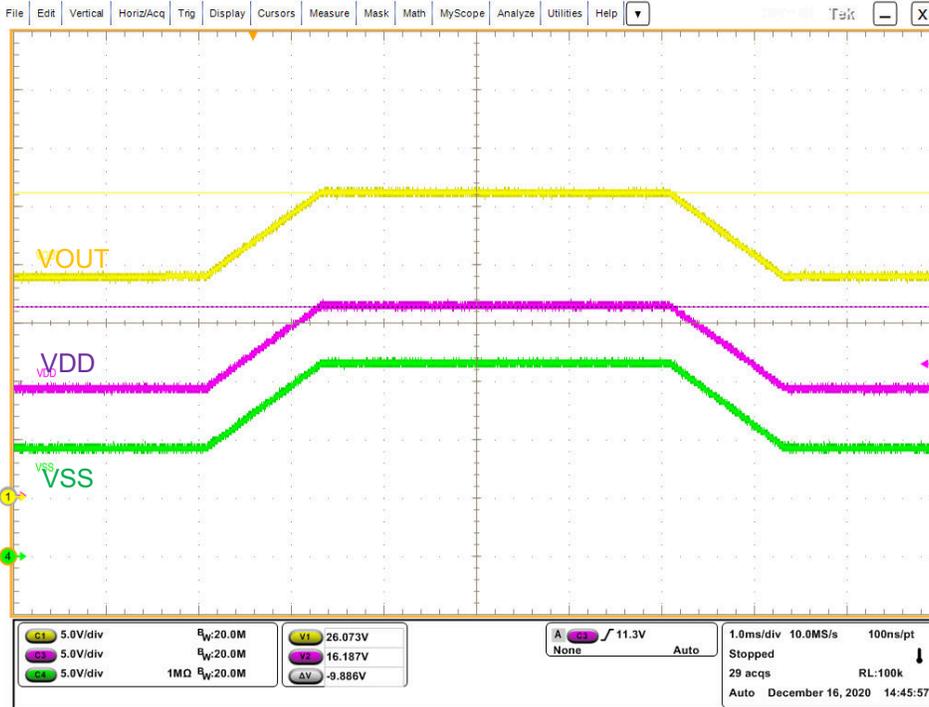


Figure 3. V_{in} 9-V to 16-V Line Transient Waveform

Summary

This document proposes an external circuit that can generate an output voltage following the input voltage adjustment and change by using the high-efficiency low-cost boost converter, TPS61041-Q1.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated