

# Three Steps to Quickly Decide Your Boost Converter's Max Output Current



Wenhao Wu

## Introduction

Boost converters are widely used for different markets, to provide higher output voltage from input supply like alkaline and Li-ion batteries. Most of boost converter do not directly specify maximum output current in data sheet. Engineers who misunderstand current capability specification from data sheet title can choose an improper small current converter for their system which actually demands heavier load. This application brief illustrates three steps to quickly know what is your boost converter's output current capability.

Additionally, this application provides two examples based on TPS61022 and TPS61099. The operating condition is given as the following:

- Input voltage  $V_{IN}$ : 1.8 V to 3.7 V;
- Output voltage  $V_{OUT}$ : 5 V;
- Operating temperature: 25°C;
- Target output current for TPS61022: 2 A;
- Target output current for TPS61099: 100 mA.

## Step 1: Know Your Device's Input Current Limit

The current specification in data sheet title represents device's typical input current limit. To make calculation, we need minimum value of input current limit. Minimum value is the worst current limit spec across variations. The higher this value is, the stronger current capability the device has.

For TPS61022, it has minimum valley current limit of 6.5 A as shown in [Table 1](#).

**Table 1. TPS61022 Current Limit Specification**

PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
$I_{LIM,SW}$	Valley current limit	$V_{IN} = 3.6\text{ V}, V_{OUT} = 5\text{ V},$	6.5	8	10	A

For TPS61099, as shown in [Table 2](#), it has minimum current limit of 0.8 A for  $V_{OUT} \geq 2.5\text{ V}$ .


**Table 2. TPS61099 Current Limit Specification**

PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
$I_{LIM}$	Current limit threshold	$V_{OUT} \geq 2.5\text{ V},$ boost operation	0.8	1	1.25	A
		$V_{OUT} < 2.5\text{ V},$ boost operation	0.5	0.75		A

## Step 2: Know Your Device's Efficiency Level at Interested Operating Condition


Efficiency data is needed to build relation between input current limit and output current. We need efficiency in the worst case to make sure device not enter current limit across operating conditions. The worst case for boost converter is at minimum input voltage, highest  $V_{OUT} \times I_{OUT}$  and highest operating temperature.

[Figure 1](#) shares TPS61022's efficiency data at  $V_{OUT}=5\text{ V}$ . We know the efficiency for  $V_{IN}=1.8\text{ V}$  and  $I_{OUT}=2\text{ A}$  is around 87%.

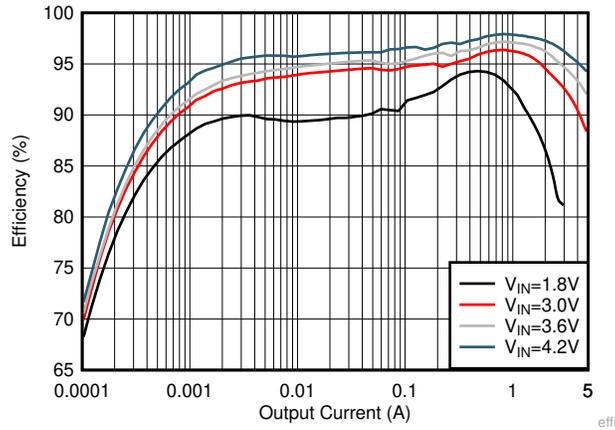

**Figure 1. TPS61022 Load Efficiency with Different Input in Auto PFM**

Figure 1 is TPS61099's efficiency data at  $V_{OUT}=5$  V. It does not have efficiency at  $V_{IN}=1.8$  V, so we use lower  $V_{IN}=1.5$  V curve for approximation. At output current of 100 mA, the efficiency is about 88%.

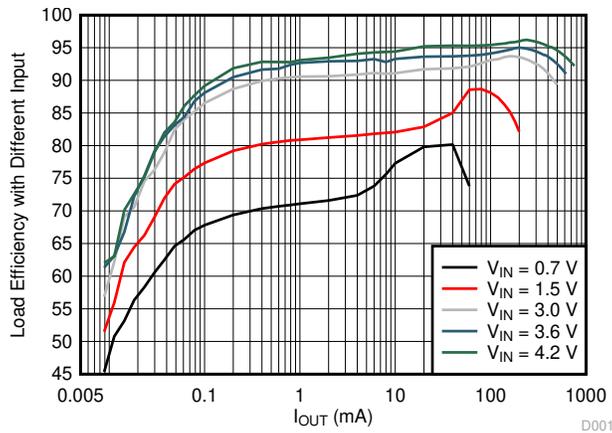

**Figure 2. TPS61099 Load Efficiency with Different Inputs**

### Step 3: Know Your Boost Converter's Output Current Capability

Equation 1 illustrates maximum output current calculation.

$$I_{OUT,MAX} = \frac{V_{IN,MIN} \cdot (I_{IN,MIN} \pm 0.5 \cdot \Delta I_L) \cdot \eta}{V_{OUT}} \quad (1)$$

Inside equation, where:


$V_{IN,MIN}$  is minimum input voltage;

$I_{IN,MIN}$  is minimum input current limit in Step 1;

$\Delta I_L$  is inductor current ripple;

$\eta$  is efficiency data in Step 2.

For device using valley current limit, half of inductor current ripple can be added in. On the other hand, device that uses peak current limit must minus half of inductor current to make calculation more accurate. Figure 3 shows how valley current limit and peak current limit is influencing average input current differently.

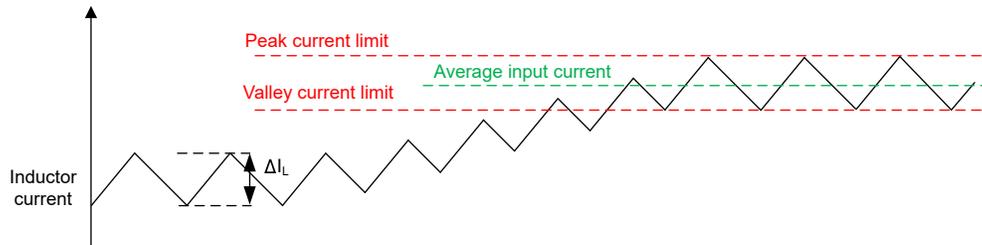

**Figure 3. Influence of Peak and Valley Current Limit to Input Average Current**

TPS61022 uses valley current limit. Maximum output current at operating condition is calculated as Equation 2 of 2.1238 A. The inductor ripple is given based on 2.2 uH inductance.

$$I_{OUT,MAX} = \frac{1.8V \cdot (6.5A + 0.5 \cdot 0.562A) \cdot 87\%}{5V} = 2.1238A \quad (2)$$

TPS61099 uses peak current limit. As a result of hysteretic control, its inductor current ripple is constant. Refer to Table 3, inductor current ripple at  $V_{OUT}=5\text{ V}$  is 350 mA. Maximum output current is calculated in as 198 mA.

**Table 3. TPS61099 Inductor Current Ripple Specification**

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
$I_{LH}$	Inductor current ripple	$V_{OUT} = 5\text{ V}$	350		mA
		$V_{OUT} = 3.3\text{ V}$	300		mA
		$V_{OUT} = 1.8\text{ V}$	250		mA

$$I_{OUT,MAX} = \frac{1.8V \cdot (0.8A - 0.5 \cdot 0.35A) \cdot 88\%}{5V} = 198\text{mA} \quad (3)$$

## Conclusion

Boost converters' data sheet does not directly specify their maximum output current. Engineers can calculate the result based on data sheet spec using three steps in this application brief. It is recommended to leave some margin over calculated maximum output current to prevent device from entering current limit, because of temperature rise and external components degradations.

## Related Documentation

1. [TPS61022 8-A Boost Converter with 0.5-V Ultra-low Input Voltage](#)
2. [TPS61099x Synchronous Boost Converter with Ultra-Low Quiescent Current](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated