

# Peak Current Mode Converter Secondary Stage Filter Design for Low Ripple Power – Part I: Filter Design for Output Ripple Reduction



Andrew Xiong, Miranda Gu

## ABSTRACT

In power design for applications such as ADC, RF transceiver and analog front end (AFE), output voltage ripple is an important factor for power quality evaluation. In previous DC-DC power supply, two-stage power design, including buck converter and LDO, are normally used to support low output voltage ripple requirement. In recent years, a type of power design using buck converter and secondary stage passive filter attracts more attention. Compared with conventional design with LDO, reduced design size and total efficiency improvement can be achieved. But a pair of conjugate poles can be introduced by the added passive filter, which threatens the loop stability.

In buck regulators portfolio of TI, low ripple and low noise power designs TPS6291x and TPSM8291x (3V-17V input) with unique integrated compensation can cover 12V input rail. To fill the gap of one-stage low ripple power design with higher input voltage, the design method of second stage filter for a general purpose peak current mode buck converter is introduced in this application note series. TPS62933F with 3.8V to 30V input and 3A max current is used as the example to illustrate the design method.

## Table of Contents

1 Introduction.....	2
2 Components Selection for Secondary Stage Filter.....	2
3 Experimental Validation.....	4
4 How to Estimate Inductance of Ferrite Bead for Ripple Reduction.....	5
5 Summary.....	7
6 References.....	7
7 Appendix.....	8

## List of Figures

Figure 2-1. Buck Converter with Second Stage Filter.....	2
Figure 2-2. Loop Gain Magnitude Plot of Equation (2).....	3
Figure 3-1. Output Voltage Ripple Without Second Stage Filter.....	4
Figure 3-2. Output Voltage Ripple with Second Stage Filter.....	5
Figure 4-1. BLE18PS080SN1 Impedance VS Frequency.....	5
Figure 4-2. BLM18SN220TH1 Impedance VS Frequency.....	5
Figure 4-3. BLE18PS080SN1 Inductance VS Frequency.....	6
Figure 4-4. BLM18SN220TH1 Inductance VS Frequency.....	6

## Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction

For the power of signal processing system design utilizing ADCs, PLLs and RF transceivers, low output voltage ripple is an important factor for power quality evaluation. In some power design designed to achieve low output voltage ripple, normally a buck converter is used for voltage step down as first stage and an LDO is used to filter ripple as second stage. However, the BOM cost, design size and conversion efficiency can cause concern in some compact or cost-effective application.

In recent years, a new low ripple power design attracts more attention by using a secondary stage passive LC filter combined with buck converter. Compared with conventional design with LDO, reduced design size and efficiency improvement can be achieved. See [Powering the AFE7920 with the TPS62913 Low-Ripple and Low-Noise Buck Converter](#) application note. But a pair of conjugate poles can be introduced by the added passive filter, which threatens the loop stability. To overcome the challenge, some buck converters are designed with unique internal compensation to support second stage LC filter, such as TPS62912/3 and TPMS82912/3 known as low noise and low ripple power design. See [TPS6291x 3-V to 17-V, 2-A/3-A Low Noise and Low Ripple Buck Converter with Integrated Ferrite Bead Filter Compensation](#) data sheet.

Low ripple and low noise normally indicate two different features of power supply. Ripple refers to the output voltage variation with switching frequency, which is measured by scope and reduced by using second stage LC filter. Noise normally refers to the voltage variation in frequency range of 100Hz-100kHz, which is usually measured with noise spectrum and limited by unique IC design.

For some application which only requires low ripple but not low noise, a second stage LC filter design method is proposed in this application note for general purpose peak current mode buck regulators, which can reduce output voltage ripple amplitude effectively with ensured loop stability. In Part I, the second stage filter components selection method to achieve required output voltage ripple is introduced. In Part II, the stability analysis and design methods are introduced. The proposed method is validated by experiments with internally compensated peak current mode converter TPS6293F. See [TPS6293x 3.8-V to 30-V, 2-A, 3-A Synchronous Buck Converters in a SOT583 Package](#) data sheet.

## 2 Components Selection for Secondary Stage Filter

Figure 2-1 shows the scheme of buck converter with second stage filter. A second-order low pass filter is formed by inductor  $L_2$  and capacitor  $C_2$ . A new pair of conjugate poles is introduced with the filter, which can reduce the output voltage ripple and noise at switching frequency through the high frequency gain attenuation. The selection method of inductor  $L_2$  and capacitor  $C_2$  is analyzed in this section.

 


Figure 2-1. Buck Converter with Second Stage Filter

In several previous studies, the expression of output voltage ripple after the 1<sup>st</sup> stage LC filter is already derived, as shown in [Equation 1](#). Also see the [Output Ripple Voltage for Buck Switching Regulator](#) application note.

$$V_{o1\text{-ripple}} = \frac{V_o \left(1 - \frac{V_o}{V_{in}}\right)}{f_{sw} L} \left( r_c + \frac{1}{8f_{sw} C_0} \right) \quad (1)$$

where,  $V_{o1-ripple}$  is the peak to peak amplitude of output voltage ripple after 1<sup>st</sup> stage.  $V_o$  is output voltage and  $V_{in}$  is input voltage of buck converter.  $f_{sw}$  is switching frequency.  $L$  and  $C_o$  are the inductance and capacitance of the 1<sup>st</sup> stage filter respectively.  $r_c$  is the ESR of capacitor  $C_o$ .


The transfer function of second stage filter is shown as Equation 2.

$$G_{vv-2nd}(s) = \frac{R_L}{s^2 R_L L_2 C_2 + s L_2 + R_L} \quad (2)$$

where  $R_L$  is output load resistance. Since MLCC is normally used as capacitor  $C_2$  to reduce output ripple for second stage, the ESR of  $C_2$  is ignored.

A pair of conjugate poles is included in transfer function Equation 2. The poles frequency can be approximately expressed as Equation 3. The loop gain amplitude plot is shown as Figure 2-2.

$$f_2 \approx \frac{1}{2\pi} \sqrt{\frac{1}{L_2 C_2}} \quad (3)$$

 

**Figure 2-2. Loop Gain Magnitude Plot of Equation (2)**

To simplify the relation, the effects of conjugate poles quality factor are ignored and the gain is seen as attenuation with -40dB/dec slope after frequency  $f_2$ . The relation as Equation 4 can be derived then.

$$\frac{0dB - 20\lg(A_{sw})}{\lg(f_2) - \lg(f_{sw})} = -40dB/dec \quad (4)$$

where,  $A_{sw}$  is the gain amplitude at switching frequency  $f_{sw}$ .

The expression of  $A_{sw}$  can be derived with Equation 5.

$$A_{sw} = \frac{f_2^2}{f_{sw}^2} = \frac{1}{4\pi^2 f_{sw}^2 L_2 C_2} \quad (5)$$

Applying the attenuation gain  $A_{sw}$  on  $V_{o1-ripple}$ , second stage ripple  $V_{o2-ripple}$  is expressed as Equation 6.

$$V_{o2-ripple} = A_{sw} V_{o1-ripple} = \frac{V_o \left(1 - \frac{V_o}{V_{in}}\right) \left(r_c + \frac{1}{8f_{sw} C_o}\right)}{4\pi^2 f_{sw}^3 L_2 C_2} \quad (6)$$

To meet the requirement  $V_{o2-ripple} \leq V_{o2-ripple-target}$ , the limitation for the selection of  $L_2$  and  $C_2$  can be received with Equation 7.

$$L_2 C_2 \geq \frac{V_o \left(1 - \frac{V_o}{V_{in}}\right) \left(r_c + \frac{1}{8f_{sw} C_o}\right)}{4\pi^2 f_{sw}^3 L V_{o2-ripple-target}} \quad (7)$$

As shown, only the limitation for  $(L_2 \times C_2)$  is given in Equation 7, while no limitation is given for  $L_2$  and  $C_2$  respectively. The inductance and capacitance can be determined with the consideration of BOM cost, DCR loss, and so on.


In Part II of this application note series, the impacts of added passive filter on loop stability can be further analyzed and the components selection range with stability restriction can be further derived then. The completed components selection range and application design method is received by considering both output voltage ripple restriction in this paper and stability restriction in next papers.

### 3 Experimental Validation

The experimental validation is completed with PCM converter TPS62933F. Operating condition is:  $V_{in}=24V$ ,  $V_{out}=1.2V$ ,  $f_{sw}=500kHz$ ,  $I_{out}=0A$ . Required output voltage ripple amplitude is smaller than 800uV pk-pk.

As comparison, an application case without second stage filter is given at first. With typical recommended components value in data sheet,  $L=2.2\ \mu H$  and  $C_o=94\ \mu F$  are selected for this operating condition. 2 x 47uF capacitors are used for the 94uF  $C_o$ .

The output voltage ripple test waveform is shown as Figure 3-1, the output voltage ripple pk-pk amplitude is about 5.7mV and it is much larger than the requirement.

 

**Figure 3-1. Output Voltage Ripple Without Second Stage Filter**

Then the proposed components selection method of second stage filter is verified. With same 2 x 47uF as the total capacitance for both first stage and second stage filters, we set the  $C_o=1 \times 47\ \mu F$  and  $C_2=1 \times 47\ \mu F$ . Substituting all parameters into Equation 7,  $L_2 \geq 14.9nH$  could be got as the restriction for 800uV output voltage ripple.

Select  $L_2=20nH$  and Figure 3-2 shows the output voltage ripple with second stage filter. The output voltage ripple amplitude is 640uV pk-pk and could satisfy the 800uV requirement.

 


Figure 3-2. Output Voltage Ripple with Second Stage Filter

The effectiveness of proposed design method is verified by the example. More experimental results are shown in Section 7.

#### 4 How to Estimate Inductance of Ferrite Bead for Ripple Reduction

In real implementation of 2<sup>nd</sup> stage filter, ferrite beads are often used as the L<sub>2</sub> of 2<sup>nd</sup> stage filter to provide nH level inductance. In the specs and data of a ferrite bead, normally an impedance value at a certain frequency at 100MHz and an impedance curve related with frequency are given.

An intuitive approach to estimate the inductance is dividing the given impedance by 2πF (like 2π x 100MHz). But that is not always correct, and we need to read the impedance curve to check if the inductance is dominant factor at given frequency point. Here we use two ferrite beads from Murata as examples for illustration: BLE18PS080SN1 and BLM18SN220TH1.

In the specs of those two ferrite beads, the impedance value at 100MHz are given. But as shown in Figure 4-1 and Figure 4-2, the dominant factors of impedance are different in those two parts at 100MHz frequency.

 


Figure 4-1. BLE18PS080SN1 Impedance VS Frequency

 



Figure 4-2. BLM18SN220TH1 Impedance VS Frequency

In **Figure 4-1**, inductive reactance X determined by L is the dominant part of impedance Z at 100MHz for BLE18PS080SN1. So, if assuming the inductance has small variation with frequency, it makes sense to estimate the L value by using impedance  $8.5\Omega$  divide  $(2\pi \times 100\text{MHz})$ , and we can get inductance 13.5nH at 100MHz.


But in **Figure 4-2**, the inductive reactance X determined by L is not the dominant part of impedance Z at 100MHz for BLM18SN220TH1. So we cannot use similar method to directly calculate inductance based on the given impedance value at 100MHz. Instead, we can read an inductive reactance value from impedance at lower frequency.

Consider that we use 500kHz switching frequency of TPS62933F, a more accurate value can be read from lowest frequency in the given curve, which is 1MHz point.

**Figure 4-3** and **Figure 4-4** show above two beads inductance VS frequency curves [7]. We can use BLE18PS080SN1 1MHz inductance 15.3nH, BLM18SN220TH1 1MHz inductance 103.4nH during 2<sup>nd</sup> LC filter design.

 

**Figure 4-3. BLE18PS080SN1 Inductance VS Frequency**

 

**Figure 4-4. BLM18SN220TH1 Inductance VS Frequency**

## 5 Summary

A components selection method for second stage filter is proposed in this application note to satisfy low output ripple requirement. With frequency domain analysis, the high frequency gain attenuation effects of second stage filter are studied first. Applying the gain attenuation effects on first stage output voltage ripple, the relation between second stage filter components value and second stage output voltage ripple is derived, which can directly guide the components selection.

To be noted, the effects of second stage filter on converter loop stability is not considered in this application note. In the [Peak Current Mode Converter Secondary Stage Filter Design for Low Ripple Power – Part II: Hybrid Sense Network Design for Stability](#) application note, the stability analysis and components selection method for stability restriction are discussed.

## 6 References

1. Texas Instruments, [Powering the AFE7920 with the TPS62913 Low-Ripple and Low-Noise Buck Converter](#), application note.
2. Texas Instruments, [TPS6291x 3-V to 17-V, 2-A/3-A Low Noise and Low Ripple Buck Converter with Integrated Ferrite Bead Filter Compensation](#), data sheet.
3. Texas Instruments, [TPS6293x 3.8-V to 30-V, 2-A, 3-A Synchronous Buck Converters in a SOT583 Package](#), data sheet.
4. Texas Instruments, [Output Ripple Voltage for Buck Switching Regulator](#), application note.
5. Murata, [SimSurfing Design Tool](#), simulation tool.
6. Texas Instruments, [Peak Current Mode Converter Secondary Stage Filter Design for Low Ripple Power – Part II: Hybrid Sense Network Design for Stability](#), application note.

## 7 Appendix

For easy validation, the components value  $L$ ,  $C_o$  and  $L_2$  are fixed and given first. The limits of  $C_2$  are calculated with [Equation 7](#) and verified by experiments.

$V_{in}$ (V)	$V_o$ (V)	$f_{sw}$ (kHz)	$L$ ( $\mu$ H)	$C_o$ ( $\mu$ F)	$L_2$ (nH)	Required Ripple (mV)	$C_2$ Low Limit ( $\mu$ F)	$C_2$ selection ( $\mu$ F)	Measured Ripple (mV)
12	1.2	1000	1	47	20	1	3.64	4.7	<0.8
12	1.6	1000	1.5	47	20	1	3.11	4.7	<0.8
24	1.2	500	2.2	47	20	1	27.96	30	<0.8
24	1.6	500	3.3	47	20	1	24.44	30	<0.8

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated