

Improve TLC59283 Control Loop Stability for Appliance Application



Jared Zhou, Qingwei Shen

ABSTRACT

TLC59283 is a 16-channel constant-current LED driver which is widely use in household appliances market. As the control and indication function has become increasingly rich and diverse, multi-board system is the one of main design to address this requirement. And with that, the parasitic parameters become larger with the increasing of the trace and cable length. This can change the loop characteristics, especially for the current sink control loop. The increased parasitic inductance can lead to loop stability issues, in some specific application conditions, the high frequency harmonic can be observed on current sink and external FETs. This paper explains the cause of the high frequency harmonic and ringing, and also provide the design to solve the issues.

Table of Contents

1 Introduction of Time-Multiplexing With TLC59283	2
2 TLC59283 Ringing Simulation Assessment	3
2.1 Small Parasitic Inductance of Vin and GND On-Board Without C_sink	3
2.2 Parasitic Inductance of Vin and GND On-Board With 4.7nF C_sink	5
2.3 Parasitic Inductance of Vin and GND on Customer's Board Without C_sink	6
2.4 Parasitic Inductance of Vin and GND on Customer's Board With 4.7nF C_sink	8
3 TLC59283 Ringing Bench Assessment	8
3.1 Bench Test Without R_sink and C_sink	8
3.2 Bench Test With 1nF C_sink	9
3.3 Bench Test With 10nF C_sink	9
3.4 Bench Test With 150 Ω R_sink	10
4 Calculation of Resistor Value in RC Circuit	11
5 Summary	11
6 References	11

Trademarks

All trademarks are the property of their respective owners.

1 Introduction of Time-Multiplexing With TLC59283

TI proposed a scheme to realize time-multiplexing with TLC59283 if there are not enough I/Os in the system to control the transistor, a block diagram similar to [Figure 1-1](#) can be used to drive 64 LEDs. TLC59283 uses eight PNP transistors to switch the common lines and forms a 8-multiplexing scheme. The eight transistors are controlled by the outputs of the TLC59283 so it reduces the I/O count. The more details can be seen in [Use TLC59283 for LED Indication with Better Brightness Uniformity, Smaller Size, and Ghosting Elimination](#).

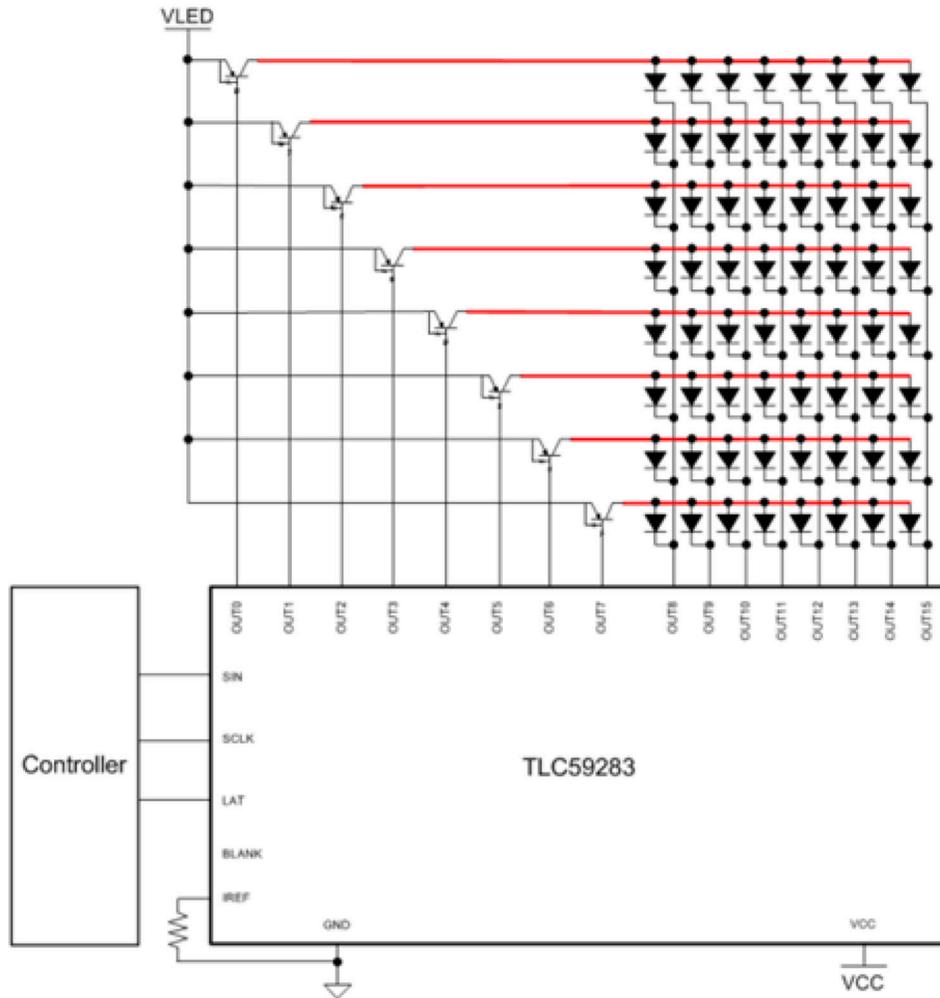


Figure 1-1. Time-Multiplexing Circuit Using TLC59283 With Less MCU I/Os

In the market of smart home appliances, the previous proposed scheme can cause output ringing since the leads are so long to result a relatively large parasitic inductance. This paper proposed a design for the ringing phenomenon and provided the result of simulation and bench test.

2 TLC59283 Ringing Simulation Assessment

The recommendation is to add capacitor in parallel at the output to reduce the output ringing. If possible, for best practices, connect a resistor in a series. [Figure 2-1](#) shows the key parasitic inductance.

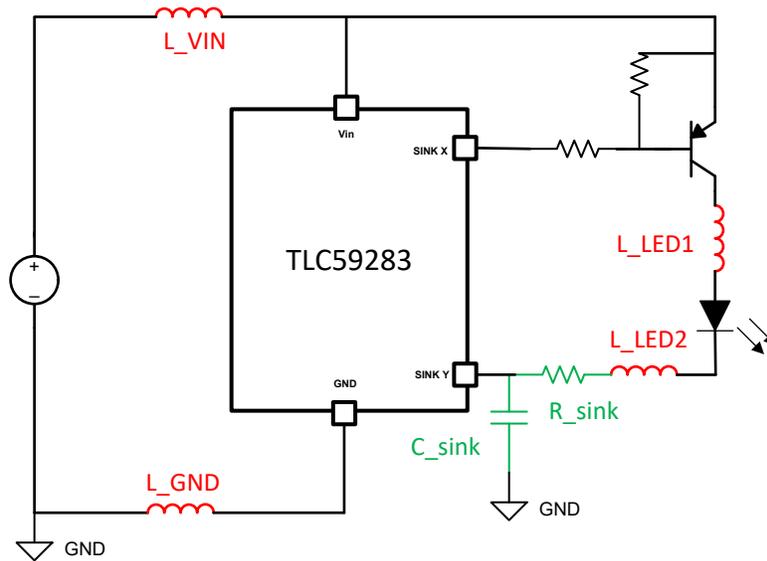


Figure 2-1. Key Parasitic Inductance

2.1 Small Parasitic Inductance of Vin and GND On-Board Without C_{sink}

[Figure 2-2](#) is the simulation with ideal small parasitic inductance at the condition of $L_{VIN}=20nH$, $L_{GND}=10nH$, $L_{LED1}=10nH$, $L_{LED2}=10nH$, $V_{in}=5V$.

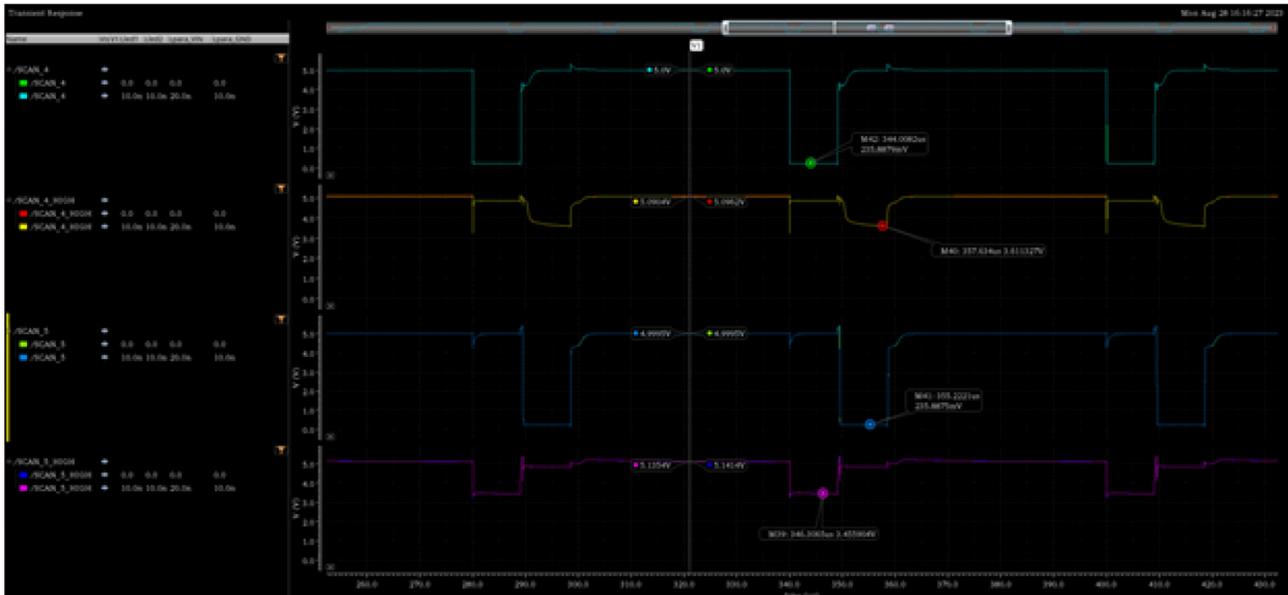


Figure 2-2. Small Parasitic Inductance of Vin and GND On-Board Without C_{sink}

2.1.1 Only Add L_LED1

Only add L_LED1, ringing starts to appear when L_LED1 > 610nH

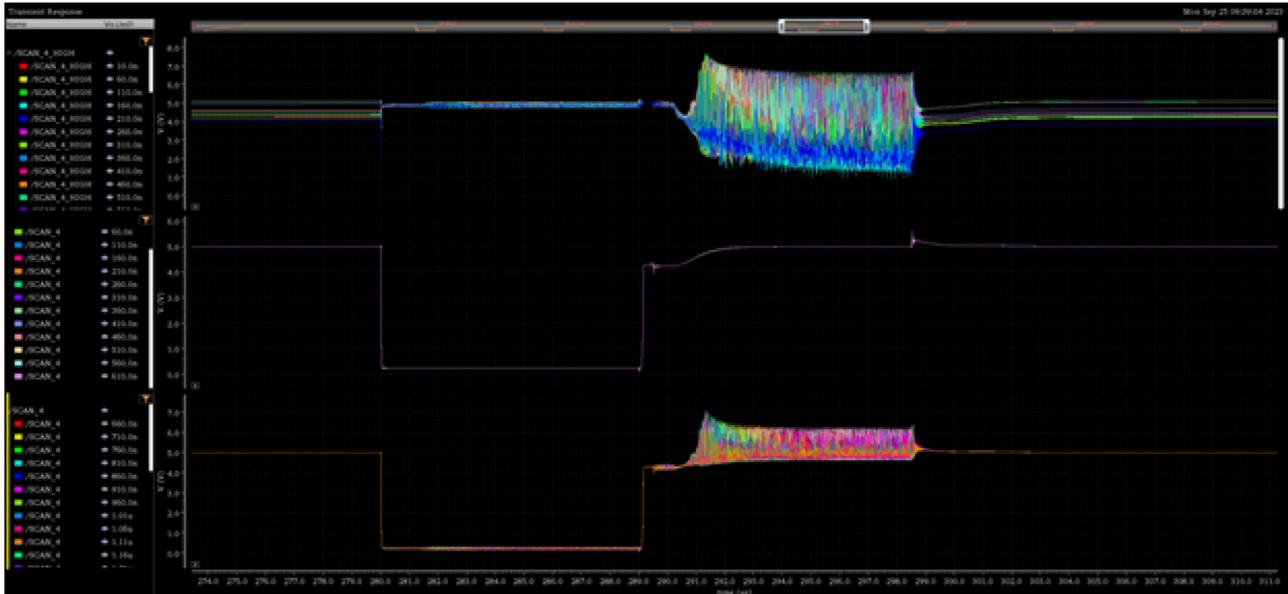


Figure 2-3. Only Add L_LED1 Without C_sink in Parasitic Inductance

2.1.2 Only Add L_LED2

Only add L_LED2, ringing starts to appear when L_LED2 > 560nH.

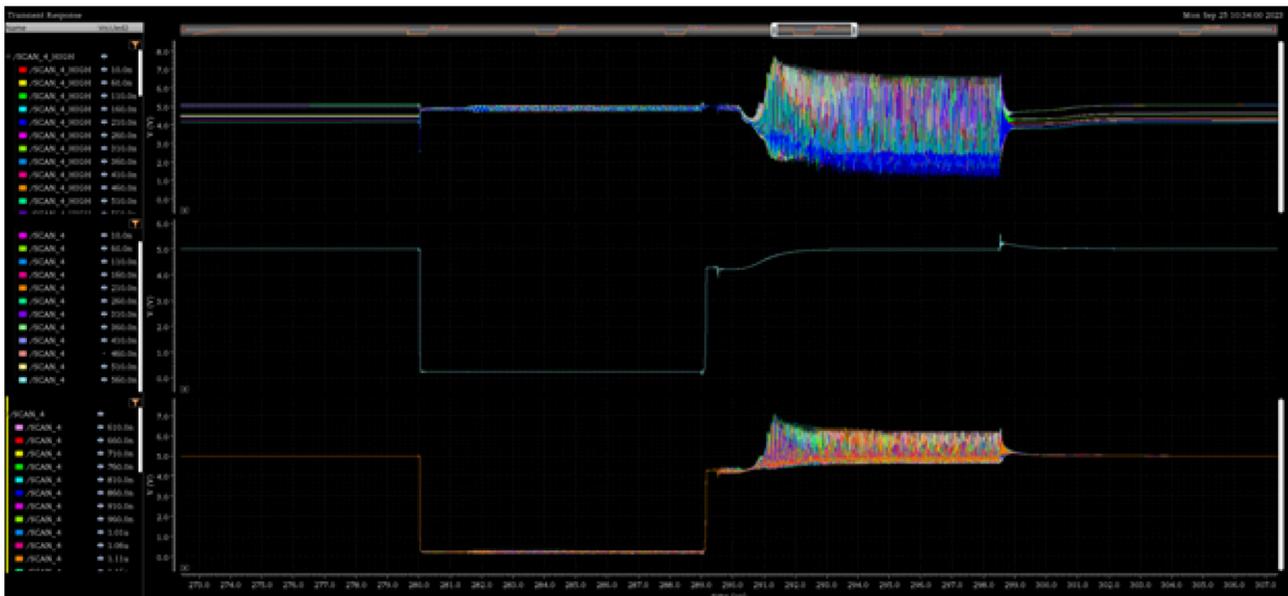


Figure 2-4. Only add L_LED2 without C_sink in Parasitic Inductance

2.2 Parasitic Inductance of Vin and GND On-Board With 4.7nF C_sink

2.2.1 L_LED1 Reach 3uH

The conditions are still at Vin=5V, L_VIN=20nH, L_GND=10nH, L_LED2=10nH, only add L_LED1, ringing does not appear even when L_LED1 reaches 3uH.

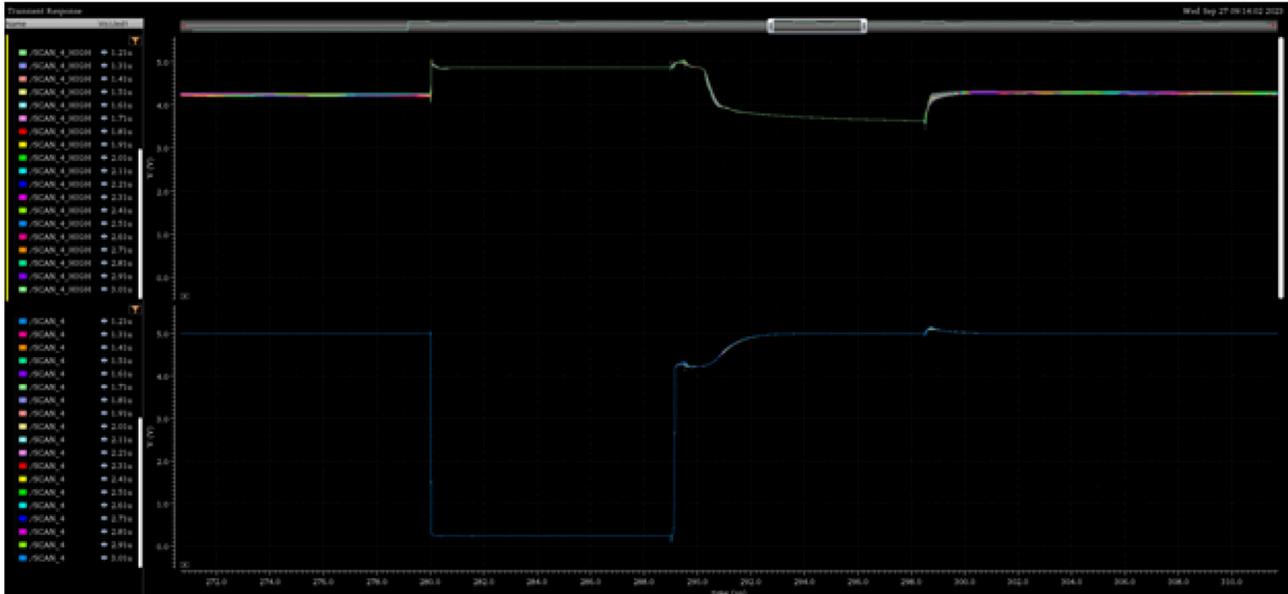


Figure 2-5. Only add L_LED1 with C_sink in Parasitic Inductance

2.2.2 L_LED2 Reach 3uH

The conditions are still at Vin=5 V, L_VIN=20nH, L_GND=10nH, L_LED2=10nH, only add L_LED1, ringing does not appear even when L_LED1 reaches 3uH.

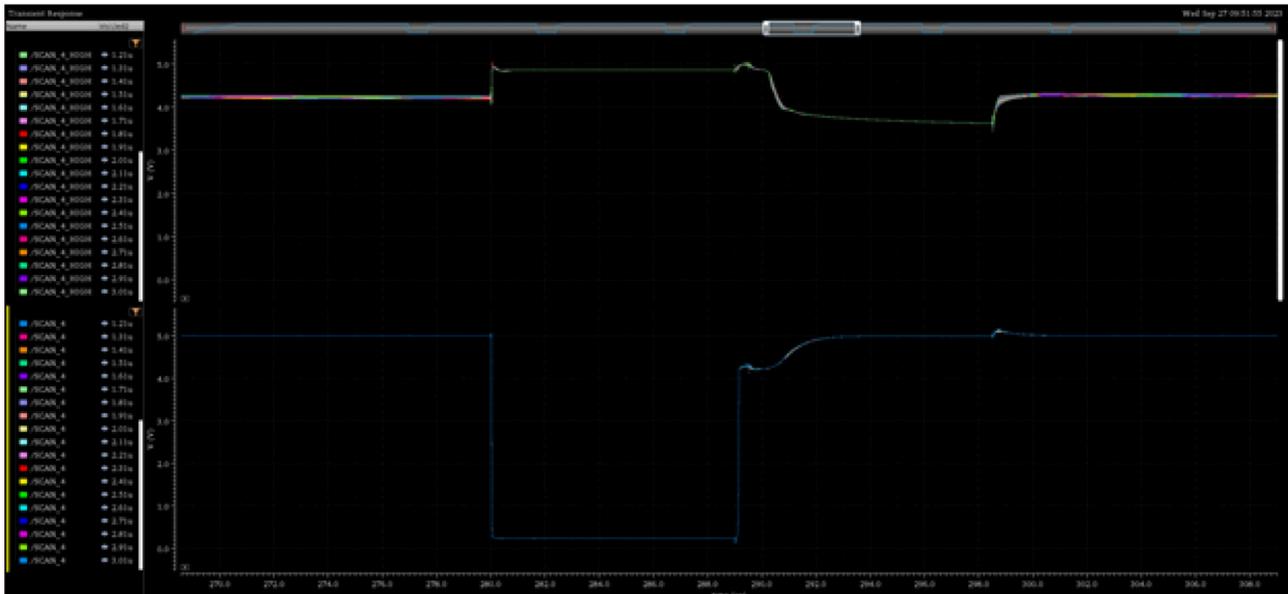


Figure 2-6. Only Add L_LED2 With C_sink in Parasitic Inductance

2.3 Parasitic Inductance of Vin and GND on Customer's Board Without C_sink

Vin=5V, L_VIN=100nH, L_GND=80nH, L_LED1=10nH, L_LED2=10nH

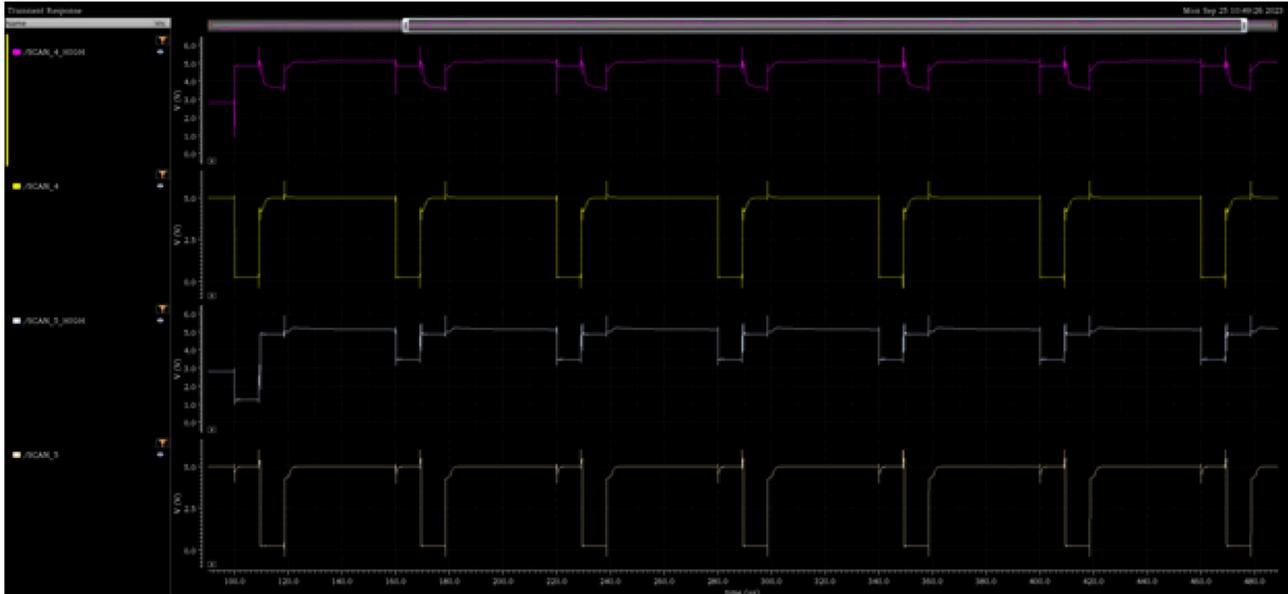


Figure 2-7. The parasitic inductance of Vin&GND on customer's board without C_sink

2.3.1 Only Add L_LED1

Only add L_LED1, ringing starts to appear when L_LED1 > 370nH

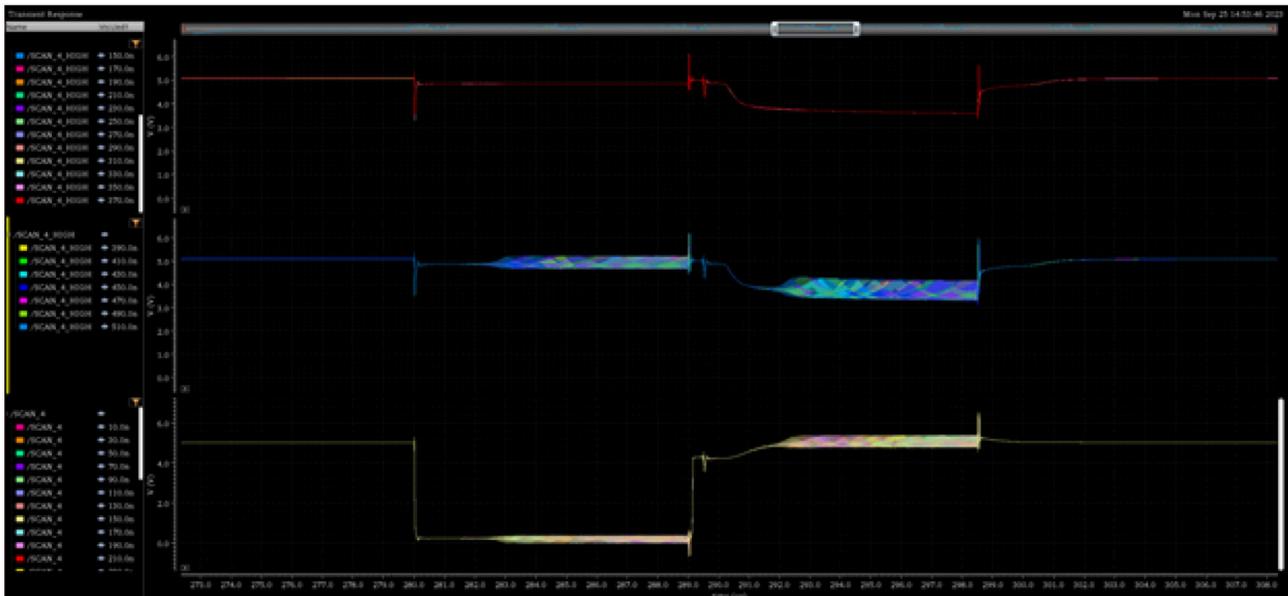


Figure 2-8. Only add L_LED1 on Customer's Board Without C_sink

2.3.2 Only Add L_LED2

Only add L_LED2, ringing starts to appear when L_LED2 > 370nH

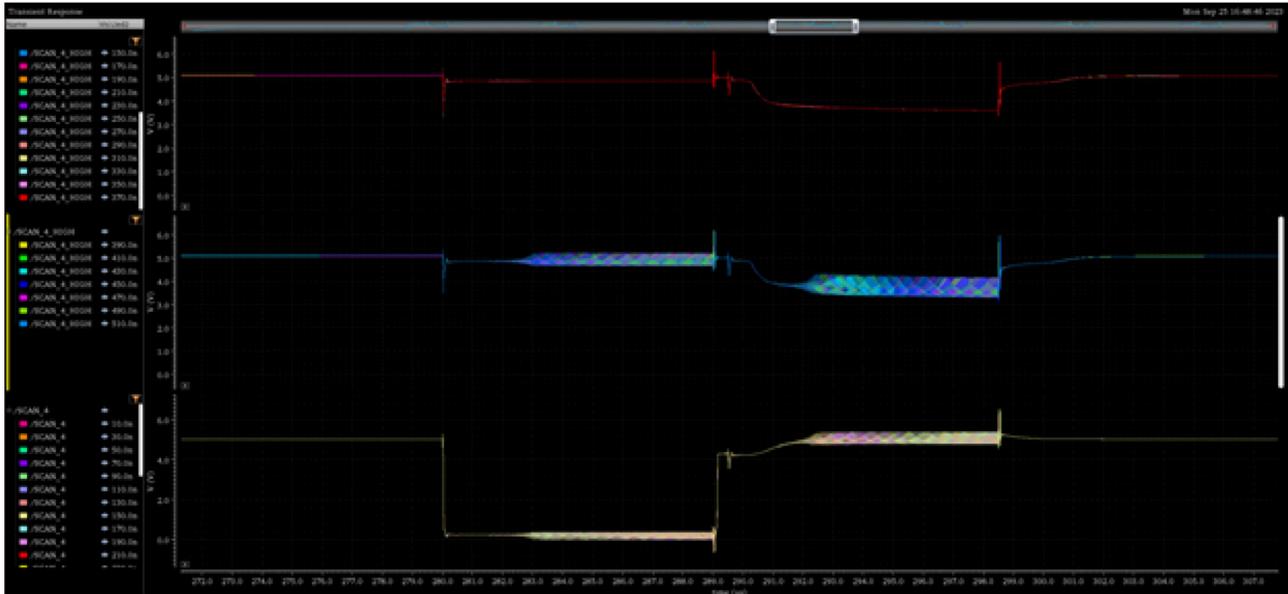


Figure 2-9. Only Add L_LED2 on Customer’s Board Without C_sink

2.3.3 Add L_LED1 and L_LED2

Only L_LED1 and L_LED2 of the same values, ringing starts to appear when L_LED1 = L_LED2 = 200nH

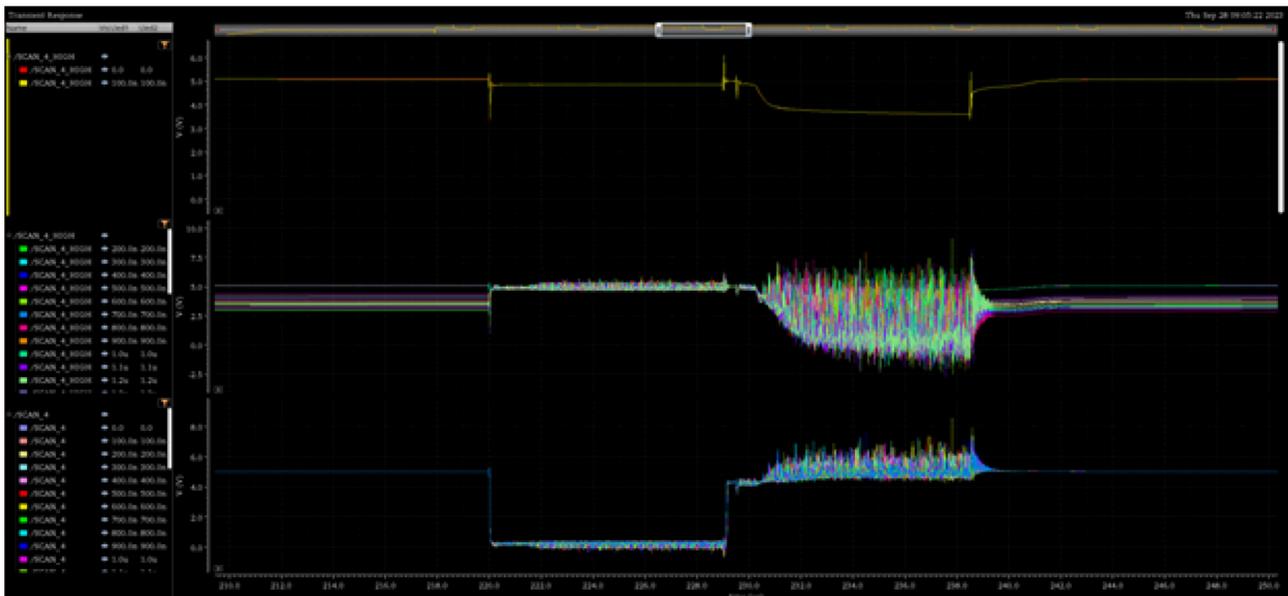


Figure 2-10. Add L_LED1 and L_LED2 on Customer’s Board Without C_sink

2.4 Parasitic Inductance of Vin and GND on Customer's Board With 4.7nF C_{sink}

V_{in}=5V, L_{VIN}=100nH, L_{GND}=80nH, add L_{LED1} and L_{LED2} of the same values, ringing does not appear even when L_{LED1} and L_{LED2} reaches 3uH.

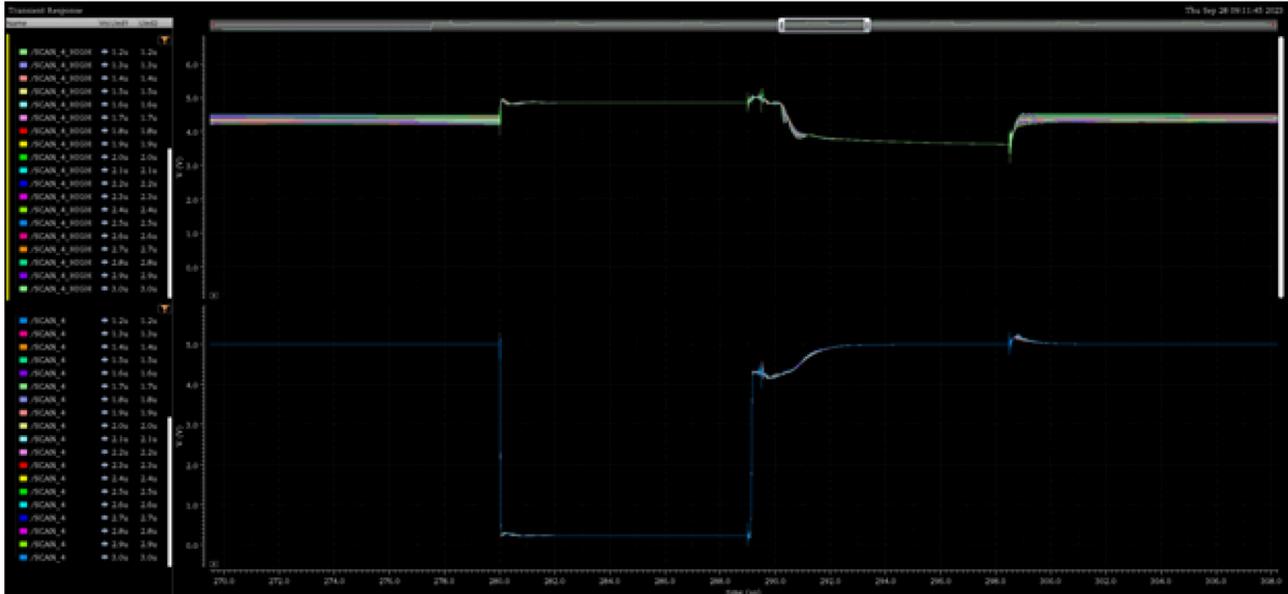


Figure 2-11. Parasitic Inductance of Vin and GND on Customer's Board with C_{sink}

3 TLC59283 Ringing Bench Assessment

A long-term external light board was used to simulate the situation where the parasitic inductance is relatively large on the EVM board. Then, the waveform were captured with and without the RC filter circuit.

3.1 Bench Test Without R_{sink} and C_{sink}

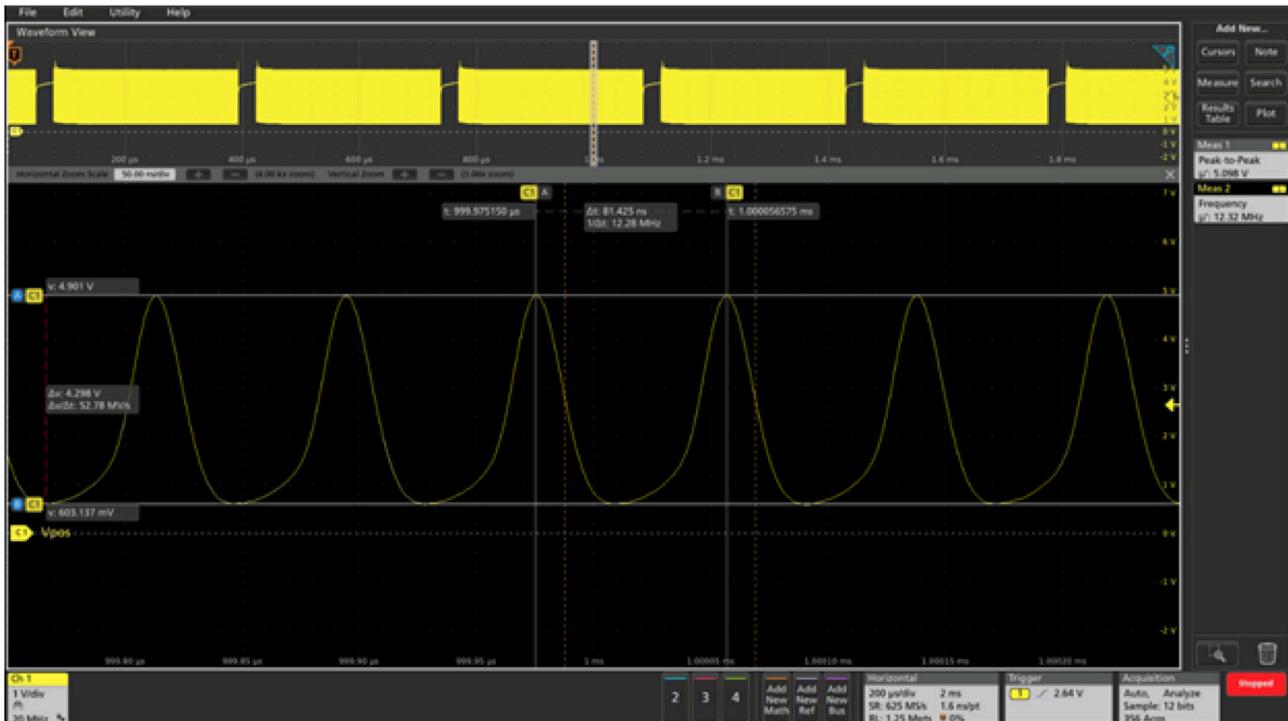


Figure 3-1. Bench Test Without R_{sink} and C_{sink}

3.2 Bench Test With 1nF C_{sink}

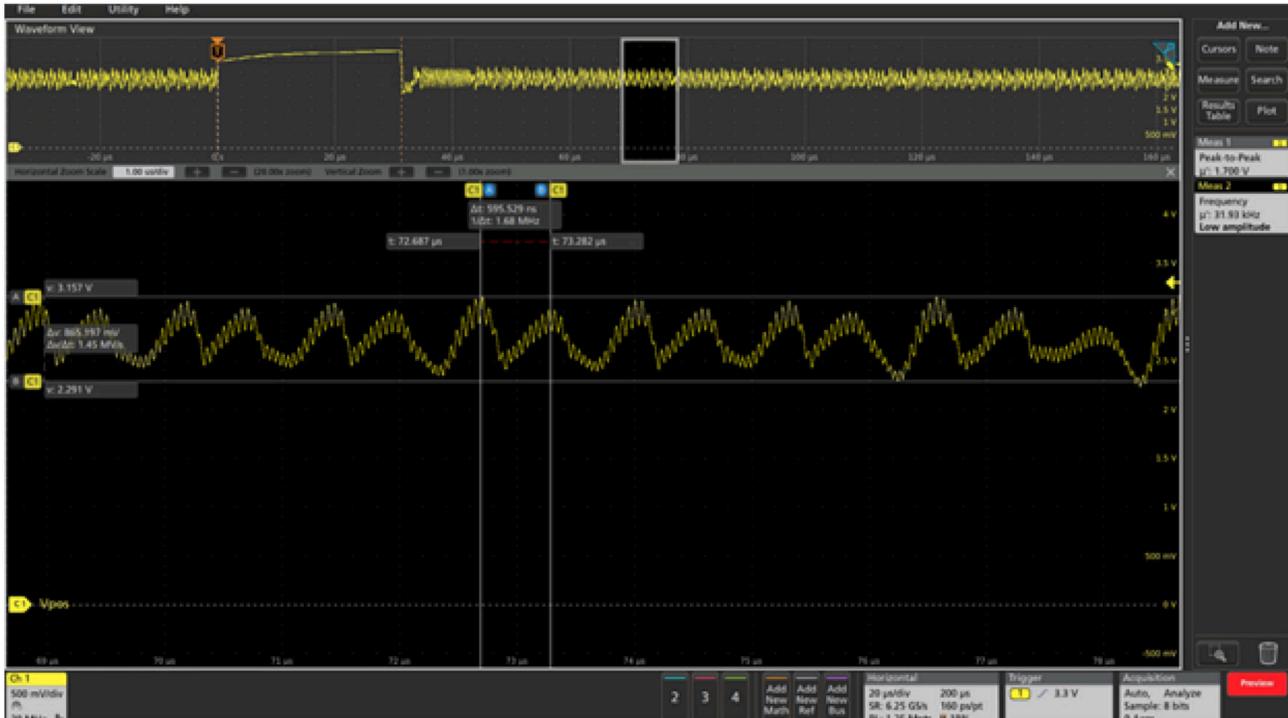


Figure 3-2. Bench Test With 1nF C_{sink}

3.3 Bench Test With 10nF C_{sink}

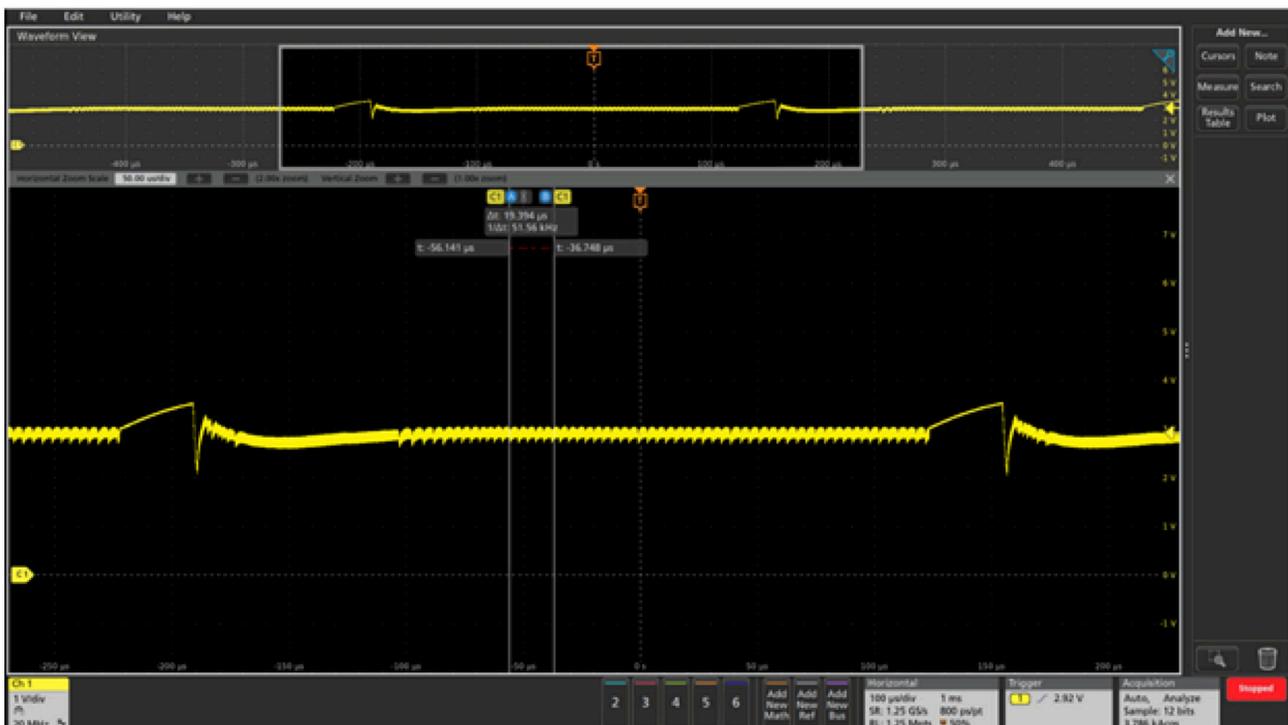


Figure 3-3. Bench Test With 10nF C_{sink}

3.4 Bench Test With 150 Ω R_{sink}

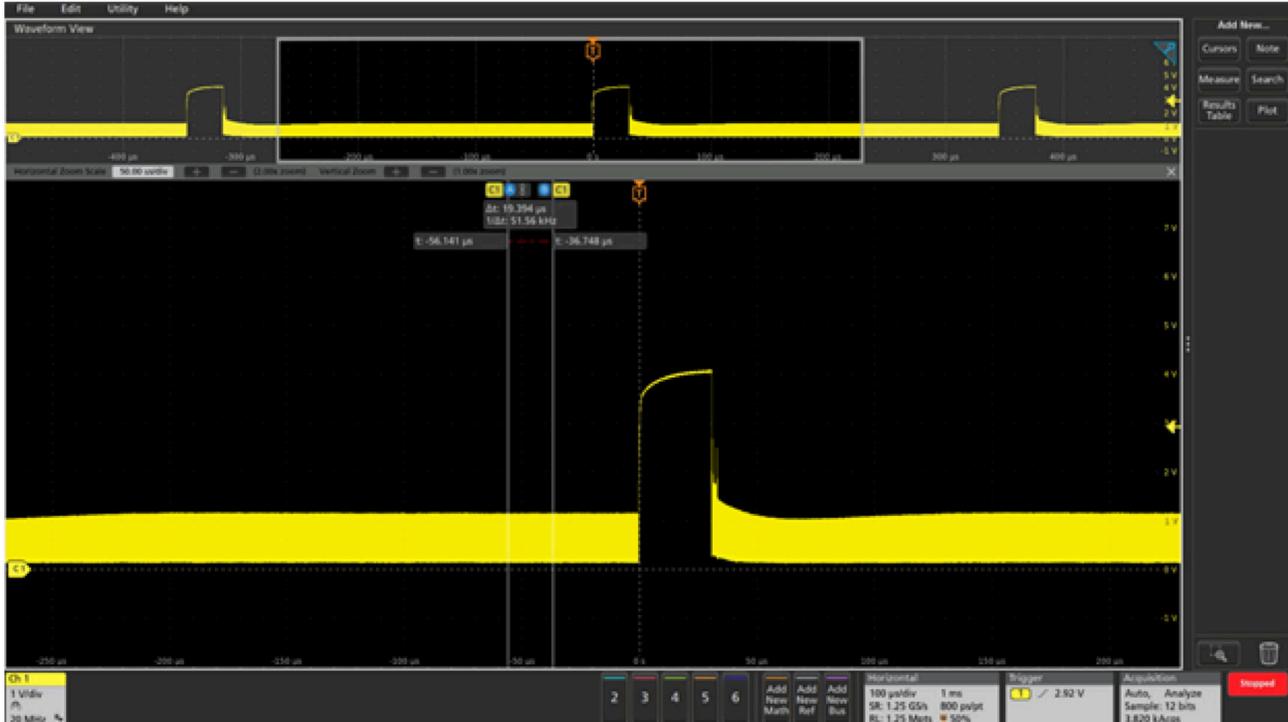


Figure 3-4. Bench Test With 150 Ω R_{sink}

3.4.1 Bench Test With 10nF C_{sink} and 150 Ω R_{sink}

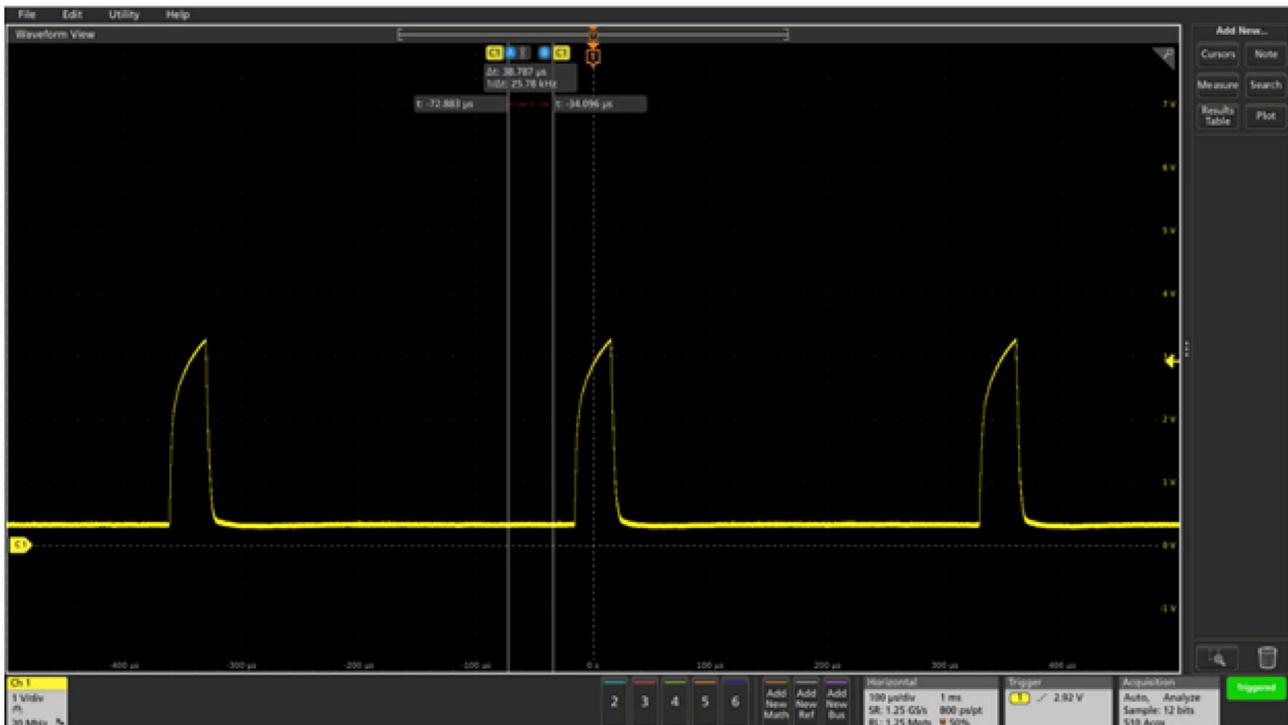


Figure 3-5. Bench Test With 10nF C_{sink} and 150 Ω R_{sink}

4 Calculation of Resistor Value in RC Circuit

Usually, the value of the series resistor is determined by the setting current. The voltage dropped on the output pin needs to satisfy the requirement minimum headroom voltage.

We assume the minimum headroom voltage of output is 0.5 V. Therefore, the calculation needs to

$$V_o = V_{LED} - V_d - V_f - I_{set} * R > 0.5V \quad (1)$$

V_o	The output voltage
V_{LED}	The voltage of VLED
V_d	The voltage dropped on the BJT
V_f	The forward voltage of LED
I_{set}	The setting current
R	The value of series resistor

5 Summary

A relatively larger parasitic inductance does cause TLC59283 output ringing, but this can be solved by adding an RC circuit. We recommend to connect a 10 nF capacitor in parallel and connect a resistor in series with the output. The value of series resistor can be referred below calculation.

6 References

- Texas Instruments, [TLC59283, 16-Channel, Constant-Current LED Driver with Pre-Charge FET](#), data sheet.
- Texas Instruments, [Use TLC59283 for LED Indication with Better Brightness](#), data sheet.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated