

Solving Power Design Challenges in Oscilloscope Applications



Bruce Lu

A higher real-time sample rate and portability are two major trends for new oscilloscope products, along with more powerful digital circuits and a smaller board size. To support this, power systems with better dynamic load performance and higher power density are preferred. Low noise and low output ripple are also required by sensitive analog components for generating high-accuracy images. Although 12 V is still the most common intermediate rail, 24-V architectures are becoming increasingly popular. In this article, common design challenges associated with using buck regulators for oscilloscope power are discussed.

Table 1 lists DC/DC buck regulators recommended for oscilloscope power designs, including converters with optional frequency synchronization and integrated inductor module options.

Table 1. Oscilloscope Power Management Devices

	GPN	V _{IN}	I _{OUT}	Fsync	Features	Module Option
Fast Transient Response	TPS563252	3 V–17 V	3 A		Fast transient response, Ease of use, 1.2 MHz 3 A, wide range of V _{OUT} , ECO/FCCM/OOA	TPSM863252
	TPS563257	3 V–17 V	3 A			TPSM863257
	TPS568231	3.8 V–17 V	8 A		Fast transient response, P2P 8 A/12 A family, 400/800/1200 KHz, ECO/FCCM, Adj soft start	
	TPS56C231	3.8 V–17 V	12 A			
	TPS548A28	2.7 V–16 V	15 A		Fast transient response, P2P 15/20-A family, 600/800/1000 KHz, Adj soft start	TPSM8A28
	TPS548A29	2.7 V–16 V	20 A			TPSM8A29
High Power Density	TPS543320	4 V–18 V	3 A	√	Highest efficiency 12 V/6 A converter in the market, P2P 3/6/8 A family, ±0.5 % accuracy, selectable Fsw: 500 KHz/750 KHz/1 MHz/1.5 MHz/2.2 MHz, Fsync. Power good, Adj soft start	TPSM843320
	TPS543620	4 V–18 V	6 A	√		TPSM843620
	TPS543820	4 V–18 V	8 A	√		TPSM843820
	TPS541620	4.5 V–15 V	Dual 6 A	√	Dual-channel, Small size, 500 KHz/1 MHz/1.5 MHz/2 MHz, Adj soft start, Fsync	TPSM5D1806
	TPS543A22	4 V–18 V	12 A	√	Highest power density 25-A converter, P2P12/16/20/25-A family, ±0.5 % accuracy, Selectable Fsw: 500 KHz/750 KHz/1 MHz/1.5 MHz/2.2 MHz, Fsync. Power good, Adj soft start	TPSM843A22
	TPS543A26	4 V–18 V	16 A	√		TPSM843A26
	TPS543B22	4 V–18 V	20 A	√		TPSM843B22
	TPS543B25	4 V–18 V	25 A	√		
Low noise	TPS62912	3 V–17 V	2 A	√	Eliminates LDO and passive post filtering, low noise/ripple, Spread spectrum modulation, 1 MHz/2.2 MHz, Fsync	TPSM82912
	TPS62913	3 V–17 V	3 A	√		TPSM82913
Digital Interface	TPS546D24A	2.95 V–16 V	40 A	√	PMBus with telemetry, Stack x4, Over 90% efficiency 12 V _{IN} , 1 V _{OUT} , 500 kHz from 15 A–25 A. 275 KHz–1.5 MHz, Fsync	TPSM8D6C24
	TPS546B24A	2.95 V–16 V	20 A	√		TPSM8D6B24
	TPS546A24A	2.95 V–16 V	10 A	√		
24 V rails	TPS62933	3.8 V–30 V	3 A		Wide V _{IN} range, 200 KHz to 2.2 MHz selectable frequency, EN, Light load efficiency, Adj soft start, Spread spectrum modulation	
	TPS62932	3.8 V–30 V	2 A			
	TPS56637	4.5 V–28 V	6 A		High efficiency, ECO/FCCM/OOA, Selectable Fsw: 500 KHz/800 KHz/1.2MHz, Large duty support, power good, Adj soft start	TPSM86638
	TPS56837	4.5 V–28 V	8 A			TPSM86838

Challenges

Fast Transient Response for CPU and FPGA Core Voltage

When an oscilloscope is conducting signal sampling and processing, the load current drawn by digital circuits such as CPU and FPGA can change rapidly. To regulate the output voltage within a small range of undershoot and overshoot, power devices with fast transient response behavior are required in most oscilloscope power designs. Without this behavior, the CPU/FPGA can not receive a stable input voltage, decreasing system performance. A key device designed for solving this challenge is TPSM863257. Rather than requiring large output capacitance like a current mode regulator, TPSM863257 uses comparator-based D-CAP3™ control mode to achieve fast transient response, as shown in Figure 1, ΔV_{OUT} within $\pm 3\% V_{OUT}$. In addition, TPSM863257 is easy to use with minimized external components and is available for large-duty operation support.

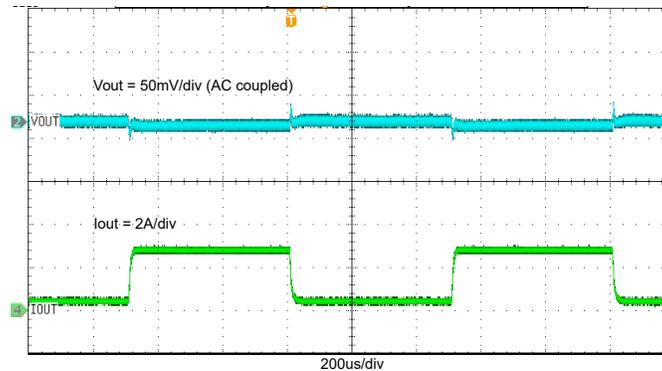


Figure 1. TPSM863257 Transient Response with 12 V to 1.05 V, 0.3 A to 2.7 A, 1 A/ μ s SR

Noise Emissions

Because the ADCs, DACs and AFEs in oscilloscopes are sensitive to the radiated emissions, low noise buck regulators with less EMI emission are preferred. TPS62913 and TPSM82913 are designed for low EMI options for 12-V input rails. TPS62913 and TPSM82913 can support frequency spread spectrum modulation, which helps with lowering EMI noise. Spread spectrum eliminates peak emissions at specific frequencies by spreading emissions across a wider range of frequencies than a part with fixed frequency operation. Compared with a traditional switching regulator + LDO option, TPS62913 and TPSM82913 can achieve less than 20- μ Vrms noise in a single chip option. And less than 10- μ Vrms output ripple can also be achieved by implementing internal compensation of a ferrite beam filter, as shown in Figure 2 and Figure 3.

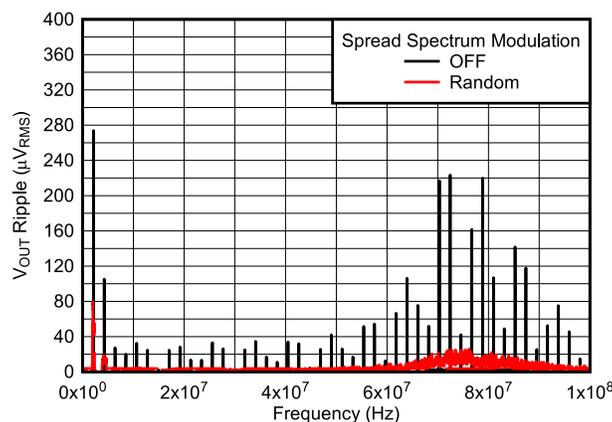


Figure 2. V_{OUT} Ripple FFT of TPS62913 at 12 V_{IN} to 3.3 V_{OUT} , 2.2 MHz

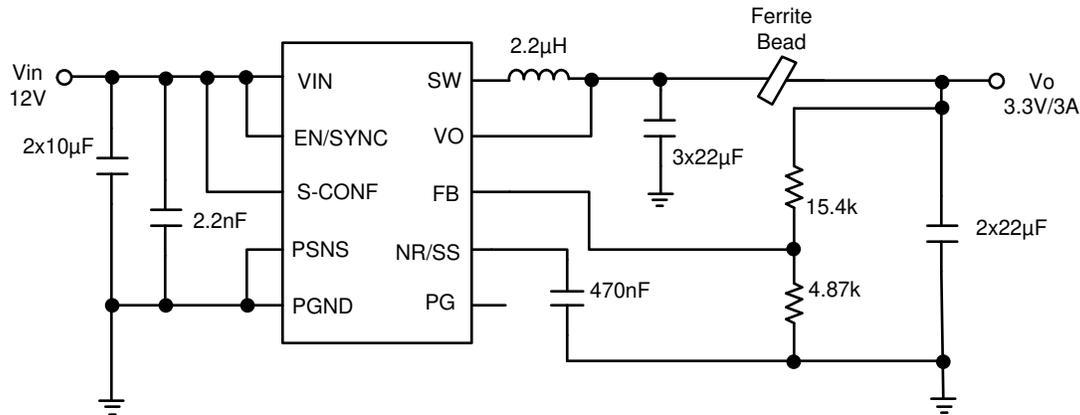


Figure 3. Typical Application with Integrated Ferrite Bead Filter Compensation

Power Density

For both high-end and portable oscilloscopes' power designs, board area and height are becoming limiting factors as power demands increase. Power engineers must reduce their circuit design area and improve efficiency to achieve higher power density. TPSM5D1806 has input voltage ranging from 4.5 V to 15 V, an output current of dual 6 A and a small package size (5.5 mm × 8 mm × 1.8 mm), which can help to achieve high power density and optimized design layout. When connecting the two outputs of TPSM5D1806 for current sharing, the module can supply up to 12 A, as shown in Figure 4. TPSM5D1806 also offers high efficiency and can achieve up to 92% at the condition of 12 V_{IN} to 5 V_{OUT}, 3-A output current and switching frequency of 2 MHz.

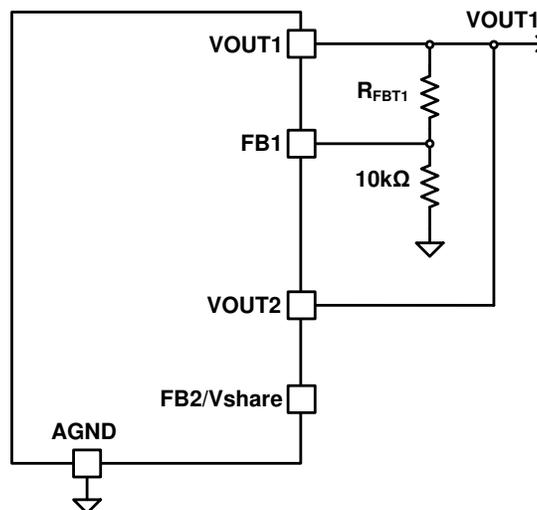


Figure 4. Single Device, Current Sharing

Monitoring Power Parameters

Another challenge of oscilloscope power design is to monitor key parameters including output voltage and input current. Oscilloscopes need stable output voltage to verify the accuracy of signal measurement. By using buck regulators with PMBus™ interface with telemetry, you can monitor the real-time output voltage and adjust the voltage for stability. In addition, monitoring input current can help evaluate efficiency and optimize power management so as to extend battery life and reduce power consumption. Key PMBus-enabled device families designed for this challenge are the TPS546A24A family of converters and the TPSM8D6C24 family of modules.

TPS546A24A and TPSM8D6C24 are fixed frequency devices with selectable switching frequencies and are able to synchronize to the external clock, which can also help to achieve stable frequency. For TPSM8D6C24, there are a dual 35 A or single 70 A and up to a 4-phase stackable module. See the simplified application in Figure 5.

The Texas Instruments Fusion Digital Power Designer supports the TPS546A24A and TPSM8D6C24 devices. The Fusion Digital Power Designer is a graphical user interface (GUI), which can be used to configure and monitor the devices through the PMBus using a Texas Instruments USB-to-GPIO adapter. Download the Texas Instruments [Fusion Digital Power Designer](#) software package.

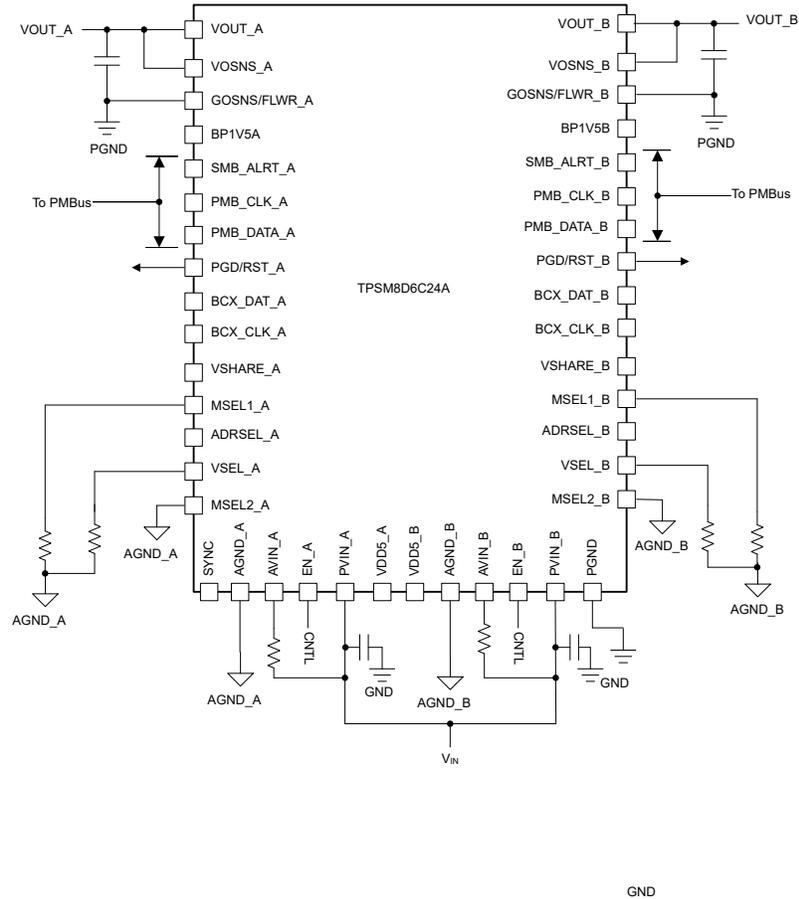


Figure 5. Simplified Application of TPSM8D6C24

Conclusion

Designing power supplies for oscilloscopes requires consideration of transient response, noise emission, power density and power parameter monitoring. TI's broad portfolio of buck converters and modules is well-equipped to address all of these power design challenges in both 12-V and 24-V input rails with various output currents.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated