

TEXAS INSTRUMENTS

Title DM355 Power Reference Design		
Size B	Number PMP3779	Rev A
Date 03/17/08	Drawn by K Ohn	
Filename PMP3779.sch	Sheet of	

Filename: DM355_bom.xls

Date: 12/10/2008

DM355 Reference Design BOM

Count	RefDes	Value	Description	Size	Part Number	MFR
2	Q1	2N2222	Transistor, NPN, 40V, 200mA, 625mW	TO-92	2N3904	Fairchild
	Q2	2N2222	Transistor, NPN, 40V, 200mA, 625mW	TO-92	2N3904	Fairchild
3	C2	0.1uF	Capacitor, Ceramic, 50V, C0G, 5%	603	C1608C0G1H220J	TDK
3	C1, C4, C10	10uF	Capacitor, Ceramic, 6.3V, X5R, 20%	603	GRM188R60J106ME47D	muRata
1	C3	180nF	Capacitor, Ceramic, 50V, C0G, 5%	603	C1608C0G1H220J	TDK
2	C5, C7	0.1uF	Capacitor, Ceramic, 50V, C0G, 5%	603	C1608C0G1H220J	TDK
3	C6, C8, C9	1uF	Capacitor, Ceramic, 6.3V, X5R, 20%	603	GRM188R60J106ME47D	muRata
1	R1	1.8k	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R2	30.1k	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R3	47.5k	Resistor, Chip, 1/10W, yy%	805	Std	Std
1	R4	100k	Resistor, Chip, 1/10W, yy%	805	Std	Std
1	R5	475k	Resistor, Chip, 1/10W, yy%	805	Std	Std
1	R6	28k	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	R7	56.2k	Resistor, Chip, 1/16W, 1%	603	Std	Std
1	U1	TPS79501DCQ	IC, LDO Linear Regulator Ultralow-Noise High PSRR Fast RF, 500mA, xxV	SOT223-6	TPS79501DCQ	TI
1	U2	TPS79533DCQ	IC, LDO Linear Regulator Ultralow-Noise High PSRR Fast RF, 500mA, 3.3V	SOT223-6	TPS79533DCQ	TI
1	U3	TPS73101DBV	IC, Cap-Free NMOS, 150mA LDO Regulator With Reverse Current Protection	SOT23-5	TPS73101DBV	TI

1 Block Diagram

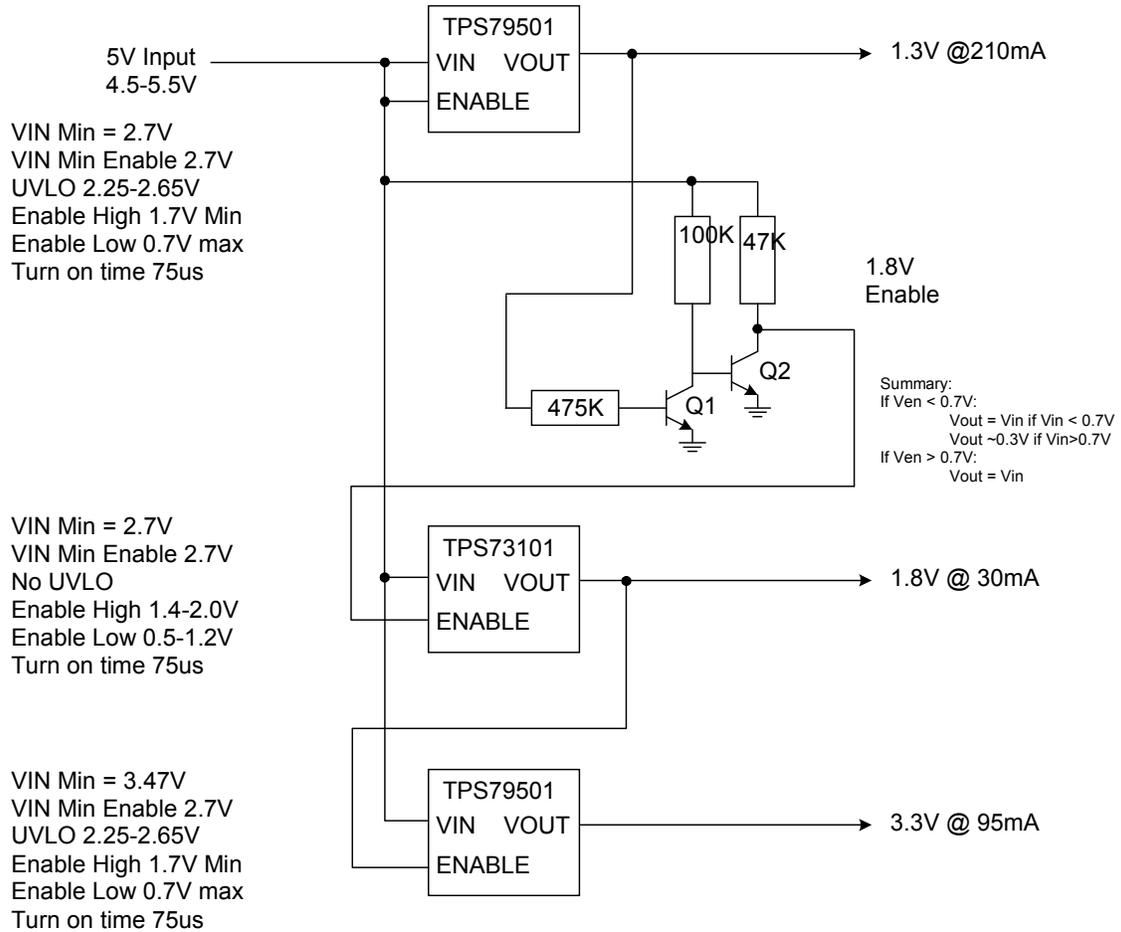


Figure 1. Block Diagram of Power Design

2 Power Up

The figure below shows the startup waveforms after ENABLE is applied. The outputs voltages shown are at full load. (Enable=2.00V/div, 1.3-V=1.00V/div, 1.8-V=1.00V/div, 3.3-V=2.00V/div, 500us/div)

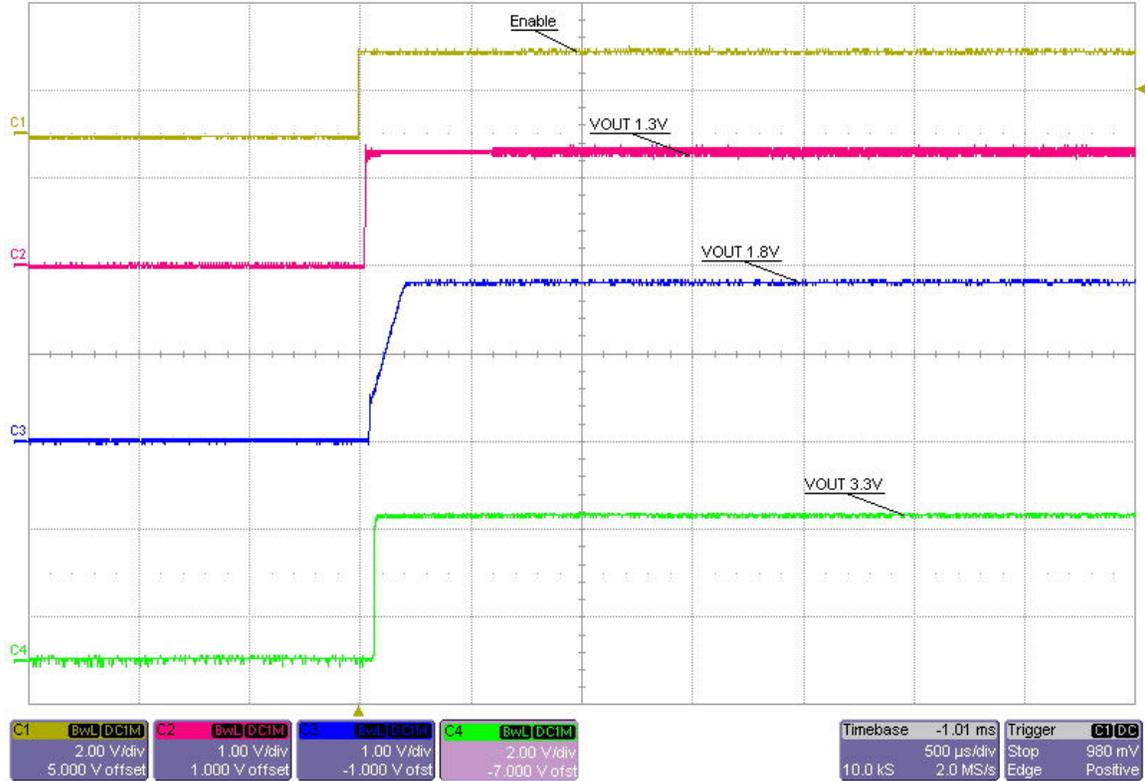


Figure 2. Power Up with 5-V Input and ENABLE Voltage

Once ENABLE is pulled high, the 1.3-V rail comes up and the 1.8V and 3.3V come up together later.

3 Power Down

The figure below shows the power down waveforms after ENABLE is pulled low. The outputs voltages shown are at full load. (Enable=2.00V/div, 1.3-V=1.00V/div, 1.8-V=1.00V/div, 3.3-V=2.00V/div, 500us/div)

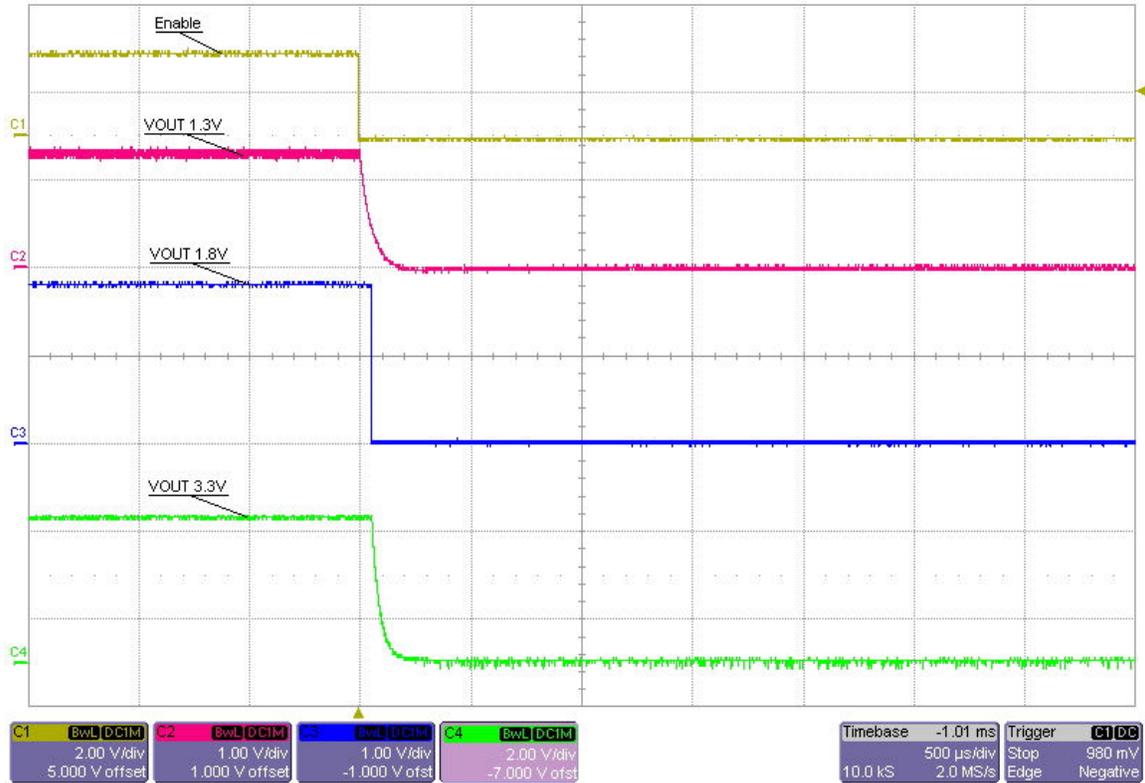


Figure 3. Power Down with 5-V Input and ENABLE Voltage

Once ENABLE is pulled low, the 1.3-V rail starts to come down first, and 1.8V and 3.3V come down after 50 μ s.

Thermal Considerations:

TPS79501: (from page 11 of TPS79501 datasheet)

$$V_{in}=5V, V_{out}=1.3V, I_{out}=210mA$$

$$P_D = (5 - 1.3) * (210) = 780mW$$

For Ambient temperature of 85C

$$R_{\theta JA} = \frac{(125 - 85)C}{780mW} = 51.3 \frac{C}{W}$$

Using Figure 26 of TPS79501 datasheet, with no airflow, the ground plane needs to be approximately 1.5 in² to dissipate 780mW.

<http://focus.ti.com/lit/ds/symlink/tps79501.pdf>

TPS79533: (from page 11 of TPS79501 datasheet)

$$V_{in}=5V, V_{out}=3.3V, I_{out}=95mA$$

$$P_D = (5 - 3.3) * (95) = 162mW$$

For Ambient temperature of 85C

$$R_{\theta JA} = \frac{(125 - 85)C}{162mW} = 247 \frac{C}{W}$$

Using Figure 26 of TPS79501 datasheet, with no airflow, the ground plane needs to be approximately 0.1 in² to dissipate 247mW.

<http://focus.ti.com/lit/ds/symlink/tps79533.pdf>

TPS73101: (from page 11 of TPS79501 datasheet)

$$V_{in}=5V, V_{out}=1.8, I_{out}=30mA$$

$$P_D = (5 - 1.8) * (30) = 96mW$$

For Ambient temperature of 85C, TPS73101 can dissipate 155mW. (page 2 of TPS73101 datasheet power dissipation ratings for Low-K JEDEC board).

<http://focus.ti.com/lit/ds/symlink/tps73101.pdf>

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated