

Texas Instruments TPS62410 & TPS73218

| | | | | | |
|----------|------------------|----------|-------------------------------|--------------|--|
| Title | | | Primus Processor Power Supply | | |
| Size | Number | Rev | | B | |
| B | PMP4078 | B | | B | |
| Date | Mon Feb 15, 2010 | Drawn by | | T. Olabumuyi | |
| Filename | PMP4078_REVB.SCH | Sheet | | 1 of 1 | |

Filename: PMP4078_REVB_bom.xls

Date: 02/15/2010

PMP4078_REVA BOM

| COUNT | RefDes | Value | Description | Size | Part Number | MFR | AREA |
|-------|----------------|-------------|--|--------------------|----------------|-----------|--------|
| 1 | C1 | 33pF | Capacitor, Ceramic, vvV, [temp], [tol] | 0402 | std | std | 2800 |
| 2 | C2, C7 | 22uF | Capacitor, Ceramic, 10V, X5R, 10%, 22uF | 0805 | C2012X5R1A226K | TDK | 10560 |
| 2 | C3, C4 | 1uF | Capacitor, Ceramic, 6.3V, X5R, 15% | 0402 | Std | TDK | 2800 |
| 2 | C5, C6 | 10uF | Capacitor, Ceramic, 10V, X5R, 10% | 0805 | C2012X5R1A106K | TDK | 10560 |
| 2 | L1, L2 | 3.3uH | Inductor, SMT, 1.5 A, 130 milliohm | 0.118 x 0.118 inch | LPS3015-332MLB | Coilcraft | 26,560 |
| 1 | R1 | 182k | Resistor, Chip, 1/16W, x% | 0402 | Std | Std | 2800 |
| 1 | R2 | 825k | Resistor, Chip, 825k, 1/16W, x% | 0402 | Std | Std | 2800 |
| 1 | R3 | 215k | Resistor, Chip, 215k, 1/16W, x% | 0402 | Std | Std | 2800 |
| 1 | R4 | 210k | Resistor, Chip, 1/16W, x% | 0402 | Std | Std | 2800 |
| | TP1, TP2, TP3, | | | | | | |
| 5 | TP4, TP5 | 5006 | Test Point, Black, Thru Hole Compact Style | 0.125 x 0.125 inch | 5006 | Keystone | |
| 1 | U1 | TPS73218DBV | IC, 250mA, Low Iq, Wide Bandwidth, LDO Linear Regulators | SOT23-5 | TPS73218DBV | TI | 23360 |
| 1 | U2 | TPS62410DRC | IC, 2.25 MHz Dual Step Down Converter | QFN10 | TPS62400DRC | TI | 36.229 |



TEXAS
INSTRUMENTS
OMAP-L137 / C6747 / C6745 / C6743
TPS62410, TPS73218 – (PMP4078)
3/24/2010

The following test report includes measurements for the following output voltage rails using a **5V input**.

This design meets the power sequencing requirements required by OMAP-L137 / C6747 / C6745 / C6743.

Contents

Start-Up Waveform

- Unloaded
- Fully Loaded

TPS62410 – Dual Buck (1.2V@0.66A & 3.3V@0.165A)

- Output Ripple
- Output Transient
- Switch Node
- Efficiency
- Regulation

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report



Start Up Waveform

Ch 1: 1.2V unloaded
Ch 2: 3.3V unloaded
Ch 3: 1.8V unloaded

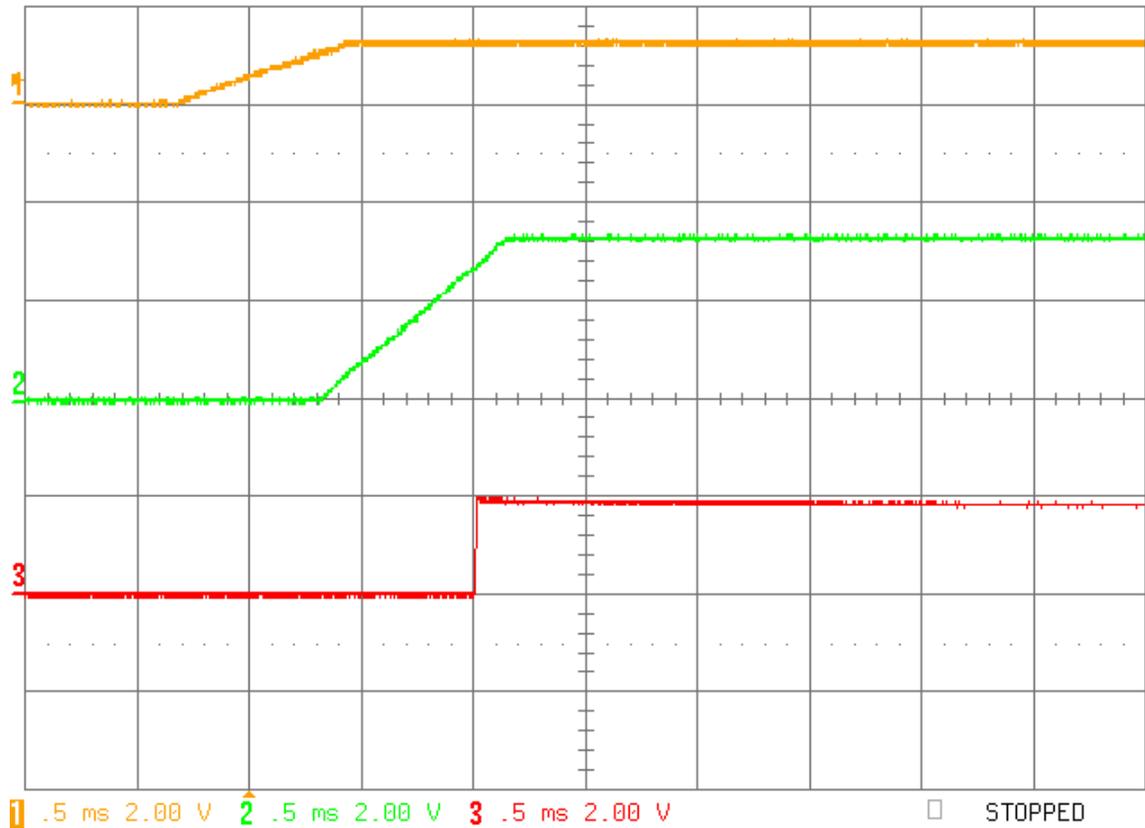


Fig 1: Start up waveform with outputs unloaded

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

Start Up Waveform

Ch 1: 1.2V @ 0.66A (DUAL BUCK OUT 1 TPS62410)
Ch 2: 3.3V @ 0.165A (DUAL BUCK OUT 2 TPS62410)
Ch 3: 1.8V @ 0.05A (LDO TPS 73218)

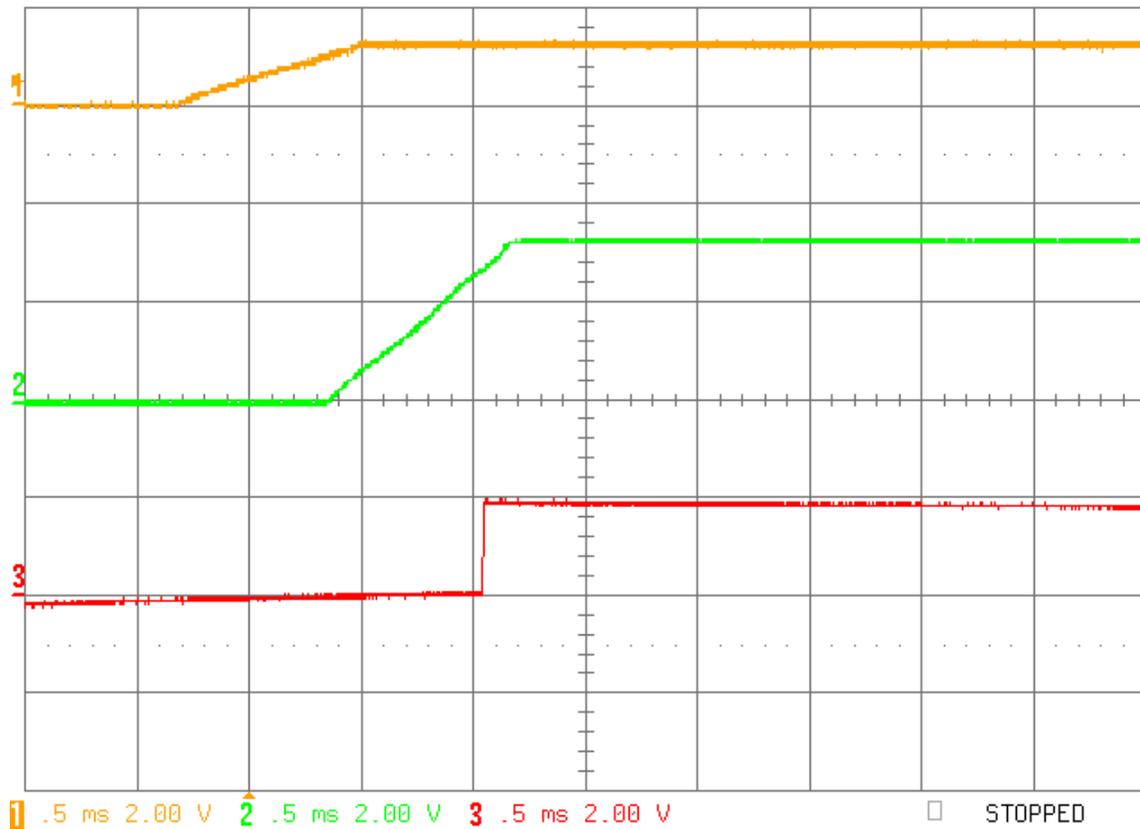


Fig 2: Start up waveform with all outputs fully loaded

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

Dual Buck - TPS62410

NOTES ON POWER SAVE MODE

In this application, MODE/DATA pin is tied low, ensuring the device automatically transitions between power save mode and Pulse Width Modulation (PWM) mode. This increases the efficiency at light loads, at the expense of increase ripple noise. At light loads the converter operates in Pulse Frequency Modulation (PFM) mode.

OUTPUT RIPPLE

Low Line (3.6Vin)

Output Ripple – 1.2V @ 0.66A (TPS 62410 – DCDC 1)

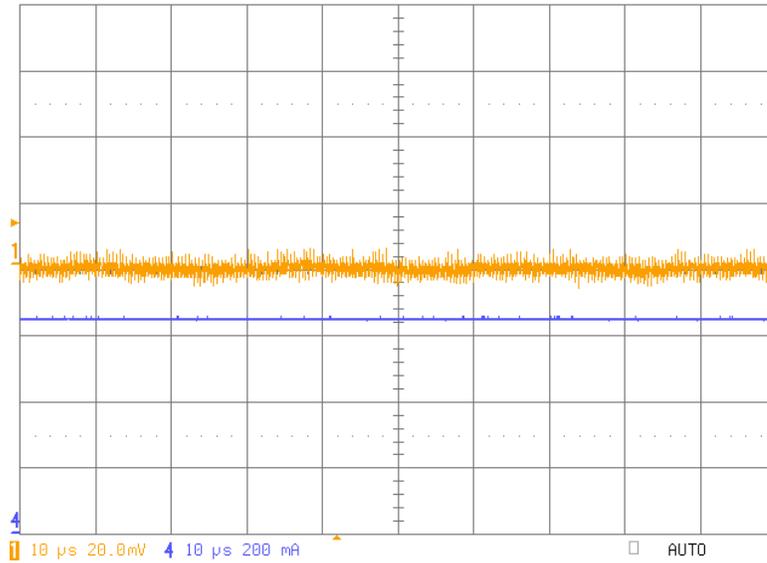


Fig 3: Output ripple on 1.2V @ 0.66A with 3.6Vin (Low line), Ch1: Output ripple, Ch4: Output load

Output Ripple – 3.3V @ 0.165A (TPS 62410 – DCDC2)

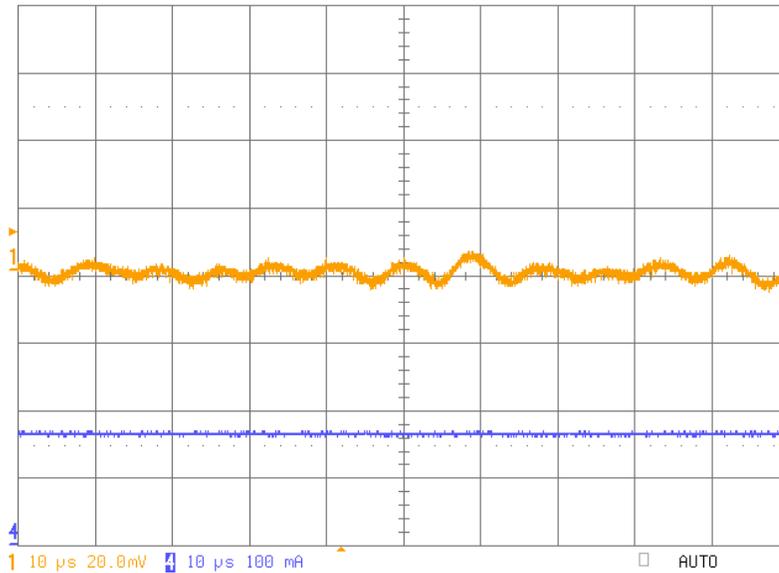


Fig 4: Output ripple on 3.3V @ 0.165A with 3.6Vin (Low Line), Ch1: Output ripple, Ch4: Output load

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

High Line (6Vin)

At high line, with 165mA current on 3.3V output, the controller is operating in transition between PFM and PWM mode, this affects the 1.2V output hence the increased ripple on the outputs as shown in waveform in fig 5 and fig 7.

Output Ripple – 1.2V @ 0.66A (TPS 62410 – DCDC 1)

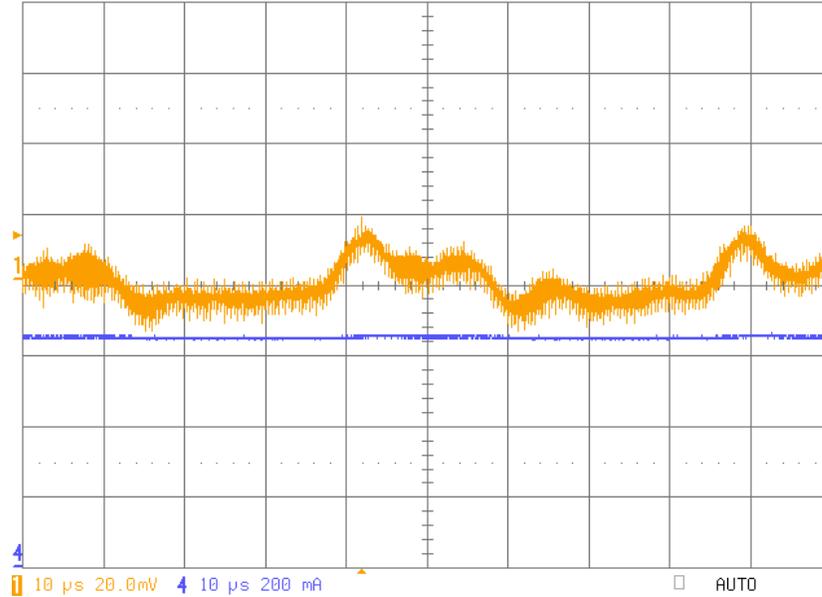


Fig 5: Output ripple on 1.2V @ 0.66A with 6Vin (high line), Ch1: Output ripple, Ch4: Output load

Output Ripple – 3.3V @ 0.04A (TPS 62410 – DCDC2) – Light Load

Device operates in full PFM mode. Fig 6 shows a relatively reduced ripple compared to fig 7

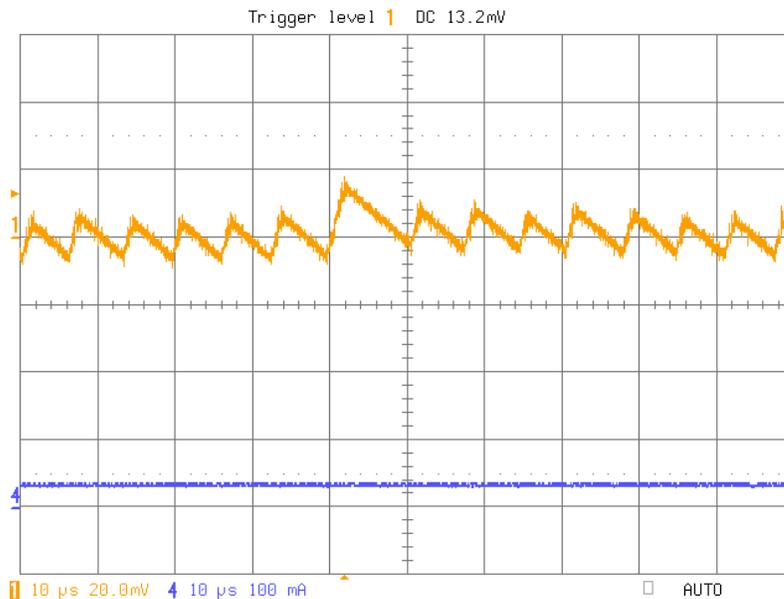


Fig 6: Output ripple on 3.3V @ 0.04A with 6Vin (high line), Ch1: Output ripple, Ch4: Output load

Output Ripple – 3.3V @ 0.165A (TPS 62410 – DCDC2) – Transitioning between modes

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

Device operates in transition between PFM and PWM, hence the increased ripple

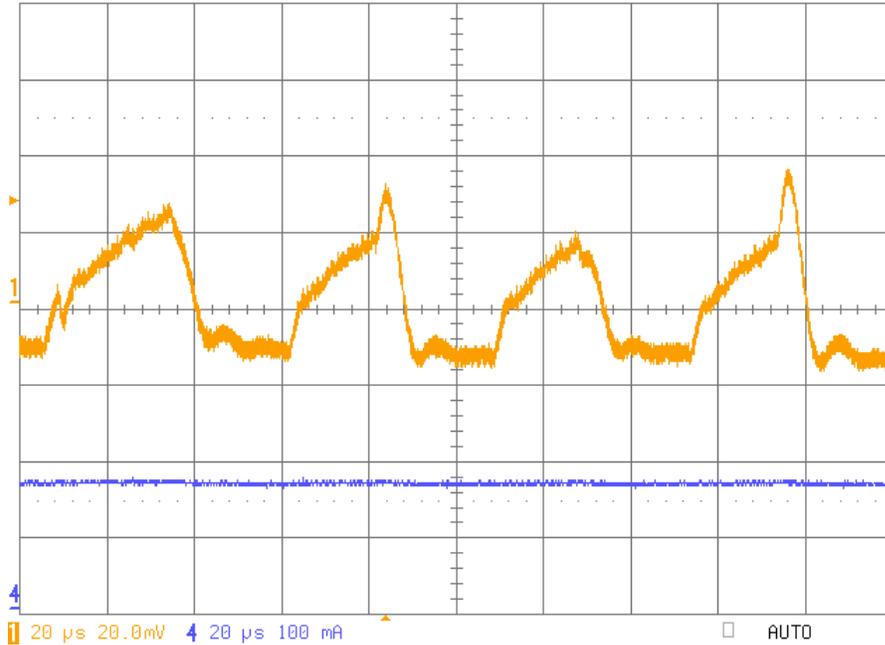


Fig 7: Output ripple on 3.3V @ 0.165A with 6Vin (high line), Ch1: Output ripple, Ch4: Output load

Output Ripple – 3.3V @ 0.2A (TPS 62410 – DCDC2) – PWM Mode

Device operates PWM, hence the reduced ripple

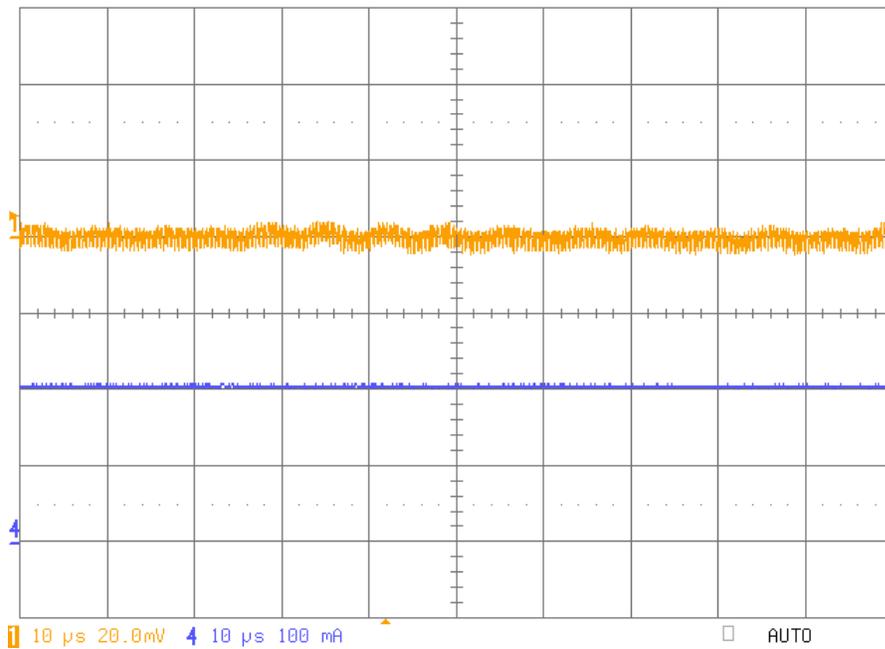


Fig 8: Output ripple on 3.3V @ 0.2A with 6Vin (high line), Ch1: Output ripple, Ch4: Output load

TRANSIENT RESPONSE

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

Low Line (3.6Vin)

50% to 100% Transient – 1.2V @ 0.66A (TPS 62410 – DCDC 1)

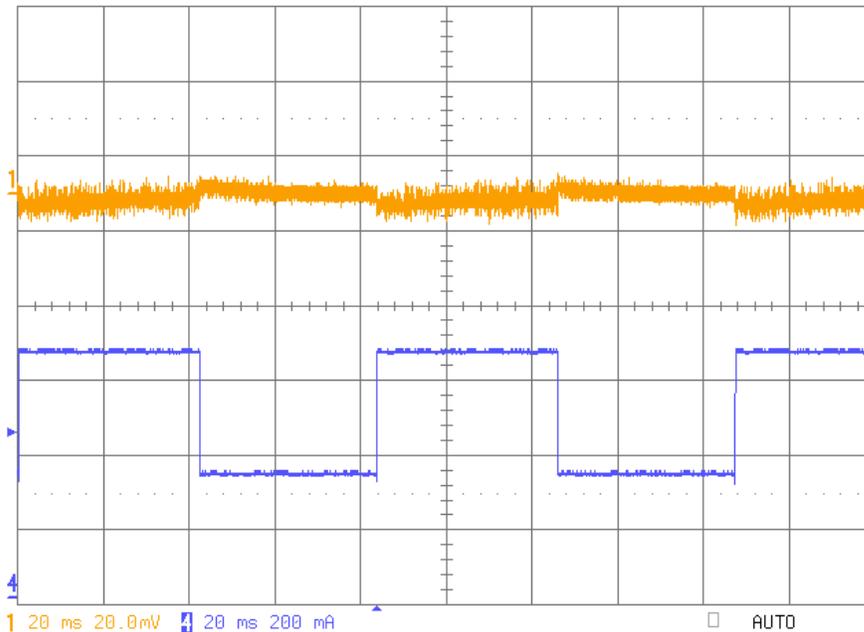


Fig 9: 50% to 100% transient 1.2V @0.66A output with 3.6Vin. Ch 1: 1.2V output; Ch 4: Load current

50% to 100% Transient – 3.3V @ 0.165A (TPS 62410 – DCDC2)

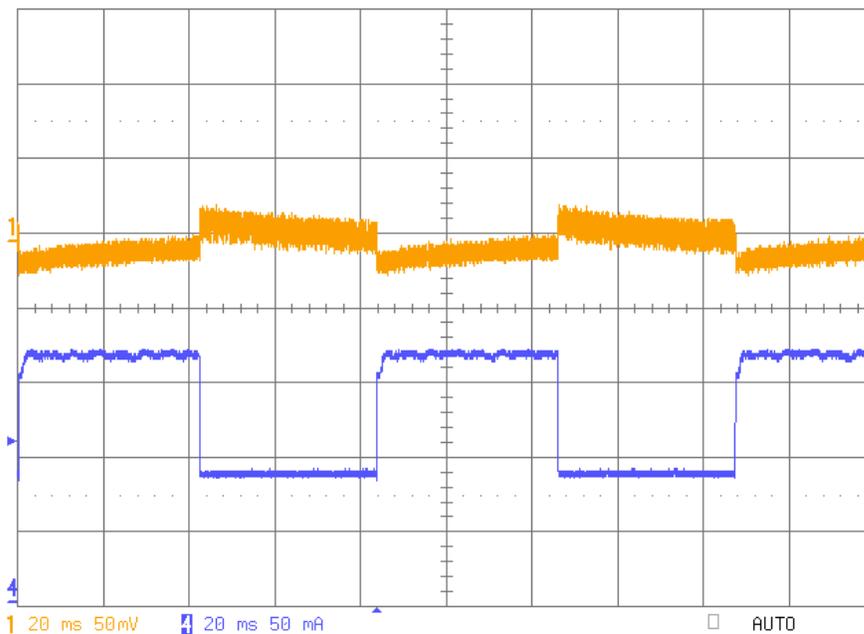


Fig 10: 50% to 100% transient 3.3V @ 0.165A output with 3.6Vin.
Ch 1: 3.3V output; Ch 4: Load current

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

High Line (6Vin)

50% to 100% Transient – 1.2V @ 0.66A (TPS 62410 – DCDC 1)

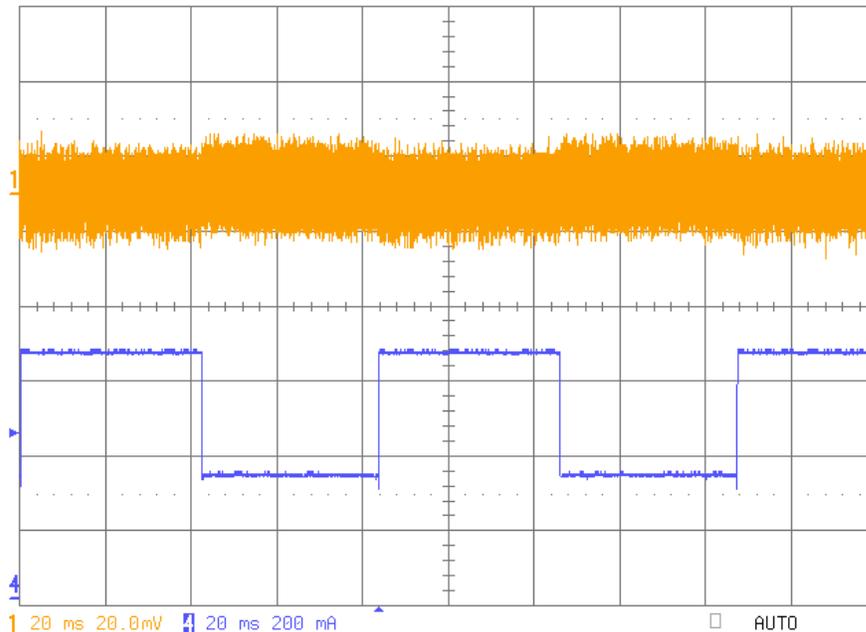


Fig 11: 50% to 100% transient 1.2V @ 0.66A output with 6Vin.
Ch 1: 1.2V output; Ch 4: Load current

50% to 100% Transient – 3.3V @ 0.165A (TPS 62410 – DCDC2)

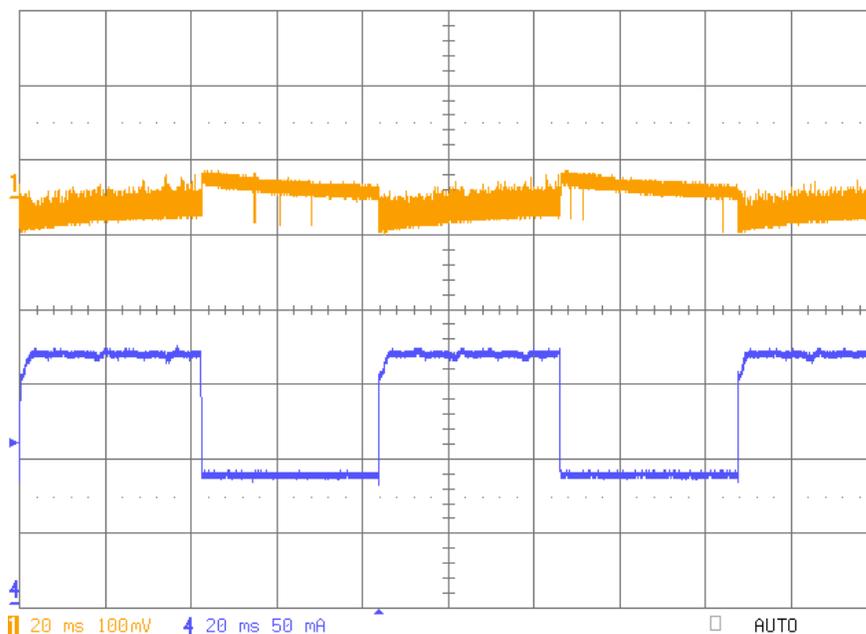


Fig 12: 50% to 100% transient 3.3V @ 0.66A output with 6Vin.
Ch 1: 3.3V output; Ch 4: Load current

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

SWITCH NODE

Fig 13 and 14 shows the switch node with both converters in PWM mode and 5V input
Switch Node – 1.2V @ 0.66A (TPS 62410 – DCDC 1)

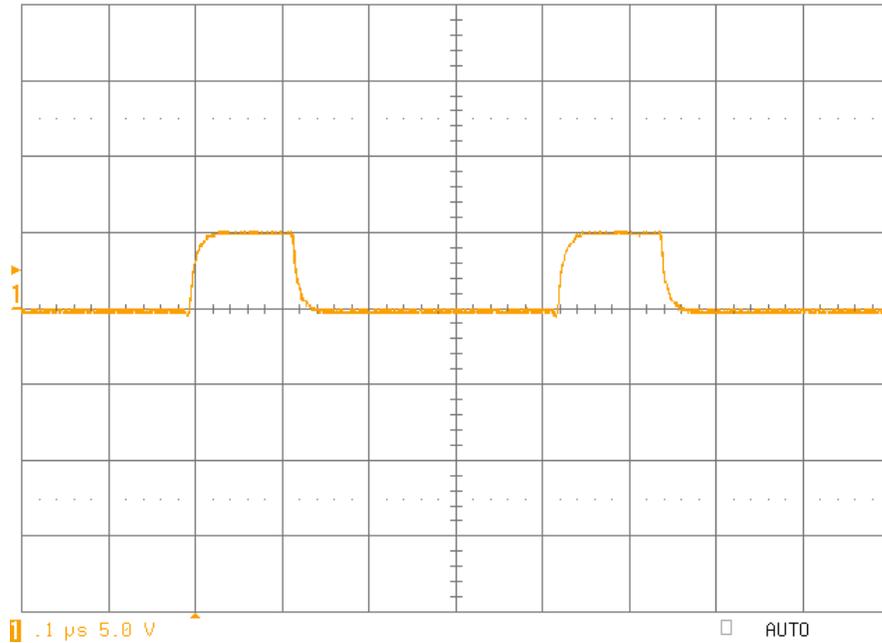


Fig 13: Switch Node on 1.2V@ 0.66A (PWM Mode)

Switch Node – 3.3V @ 0.165A (TPS 62410 – DCDC2)

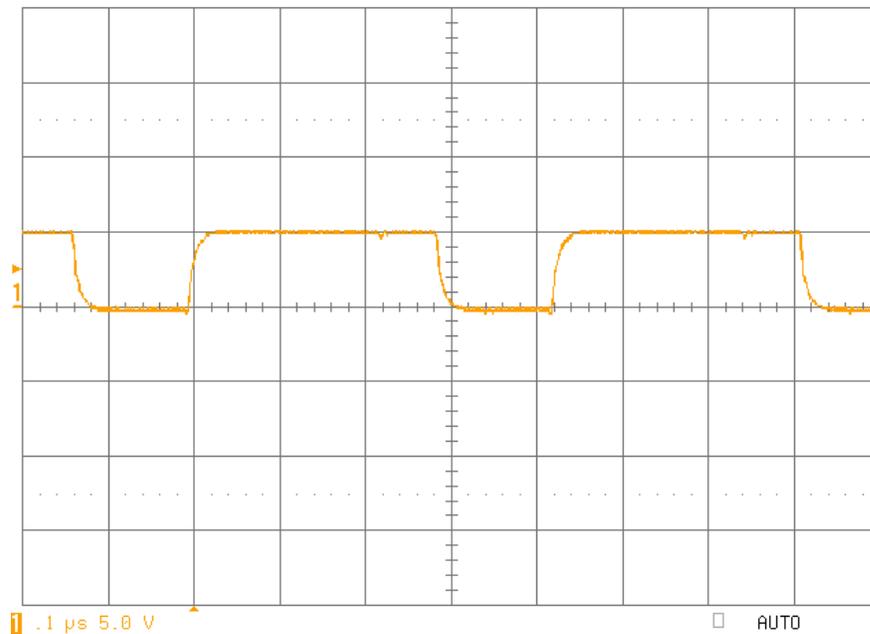


Fig 14: Switch Node on 3.3V@ 0.2A (PWM Mode)

Combined Efficiency (3.3V & 1.2V)

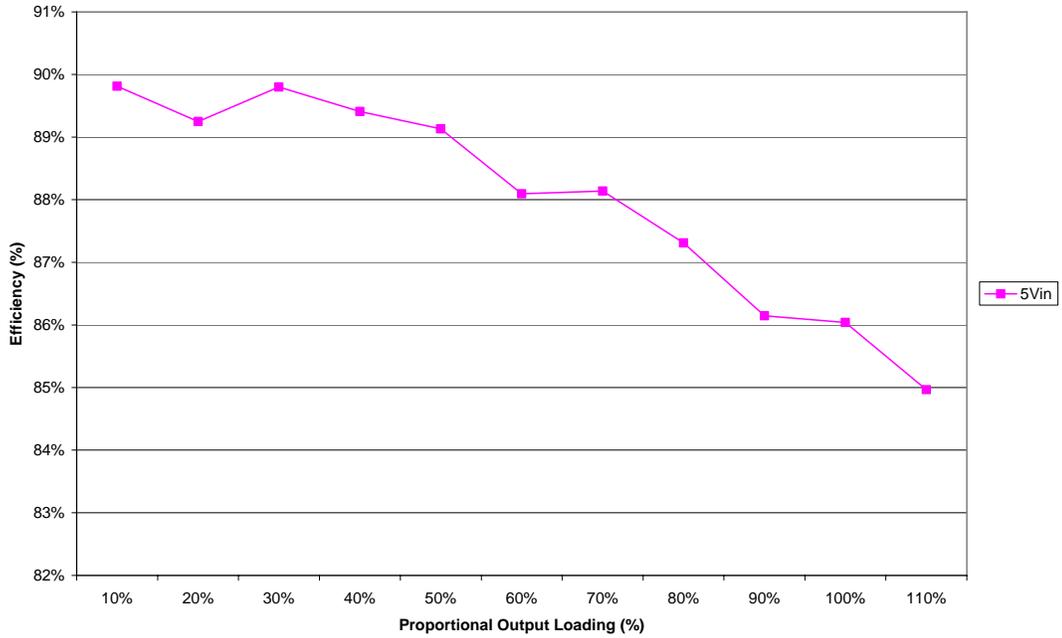


Fig 15: Combined Efficiency of 3.3V and 1.2V

OMAP-L137 / C6747 / C6745 / C6743

TPS62410, TPS73218 Test Report

LOAD REGULATION

TPS 62410 -& 1.2V@0.66A

1.2V@0.66A Load Regulation

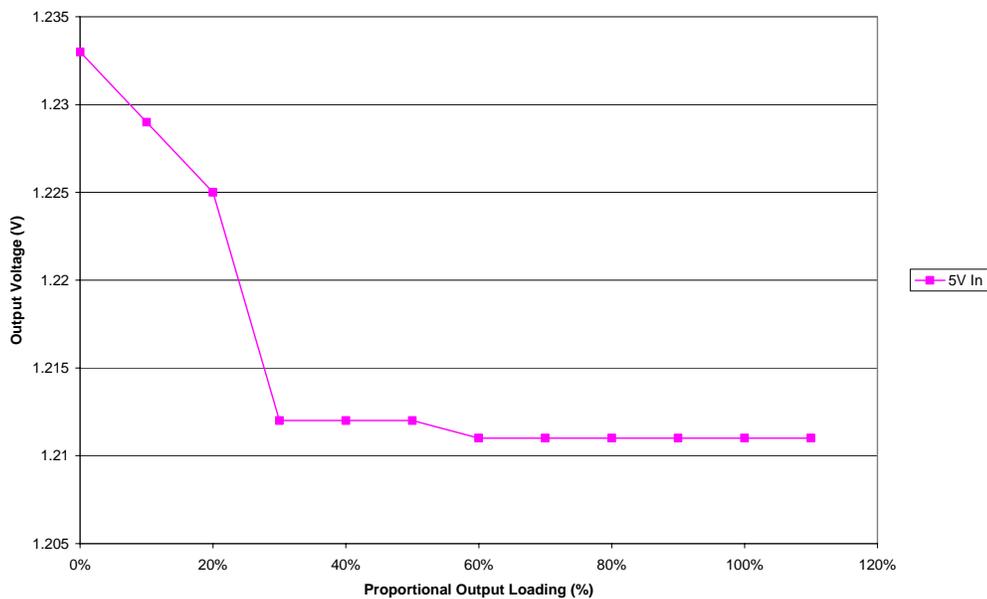


Fig 16: Load regulation on 1.2V output, 3.3V output is proportionally loaded

TPS 62410 - 3.3V@0.165A

3.3V@0.165A Load Regulation

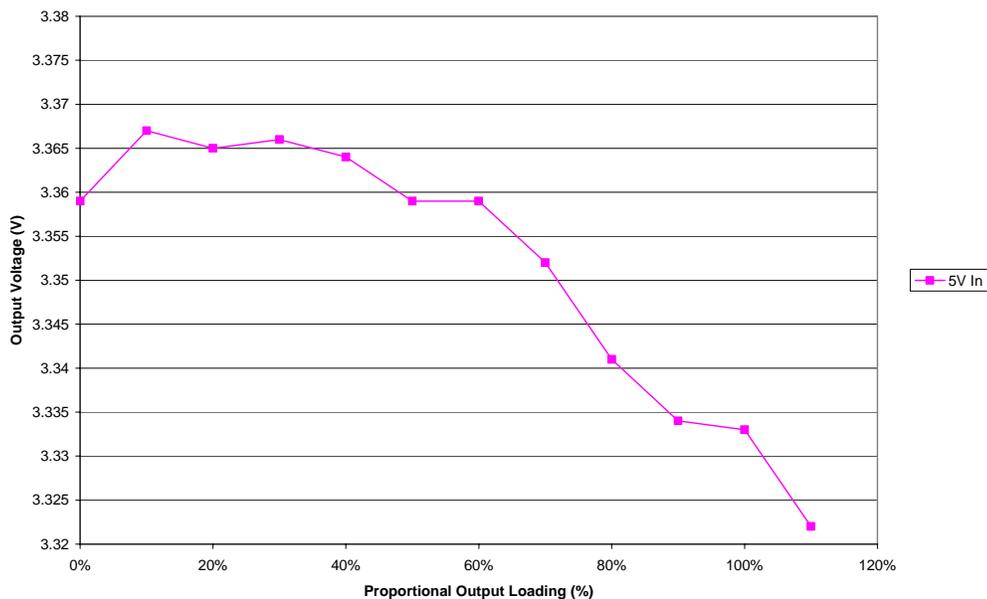


Fig 17: Load regulation on 3.3V output, 1.2V output is proportionally loaded

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|-----------------------------|--|----------------------------|--|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DLP® Products | www.dlp.com | Communications and Telecom | www.ti.com/communications |
| DSP | dsp.ti.com | Computers and Peripherals | www.ti.com/computers |
| Clocks and Timers | www.ti.com/clocks | Consumer Electronics | www.ti.com/consumer-apps |
| Interface | interface.ti.com | Energy | www.ti.com/energy |
| Logic | logic.ti.com | Industrial | www.ti.com/industrial |
| Power Mgmt | power.ti.com | Medical | www.ti.com/medical |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| RFID | www.ti-rfid.com | Space, Avionics & Defense | www.ti.com/space-avionics-defense |
| RF/IF and ZigBee® Solutions | www.ti.com/lprf | Video and Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless-apps |

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated