

Powering the DM335 and DM355 with the TPS650061

Daniel Acevedo
Battery Power Applications

ABSTRACT

This document details the design considerations of a low-cost power solution for the TMS320DM335 and TMS320DM355 (DM335/55) low-power application processors with a TPS650061, three-rail Power Management Unit (PMU) or Power Management IC (PMIC).

Portable application solution size demands a high level of integration and the DM335/55 require at least three different voltage rails with specific sequencing and reset requirements. The TPS650061 is a highly integrated low-cost power solution that can provide the 1.3 V, 1.8 V and 3.3 V rails and $\overline{\text{RESET}}$ signal required by the DM335/55. The TPS650061 has a single step-down converter, two low dropout regulators and a voltage supervisor.

Included in this document is a power solution for the DM335/55. Power requirements, illustrated schematic, operation waveforms and bill of materials are included.

Contents

1	Power Requirements	2
1.1	Power-On Sequence	2
1.2	Power-Off Sequence	2
1.3	Power Solution	3
2	Schematic, Waveforms, and Bill of Materials	4
2.1	Schematic	4
2.2	Waveforms	5
2.3	Bill of Materials	6
3	Conclusion	6
4	References	6

List of Figures

1	TPS650061 and DM335/55 Simplified Block Diagram	2
2	TPS650061 Schematic Diagram	4
3	TPS650061 Power-Up, Ch. 1 - VIN, Ch. 2 - 1.3V Rail, Ch. 3 - 1.8V Rail, Ch. 4 - 3.3V Rail.....	5
4	TPS650061 Power-Up and $\overline{\text{RESET}}$, Ch. 1 - $\overline{\text{RESET}}$, Ch. 2 - 1.3V Rail, Ch. 3 - 1.8V Rail, Ch. 4 - 3.3V Rail	5
5	TPS650061 Power-Off Sequence, Ch. 1 - $\overline{\text{RESET}}$, Ch. 2 - 1.3V Rail, Ch. 3 - 1.8V Rail, Ch. 4 - 3.3V Rail	5

List of Tables

1	DM335/55 Power Requirements	2
2	Bill of Materials	6

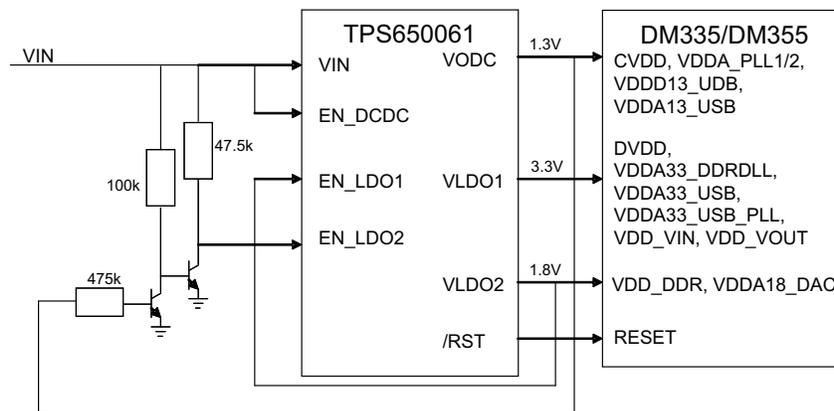


Figure 1. TPS650061 and DM335/55 Simplified Block Diagram

1 Power Requirements

The DM335/55 power requirements are listed in [Table 1](#).

Table 1. DM335/55 Power Requirements

Rail Name	Voltage (V)	I _{max} (mA)	Tolerance	Power-On	Power-Off
CVDD, VDDA_PLL1, VDDA_PLL2, VDDD13_USB, VDDA13_USB	1.3	210	±5%	1 st	2 nd
VDD_DDR, VDDA18_DAC	1.8	30	±5%	2 nd	1 st
DVDD, VDDA33_DDRDLL, VDDA33_USB, VDDA33_USB_PLL, VDD_VIN, VDD_VOUT	3.3	95	±5%	2 nd	1 st

The TPS650061 meets these power requirements with its single step-down converter, two low dropout regulators and voltage supervisor.

1.1 Power-On Sequence

To meet the DM335/55 power-on requirements, the 1.3V rail must power on first, then both the 1.8V rail and the 3.3V. After all 3 rails are powered on RESET may be released.

The power-on sequence is described in the following text from the DM335/355 datasheet.

Per the excerpt from the DM335/55 datasheet, the device should be powered-on in the following order:

1. Power on 1.3 V: CVDD, VDDA_PLL1/2, VDDD13_USB, VDDA13_USB
2. Power on 1.8 V: VDD_DDR, VDDA18_DAC
3. Power on 3.3 V: DVDD, VDDA33_DDRDLL, VDDA33_USB, VDDA33_USB_PLL, VDD_VIN, VDD_VOUT

You may power-on the 1.8 V and 3.3 V power supplies simultaneously

1.2 Power-Off Sequence

The DM335/55 power-down requirements state that the 1.8 V and 3.3 V supplies should power off together, before the 1.3 V supply as describe in the DM335/355 datasheet excerpt below:

1. Power off 3.3 V: DVDD, VDDA33_DDRDLL, VDDA33_USB, VDDA33_USB_PLL, VDD_VIN, VDD_VOUT
2. Power off 1.8 V: VDD_DDR, VDDA18_DAC
3. Power off 1.3 V: CVDD, VDDA_PLL1/2, VDDD13_USB, VDDA13_USB

You may power-off the 1.8 V and 3.3 V power supplies simultaneously.

Power-off the 1.8V/3.3V supply before or within 10usec of power-off of the 1.3 V supply

1.3 Power Solution

To best achieve this power up/down sequence and minimize cost, two 2N222 transistors are used in conjunction with the TPS650061.

- The enable for the 1.3V supply (EN_DCDC) is connected to VIN.
- The output, VODC, is connected to the base of an NPN transistor, Q1. The collector of Q1 has a 100 kΩ pull-up to VIN; the emitter is connected to ground.
- The collector of Q1 is also connected to the base of another NPN transistor, Q2. The collector of Q2 has a 47.5k pull-up to VIN; the emitter is connected to ground
- The collector of Q2 is also connected to the enable of the 1.8 V supply (EN_LDO2).
- The 1.8 V supply (VLDO2) is connected to the enable of the 3.3 V supply (EN_LDO1).
- When VIN is applied, it will turn on the 1.3 V supply (VODC) and Q2; keeping EN_VLDO2 tied to ground.
- VODC will then turn on Q1 which will turn-off Q2 and enable VLDO2 when EN_LDO2 gets pulled-up to VIN.
- VLDO2 will enable VLDO1.
- During power-off, the 3.3 V rail ramps down with VIN as VIN nears VOUT, then the 1.8 V rail, then the 1.3 V rail.
- A resistor divider connects RSTSNS to VLDO1, the \overline{MR} pin is connected to VODC and the pin \overline{RST} is pulled up to VLDO2. This will assert the reset to 1.8 V only when all three supplies are up.
- Additionally, to add deglitch time to the \overline{RESET} , a capacitor (C5) can be added in parallel with the top resistor of the RTSNS divider.

The proper connections for the power-on/off sequence are shown in [Figure 1](#).

2.2 Waveforms

The following waveforms demonstrate the startup and power down sequence of the TPS650061 as required by the DM335/55. **Figure 3**, shows the TPS650061 power on sequence of 1.3V then 1.8 V and 3.3 V. **Figure 4** shows the reset pin, RST, being released after the voltage on RSTNS rises above the threshold and after the reset recovery time, t_{RST} , is exceeded. **Figure 5** shows the power down sequence, 3.3 V and 1.8 V then the 1.3 V supply. For the following tests, the 1.3V supply had a 200mA load, the 1.8V supply had a 95mA load and the 3.3V supply had a 30mA load.

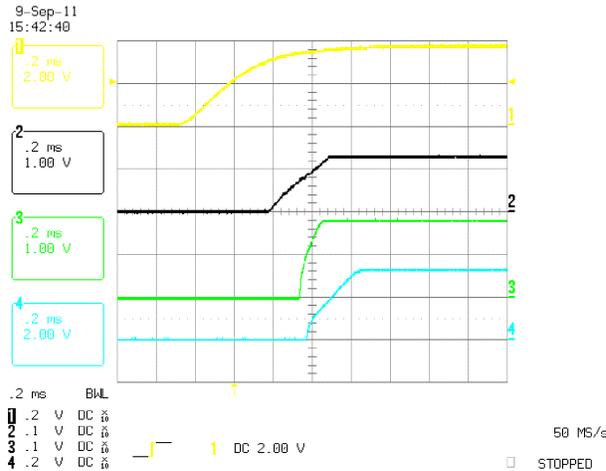


Figure 3. TPS650061 Power-Up, Ch. 1 - VIN, Ch. 2 - 1.3V Rail, Ch. 3 - 1.8V Rail, Ch. 4 - 3.3V Rail

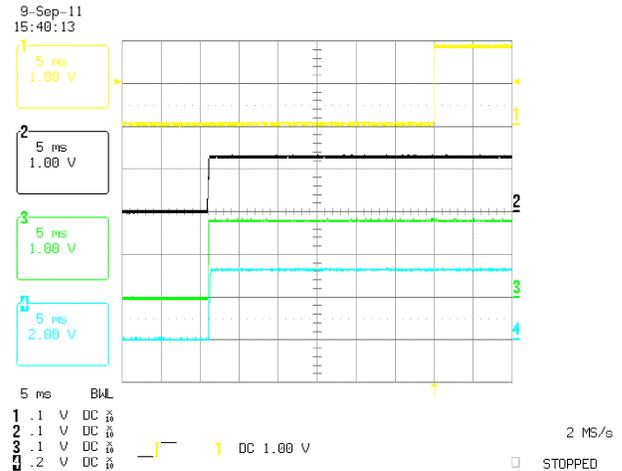


Figure 4. TPS650061 Power-Up and RESET, Ch. 1 - RESET, Ch. 2 - 1.3V Rail, Ch. 3 - 1.8V Rail, Ch. 4 - 3.3V Rail

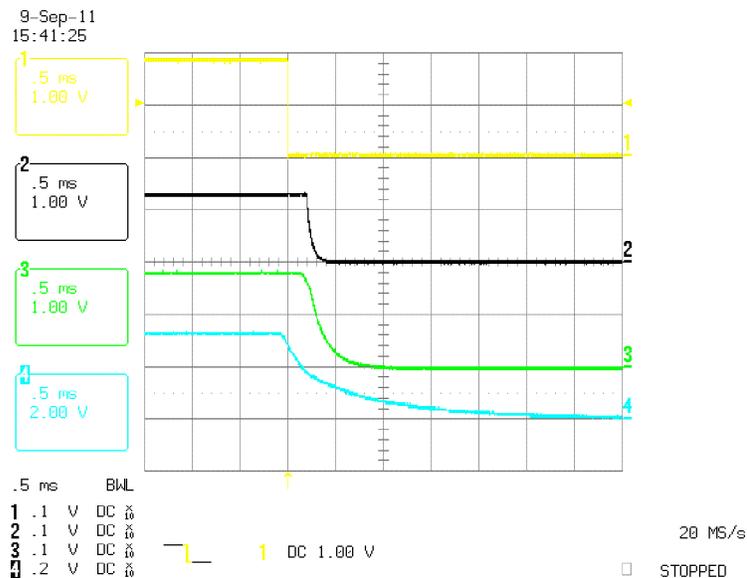


Figure 5. TPS650061 Power-Off Sequence, Ch. 1 - RESET, Ch. 2 - 1.3V Rail, Ch. 3 - 1.8V Rail, Ch. 4 - 3.3V Rail

2.3 Bill of Materials

The bill of materials is displayed in [Table 2](#).

Table 2. Bill of Materials

Count	RefDes	Value	Description	Size	Part Number	MFR
4	C1, C6, C8, C9	10uF	Capacitor, Ceramic, 10V, X5R, 10%,	0805	Std	Std
2	C2, C3	2.2uF	Capacitor, Ceramic, 10V, X5R, 10%	0603	Std	Std
1	C4	0.1uF	Capacitor, Ceramic, 16V, X7R, 10%	0603	Std	Std
1	C7	22pF	Capacitor, Ceramic, 50V, C0G, 5%	0603	Std	Std
1	L1	2.2uH	Inductor, SMT, 2.0A, 110milliohm	0.118 x 0.118 inch	LPS3015-222ML	Coilcraft
2	Q1, Q2	2N2222	Transistor, NPN, 40V	SOT-23	2N2222	Std
2	R2, R9	47.5k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R3	976k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
2	R5, R7	475k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R4	232K	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R6	402k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	R8	100k	Resistor, Chip, 1/16W, 1%	0603	Std	Std
1	U1	TPS650061RUK	IC, 2.25 MHz Step Down Converter with Dual LDOs and SVS	QFN	TPS650061RUK	TI

3 Conclusion

The TPS650061 provides a low cost, comprehensive power solution for the DM335/55. A 1.3 V rail (capable of supplying 1 A) is powered on followed by a 1.8 V rail (300 mA) then a 3.3 V rail (300 mA). Once all three supplies have reached regulation, **RESET** goes high (i.e. rises to its pull-up voltage). For power-down, the 1.8 V and 3.3 V turn off before the 1.3 V rail. This meets the power requirements of the DM335/55.

4 References

1. TPS650061 Datasheet ([SLVS810B](#))
2. DM335 Datasheet ([SPRS528](#))
3. DM355 Datasheet ([SPRS463](#))
4. 5Vin DM355 Power using LDO's ([SLVR331B](#))

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated