

# Analysis of fully differential amplifiers

By Jim Karki

Systems Specialist, High-Speed Amplifiers

## Introduction

The August issue of *Analog Applications Journal* introduced the fully differential amplifiers from Texas Instruments and illustrated their basic operation (see Reference 1). This article explores the topic more deeply by analyzing gain and noise. The fully differential amplifier has multiple feedback paths, and circuit analysis requires close attention to detail. Care must be taken to include the  $V_{OCM}$  pin for a complete analysis.

## Circuit analysis

Circuit analysis of fully differential amplifiers follows the same rules as normal single-ended amplifiers, but subtleties are present that may not be fully appreciated until a full analysis is done. The analysis circuit shown in Figure 1 is used to calculate a generalized circuit formula and block

diagram from which specific circuit configurations can be easily solved. The voltage definitions are required to arrive at practical solutions.

$A_F$  is used to represent the open-loop differential gain of the amplifier such that  $(V_{OUT+}) - (V_{OUT-}) = A_F(V_P - V_N)$ . This assumes that the gains of the two sides of the differential amplifier are well matched and that variations are insignificant. With negative feedback, this is typically the case when  $A_F \gg 1$ .

### Input voltage definitions:

$$V_{ID} = (V_{IN+}) - (V_{IN-}) \tag{1}$$

$$V_{IC} = \frac{(V_{IN+}) + (V_{IN-})}{2} \tag{2}$$

### Output voltage definitions:

$$V_{OD} = (V_{OUT+}) - (V_{OUT-}) \tag{3}$$

$$V_{OC} = \frac{(V_{OUT+}) + (V_{OUT-})}{2} \tag{4}$$

$$(V_{OUT+}) - (V_{OUT-}) = A_F (V_P - V_N) \tag{5}$$

$$V_{OC} = V_{OCM} \tag{6}$$

There are two amplifiers: the main differential amplifier (from  $V_{IN}$  to  $V_{OUT}$ ) and the  $V_{OCM}$  error amplifier. The operation of the  $V_{OCM}$  error amplifier is the simpler of the two and will be considered first. It may help to review the simplified schematic shown in Reference 1.

$V_{OUT+}$  and  $V_{OUT-}$  are filtered and summed by an internal RC network. The  $V_{OCM}$  amplifier samples this voltage and compares it to the voltage applied to the  $V_{OCM}$  pin. An internal feedback loop is used to drive "error" voltage of the  $V_{OCM}$  error amplifier (the voltage between the input pins) to zero, so that  $V_{OC} = V_{OCM}$ . This is the basis of the voltage definition given in Equation 6.

There is no simple way to analyze the main differential amplifier except to sit down and write some node equations, then do the algebra to massage them into practical form. We will first derive a solution based solely on nodal analysis. Then we will make use of the voltage definitions given in Equations 1–6 to derive solutions for the output voltages, looking at them single-ended; i.e.,  $V_{OUT+}$  and  $V_{OUT-}$ . These are then used to calculate  $V_{OD}$ .

Figure 1. Analysis circuit


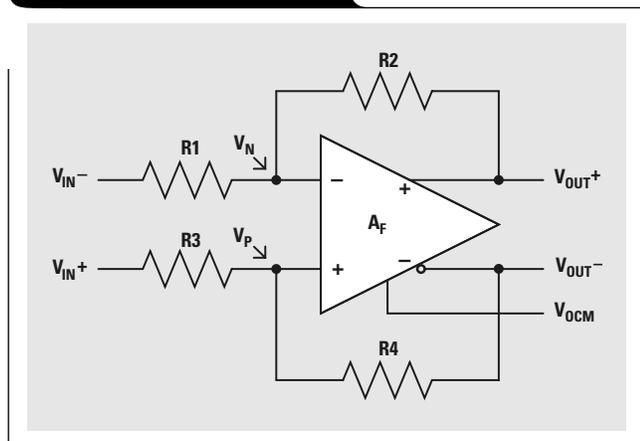


Figure 2. Block diagram

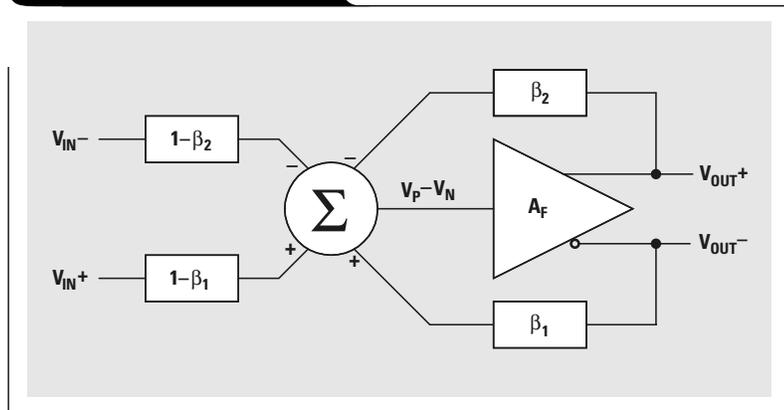

Solving the node equations at  $V_N$  and  $V_P$  yields

$$V_N = (V_{IN-}) \left( \frac{R_2}{R_1 + R_2} \right) + (V_{OUT+}) \left( \frac{R_1}{R_1 + R_2} \right) \quad \text{and} \quad V_P = (V_{IN+}) \left( \frac{R_4}{R_3 + R_4} \right) + (V_{OUT-}) \left( \frac{R_3}{R_3 + R_4} \right).$$

By setting  $\beta_1 = \left( \frac{R_3}{R_3 + R_4} \right)$  and  $\beta_2 = \left( \frac{R_1}{R_1 + R_2} \right)$ ,  $V_N$  and  $V_P$  can be rewritten as

$$V_N = (V_{IN-})(1 - \beta_2) + (V_{OUT+})(\beta_2), \quad \text{and} \quad (7)$$

$$V_P = (V_{IN+})(1 - \beta_1) + (V_{OUT-})(\beta_1). \quad (8)$$

With Equations 7 and 8, a block diagram of the main differential amplifier can be constructed, like that shown in Figure 2. Block diagrams are useful tools for understanding circuit operation and investigating other variations.

By using the block diagram, or combining Equations 7 and 8 with Equation 5, we can find the input-to-output relationship:

$$(V_{OUT+})(1 + A_F\beta_2) - (V_{OUT-})(1 + A_F\beta_1) = A_F[(V_{IN+})(1 - \beta_1) - (V_{IN-})(1 - \beta_2)]. \quad (9)$$

Although accurate, Equation 9 is somewhat cumbersome when the feedback paths are not symmetrical. By using the voltage definitions given in Equations 1–4 and Equation 6, we can derive more practical formulas.

Substituting  $(V_{OUT-}) = 2V_{OC} - (V_{OUT+})$ , and  $V_{OC} = V_{OCM}$ , we can write

$$(V_{OUT+})(2 + A_F\beta_1 + A_F\beta_2) - 2V_{OCM}(1 + A_F\beta_1) = A_F[(V_{IN+})(1 - \beta_1) - (V_{IN-})(1 - \beta_2)], \quad \text{or}$$

$$(V_{OUT+}) = \frac{1}{(\beta_1 + \beta_2)} \frac{(V_{IN+})(1 - \beta_1) - (V_{IN-})(1 - \beta_2) + 2V_{OCM} \left( \frac{1}{A_F} + \beta_1 \right)}{\left( 1 + \frac{2}{A_F\beta_1 + A_F\beta_2} \right)}. \quad (10)$$

With the “ideal” assumption  $A_F\beta_1 \gg 1$  and  $A_F\beta_2 \gg 1$ , this reduces to

$$(V_{OUT+}) = \frac{(V_{IN+})(1 - \beta_1) - (V_{IN-})(1 - \beta_2) + 2V_{OCM}\beta_1}{(\beta_1 + \beta_2)}. \quad (11)$$

$V_{OUT-}$  is derived in a similar manner:

$$(V_{OUT-}) = \frac{1}{(\beta_1 + \beta_2)} \frac{-(V_{IN+})(1 - \beta_1) + (V_{IN-})(1 - \beta_2) + 2V_{OCM} \left( \frac{1}{A_F} + \beta_2 \right)}{\left( 1 + \frac{2}{A_F\beta_1 + A_F\beta_2} \right)}. \quad (12)$$

Again, assuming  $A_F\beta_1 \gg 1$  and  $A_F\beta_2 \gg 1$ , this reduces to

$$(V_{OUT-}) = \frac{-(V_{IN+})(1 - \beta_1) + (V_{IN-})(1 - \beta_2) + 2V_{OCM}(\beta_2)}{(\beta_1 + \beta_2)}. \quad (13)$$

To calculate  $V_{OD} = (V_{OUT+}) - (V_{OUT-})$ , subtract Equation 12 from Equation 10:

$$V_{OD} = \frac{1}{(\beta_1 + \beta_2)} \frac{2[(V_{IN+})(1 - \beta_1) - (V_{IN-})(1 - \beta_2)] + 2V_{OCM}(\beta_1 - \beta_2)}{\left( 1 + \frac{2}{A_F\beta_1 + A_F\beta_2} \right)}. \quad (14)$$

Continued on next page

Continued from previous page

Again, assuming  $A_F\beta_1 \gg 1$  and  $A_F\beta_2 \gg 1$ , this reduces to

$$V_{OD} = \frac{2[(V_{IN+})(1-\beta_1)-(V_{IN-})(1-\beta_2)]+2V_{OCM}(\beta_1-\beta_2)}{(\beta_1+\beta_2)} \quad (15)$$

It can be seen from Equations 11, 13, and 15 that even though the obvious use of a fully differential amplifier is with symmetrical feedback, the gain can be controlled with only one feedback path.

Using matched resistors  $R1 = R3$  and  $R2 = R4$  in the analysis circuit of Figure 1 balances the feedback paths so that  $\beta_1 = \beta_2 = \beta$ , and the transfer function is

$$\frac{(V_{OUT+})-(V_{OUT-})}{(V_{IN+})-(V_{IN-})} = \frac{A_F}{(1+A_F\beta)} = \frac{1-\beta}{\beta} \times \frac{1}{\left(1+\frac{1}{A_F\beta}\right)}$$

The common-mode voltages at the input and output do not enter into the equation,  $V_{IC}$  is rejected, and  $V_{OC}$  is set by the voltage at  $V_{OCM}$ . The ideal gain (assuming  $A_F\beta \gg 1$ ) is set by the ratio

$$\frac{1-\beta}{\beta} = \frac{R2}{R1}$$

Note that the normal inversion we might expect, given two balanced inverting amplifiers, is accounted for by the output voltage definitions, resulting in a positive gain.

Many applications require that a single-ended signal be converted to a differential signal. The circuits in Figures 3–7 show various approaches. Using Equations 11, 13, and 15, we can easily derive circuit solutions.

With a slight variation of Figure 1 as shown in Figure 3, single-ended signals can be amplified and converted to differential signals.  $V_{IN-}$  is now grounded and the signal is applied to  $V_{IN+}$ . Substituting  $V_{IN-} = 0$  in Equations 11, 13, and 15 results in

$$(V_{OUT+}) = \frac{(V_{IN+})(1-\beta_1)+2V_{OCM}\beta_1}{(\beta_1+\beta_2)}$$

$$(V_{OUT-}) = \frac{2V_{OCM}\beta_2-(V_{IN+})(1-\beta_1)}{(\beta_1+\beta_2)}, \text{ and}$$

$$V_{OD} = \frac{2(V_{IN+})(1-\beta_1)+2V_{OCM}(\beta_1-\beta_2)}{(\beta_1+\beta_2)}$$

If the signal is not referenced to ground, the reference voltage will be amplified along with the desired signal, reducing the dynamic range of the amplifier. To strip unwanted dc offsets, use a capacitor to couple the signal to  $V_{IN+}$ . Keeping  $\beta_1 = \beta_2$  will prevent  $V_{OCM}$  from causing an offset in  $V_{OD}$ .

The circuits in Figures 4–7 have nonsymmetrical feedback. This causes  $V_{OCM}$  to influence  $V_{OUT+}$  and  $V_{OUT-}$  differently, making  $V_{OCM}$  show up in  $V_{OD}$ . This will change the operating points between the internal nodes in the

Figure 3. Single-ended to differential amplifier

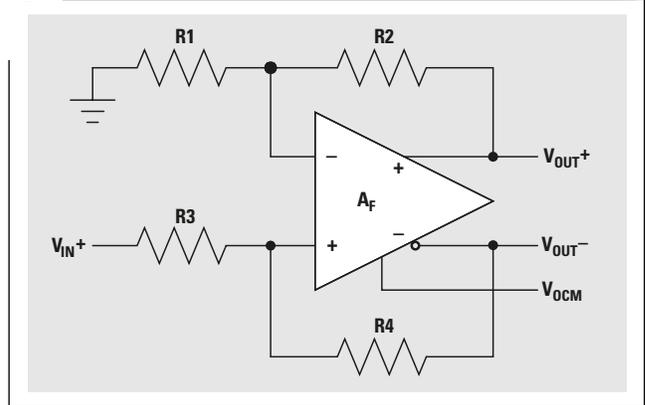


Figure 4.  $\beta_1 = 0$

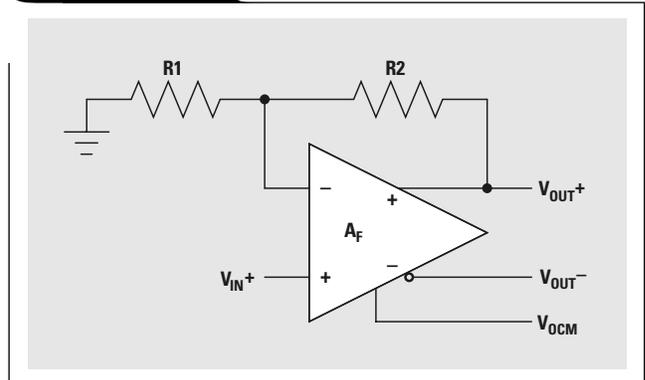


Figure 5.  $\beta_2 = 0$

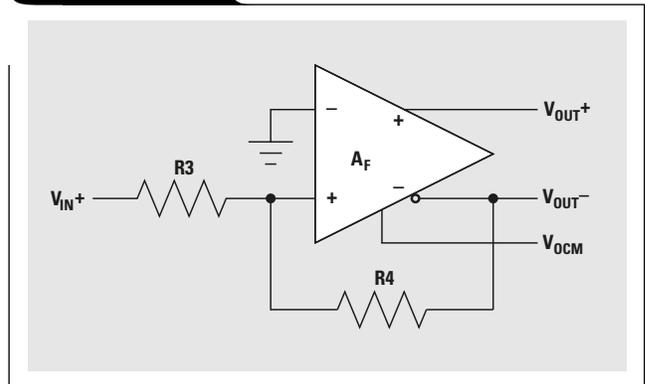
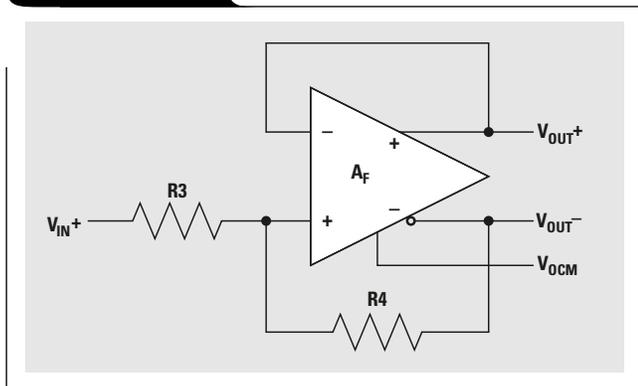
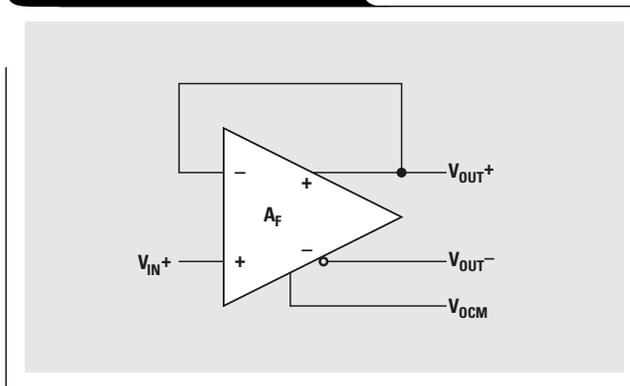


Figure 6.  $\beta_2 = 1$ Figure 7.  $\beta_1 = 0$ , and  $\beta_2 = 1$ 

differential amplifier, and matching of the open-loop gains will degrade. CMRR is not a real issue with single-ended inputs, but the analysis points out that CMRR is severely compromised when nonsymmetrical feedback is used. In the discussion of noise analysis that follows, it is shown that nonsymmetrical feedback also increases noise introduced at the  $V_{OCM}$  pin. For these reasons, even though the circuits shown in Figures 4–7 have been tested to prove they work in accordance with the equations given, they are presented mainly for instructional purposes. They are not recommended without extensive lab testing to prove their worthiness in your application.

In the circuit shown in Figure 4,  $V_{IN-} = 0$  and  $\beta_1 = 0$ . The output voltages are

$$(V_{OUT+}) = \frac{(V_{IN+})}{\beta_2},$$

$$(V_{OUT-}) = 2V_{OCM} - \frac{(V_{IN+})}{\beta_2}, \text{ and}$$

$$V_{OD} = \frac{2(V_{IN+})}{\beta_2} - 2V_{OCM}.$$

With  $\beta_1 = 0$ , this circuit is similar to a noninverting amplifier.

In the circuit shown in Figure 5,  $V_{IN-} = 0$  and  $\beta_2 = 0$ . The output voltages are

$$(V_{OUT+}) = \frac{(V_{IN+})(1-\beta_1)}{\beta_1} + 2V_{OCM},$$

$$(V_{OUT-}) = \frac{-(V_{IN+})(1-\beta_1)}{\beta_1}, \text{ and}$$

$$V_{OD} = \frac{2(V_{IN+})(1-\beta_1)}{\beta_1} + 2V_{OCM}.$$

With  $\beta_2 = 0$ , the gain is twice that of an inverting amplifier (without the minus sign).

In the circuit shown in Figure 6,  $V_{IN-} = 0$  and  $\beta_2 = 1$ . The output voltages are

$$(V_{OUT+}) = \frac{(V_{IN+})(1-\beta_1) + 2V_{OCM}\beta_1}{\beta_1 + 1},$$

$$(V_{OUT-}) = \frac{2V_{OCM} - (V_{IN+})(1-\beta_1)}{\beta_1 + 1}, \text{ and}$$

$$V_{OD} = \frac{2(V_{IN+})(1-\beta_1) + 2V_{OCM}(\beta_1 - 1)}{(\beta_1 + 1)}.$$

The gain is 1 with  $\beta_1 = 0.333$ ; or, with  $\beta_1 = 0.6$ , the gain is 1/2.

In the circuit shown in Figure 6,  $V_{IN-} = 0$ ,  $\beta_1 = 0$ , and  $\beta_2 = 1$ . The output voltages are

$$(V_{OUT+}) = (V_{IN+}), \quad (V_{OUT-}) = 2V_{OCM} - (V_{IN+}),$$

$$\text{and } V_{OD} = 2[(V_{IN+}) - V_{OCM}].$$

This circuit realizes a gain of 2 with no resistor.

Continued on next page

Continued from previous page

### Noise analysis

The noise sources are identified in Figure 8, which will be used for analysis with the following definitions.

$E_{IN}$  is the input-referred RMS noise voltage of the amplifier:  $E_{IN} \approx e_{IN} \times \sqrt{ENB}$  (assuming the 1/f noise is negligible), where  $e_{IN}$  is the input white noise spectral density in volts per square root of the frequency in Hertz, and ENB is the effective noise bandwidth.  $E_{IN}$  is modeled as a differential voltage at the input.

$I_{IN+}$  and  $I_{IN-}$  are the input-referred RMS noise currents that flow into each input. They are taken as equal and called  $I_{IN}$ .  $I_{IN} \approx i_{IN} \times \sqrt{ENB}$  (assuming the 1/f noise is negligible), where  $i_{IN}$  is the input white noise spectral density in amps per square root of the frequency in Hertz, and ENB is the effective noise bandwidth.  $I_{IN}$  develops a voltage in proportion to the equivalent input impedance seen from the input nodes. Assume the equivalent input impedance is dominated by the parallel combination of the gain setting resistors:


$$R_{EQ1} = \frac{R1R2}{R1 + R2} \quad \text{and} \quad R_{EQ2} = \frac{R3R4}{R3 + R4}$$

$E_{CM}$  is the RMS noise at the  $V_{OCM}$  pin, taking into account the spectral density and bandwidth as with the input-referred noise sources.

Noise current into the  $V_{OCM}$  pin will develop a noise voltage across the impedance seen from the node. It is assumed that proper bypassing of the  $V_{OCM}$  pin is done to reduce the effective bandwidth, so this voltage is negligible. If this is not the case, the added noise should be added to  $E_{CM}$  in a similar manner, as shown below.

$E_{R1}$  through  $E_{R4}$  are the RMS noise voltages from the resistors, calculated by  $E_{Rn} = \sqrt{4kTR \times ENB}$ , where n is the resistor number, k is Boltzmann's constant ( $1.38 \times 10^{-23} \text{J/K}$ ), T is the absolute temperature in Kelvin (K), R is the resistance in ohms ( $\Omega$ ), and ENB is the effective noise bandwidth.

Figure 8. Noise analysis circuit

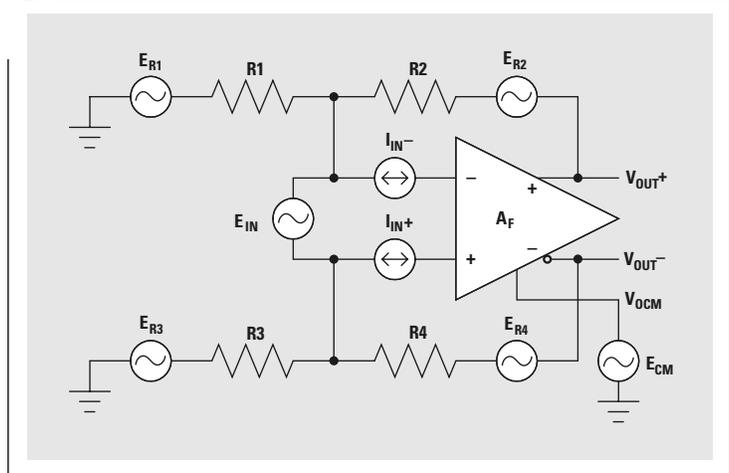

$E_{OD}$  is the differential RMS output noise voltage.  $E_{OD} = A(E_{ID})$ , where  $E_{ID}$  is the input noise source, and A is the gain from the source to the output. Half of  $E_{OD}$  is attributed to the positive output ( $+E_{OD}/2$ ), and half is attributed to the negative output ( $-E_{OD}/2$ ). Therefore,  $(+E_{OD}/2)$  and  $(-E_{OD}/2)$  are correlated to one another and to the input source, and can be directly added together; i.e.,

$$\left( \frac{+E_{OD}}{2} \right) - \left( \frac{-E_{OD}}{2} \right) = E_{OD} = A(E_{ID})$$

Independent noise sources typically are not correlated. To combine noncorrelated noise voltages, a sum-of-squares technique is used. The total RMS voltage squared is equal to the square of the individual RMS voltages added together. The output noise voltages from the individual noise sources are calculated one at a time and then combined in this fashion.

The block diagram shown in Figure 9 helps in analyzing the amplifier's noise sources.

Considering only  $E_{IN}$ , from the block diagram we can write:

$$E_{OD} = A_F \left[ E_{IN} + \frac{(-E_{OD})\beta_1}{2} - \frac{(+E_{OD})\beta_2}{2} \right]$$


Solving yields

$$E_{OD} = \left( \frac{2E_{IN}}{\beta_1 + \beta_2} \right) \left( \frac{1}{1 + \frac{2}{A_F(\beta_1 + \beta_2)}} \right)$$

Assuming  $A_F\beta_1 \gg 1$  and  $A_F\beta_2 \gg 1$ ,

$$E_{OD} = \frac{2E_{IN}}{(\beta_1 + \beta_2)}$$

Figure 9. Block diagram of the amplifier's input-referred noise

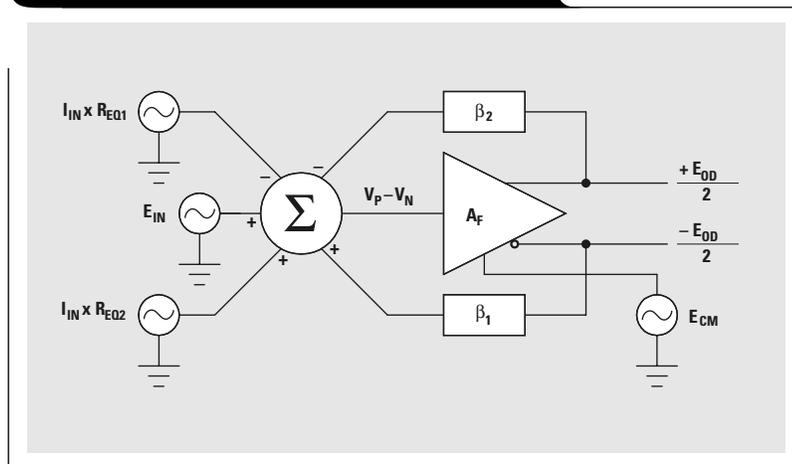

Given  $\beta_1 = \beta_2 = \beta$  (symmetrical feedback),

$$E_{\text{OUT}} = \frac{E_{\text{IN}}}{\beta},$$

the same as a standard single-ended voltage feedback op amp.

Similarly, the noise contributions from  $I_{\text{IN}} \times R_{\text{EQ1}}$  and  $I_{\text{IN}} \times R_{\text{EQ2}}$  will be

$$\frac{2I_{\text{IN}} \times R_{\text{EQ1}}}{(\beta_1 + \beta_2)} \quad \text{and} \quad \frac{2I_{\text{IN}} \times R_{\text{EQ2}}}{(\beta_1 + \beta_2)}, \text{ respectively.}$$

The  $V_{\text{OCM}}$  error amplifier will produce a common-mode noise voltage at the output equal to  $E_{\text{CM}}$ . Due to the feedback paths,  $\beta_1$  and  $\beta_2$ , a noise voltage is seen at the input that is equal to  $E_{\text{CM}}(\beta_1 - \beta_2)$ . This is amplified, just as an input, and seen at the output as a differential noise voltage equal to

$$\frac{2E_{\text{CM}}(\beta_1 - \beta_2)}{(\beta_1 + \beta_2)}.$$

Noise gain from the  $V_{\text{OCM}}$  pin ranges from 0 (given  $\beta_1 = \beta_2$ ) to a maximum absolute value of 2 (given  $\beta_1 = 1$  and  $\beta_2 = 0$ , or  $\beta_1 = 0$  and  $\beta_2 = 1$ ).

Noise from resistors R1 and R3 appears like signals at  $V_{\text{IN+}}$  and  $V_{\text{IN-}}$  in Figure 1. From the circuit analysis presented earlier, the differential output noise contribution is

$$\frac{2(E_{\text{R1}})(1 - \beta_2)}{(\beta_1 + \beta_2)} \quad \text{and} \quad \frac{2(E_{\text{R3}})(1 - \beta_1)}{(\beta_1 + \beta_2)}$$

for each resistor respectively.

Noise from resistors R2 and R4 ( $E_{\text{R2}}$  and  $E_{\text{R4}}$ , respectively) is imposed directly on the output with no amplification.

Adding the individual noise sources yields the total output differential noise:

$$E_{\text{OD}} = \sqrt{\frac{(2E_{\text{IN}})^2 + (2I_{\text{IN}} \times R_{\text{EQ1}})^2 + (2I_{\text{IN}} \times R_{\text{EQ2}})^2 + [2E_{\text{CM}}(\beta_1 - \beta_2)]^2 + [2(E_{\text{R1}})(1 - \beta_2)]^2 + [2(E_{\text{R3}})(1 - \beta_1)]^2}{(\beta_1 + \beta_2)^2} + E_{\text{R2}}^2 + E_{\text{R4}}^2}.$$

The individual noise sources are added in sum-of-squares fashion. Input-referred terms are amplified by the noise gain of the circuit:

$$G_{\text{n}} = \frac{2}{\beta_1 + \beta_2}.$$

If symmetrical feedback is used where  $\beta_1 = \beta_2 = \beta$ , the noise gain is

$$G_{\text{n}} = \frac{1}{\beta} = 1 + \frac{R_{\text{F}}}{R_{\text{G}}},$$

where  $R_{\text{F}}$  is the feedback resistor and  $R_{\text{G}}$  is the input resistor, the same as a standard single-ended voltage feedback amplifier.

## Reference

For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

### Document Title

### TI Lit. #

1. Jim Karki, "Fully differential amplifiers," *Analog Applications Journal* (August 2000), pp. 38-41 .....slyt165

### Related Web site

[amplifier.ti.com](http://amplifier.ti.com)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

## TI Worldwide Technical Support

### Internet

**TI Semiconductor Product Information Center Home Page**  
[support.ti.com](http://support.ti.com)

**TI Semiconductor KnowledgeBase Home Page**  
[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

### Product Information Centers

#### Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>		

#### Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>		

#### Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>		

#### Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>		<a href="mailto:ti-china@ti.com">ti-china@ti.com</a>

**C011905**

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**Trademarks:** All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated

SLYT157