

High-Performance Analog Products

Analog Applications Journal

Second Quarter, 2013



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as “components”) are sold subject to TI’s terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI’s terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers’ products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers’ products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI’s goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or “enhanced plastic” are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer’s risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP™ Applications	
Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E™ Community**e2e.ti.com**

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

SSZZ022F

Contents

Introduction	4
Data Converters	
Grounding in mixed-signal systems demystified, Part 2.	5
Maintaining system performance with ADCs and DACs in a noisy digital environment requires using good circuit-design techniques like proper signal routing, decoupling, and grounding. This article, the second of a two-part series, discusses the pros and cons involved in splitting the ground planes. It also explains grounding in systems with multiple converters and multiple boards.	
Power Management	
Synchronous rectification boosts efficiency by reducing power loss	9
The benefits of using synchronous rectification for buck converters and controllers are well-known. However, synchronous rectification does not always provide the same benefits for boost converters. This article compares the efficiency and power-loss performance of synchronous and nonsynchronous boost converters in low- and high-duty-cycle applications.	
Designing a negative boost converter from a standard positive buck converter	13
This article describes a method using a standard positive buck converter to form a negative boost converter. Using a boost regulator results in a smaller, more efficient, and more cost-effective design than other available options. The basic theory of operation, high-level design trade-offs, and closed-loop compensation design of an example converter are discussed.	
Digital current balancing for an interleaved boost PFC	19
Unbalanced inductor currents in a two-phase PFC boost converter can cause component thermal stress in one phase or mistrigger protection. This article discusses three digital-control methods to balance phase currents. Included are test results of each method.	
Interface (Data Transmission)	
RS-485 failsafe biasing: Old versus new transceivers	25
Legacy transceivers often require failsafe-biasing circuitry to be added in order to maintain the receiver output in a logic-high state during an idle bus. Although using modern, third-generation transceivers eliminates this requirement, upgrading is not always possible. This article provides detailed design methods to achieve efficient failsafe biasing for first- and second-generation transceivers.	
General Interest	
Introduction to capacitive touch-screen controllers	29
Today's leading smartphones and tablets incorporate capacitive touch-screen functionality. This article compares the operation of resistive versus capacitive touch screens. It also introduces three major issues facing designers of capacitive touch screens: power consumption, noise reduction, and gesture recognition.	
Index of Articles	31
TI Worldwide Technical Support	37

To view past issues of the
Analog Applications Journal, visit the Web site:

www.ti.com/aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

Introduction

The *Analog Applications Journal* is a digest of technical analog articles published quarterly by Texas Instruments. Written with design engineers, engineering managers, system designers and technicians in mind, these “how-to” articles offer a basic understanding of how TI analog products can be used to solve various design issues and requirements. Readers will find tutorial information as well as practical engineering designs and detailed mathematical solutions as they apply to the following product categories:

- Data Converters
- Power Management
- Interface (Data Transmission)
- Amplifiers: Audio
- Amplifiers: Op Amps
- Low-Power RF
- General Interest

Analog Applications Journal articles include many helpful hints and rules of thumb to guide readers who are new to engineering, or engineers who are just new to analog, as well as the advanced analog engineer. Where applicable, readers will also find software routines and program structures.

Grounding in mixed-signal systems demystified, Part 2

By Sanjay Pithadia, Analog Applications Engineer, and Shridhar More, Senior Analog Applications Engineer


This article is the second of a two-part series. Part 1 (see Reference 1) explained typical terminologies and ground planes and introduced partitioning methods. Part 2 discusses the pros and cons involved in splitting the ground planes. It also explains grounding in systems with multiple converters and multiple boards.

If the ground planes are split and the traces are run across the split as shown in Figure 1, what will be the current return path? Assuming that the two planes are connected somewhere, usually at a single point, the return current has to flow in that large loop. High-frequency currents flowing in large loops produce radiation and high ground inductance. Low-level analog currents flowing in large loops are susceptible to interference.

If the two planes are connected only at the power supply (Figure 2), the return current is forced to flow all the way back to the power-supply ground, which is a really big loop! Also, the analog and digital ground planes, which are at different RF potentials and connected with long wires, unfortunately form a very effective dipole antenna.

It is preferred to have a continuous ground plane to avoid such long ground loops, but if it is absolutely necessary to have a split ground plane and traces are run across the split, the planes should first be connected at one location to form a bridge for the return current (Figure 3). Routing all the traces so they cross at this bridge provides a return path directly underneath each of the traces, producing a very small loop area. A typical application of this

Figure 1. Signal traces crossing a split on ground plane

 

method is a weighing scale where high-resolution (≥ 20 -bit) delta-sigma analog-to-digital converters (ADCs) are used.

Other options for passing the signal over a split plane are to use optoisolators (through light), transformers (through a magnetic field), or a true differential signal (where the signal flows down one trace and returns on the other trace with no ground needed for the return current).

A better approach is *partitioning*. It is always preferable to use only one ground plane, partitioning the PCB

Figure 2. Split planes connected at power supply

 


Figure 3. Ground-plane bridge for traces


 


Figure 4. Ground-plane layouts

 

into analog and digital sections (see Figure 4b). Analog signals must be routed only in the board's analog section, and digital signals must be routed only in the board's digital section, with both on all layers. Under these conditions, the digital return currents do not flow in the analog section of the ground plane and remain under the digital signal trace. Figure 4 compares a split plane and a partitioned plane.

The only problem with partitioning is that it is difficult when analog signals are improperly routed into the board's digital section, or vice versa (Figure 5). So for any PCB layout, the important points are to use a single ground plane, partition it into analog and digital sections, and apply discipline in routing.

Grounding when multiple data converters are used on a single board

Most datasheets for data converters discuss grounding relative to a single PCB, usually the manufacturer's own evaluation board. Usually the recommendation is to split the PCB ground plane into an analog plane and a digital plane. It is further recommended that the analog ground (AGND) and digital ground (DGND) pins of a converter be tied together and that the analog and digital ground planes be connected at that same point, as shown in Figure 6. This essentially creates the system's star ground point at the mixed-signal device. As explained in Part 1, all voltages in the circuit are measured with respect to this particular point, not just to an undefined ground wherever one can clip a probe.

Figure 5. Improperly routed digital signal trace


 


Figure 6. Grounding mixed-signal devices on a single PCB

 

All noisy digital currents flow through the digital power supply to the digital ground plane and back to the digital supply, thus being isolated from the board's sensitive analog portion. The system's star ground point occurs where the analog and digital ground planes are joined together at the data converter. While this approach generally works in a simple system with a single PCB and a single data converter, it usually is not good for multcard and multiconverter systems. If there are several data converters located on different PCBs, the concept breaks down because the analog and digital ground systems are joined at each converter on the PCB, creating ground loops.


Suppose a designer is working on an eight-layer PCB that has three DACs and two ADCs. To minimize noise, the analog and digital ground planes should be connected together solidly under all the ADC and digital-to-analog converter (DAC) chips. The AGND and DGND pins should be connected to each other and to the analog ground plane, and the analog and digital ground planes should be connected individually back to the power supply. The power should enter the board in the digital partition and be fed directly to the digital circuitry, then filtered or regulated to feed the analog circuitry. Then only the digital ground plane should be connected back to the power supply. Figure 7 shows the partitioned analog and digital ground planes and the power-supply connection for a PCB with multiple data converters.

Multicard mixed-signal systems

Confusion about mixed-signal grounding has increased since designers started applying single-card grounding concepts to multicard systems. In systems having several data converters on different PCBs, the analog and digital ground planes are connected at several points, creating the possibility of ground loops and making a single-point star ground system impossible.

The best way to minimize ground impedance in a multicard system is to use a motherboard PCB as a backplane

Figure 7. Power and ground for PCB with multiple ADCs

 


for interconnections between cards. This provides a continuous ground plane to the backplane. The PCB connector should have at least 30 to 40% of its pins devoted to ground. These pins should be connected to the ground plane on the backplane motherboard. To complete the overall system grounding scheme, there are two possibilities:

1. The backplane's ground plane can be connected to the chassis ground at numerous points, thereby diffusing the various ground-current return paths. This is commonly referred to as a multipoint grounding system (Figure 8).
2. The ground plane can be connected to a single star ground point (generally at the power supply).

The first approach is most often used in all-digital systems but can also be used in mixed-signal systems, provided that the ground currents from digital circuits are sufficiently low and diffused over a large area. The low

Figure 8. Grounding scheme for multicard system

 

ground impedance is maintained all the way through the PCBs, the backplane, and ultimately the chassis. However, it is critical that good electrical contacts be made where the grounds are connected to the sheet-metal chassis. This requires self-tapping sheet-metal screws or biting washers. Special care must be taken where anodized aluminum is used for the chassis material, since its surface acts as an insulator.

The second approach, a single-point star ground, is often used in high-speed mixed-signal systems having separate analog and digital ground systems.

References

1. Sanjay Pithadia and Shridhar More, "Grounding in mixed-signal systems demystified, Part 1," *Analog Applications Journal* (1Q 2013). Available: www.ti.com/slyt499-aaj
2. H.W. Ott, "Partitioning and layout of a mixed-signal PCB," *Printed Circuit Design*, pp. 8–11, June 2001.
3. "Analog-to-digital converter grounding practices affect system performance," Application Bulletin. Available: www.ti.com/sbaa052-aaj
4. Howard Johnson. (2000, Oct. 12). "Ferrite beads," *EDN* blog.

Related Web sites

Data Converters:

www.ti.com/dc-aaj

For examples of grounding for precision data converters, visit: www.ti.com/e2egrounding-aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

Synchronous rectification boosts efficiency by reducing power loss

By **Anthony Fagnani**
Power Applications Engineer

Introduction

Some applications require the highest possible power efficiency. For example, in a harsh environment that requires a DC/DC power supply to operate in high ambient temperatures, low-power dissipation is needed to keep the junction temperature of semiconductor devices within their rated range. Other applications may have to meet the strict efficiency requirements of ENERGY STAR® specifications or green-mode criteria. Users of battery-operated applications desire the longest run time possible, and reducing the power loss can directly improve run time. Today it is well known that using a synchronous rectifier can reduce power loss and improve thermal capability. Designers of buck converters and controllers for step-down applications are already employing this technique. Synchronous boost controllers also have been developed to address power efficiency in step-up applications.

Typical application

Two typical boost applications can be used to demonstrate the difference between synchronous and nonsynchronous rectification. The first is a lower-input-voltage application that may operate at low duty cycles or, in other words, when the output voltage is close to the input voltage.


Example inputs for this system are a USB port or a lithium-ion (Li-Ion) battery pack with two or three series cells. The DC/DC power supply steps up the voltage for charging a two-cell Li-Ion battery or the battery of a tablet PC. The other application boosts the voltage of a system power rail to a high output voltage that can operate at higher duty cycles where the output voltage is much higher than the input voltage. An example input is a 12-V power rail. The high output voltage may be needed for power amplifiers, industrial PCs, or pump-and-dump energy storage for higher energy density.

To evaluate the benefits of synchronous rectification, each application is tested with a real circuit to compare efficiency and power loss. The TPS43060/61 synchronous boost controllers from Texas Instruments (TI) are used to demonstrate the synchronous designs. These current-mode boost controllers integrate the control and gate-drive circuitry for both low-side and high-side MOSFETs. TI's TPS40210 current-mode, low-side-switch boost controller is used for the nonsynchronous designs.

Basic operation

A typical block diagram for a step-up (boost) topology is shown in Figure 1. This topology consists of the low-side power MOSFET (Q1), the power inductor (L1), and the output capacitor (C1). For a synchronous topology, the high-side MOSFET (Q2) is used for the rectifying switch.

Figure 1. Synchronous and nonsynchronous boost circuits

 

In a nonsynchronous boost topology, a power diode (D1) is used. Figure 2 shows the equivalent waveforms for the voltage and current through the switches and inductor. During the ON time of Q1, the inductor current ramps up, and V_{OUT} is disconnected from V_{IN} . The output capacitor must supply the load during this time. During the OFF time, the inductor current ramps down and charges the output capacitor through the rectifying switch. The peak current in the rectifier is equal to the peak current in the switch.

Selecting the rectifying switch

Nonsynchronous controllers use an external power diode as the rectifying switch. Three main considerations when selecting the power diode are reverse voltage, forward current, and forward voltage drop. The reverse voltage should be greater than the output voltage, including some margin for ringing on the switching node. The forward current rating should be at least the same as the peak current in the inductor. The forward voltage should be small to increase efficiency and reduce power loss. The average diode current is equal to the average output current. The package of the diode chosen must be capable of handling the power dissipation.


Synchronous controllers control another MOSFET for the rectifying switch. If an n-channel MOSFET is used, a voltage higher than the output voltage must be generated for the gate driver. A bootstrap circuit is used to generate this voltage. Figure 1 also includes the typical block diagram for a standard bootstrap circuit consisting of the bootstrap capacitor (C_{BOOT}) and the bootstrap diode (D_{BOOT}). During the ON time of Q1, the bootstrap capacitor is charged to a regulated voltage (V_{CC}), which typically is regulated by a low-dropout regulator internal to the controller. When Q1 turns off, the voltage across the capacitor to ground is $V_{OUT} + V_{CC}$, and the required voltage is available to turn on the high-side switch. The control circuitry also must be more complicated to ensure that there is enough delay before the rectifying switch turns on to avoid both switches turning on at the same time. If this occurs, the output voltage shorts to ground through both switches, causing high currents that can damage the switches.

Power loss of the rectifying switch

To compare the efficiencies of the two different rectifiers, the power dissipation should be calculated. In the nonsynchronous topology, the power dissipation in the rectifying power diode is estimated with Equation 1:

$$P_{D1} = I_{OUT} \times V_{FWD} \quad (1)$$

Figure 2. Ideal voltage and current waveforms in a boost circuit

 

With a synchronous rectifier, there are two main sources of power dissipation—conduction and dead-time loss. When the low-side switch turns off, there is a time delay (t_{DELAY}) before the high-side switch turns on. During this delay, the body diode (V_{SD}) of the high-side switch conducts current. Typically this is referred to as dead time. When the high-side switch is turned on, there is also conduction loss due to the $R_{DS(ON)}$ of the MOSFET. Equation 2 calculates the duty cycle (D), and Equation 3 estimates the losses (P_{Q2}):

$$D = \frac{V_{OUT} - V_{IN}}{V_{OUT}} \quad (2)$$

$$P_{Q2} = \left(\frac{I_{OUT}^2}{1-D} \times R_{DS(ON)} \right) + \left(V_{SD} \times \frac{I_{OUT}}{1-D} \times 2 \times t_{DELAY} \times f_{SW} \right) \quad (3)$$

In an application requiring a low duty cycle, the rectifying switch conducts for a larger percentage of each switching period. However, the power loss in a nonsynchronous rectifier in a boost topology is independent of duty-cycle changes caused by variations in V_{IN} . This is because variations in V_{IN} also cause an equal but opposite change in the current the diode conducts. The rectifier loss is simply the forward voltage drop times output current per Equation 1. With a synchronous rectifier, there is some dependence on the duty cycle for power dissipation

because the conduction losses are caused by the resistance of the FET. This is unlike a diode, where the losses are caused by the forward voltage drop. A resistive conduction loss varies with current squared, leading to a dependence on duty cycle, with a higher duty cycle increasing the conduction power loss.

Efficiency of low-duty-cycle applications

To evaluate the power efficiency of low-duty-cycle applications, a synchronous design and a nonsynchronous design can be compared. The synchronous design uses the TPS43061 synchronous boost controller paired with TI's CSD86330Q3D power block. The power block integrates both the low-side and high-side MOSFETs. The nonsynchronous design uses the TPS40210 nonsynchronous boost controller and a CSD17505Q5A low-side switch, with specifications similar to those of the power block. This design has a Schottky diode for the rectifier that is rated for at least 15 V and 7 A. The smallest package size available for a Schottky diode with these ratings is a TO-277A (SMPC). A comparison of solution sizes based only on typical switch package sizes finds that the nonsynchronous switch and diode occupy an area of 65 mm², and the synchronous power-block switches occupy an area of 12 mm². The latter is a space savings of 53 mm². Both designs use the same LC filter and a 750-kHz switching frequency. Figure 3 shows the efficiency and power loss of both designs with a 12-V input and a 15-V output. The ideal duty cycle is 20%. The benefit of the synchronous rectifier is clear in this example. The full-load efficiency is improved by about 3%, whereas the power loss in the nonsynchronous design is almost double that in the synchronous design.

Efficiency of high-duty-cycle applications

To evaluate the power efficiency of high-duty-cycle applications, a synchronous and a nonsynchronous design can again be compared. The synchronous design uses the TPS43060 synchronous boost controller with a pair of power MOSFETs for the low-side and high-side switches. The MOSFETs come in a 30-mm² typical 8-pin SON package. The nonsynchronous design uses the TPS40210 nonsynchronous boost controller and one of these same MOSFETs for the low-side switch. The Schottky diode for the rectifier is rated for at least 48 V and 16 A. The Schottky rectifier is in a D²PAK package with a typical area of 155 mm². The synchronous solution saves 125 mm² of board space over

Figure 3. Measured efficiency and power loss in a low-duty-cycle application


 
 


Figure 4. Measured efficiency and power loss in a high-duty-cycle application

 

the nonsynchronous design. Both designs use the same LC filter and a 300-kHz switching frequency. Figure 4 shows the efficiency and power loss of both designs with a 12-V input and 48-V output. The ideal duty cycle is 75%. The efficiency curves show that there is no benefit in using a synchronous rectifier in this application. From 2.5 to 3.5 A of load current, the synchronous solution begins to improve efficiency. However, the primary benefit of synchronous rectification is that less board space is required.

Figure 5. Light-load efficiency of DCM and CCM designs

Light-load efficiency

Both the TPS43060 and TPS43061 used in the synchronous designs feature reverse-current detection for discontinuous-conduction mode (DCM), improving efficiency at lighter loads. This reduces conduction losses in the switches, inductor, and sense resistor, enabling the light-load efficiency to be similar to that of the nonsynchronous solutions. For reference, Figure 5 shows a dashed curve for the estimated efficiency of a converter operating in forced continuous-conduction mode (CCM). This efficiency is determined by estimating losses in the switches, inductor, and sense resistor during CCM operation. The curves show the relative improvement in efficiency at light loads for converters operating in DCM. However, for some low-noise applications or applications requiring a fast transient response from light loads, it may be preferable to sacrifice improved light-load efficiency to keep CCM operation over the entire load range.

Conclusion

The benefits of synchronous rectification are evident, especially in low-duty-cycle applications as the load current increases. However, in high-duty-cycle applications with

lower output current, a nonsynchronous design may have adequate efficiency. The lower losses with synchronous rectification can improve efficiency and reduce temperature rise and solution size.

References

1. "Low quiescent current synchronous boost DC-DC controller with wide V_{IN} range," TPS43060/61 Datasheet. Available: www.ti.com/slvsbp4-aaj
2. "4.5-V to 52-V input current mode boost controller," TPS40210/11 Datasheet. Available: www.ti.com/slus772-aaj

Related Web sites

Power Management:

www.ti.com/power-aaj

www.ti.com/csd17505q5a-aaj

www.ti.com/csd86330q3d-aaj

www.ti.com/tps40210-aaj

www.ti.com/tps43060-aaj

www.ti.com/tps43061-aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

Designing a negative boost converter from a standard positive buck converter

By Mark Pieper

Analog Field Applications

Introduction

There are very few options for the designer when it comes to creating negative voltage rails in point-of-load applications. Integrated devices that are specifically designed for this are uncommon, and other available options typically have significant drawbacks, such as being too large, noisy, inefficient, etc. If a negative voltage is available, it is advantageous to use that as the input for the converter. This article describes a method using a standard positive buck converter to form a negative boost converter, which takes an existing negative voltage and creates an output voltage with a larger (more negative) amplitude. Using a boost regulator results in a smaller, more efficient, and more cost-effective design. A complete design example using an integrated FET buck converter is provided here. The basic theory of operation, high-level design trade-offs, and closed-loop compensation design of the resulting converter are discussed.

Negative boost topology

Implementing a negative boost converter takes advantage of some parallels between the power design and control of a positive buck converter and a negative boost converter. Figure 1 depicts the basic operation of a positive buck regulator. The buck consists of a half bridge that chops V_{IN} and a filter to extract the DC component. The filtered output voltage is regulated by varying the duty cycle (D) of the upper FET. When V_{OUT} is too low, the control loop reacts by causing D to increase. When V_{OUT} is too high, D is decreased. The buck input current is discontinuous (has a higher RMS current), and the output current is continuous and equal to the inductor current waveform. The current flow through the inductor is positive, flowing away from the half bridge.

Figure 2 depicts the negative boost topology in which a more negative voltage is generated from an existing negative voltage. During D , the inductor current is increased, storing energy ($dI = -V_{IN} \times D \times T/L$). During $1 - D$, the energy is transferred to the output. When the upper FET is turned off and the lower FET is turned on, the inductor current flows into the output, supporting the load as the inductor current decreases. From Figures 1 and 2 it can be seen that the negative boost regulator resembles the positive buck regulator, except that it is level shifted

below ground. Also, V_{IN} and V_{OUT} are transposed. Notice these common features:

- The upper FET is the controlled switch.
- The inductor current flows in the same direction through the inductor (away from the half bridge).
- Increasing V_{OUT} results from increasing D .

Figure 1. Simplified positive synchronous buck regulator

 


Figure 2. Simplified negative synchronous boost regulator


 


Figure 3. Complete schematic of the example negative boost regulator

 

The significance of these similarities is that the negative boost converter can be constructed by using a readily available positive buck converter. One difference in operation is that the boost converter has a discontinuous output current and a continuous input current, the opposite of the buck converter.

Converter selection

There are three additional things that need to be considered when selecting a converter:

1. The converter should have external compensation to accommodate the different control algorithm associated with the boost converter, which will be discussed later.
2. The converter is processing current equal to the input current, not the load current, so the current rating and current limit need to be sized accordingly. For instance, neglecting the effects of efficiency (η), a 12-W, -6-V to -12-V boost converter has an output current of 1 A (12 W) and an input current of 2 A (12 W). A converter with a current rating greater than 2 A is required for this design. The output-current rating of the converter selected must be greater than that in Equation 1:

$$I_{\text{RATING}} = \frac{P_{\text{OUT}}}{\eta V_{\text{IN}(\text{min})}} \quad (1)$$

3. The converter's V_{DD} is biased by $-V_{\text{OUT}}$. When the converter is first powered on, V_{OUT} equals V_{IN} , and V_{OUT} is increased until it is in regulation. Therefore, the controller specification should allow the converter to start with $V_{\text{DD}} = | -V_{\text{IN}} |$, and the converter should be rated to operate with $V_{\text{DD}} = | -V_{\text{OUT}} |$. For instance, a design that converts a -6-V input to a -12-V output requires the controller to start with $V_{\text{DD}} = 6$ V and to continue running after start-up with $V_{\text{DD}} = 12$ V. This can be a problem when the negative input is a low voltage. A solution is to use a converter that has a V_{DD} separate from the power supply's V_{IN} . Figure 3 shows a negative boost regulator designed to convert -2.0 V to -2.2 V by using the TPS54020 from Texas Instruments (TI). Although this is a relatively low-voltage regulator, the principle is the same for any $-V_{\text{IN}}$ and $-V_{\text{OUT}}$ as long as the converter specifications support the voltages. Notice that the power to U1, pin VIN, is separate from the power ground to pin PVIN, allowing low-voltage operation.

As previously mentioned and defined in Equation 1, the current rating of the converter is driven by input current. Therefore, the power dissipation in the converter is dependent on input current.

The efficiency of the negative boost regulator (η_{BOOST}) is related to that of the positive buck regulator (η_{BUCK}) but is slightly lower. Figure 4 and Equation 2 show the relationship of the two efficiencies, which are about equal when the specified η_{BUCK} is above 90%:

$$\eta_{\text{BOOST}} = \frac{2\eta_{\text{BUCK}} - 1}{\eta_{\text{BUCK}}} \quad (2)$$

Component selection

The inductor can be chosen by using the same criteria as defined in the buck converter's data-sheet. The boost converter's input and output capacitors should be chosen based on ripple voltages required by the application, keeping in mind that the output capacitor must be rated for the higher RMS current.

Control theory

Boost converters have a different, more complicated transfer function than buck converters. As with buck converters, the transfer function is different between voltage-mode control and current-mode control. This analysis uses a current-mode-controlled boost converter based on the TPS54020, a current-mode device. The Bode-plot method is used to evaluate the stability of this control-loop design. Points of interest for stability are the phase when the open-loop gain crosses unity, and the gain when the phase crosses -180° . The open-loop gain is equal to the forward transfer function multiplied by the control transfer function, including all gains around the control loop.

The current-mode power stage ("plant" in control jargon) has the forward transfer function given in Equation 3:¹


$$G_{\text{PS}}(s) = \frac{g_M \times R_{\text{LOAD}} \times (1-D)}{2} \times \frac{\left(1 + \frac{s}{2\pi \times f_{\text{ESR}}}\right) \left(1 - \frac{s}{2\pi \times f_{\text{RHPZ}}}\right)}{1 + \frac{s}{2\pi \times f_p}} \times H_e(s), \quad (3)$$

where s is the complex Laplace variable and $H_e(s)$ represents the higher-frequency dynamics. The continuous boost has two salient control features. First, the plant is a single-pole system, owing to the effect of current-mode control. Second, there is a right-half-plane zero (RHPZ).^{1,2} The RHPZ, plant pole, and C_{OUT} equivalent-series-resistance (ESR) zero frequencies are described respectively by the following equations:

$$f_p = \frac{2}{2\pi R_{\text{LOAD}} C_{\text{OUT}}} \quad (4a)$$

$$f_{\text{ESR}} = \frac{1}{2\pi R_{\text{ESR}} C_{\text{OUT}}} \quad (4b)$$

Figure 4. Efficiency of negative boost regulator

 

$$f_{\text{RHPZ}} = \frac{R_{\text{LOAD}}}{2\pi L} \times \left(\frac{V_{\text{IN}}}{V_{\text{OUT}}}\right)^2 \quad (4c)$$

The RHPZ requires that the unity-gain bandwidth of the loop be less than the minimum RHPZ frequency, usually by a factor of 5 to 10. If lower bandwidth is desired, the RHPZ can be ignored, and so can $H_e(s)$ in Equation 3. This design uses ceramic output capacitors, so the ESR zero also can be ignored. Now the control equations simplify to

$$G_{\text{PS}}(s) = \frac{g_M \times R_{\text{LOAD}} \times (1-D)}{2 \times \left(1 + \frac{s}{2\pi \times f_p}\right)}. \quad (5)$$

Equations 3 and 5 are modified, using g_M (the compensation to output-current gain in A/V) instead of R_{SENSE} , with $g_M = 1/R_{\text{SENSE}}$.

Designing a negative boost regulator

It has been established that the forward transfer function simplifies to a single-pole system as described by Equation 5. A real control-loop example can be based on a design using TI's TPS54020EVM082, with $V_{\text{IN}} = -2.0$ V, $V_{\text{OUT}} = -3.0$ V, and $I_{\text{OUT}} = 6$ A. This electrical design can be reconfigured as a negative boost regulator consistent with the circuit in Figure 3, using many of the same components as in the EVM design. The terms "input" and "output" from here on refer to the boost mode input and output. Equation 4 can be used to calculate the minimum RHPZ as 32 kHz. The goal of the control-loop design is to have a unity-gain crossover at 1.0 kHz, so the effects of both the ESR zero and the RHPZ can be ignored.

Table 1 contains some specific parameters and values. Equation 6 uses these values to describe the forward transfer function:

$$G_{PS}(s) = \frac{R_{LOAD} \times 5.70}{1 + \frac{s \times R_{LOAD}}{13889}} \quad (6)$$

The Bode plot of $G_{PS}(s)$ is depicted in Figure 5 for four different load-resistance values. Note that the pole location and low-frequency gain are functions of load resistance. Also note that the gain slope does not vary after the pole (driven by C_{OUT}). Before the pole, the gain is dependent on the load, with the highest-frequency pole at the maximum load (minimum R_{LOAD}). A $0.5\text{-}\Omega$ load ($I_{LOAD} = 6.0\text{ A}$) results in a pole at 4.4 kHz. It can also be seen that the RHPZ causes the gain to rise and the phase to fall, which makes compensation impossible and requires cross-over to occur before the effect of the RHPZ becomes detrimental.

The plan for this design is to have unity gain in the open-loop transfer function at 1.0 kHz. The plant has a gain of approximately +9 dB at 1.0 kHz. This forward transfer function can be compensated easily with an integrator followed by a zero at the highest $G_{PS}(s)$ pole frequency, and with an overall gain that results in about -9 dB at the desired crossover of 1.0 kHz (+9 dB + -9 dB = 0 dB). This compensation approximates a single-pole rolloff characteristic through crossover and results in sufficient phase margin.

Bode stability criteria

A closed-loop system with negative feedback has a transfer function as in Equation 7:


$$Y(s) = \frac{G(s)}{1 + G(s)H(s)}, \quad (7)$$

where $G(s)$ is the forward (plant) transfer function, $H(s)$ is the negative feedback control, and $G(s)H(s)$ is the open-loop transfer function. The Bode stability criteria state that $Y(s)$ is rational except where $G(s)H(s) = -1$. In the latter case, $Y(s)$ is infinite and unstable. Two things have to happen at the same time for instability to occur. First, $|G(s)H(s)|$ must equal 1 (gain = 0 dB); second, the phase of $G(s)H(s)$ must equal -180° , corresponding to -1 . Bode plots, including both the phase margin and the gain margin, are used to evaluate how near to this condition a control design approaches. Phase margin is defined as the phase difference between $G(s)H(s)$ and -180° when the gain equals 0 dB, and gain margin refers to the negative gain when the phase equals -180° . A phase margin greater than 45° is generally considered good in power-supply design.

Table 1. Design values and TPS54020 datasheet³ parameters for negative boost regulator

PARAMETER	COMMENTS
$C_{OUT} = 144\ \mu\text{F}$	
$L = 1.1\ \mu\text{H}$	
$g_M = 17\ \text{A/V} = 1/R_{SENSE}$	g_M from datasheet = I_{SWITCH}/V_{COMP}
$g_{EA} = 0.0013\ \text{A/V}$	From datasheet
$D = (V_{OUT} - V_{IN})/V_{OUT} = 0.33$	
$V_{REF} = 0.600\ \text{V}$	From datasheet
$R_{10} = 10.0\ \text{k}\Omega$; $R_7 = 40.2\ \text{k}\Omega$	Feedback-divider gain = $0.2\ \text{V/V}$

Figure 5. Bode plots of $G_{PS}(s)$ for four different load resistances

 

Error-amplifier compensation

The error amplifier (EA) is depicted in Figure 6, and the circuit's transfer function is described by

$$G_{EA}(s) = \frac{g_{EA}R_{10}}{R_{10} + R_7} \times \frac{1}{C_1 + C_{15}} \times \frac{1}{s} \times \frac{C_{15}R_1s + 1}{\frac{C_1C_{15}}{C_1 + C_{15}} \times R_1s + 1}. \quad (8)$$

Note that the transfer function of the transconductance error amplifier includes the feedback-divider gain. If this was a voltage-feedback error amplifier, the divider would not be a gain term. Inspection of Equation 8 finds that $G_{EA}(s)$ has a pole at 0 Hz, a compensating zero at

$$f = \frac{1}{2\pi R_1 C_{15}},$$

and a higher-frequency pole at

$$f = \frac{1}{2\pi R_1 \left(\frac{C_1 C_{15}}{C_1 + C_{15}} \right)}.$$

Note that if the zero and pole are separated by a decade or more, then $C_{15} \gg C_1$. The plan is to set the gain equal to -9 dB at 1.0 kHz, place the zero at the highest $G_{PS}(s)$ pole (4.4 kHz) to compensate the pole in the plant, and place the additional pole at some higher frequency.

Evaluating $|G_{EA}(s)|$ at $f = 1.0$ kHz and setting it equal to -9 dB yields $C_1 + C_{15} \approx C_{15} = 0.117$ μ F. The nearest standard value of 0.10 μ F is chosen. Given C_{15} and the desired zero location of 4.4 kHz, R_1 can be calculated as 360 Ω . The nearest standard value of 357 Ω is chosen. The higher-frequency pole is placed at 50 kHz. This is rather arbitrary, but this pole needs to be greater than 10 times the crossover frequency to ensure that it doesn't degrade the loop-phase margin. Adding this high-frequency pole is desirable because it keeps the loop gain decreasing at higher frequency. C_1 is calculated to be 0.01 μ F. Figure 7 shows the Bode plot of the converter's final compensated loop. The predicted and measured open-loop gain and phase match closely near the 1.0 -kHz unity-gain crossover.

Test data

Figure 7 also includes the measured Bode plot of the power supply with a 0.5 - Ω load. There is good correlation near the 1.0 -kHz crossover. The predicted waveforms in Figure 7 also include the effects of the RHPZ. The gain and phase disturbance between 1.0 kHz and 10 kHz is thought to result from a nonlinear characteristic in the controller and only begins to appear at load currents above 50% . Since this occurs above the crossover, it is inconsequential to the stability of the loop.

Figure 6. Error amplifier and compensation

 


Figure 7. Bode plot of converter's final compensation loop

 


Figure 8 shows the switching waveform with a load of $0.5\ \Omega$ (6 A). As expected, it looks identical to a buck converter's switching waveform but is level shifted below ground, riding on the programmed V_{OUT} of $-3.0\ \text{V}$.

Additional considerations

Three additional points about this type of converter should be noted. First, the TPS54020 has a separate V_{IN} and V_{DD} . This enables power conversion from a low voltage (2 V in this case), which would not be possible with many other converters. Second, this negative-boost design concept is extendable to higher voltages and is limited only by the ratings of the converter selected. Third and most important, before the boost converter starts but after voltage is applied to the PVIN pin, any load current on the boost output is conducted through the body diode of the lower FET. Although the TPS54020 functions well, starting up even with a DC current, not all devices may perform in the same way. Therefore, it might be necessary to add a Schottky diode in parallel with the lower internal FET to provide an external path for this current.


Conclusion

This article demonstrates that a positive buck regulator can be used to implement a negative boost regulator and obtain good performance. The actual performance very closely matches the expected behavior, both in real-time measurements and in the Bode plot of the control loop.

References

1. Jeff Falin, Tahar Allag, and Ben Hopf, "Compensating the current-mode-controlled boost converter," Application Report. Available: www.ti.com/slva452-aaj
2. "The right-half-plane zero—a simplified explanation," Texas Instruments. Available: www.ti.com/slup084-aaj

Figure 8. Switching voltage waveform

 

3. "Small, 10-A, 4.5-V to 17-V input, SWIFT™ synchronous step-down converter with light-load efficiency," TPS54020 Datasheet. Available: www.ti.com/slvsb10-aaj
4. "TPS54020EVM-082 evaluation module (PWR082)," User's Guide. Available: www.ti.com/slvu777-aaj

Related Web sites

Power Management:

www.ti.com/power-aaj

www.ti.com/tps54020-aaj

www.ti.com/tps54020evm-aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

Digital current balancing for an interleaved boost PFC

By Bosheng Sun

Systems Engineer

Introduction

A power-factor correction (PFC) converter lets the input current track the input voltage so that the load appears like a resistor to the voltage source that powers it. The most popular power topology used in active PFC is the non-isolated boost converter. For high power levels, two boost units can connect to the same bridge rectifier and operate at 180° out of phase (Figure 1). This is called two-phase interleaved PFC. By controlling two phases' inductor currents 180° out of phase, both input- and output-current ripple can be reduced. As a result, a smaller electromagnetic-interference filter can be used, which reduces material costs. Due to discrepancies between the two sets of components used in the two boost circuits, the two inductor currents inevitably will be different. This situation gets worse when PFC enters continuous-conduction mode (CCM). While the unbalanced current causes more thermal stress on one phase, it may also mistrigger over-current protection. Therefore, a current-balancing mechanism is necessary for the interleaved PFC design.¹⁻⁴

This article discusses three different digital-control methods of balancing inductor currents. The first method

senses the inductor current on each switching cycle, compares the current difference between the two phases, then adjusts the duty ratio of one phase cycle-by-cycle. The second method only adjusts the duty ratio in each half AC cycle. The third method uses two independent current loops to control each phase individually. Since these loops share the same current reference, the current is balanced automatically.

Method 1: Cycle-by-cycle duty-ratio adjustment

In this approach, a shunt is used to sense the total current. An average-current mode control is employed to force the input current to track input voltage. The pulse-width-modulation (PWM) controller generates two signals, each with the same duty ratio but shifted by 180° to drive the two boost stages. A current transformer (CT) is put right above the MOSFET in each phase to sense the switching current. The CT outputs are sampled and compared to each other; then the error is multiplied by a gain K , and the multiplier output is used to adjust the duty ratio of phase 2 accordingly. For example, if phase 1 has higher current than phase 2, the error is positive. The multiplier

Figure 1. A two-phase interleaved PFC


 



Figure 2. Cycle-by-cycle duty-ratio adjustment

 

output, which is also positive, increases the duty ratio of phase 2 and thus its current. This configuration is shown in Figure 2.

Properly sampling the CT currents is critical for this approach. Since the CT outputs are saw waves, both currents need to be sampled at the same point for a fair comparison. An example would be to sample both at the middle of the switch's ON time, as shown in Figure 3. Here the unbalanced current causes different magnitudes of CT output.

Figure 3. Sampling CT signal

 

With proper sampling of the CT currents, the cycle-by-cycle approach gives good current balancing. Figure 4 shows test results from a 360-W, digitally controlled interleaved PFC. As can be seen, there is a big difference between the inductor currents, but they almost overlap after being balanced.

Because the second-phase duty ratio is adjusted on each switching cycle, and the adjustment may be different for each cycle since the current difference may vary between cycles, this method inevitably brings high-frequency noise to the AC input current. Figure 5a shows that the waveform of the AC input current before current balancing is smooth and clean. Once current balancing is introduced, high-frequency noise appears (Figure 5b).

Method 2: Half-AC-cycle duty-ratio adjustment

Since adjusting the duty ratio on each switching cycle brings high-frequency noise to the total input current, it seems reasonable to try adjusting the duty ratio only once in each half AC cycle. Either average or peak inductor current in each half AC cycle can be used for current balancing. An example is to force the peak inductor currents to be equal in each half AC cycle by using a configuration similar to that in Figure 2. I_{CT1} and I_{CT2} are still sampled in each switching cycle, and the firmware finds out the peak value of I_{CT1} and I_{CT2} in each half AC cycle. These peak values are then compared, and the error is used to adjust the duty ratio. Since the current difference is calculated only once in each half AC cycle,

Figure 4. Inductor currents


 


Figure 5. AC input current

 

the same duty-ratio adjustment is applied to the next half AC cycle. This essentially solves the issue of high-frequency noise. Test results showed that the AC current's waveform was almost the same as before current balancing was enabled; the high-frequency noise went away.


This approach also has a drawback. Because the relationship of the duty ratio to the input-current transfer function is different for continuous-conduction mode (CCM) and discontinuous-conduction mode (DCM),⁵ the converter dynamics may change abruptly. Applying the same duty-ratio adjustment along the half AC cycle distorts the inductor current (Figure 6) even though the total input current is still sinusoidal. Moreover, because of discrepancies between the two component sets used in the two boost circuits, the circuits enter CCM at different points in each half AC cycle. Thus, the distortions of the two phases are also different. On the other hand, unlike the unbalanced currents in Figure 4a, this approach can force the peak values of inductor currents in each half AC cycle to be equal, so the current does get balanced to some level.

Method 3: Dual current-control loops

In the preceding approaches, there is only one current-control loop. The total current is used for current-loop control, and the two phases get the same duty ratio from the same control loop. If two current-control loops with the same current reference are used, with each controlling one phase individually, the closed-loop control will force the current to be balanced automatically, making duty-ratio adjustments unnecessary.

For analog controllers, adding one more loop means adding another compensation network and another feedback pin. Inevitably, this increases the cost and design effort. With a general digital controller, the current-control loop is implemented by firmware. Adding a second loop means adding extra code, which at first seems to be a good solution. However, the extra code takes extra CPU execution time. The CPU that used to do only one loop calculation now needs to do two. For this to happen without causing any interruption overflow, the CPU speed needs to be increased. This requires a higher-cost CPU with more power consumption. Another choice can be to

Figure 6. Inductor currents after half-AC-cycle current balancing

 


reduce the control-loop speed—for example, from 50 kHz to 25 kHz. The CPU speed can then be kept the same, and the dual-loop calculation can be completed without causing any interruption overflow. However, the loop bandwidth suffers due to the reduced control-loop speed, and a reduced bandwidth deteriorates PFC performance.

Integrated control solution

A second-generation digital controller such as the Texas Instruments UCD3138 offers a different solution. This is a fully programmable digital controller, but the control loop is implemented by hardware. Based on the proportional integral derivative (PID), the control loop is a two-pole, two-zero digital compensator. All the loop calculations are done by hardware with a speed of up to 2 MHz. The firmware just needs to configure the PID coefficients. This allows a low-speed CPU to be used because it needs to do only the low-speed tasks, such as housekeeping and communication. Moreover, the UCD3138 has three independent loops inside the chip, so the dual current-control loops can be implemented without any extra hardware or a

Figure 7. Dual current-control loops with UCD3138

 

higher-speed CPU. Figure 7 shows the configuration of these dual control loops implemented with the UCD3138. The current-feedback signal from each phase needs to be measured. Normally, a CT placed above the MOSFET can be used. Since no current shunt is needed, this configuration also can improve efficiency.

Because the CT is placed right above each switch (Figure 7), it senses only the switching current. This is only the rising part of the inductor current, whereas each current loop controls the average inductor current. The CT current signal is still sampled at the middle of the PWM ON time (Figure 3). It is an instantaneous value, represented as I_{SENSE} in Figures 8 and 9. The sampled switching current (I_{SENSE}) is equal to the average PFC inductor current only when the current is continuous (Figure 8). When the current becomes discontinuous (Figure 9), I_{SENSE} is no longer equal to the average PFC inductor current. In order to control the average inductor current, the relationship between the middle point where I_{SENSE} is sampled and the average inductor current over a switching period needs to be derived and applicable to both CCM and DCM.

Figure 8. Sensed current waveform at CCM


 


Figure 9. Sensed current waveform at DCM

 

For a boost-type converter in steady-state operation, the volt-second of the boost inductor maintains balance in each switching period:

$$t_{\text{ON}} \times V_{\text{IN}} = t_{\text{OFF}} \times (V_{\text{OUT}} - V_{\text{IN}}), \quad (1)$$

where t_{A} is the current rising time (PWM ON time), t_{B} is the current falling time (PWM OFF time), V_{IN} is input voltage, and V_{OUT} is output voltage, assuming all power devices are ideal. From Figures 8 and 9, the average inductor current (I_{AVE}) can be calculated in terms of I_{SENSE} :

$$I_{\text{AVE}} = I_{\text{SENSE}} \times \frac{t_{\text{A}} + t_{\text{B}}}{t}, \quad (2)$$

where t is the switching period. Combining Equations 1 and 2 results in

$$I_{\text{SENSE}} = \frac{I_{\text{AVE}} \times t \times (V_{\text{OUT}} - V_{\text{IN}})}{t_{\text{A}} \times V_{\text{OUT}}}. \quad (3)$$

Through Equation 3, the average inductor current (I_{AVE}) is interpreted via instantaneous switching current (I_{SENSE}). I_{AVE} is the desired current, and I_{SENSE} is the current reference for the current-control loops. The real instantaneous switching currents are sensed and compared with this reference, and the error is sent to the current-control loops.

Figure 10 shows the test result of this approach. As shown in Figure 4, even though the two inductor currents have a wide variance, they almost overlap completely after current balancing is enabled. Meanwhile, the total AC current remains smooth and clean.


Conclusion

Three different digital-control methods of balancing inductor currents have been evaluated for an interleaved boost PFC. By comparing the current difference and adjusting the duty ratio cycle-by-cycle, the current can be balanced very well. However, this method also injects high-frequency noise into the total input current. Adjusting the duty ratio only once in each half AC cycle eliminates the high-frequency noise, but each individual inductor current gets distorted even though the total AC current is sinusoidal. A better approach is to use two current loops, with each controlling one phase individually. Since the two current loops share the same current reference, the current is balanced automatically. With a digital controller, the cost for a second loop is just a few extra codes. Test results show that the third approach gives the best performance.

References

1. Byung-Sun Min, Nam-ju Park, and Dong-seok Seok Hyun, "A novel current sharing technique for interleaved boost converter," in *Proc. 2007 IEEE Power Electron. Specialists Conf.*, Orlando, Fla., pp. 2658–2663.
2. Marco Soldano et al., "A new current balancing method for digitally controlled interleaved PFC," in *Proc. 2012 IEEE Applied Power Electron. Conf. and Expo.*, Orlando, Fla., pp. 299–303.

Figure 10. Inductor currents balanced with UCD3138 dual control loops

 

3. Laszlo Balogh and Richard Redl, "Power-factor correction with interleaved boost converters in continuous-inductor-current mode," in *Proc. 1993 IEEE Applied Power Electron. Conf. and Expo.*, San Diego, Calif., pp. 168–174.
4. Q. Zhang, A. Qiu, J. Ying, and J. Zeng, "Current sharing method and apparatus for alternately controlling parallel connected boost PFC circuits," U.S. Patent 7116087, Oct. 3, 2006.
5. Koen De Gussemme et al., "Digitally controlled boost power-factor-correction converters operating in both continuous and discontinuous conduction mode," *IEEE Trans. Ind. Electron.*, vol. 52, no. 1, pp. 88–97, Feb. 2005.

Related Web sites

Power Management:

www.ti.com/power-aaj

www.ti.com/ucd3138-aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

RS-485 failsafe biasing: Old versus new transceivers

By Thomas Kugelstadt
Senior Applications Engineer

It is incredible that an industrial interface standard such as RS-485, having been around for 30 years, still appears obscure to many industrial-network designers. While there should be plenty of literature available explaining the standard fundamentals, the Texas Instruments (TI) application team continues to receive basic questions on a weekly basis, such as how to apply failsafe biasing to an idle bus.

Failsafe biasing refers to the technique of providing a differential voltage to a terminated, idle bus in order to maintain the receiver output of a bus transceiver in a logic-high state. This technique is commonly required when legacy transceiver designs are used for designing bus networks.

Legacy designs such as transceiver X in Table 1 possess a wide input sensitivity of ± 200 mV. This means that small input signals between +200 mV and -200 mV can turn the receiver output either high or low, thus making the output state indeterminate.

During a data transmission, the differential line voltage of a fully loaded bus is required to be higher than ± 1.5 V, which is well above the transceiver's input sensitivity. However, during a handover of bus access from one node to another, or during a transmission pause, the bus idles. Then the low-impedance termination resistors, connecting the two conductors of the differential signal pair with each other, cause the differential bus voltage to be 0 V, right in the middle of the transceiver's input sensitivity, which produces an indeterminate output.

Therefore, to keep the receiver outputs at a logic high during bus idling, a positive, differential failsafe voltage higher than a receiver's positive input threshold (V_{IT+}) must be applied to the bus.

Table 1 shows that the theoretically required failsafe levels decrease with the receiver's positive input threshold from one generation to the next. While transceiver X

requires a minimum of +200 mV of failsafe biasing, transceivers Y and Z can do without it as their positive input thresholds are below 0 V. Unfortunately, these values apply only in noise-free environments such as laboratories or the Earth's poles, and certainly not in the harsh environments of industrial factories where RS-485 networks are commonly installed.

Differential noise induced into the bus wires can falsely trigger a receiver input if the projected noise magnitude has not been included in the failsafe voltage calculation. Using a twisted-pair bus cable helps to convert noise induced along the cable run into common-mode noise. This noise is then rejected by the receiver's differential input. However, cable irregularities as well as noise induced at the bus node connectors might contribute to differential noise that cannot be rejected by a receiver.

Figure 1 on the next page shows that when a noise signal is superimposed onto the positive input threshold levels of transceivers X and Y, the minimum hysteresis voltage determines at which noise level the receiver output will assume the wrong logic state. Table 1, in which the receiver parameters have been extracted from different datasheets, gives a minimum hysteresis level only for transceiver Z. For the two older transceivers, X and Y, only typical hysteresis values are provided. In a situation such as determining the minimum failsafe value for a worst-case scenario, typical values are meaningless. In fact, the TI application team has measured minimum hysteresis voltages for both transceivers X and Y that were nearly half the specified typical values.

Furthermore, there is the possibility that for a given transceiver the hysteresis window might be located anywhere between the positive and negative input thresholds. Hence, for a worst-case calculation, one must assume that the hysteresis window is at the uppermost positive

Table 1. Receiver input sensitivities of first-, second-, and third-generation (X, Y, and Z) transceivers

TRANSCIVER	POSITIVE-GOING INPUT THRESHOLD VOLTAGE, V_{IT+} (mV)			NEGATIVE-GOING INPUT THRESHOLD VOLTAGE, V_{IT-} (mV)			INPUT HYSTERESIS VOLTAGE, V_{Hys} (mV)			RECEIVER OUTPUT IS INDETERMINATE WHEN
	MIN	TYP	MAX	MIN	TYP	MAX	MIN	TYP	MAX	
X (SN65LBC176)			200	-200				50		$-0.2 \text{ V} < V_{AB} < 0.2 \text{ V}$
Y (SN65HVD12)			-10	-200				35		$-0.2 \text{ V} < V_{AB} < 0.01 \text{ V}$
Z (SN65HVD72)		-70	-20	-200	-150		50	80		$-0.2 \text{ V} < V_{AB} < 0.07 \text{ V}$

threshold limit. Therefore, to determine a sufficiently high failsafe-biasing voltage, the projected peak-to-peak noise level must be added to the positive input threshold voltage: $V_{AB(min)} = V_{IT+} + V_{N(PP_max)}$.

For a well-balanced bus with a noise level of $V_{N(PP_max)} = 50\text{ mV}$, using transceiver X requires a differential failsafe voltage of $V_{AB(min)} = 200\text{ mV} + 50\text{ mV} = 250\text{ mV}$ (Figure 1).

Operating transceiver Y at the same noise level without external biasing could be risky, particularly when considering a significantly smaller minimum hysteresis than the nominal value. Again, adding the noise level to the positive input threshold provides a minimum failsafe voltage of $V_{AB(min)} = -10\text{ mV} + 50\text{ mV} = 40\text{ mV}$.

The more modern third-generation transceiver Z can maintain a stable output without failsafe biasing. Its positive

input threshold of -20 mV and the specified minimum hysteresis of 50 mV allow for a maximum peak-to-peak noise level of 140 mV , which is almost three times the noise immunity of legacy devices with external biasing.

If it is not possible to use modern transceivers, the calculation methods presented in the following section can be used to optimize the failsafe-biasing networks required by legacy transceivers.

Failsafe biasing for legacy transceivers

Figure 2 shows a terminated RS-485 bus with its distributed network nodes and a failsafe-biasing network consisting of two biasing resistors (R_{FS}) and a termination resistor (R_{T1}). With the majority of RS-485 applications being master/slave systems, the failsafe-biasing network is

Figure 1. The need for failsafe biasing depends on the transceiver


 


Figure 2. RS-485 bus with failsafe-biasing network for legacy transceivers

 

commonly installed at the master end of the bus, while the other cable end receives a termination resistor (R_{T2}) matching the characteristic line impedance (Z_0).

The major drawback of failsafe biasing is its common-mode loading. A common-mode load is the resistance between a signal conductor and the local transceiver ground. Transceivers have a high common-mode load, primarily because the receiver's input-voltage divider (Figure 3) reduces the input signal by a factor of 10 or more.

The internal resistor network, imposing a common-mode load on each of the A and B bus terminals, can be represented by a combined input resistance (R_{IN}). The total common-mode resistance of an entire transceiver network then can be expressed through an equivalent input resistance (R_{INEQ}) for both the A and the B line.

The RS-485 standard specifies a maximum common-mode load per bus line with $375\ \Omega$. Initially this value is allocated for only the bus transceivers. Implementing a failsafe-biasing network can consume a significant amount of this loading, therefore allowing only a reduced number of transceivers to be connected to the bus.

Figure 4 presents a lumped equivalent circuit of an RS-485 bus. This circuit allows the failsafe resistor values to be determined as a function of the required failsafe bus voltage (V_{AB}), the supply voltage (V_S), the common-mode loading caused by R_{FS} and R_{INEQ} , and the characteristic line impedance (Z_0). Determining the currents into nodes A and B and solving for the respective line voltages (V_A and V_B) yields

$$\frac{V_S - V_A}{R_{FS}} = \frac{V_A - V_B}{R_{T1}} + \frac{V_A - V_B}{R_{T2}} + \frac{V_A}{R_{INEQ}} \Rightarrow$$

$$V_A = R_{INEQ} \times \left[\frac{V_S - V_A}{R_{FS}} - (V_A - V_B) \times \left(\frac{1}{R_{T1}} + \frac{1}{R_{T2}} \right) \right]$$

for Node A, and


$$\frac{V_B}{R_{FS}} = \frac{V_A - V_B}{R_{T1}} + \frac{V_A - V_B}{R_{T2}} - \frac{V_B}{R_{INEQ}} \Rightarrow$$

$$V_B = R_{INEQ} \times \left[(V_A - V_B) \times \left(\frac{1}{R_{T1}} + \frac{1}{R_{T2}} \right) - \frac{V_B}{R_{FS}} \right]$$

for Node B. Allowing for the difference between the two line voltages and assuring failsafe biasing under minimum supply conditions permits the required minimum failsafe bus voltage to be determined:

$$V_{AB(\min)} = \frac{V_{S(\min)}}{R_{FS}} \times \frac{1}{\frac{1}{R_{INEQ}} + \frac{1}{R_{FS}} + 2 \left(\frac{1}{R_{T1}} + \frac{1}{R_{T2}} \right)} \quad (1)$$

Figure 3. Common-mode input resistance of the receiver section

 

Because R_{FS} in combination with R_{INEQ} makes up the total common-mode load for a signal line, the parallel value of the two must not exceed the specified maximum of $375\ \Omega$, which is expressed through

$$R_{FS} \parallel R_{INEQ} = 375\ \Omega \text{ or } \frac{1}{R_{INEQ}} + \frac{1}{R_{FS}} = \frac{1}{375\ \Omega} \quad (2)$$

At the remote cable end, the termination resistor (R_{T2}) must match the characteristic line impedance (Z_0):

$$R_{T2} = Z_0 \text{ or } \frac{1}{R_{T2}} = \frac{1}{Z_0} \quad (3)$$


At the biasing network, the parallel combination of R_{T1} and the two failsafe resistors must also match Z_0 :

$$R_{T1} \parallel 2R_{FS} = Z_0 \text{ or } \frac{1}{R_{T1}} = \frac{1}{Z_0} - \frac{1}{2R_{FS}} \quad (4)$$

Inserting Equations 2, 3, and 4 into Equation 1 then yields the bus failsafe voltage:

$$V_{AB(\min)} = \frac{V_{S(\min)}}{R_{FS} \left(\frac{1}{375\ \Omega} + \frac{4}{Z_0} \right) - 1} \quad (5)$$

Figure 4. Lumped equivalent circuit

 

Solving Equation 5 for R_{FS} provides the value of each failsafe-biasing resistor:

$$R_{FS} = \left(\frac{V_{S(\min)}}{V_{AB(\min)}} + 1 \right) \times \frac{1}{\frac{1}{375 \Omega} + \frac{4}{Z_0}} \quad (6)$$

After R_{FS} is known, R_{T1} can be derived from Equation 4. Once the failsafe network has been established, the maximum number of transceivers that can be connected to the bus can be determined through

$$n \leq \frac{12 \text{ k}\Omega}{UL_{XCVR}} \times \left(\frac{1}{375 \Omega} - \frac{1}{R_{FS}} \right), \quad (7)$$

where UL_{XCVR} is the unit-load (UL) rating of the transceiver. A typical design procedure would be to calculate R_{FS} via Equation 6 first, then determine R_{T1} via Equation 4 while making $R_{T2} = Z_0$. Finally, Equation 7 would be used to calculate the maximum number of bus transceivers possible.

The design examples in Table 2 show the typical design procedure. This table also highlights the differences in failsafe biasing between a network using 1-UL, 5-V transceivers (X) and one using 1/8-UL, 3.3-V transceivers (Y).

Conclusion

Failsafe biasing with the high failsafe voltages required for first-generation transceivers causes heavy common-mode loading and necessitates a reduction in bus transceiver count. Using second-generation transceivers with less input sensitivity and lower unit loading improves the situation at low noise levels by allowing for a high transceiver count. The best of both worlds, however, can be accomplished only with modern third-generation transceivers, such as

TI's 3-V SN65HVD7x family and 5-V SN65HVD8x family. These new transceivers have the following advantages:

- They don't require an external bias resistor network that can impose heavy common-mode loading on the bus, reducing the number of transceivers that can be connected to the bus.
- Therefore they allow for up to 256 transceivers on a bus.
- They tolerate high noise levels.
- They are robust against 12-kV IEC ESD and 4-kV IEC burst transients.
- They are less expensive than legacy transceivers, and some come in much smaller packages that provide cost and space savings.
- The designer doesn't have to spend time going through a mathematical treatise like the one in this article.

References

1. "Interface circuits for TIA/EIA-485 (RS-485)," Application Report. Available: www.ti.com/slla036-aaj
2. "3.3V-supply RS-485 with IEC ESD protection," SN65HVD72/75/78 Datasheet. Available: www.ti.com/sllse11-aaj

Related Web sites

Interface (Data Transmission):

www.ti.com/interface-aaj

www.ti.com/sn65hvd12-aaj

www.ti.com/sn65hvd72-aaj

www.ti.com/sn65hvd82-aaj

www.ti.com/sn65lbc176-aaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaj

Table 2. Examples of how failsafe biasing affects bus transceiver count

TRANSCIVER X	TRANSCIVER Y
$V_{S(\min)} = 4.75 \text{ V}$, $V_{IT+} = 200 \text{ mV}$, $UL_{XCVR} = 1 \text{ UL}$ $R_{T2} = 120 \Omega$ ($R_{T2} = Z_0$)	$V_{S(\min)} = 3.05 \text{ V}$, $V_{IT+} = -10 \text{ mV}$, $UL_{XCVR} = 1/8 \text{ UL}$ $R_{T2} = 120 \Omega$ ($R_{T2} = Z_0$)
Assuming $V_{N(\text{PP}_{\max})} = 50 \text{ mV}$ yields: $V_{AB(\min)} = V_{IT+} + V_{N(\text{PP}_{\max})} = 250 \text{ mV}$	Assuming $V_{N(\text{PP}_{\max})} = 50 \text{ mV}$ yields: $V_{AB(\min)} = V_{IT+} + V_{N(\text{PP}_{\max})} = 40 \text{ mV}$
Applying Equation 6 yields: $R_{FS} = 555.5 \Omega$. Choosing the closest E192 value makes $R_{FS} = 556 \Omega$.	Applying Equation 6 yields: $R_{FS} = 2.11 \text{ k}\Omega$. Choosing the closest E192 value makes $R_{FS} = 2.10 \text{ k}\Omega$.
Applying Equation 4 yields: $R_{T1} = 134.5 \Omega$. Choosing the closest E192 value makes $R_{T1} = 135 \Omega$.	Applying Equation 4 yields: $R_{T1} = 123.5 \Omega$. Choosing the closest E192 value makes $R_{T1} = 124 \Omega$.
Applying Equation 7 yields: $n = 10$ transceivers	Applying Equation 7 yields: $n = 210$ transceivers

Introduction to capacitive touch-screen controllers

By Eric Siegel

Business Development Manager, Touch-Screen Controllers

Introduction

Resistive touch screens had their heyday, but their use has irrefutably declined. There are clear instances where they are no doubt better suited for low-cost designs whose users must wear gloves, such as in medical, industrial, and military environments. But capacitive touch screens have gained in popularity, and the leading smartphones and tablets on the market today incorporate capacitive touch-screen functionality.

Resistive versus capacitive touch screens

Both resistive and capacitive touch screens use indium tin oxide (ITO) sensors, but in vastly different ways. Unlike its resistive predecessor, which uses the mechanical action of human touch to connect two flexible layers of ITO together (Figure 1a), capacitive touch-screen control leverages the fact that humans are basically walking capacitors. Touching ITO changes the capacitive levels that the system can see (Figure 1b).

There are two things that give capacitive touch-screen control its edge to consumers:

1. A capacitive touch screen uses two layers, and in some cases one, of ITO. It uses a patterned sensor similar to a checkerboard (Figure 2), so it is possible to have only one full sheet covering the LCD, providing a clearer screen.
2. Since capacitive touch-screen control uses an electro-capacitive method of detection, a layer of safety glass can be placed on top of the structure to seal it, as opposed to using a flexible sheet of polyurethane for a resistive screen. This provides consumers with a more durable design.

Design considerations for capacitive touch screens

There are three major issues facing designers of capacitive touch screens: power consumption, noise reduction, and gesture recognition. The remainder of this article takes a look at each of these.

Power consumption

With so many battery-powered devices in existence today, power consumption is one of the more critical system components to consider. A device like the TSC3060 from Texas Instruments (TI) was designed with low power in mind. In typical operating conditions, it consumes less

Figure 1. Comparison of touch-screen designs


 


Figure 2. ITO rows and columns are overlaid to make one full sensor sheet

 

than 60 mA. It can go as low as 11 μ A while monitoring for a touch. This is at least one order of magnitude less than its competitors under similar operation.

Many solutions on the market were designed first as microcontrollers, then evolved into capacitive touch-screen controllers. Devices created solely as capacitive touch-screen controllers don't include the extra hardware of their predecessors that can consume extra current and clock cycles. Most systems already have a main central processor, be it a digital signal processor, a microprocessor, or a microcontroller unit (MCU). So why add another engine to a system that's finely tuned? The TSC3060 was purposely designed without a microcontroller.

Noise reduction

A superlong battery life won't matter much if the controller can't discern between actual touches and potential sources of crosstalk. A major source of noise in touch-screen designs typically comes from the LCD, which is subject to significant trade-offs in terms of quality versus cost. AC common-ground LCDs are usually cheaper but have a higher noise level. DC common-ground LCDs have a DC shield on them, thus reducing the noise generated but increasing the cost.

One typical technique to help reduce the amount of noise observed by the ITO sensor and in turn the touch-screen controller is to keep an air gap between the LCD and the ITO. This creates some distance between the two and reduces crosstalk interaction. Another way to deal with noise is to use filters. For example, the TSC3060 includes a set of programmable mixed-signal filters for noise reduction. These filters are implemented into the hardware via an integrated MCU. This means they will execute their task at hand faster than a filter in the software could. The faster response to real touch coordinates can also potentially reduce overall system resource consumption.

Gesture recognition

The final design concern is gesture recognition. Gestures don't have to be grand, complicated flourishes. A gesture is as simple as a single finger swipe. A system host MCU can easily recognize simple gestures like pinch, pull, zoom, rotate, and double and triple tap, and can do object rejection "in house." Adding a specialty engine for gesture recognition just increases power consumption in favor of what is potentially only a small reduction in system MCU bandwidth processing. In addition, the specialty engine may accomplish gesture recognition by running proprietary algorithms that designers aren't allowed to see. A device like the TSC3060 pushes this task to the host processor, which is already present in the system and allows designers the freedom to develop their own royalty-free algorithms to tweak as they see fit.

Conclusion

This article has compared some of the features and benefits of resistive and capacitive touch-screen controllers and has explained why the latter are gaining in popularity. It has also presented the three main considerations in designing touch-screen controllers—power consumption, noise reduction, and gesture recognition—and has offered some possible solutions.

Related Web sites

To learn about TI's full line of TouchPath™ products, visit:

www.ti.com/touch-aa-j

For design questions regarding touch systems, visit:

www.ti.com/touchforum-aa-j

Subscribe to the AAJ:

www.ti.com/subscribe-aa-j

Index of Articles

Title	Issue	Page	Lit. No.
Data Converters			
Grounding in mixed-signal systems demystified, Part 2	2Q 2013	5	SLYT512
Add a digitally controlled PGA with noise filter to an ADC	1Q 2013	9	SLYT500
Grounding in mixed-signal systems demystified, Part 1	1Q 2013	5	SLYT499
WEBENCH® tools and the photodetector's stability	4Q, 2012	5	SLYT487
How delta-sigma ADCs work, Part 2	4Q, 2011	5	SLYT438
How delta-sigma ADCs work, Part 1	3Q, 2011	13	SLYT423
Clock jitter analyzed in the time domain, Part 3	3Q, 2011	5	SLYT422
The IBIS model, Part 3: Using IBIS models to investigate signal-integrity issues	2Q, 2011	5	SLYT413
The IBIS model, Part 2: Determining the total quality of an IBIS model	1Q, 2011	5	SLYT400
The IBIS model: A conduit into signal-integrity analysis, Part 1	4Q, 2010	11	SLYT390
Clock jitter analyzed in the time domain, Part 2	4Q, 2010	5	SLYT389
Clock jitter analyzed in the time domain, Part 1	3Q, 2010	5	SLYT379
How digital filters affect analog audio-signal levels	2Q, 2010	5	SLYT375
How the voltage reference affects ADC performance, Part 3	4Q, 2009	5	SLYT355
How the voltage reference affects ADC performance, Part 2	3Q, 2009	13	SLYT339
Impact of sampling-clock spurs on ADC performance	3Q, 2009	5	SLYT338
How the voltage reference affects ADC performance, Part 1	2Q, 2009	5	SLYT331
Stop-band limitations of the Sallen-Key low-pass filter	4Q, 2008	5	SLYT306
A DAC for all precision occasions	3Q, 2008	5	SLYT300
Understanding the pen-interrupt (PENIRQ) operation of touch-screen controllers	2Q, 2008	5	SLYT292
Using a touch-screen controller's auxiliary inputs	4Q, 2007	5	SLYT283
Calibration in touch-screen systems	3Q, 2007	5	SLYT277
Conversion latency in delta-sigma converters	2Q, 2007	5	SLYT264
Clamp function of high-speed ADC THS1041	4Q, 2006	5	SLYT253
Using the ADS8361 with the MSP430™ USI port	3Q, 2006	5	SLYT244
Matching the noise performance of the operational amplifier to the ADC	2Q, 2006	5	SLYT237
Understanding and comparing datasheets for high-speed ADCs	1Q, 2006	5	SLYT231
Low-power, high-intercept interface to the ADS5424 14-bit, 105-MSPS converter for undersampling applications	4Q, 2005	10	SLYT223
Operating multiple oversampling data converters	4Q, 2005	5	SLYT222
Simple DSP interface for ADS784x/834x ADCs	3Q, 2005	10	SLYT210
Using resistive touch screens for human/machine interface	3Q, 2005	5	SLYT209A
Implementation of 12-bit delta-sigma DAC with MSC12xx controller	1Q, 2005	27	SLYT076
Clocking high-speed data converters	1Q, 2005	20	SLYT075
14-bit, 125-MSPS ADS5500 evaluation	1Q, 2005	13	SLYT074
Supply voltage measurement and ADC PSRR improvement in MSC12xx devices	1Q, 2005	5	SLYT073
Streamlining the mixed-signal path with the signal-chain-on-chip MSP430F169	3Q, 2004	5	SLYT078
ADS809 analog-to-digital converter with large input pulse signal	1Q, 2004	8	SLYT083
Two-channel, 500-kSPS operation of the ADS8361	1Q, 2004	5	SLYT082
Evaluation criteria for ADSL analog front end	4Q, 2003	16	SLYT091
Calculating noise figure and third-order intercept in ADCs	4Q, 2003	11	SLYT090
ADS82x ADC with non-uniform sampling clock	4Q, 2003	5	SLYT089
Interfacing op amps and analog-to-digital converters	4Q, 2002	5	SLYT104
Using direct data transfer to maximize data acquisition throughput	3Q, 2002	14	SLYT111
MSC1210 debugging strategies for high-precision smart sensors	3Q, 2002	7	SLYT110
Adjusting the A/D voltage reference to provide gain	3Q, 2002	5	SLYT109
Synchronizing non-FIFO variations of the THS1206	2Q, 2002	12	SLYT115
SHDSL AFE1230 application	2Q, 2002	5	SLYT114
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	1Q, 2002	5	SLYT123
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5	SLYT129
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware	February 2001	11	SLYT138

Title	Issue	Page	Lit. No.
Data Converters (Continued)			
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616	February 2001	7	SLYT137
Building a simple data acquisition system using the TMS320C31 DSP	February 2001	1	SLYT136
Using quad and octal ADCs in SPI mode	November 2000	15	SLYT150
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm	November 2000	8	SLYT149
Smallest DSP-compatible ADC provides simplest DSP interface	November 2000	1	SLYT148
Efficiently interfacing serial data converters to high-speed DSPs	August 2000	10	SLYT160
Higher data throughput for DSP analog-to-digital converters	August 2000	5	SLYT159
New DSP development environment includes data converter plug-ins	August 2000	1	SLYT158
Introduction to phase-locked loop system modeling	May 2000	5	SLYT169
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1	SLYT168
The operation of the SAR-ADC based on charge redistribution	February 2000	10	SLYT176
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1	SLYT175
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5	SLYT184
Precision voltage references	November 1999	1	SLYT183
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7	SLYT193
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4	SLYT192
Aspects of data acquisition system design	August 1999	1	SLYT191
Power Management			
Digital current balancing for an interleaved boost PFC	2Q 2013	19	SLYT517
Designing a negative boost converter from a standard positive buck converter	2Q 2013	13	SLYT516
Synchronous rectification boosts efficiency by reducing power loss	2Q 2013	9	SLYT515
How to pick a linear regulator for noise-sensitive applications	1Q 2013	25	SLYT504
35-V, single-channel gate drivers for IGBT and MOSFET renewable-energy applications	1Q 2013	22	SLYT503
Power MOSFET failures in mobile PMUs: Causes and design precautions	1Q 2013	17	SLYT502
Design of a 60-A interleaved active-clamp forward converter	1Q 2013	13	SLYT501
Simple open-circuit protection for boost converters in LED driver applications	4Q, 2012	21	SLYT490
LDO noise examined in detail	4Q, 2012	14	SLYT489
Harnessing wasted energy in 4- to 20-mA current-loop systems	4Q, 2012	10	SLYT488
Designing a Qi-compliant receiver coil for wireless power systems, Part 1	3Q, 2012	8	SLYT479
Easy solar-panel maximum-power-point tracking for pulsed-load applications	3Q, 2012	5	SLYT478
Design considerations for a resistive feedback divider in a DC/DC converter	2Q, 2012	18	SLYT469
Charging a three-cell nickel-based battery pack with a Li-Ion charger	2Q, 2012	14	SLYT468
Remote sensing for power supplies	2Q, 2012	12	SLYT467
A solar-powered buck/boost battery charger	2Q, 2012	8	SLYT466
Controlling switch-node ringing in synchronous buck converters	2Q, 2012	5	SLYT465
High-efficiency AC adapters for USB charging	1Q, 2012	18	SLYT451
Downslope compensation for buck converters when the duty cycle exceeds 50%	1Q, 2012	14	SLYT450
Benefits of a multiphase buck converter	1Q, 2012	8	SLYT449
Turbo-boost charger supports CPU turbo mode	1Q, 2012	5	SLYT448
Solar lantern with dimming achieves 92% efficiency	4Q, 2011	12	SLYT440
Solar charging solution provides narrow-voltage DC/DC system bus for multicell-battery applications	4Q, 2011	8	SLYT439
A boost-topology battery charger powered from a solar panel	3Q, 2011	17	SLYT424
Challenges of designing high-frequency, high-input-voltage DC/DC converters	2Q, 2011	28	SLYT415
Backlighting the tablet PC	2Q, 2011	23	SLYT414
I _Q : What it is, what it isn't, and how to use it	2Q, 2011	18	SLYT412
Benefits of a coupled-inductor SEPIC converter	2Q, 2011	14	SLYT411
Implementation of microprocessor-controlled, wide-input-voltage, SMBus smart battery charger	2Q, 2011	11	SLYT410
Fine-tuning TI's Impedance Track™ battery fuel gauge with LiFePO ₄ cells in shallow-discharge applications	1Q, 2011	13	SLYT402
An introduction to the Wireless Power Consortium standard and TI's compliant solutions	1Q, 2011	10	SLYT401
Save power with a soft Zener clamp	4Q, 2010	19	SLYT392

Title	Issue	Page	Lit. No.
Power Management (Continued)			
A low-cost, non-isolated AC/DC buck converter with no transformer	4Q, 2010	16	SLYT391
Computing power going “Platinum”	3Q, 2010	13	SLYT382
Coupled inductors broaden DC/DC converter usage.	3Q, 2010	10	SLYT380
Designing DC/DC converters based on ZETA topology.	2Q, 2010	16	SLYT372
Discrete design of a low-cost isolated 3.3- to 5-V DC/DC converter	2Q, 2010	12	SLYT371
Power-supply design for high-speed ADCs.	1Q, 2010	12	SLYT366
Li-Ion battery-charger solutions for JEITA compliance	1Q, 2010	8	SLYT365
Fuel-gauging considerations in battery backup storage systems	1Q, 2010	5	SLYT364
Efficiency of synchronous versus nonsynchronous buck converters.	4Q, 2009	15	SLYT358
Designing a multichemistry battery charger	4Q, 2009	13	SLYT357
Using power solutions to extend battery life in MSP430™ applications	4Q, 2009	10	SLYT356
Reducing radiated EMI in WLED drivers	3Q, 2009	17	SLYT340
Selecting the right charge-management solution.	2Q, 2009	18	SLYT334
Designing a linear Li-Ion battery charger with power-path control	2Q, 2009	12	SLYT333
Taming linear-regulator inrush currents.	2Q, 2009	9	SLYT332
Using a portable-power boost converter in an isolated flyback application	1Q, 2009	19	SLYT323
Cell balancing buys extra run time and battery life.	1Q, 2009	14	SLYT322
Improving battery safety, charging, and fuel gauging in portable media applications	1Q, 2009	9	SLYT321
Paralleling power modules for high-current applications	1Q, 2009	5	SLYT320
Designing DC/DC converters based on SEPIC topology	4Q, 2008	18	SLYT309
Compensating and measuring the control loop of a high-power LED driver	4Q, 2008	14	SLYT308
Getting the most battery life from portable systems.	4Q, 2008	8	SLYT307
New current-mode PWM controllers support boost, flyback, SEPIC, and LED-driver applications	3Q, 2008	9	SLYT302
Battery-charger front-end IC improves charging-system safety.	2Q, 2008	14	SLYT294
Understanding output voltage limitations of DC/DC buck converters	2Q, 2008	11	SLYT293
Using a buck converter in an inverting buck-boost topology	4Q, 2007	16	SLYT286
Host-side gas-gauge-system design considerations for single-cell handheld applications	4Q, 2007	12	SLYT285
Driving a WLED does not always require 4 V	4Q, 2007	9	SLYT284
Simultaneous power-down sequencing with the TPS74x01 family of linear regulators	3Q, 2007	20	SLYT281
Get low-noise, low-ripple, high-PSRR power with the TPS717xx	3Q, 2007	17	SLYT280
TPS6108x: A boost converter with extreme versatility.	3Q, 2007	14	SLYT279
Power-management solutions for telecom systems improve performance, cost, and size.	3Q, 2007	10	SLYT278
Current balancing in four-pair, high-power PoE applications.	2Q, 2007	11	SLYT270
Enhanced-safety, linear Li-Ion battery charger with thermal regulation and input overvoltage protection	2Q, 2007	8	SLYT269
Power management for processor core voltage requirements	1Q, 2007	11	SLYT261
LDO white-LED driver TPS7510x provides incredibly small solution size	1Q, 2007	9	SLYT260
Selecting the correct IC for power-supply applications.	1Q, 2007	5	SLYT259
Fully integrated TPS6300x buck-boost converter extends Li-Ion battery life	4Q, 2006	15	SLYT256
bq25012 single-chip, Li-Ion charger and dc/dc converter for <i>Bluetooth</i> ® headsets.	4Q, 2006	13	SLYT255
A 3-A, 1.2-V _{OUT} linear regulator with 80% efficiency and P _{LOST} < 1 W	4Q, 2006	10	SLYT254
Complete battery-pack design for one- or two-cell portable applications.	3Q, 2006	14	SLYT248
Single-chip bq2403x power-path manager charges battery while powering system.	3Q, 2006	12	SLYT247
TPS65552A powers portable photoflash.	3Q, 2006	10	SLYT246
TPS61059 powers white-light LED as photoflash or movie light	3Q, 2006	8	SLYT245
Powering today’s multi-rail FPGAs and DSPs, Part 2	2Q, 2006	18	SLYT240
Wide-input dc/dc modules offer maximum design flexibility	2Q, 2006	13	SLYT239
TLC5940 PWM dimming provides superior color quality in LED video displays	2Q, 2006	10	SLYT238
Practical considerations when designing a power supply with the TPS6211x	1Q, 2006	17	SLYT234
TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)	1Q, 2006	14	SLYT233
Powering today’s multi-rail FPGAs and DSPs, Part 1	1Q, 2006	9	SLYT232
TLC5940 dot correction compensates for variations in LED brightness.	4Q, 2005	21	SLYT225
Li-Ion switching charger integrates power FETs.	4Q, 2005	19	SLYT224
New power modules improve surface-mount manufacturability	3Q, 2005	18	SLYT212
Miniature solutions for voltage isolation.	3Q, 2005	13	SLYT211
Understanding power supply ripple rejection in linear regulators.	2Q, 2005	8	SLYT202

Title	Issue	Page	Lit. No.
Power Management (Continued)			
Understanding noise in linear regulators	2Q, 2005	5	SLYT201
A better bootstrap/bias supply circuit	1Q, 2005	33	SLYT077
Tips for successful power-up of today's high-performance FPGAs	3Q, 2004	11	SLYT079
LED-driver considerations	1Q, 2004	14	SLYT084
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2	4Q, 2003	21	SLYT092
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1	3Q, 2003	13	SLYT097
Soft-start circuits for LDO linear regulators	3Q, 2003	10	SLYT096
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down	3Q, 2003	5	SLYT095
Using the TPS61042 white-light LED driver as a boost converter	1Q, 2003	7	SLYT101
Load-sharing techniques: Paralleling power modules with overcurrent protection	1Q, 2003	5	SLYT100
Understanding piezoelectric transformers in CCFL backlight applications	4Q, 2002	18	SLYT107
Power conservation options with dynamic voltage scaling in portable DSP designs	4Q, 2002	12	SLYT106
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	4Q, 2002	8	SLYT105
Powering electronics from the USB port	2Q, 2002	28	SLYT118
Optimizing the switching frequency of ADSL power supplies	2Q, 2002	23	SLYT117
SWIFT™ Designer power supply design program	2Q, 2002	15	SLYT116
Why use a wall adapter for ac input power?	1Q, 2002	18	SLYT126
Comparing magnetic and piezoelectric transformer approaches in CCFL applications	1Q, 2002	12	SLYT125
Power control design key to realizing InfiniBand™ benefits	1Q, 2002	10	SLYT124
Runtime power control for DSPs using the TPS62000 buck converter	July 2001	15	SLYT131
Power supply solution for DDR bus termination	July 2001	9	SLYT130
–48-V/+48-V hot-swap applications	February 2001	20	SLYT140
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions	February 2001	15	SLYT139
Comparison of different power supplies for portable DSP solutions working from a single-cell battery	November 2000	24	SLYT152
Understanding the load-transient response of LDOs	November 2000	19	SLYT151
Optimal output filter design for microprocessor or DSP power supply	August 2000	22	SLYT162
Advantages of using PMOS-type low-dropout linear regulators in battery applications	August 2000	16	SLYT161
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A	May 2000	14	SLYT171
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11	SLYT170
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20	SLYT178
Power supply solutions for TI DSPs using synchronous buck converters	February 2000	12	SLYT177
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14	SLYT187
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10	SLYT186
TI TPS5602 for powering TI's DSP	November 1999	8	SLYT185
Migrating from the TI TL770x to the TI TLC770x	August 1999	14	SLYT196
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13	SLYT195
Stability analysis of low-dropout linear regulators with a PMOS pass element	August 1999	10	SLYT194
Interface (Data Transmission)			
RS-485 failsafe biasing: Old versus new transceivers	2Q 2013	25	SLYT514
Design considerations for system-level ESD circuit protection	4Q, 2012	28	SLYT492
How to design an inexpensive HART transmitter	4Q, 2012	24	SLYT491
Data-rate independent half-duplex repeater design for RS-485	3Q, 2012	15	SLYT480
Extending the SPI bus for long-distance communication	4Q, 2011	16	SLYT441
Industrial data-acquisition interfaces with digital isolators	3Q, 2011	24	SLYT426
Isolated RS-485 transceivers support DMX512 stage lighting and special-effects applications	3Q, 2011	21	SLYT425
Designing an isolated I ² C Bus® interface by using digital isolators	1Q, 2011	17	SLYT403
Interfacing high-voltage applications to low-power controllers	4Q, 2010	20	SLYT393
Magnetic-field immunity of digital capacitive isolators	3Q, 2010	19	SLYT381
Designing with digital isolators	2Q, 2009	21	SLYT335
Message priority inversion on a CAN bus	1Q, 2009	25	SLYT325
RS-485: Passive failsafe for an idle bus	1Q, 2009	22	SLYT324
Cascading of input serializers boosts channel density for digital inputs	3Q, 2008	16	SLYT301

Title	Issue	Page	Lit. No.
Interface (Data Transmission) (Continued)			
When good grounds turn bad—isolate!	3Q, 2008	11	SLYT298
Enabling high-speed USB OTG functionality on TI DSPs	2Q, 2007	18	SLYT271
Detection of RS-485 signal loss	4Q, 2006	18	SLYT257
Improved CAN network security with TI's SN65HVD1050 transceiver	3Q, 2006	17	SLYT249
Device spacing on RS-485 buses	2Q, 2006	25	SLYT241
Maximizing signal integrity with M-LVDS backplanes	2Q, 2005	11	SLYT203
Failsafe in RS-485 data buses	3Q, 2004	16	SLYT080
The RS-485 unit load and maximum number of bus connections	1Q, 2004	21	SLYT086
Estimating available application power for Power-over-Ethernet applications	1Q, 2004	18	SLYT085
Power consumption of LVPECL and LVDS	1Q, 2002	23	SLYT127
The SN65LVDS33/34 as an ECL-to-LVTTL converter	July 2001	19	SLYT132
The Active Fail-Safe feature of the SN65LVDS32A	November 2000	35	SLYT154
A statistical survey of common-mode noise	November 2000	30	SLYT153
Performance of LVDS with different cables	August 2000	30	SLYT163
LVDS: The ribbon cable connection	May 2000	19	SLYT172
LVDS receivers solve problems in non-LVDS applications	February 2000	33	SLYT180
Skew definition and jitter analysis	February 2000	29	SLYT179
Keep an eye on the LVDS input levels	November 1999	17	SLYT188
TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS)	August 1999	16	SLYT197
Amplifiers: Audio			
Precautions for connecting APA outputs to other devices	2Q, 2010	22	SLYT373
Audio power amplifier measurements, Part 2	1Q, 2002	26	SLYT128
Audio power amplifier measurements	July 2001	40	SLYT135
An audio circuit collection, Part 3	July 2001	34	SLYT134
An audio circuit collection, Part 2	February 2001	41	SLYT145
Notebook computer upgrade path for audio power amplifiers	February 2001	27	SLYT142
1.6- to 3.6-volt BTL speaker driver reference design	February 2001	23	SLYT141
An audio circuit collection, Part 1	November 2000	39	SLYT155
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs	February 2000	39	SLYT182
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier	August 1999	24	SLYT199
Reducing the output filter of a Class-D amplifier	August 1999	19	SLYT198
Amplifiers: Op Amps			
Using a fixed threshold in ultrasonic distance-ranging automotive applications	3Q, 2012	19	SLYT481
Source resistance and noise considerations in amplifiers	2Q, 2012	23	SLYT470
Measuring op amp settling time by using sample-and-hold technique	1Q, 2012	21	SLYT452
Converting single-ended video to differential video in single-supply systems	3Q, 2011	29	SLYT427
Using single-supply fully differential amplifiers with negative input voltages to drive ADCs	4Q, 2010	26	SLYT394
Operational amplifier gain stability, Part 3: AC gain-error analysis	3Q, 2010	23	SLYT383
Operational amplifier gain stability, Part 2: DC gain-error analysis	2Q, 2010	24	SLYT374
Interfacing op amps to high-speed DACs, Part 3: Current-sourcing DACs simplified	1Q, 2010	32	SLYT368
Signal conditioning for piezoelectric sensors	1Q, 2010	24	SLYT369
Operational amplifier gain stability, Part 1: General system analysis	1Q, 2010	20	SLYT367
Interfacing op amps to high-speed DACs, Part 2: Current-sourcing DACs	4Q, 2009	23	SLYT360
Using fully differential op amps as attenuators, Part 3: Single-ended unipolar input signals	4Q, 2009	19	SLYT359
Using the infinite-gain, MFB filter topology in fully differential active filters	3Q, 2009	33	SLYT343
Interfacing op amps to high-speed DACs, Part 1: Current-sinking DACs	3Q, 2009	24	SLYT342
Using fully differential op amps as attenuators, Part 2: Single-ended bipolar input signals	3Q, 2009	21	SLYT341
Using fully differential op amps as attenuators, Part 1: Differential bipolar input signals	2Q, 2009	33	SLYT336
Output impedance matching with fully differential operational amplifiers	1Q, 2009	29	SLYT326
A dual-polarity, bidirectional current-shunt monitor	4Q, 2008	29	SLYT311
Input impedance matching with fully differential amplifiers	4Q, 2008	24	SLYT310
A new filter topology for analog high-pass filters	3Q, 2008	18	SLYT299
New zero-drift amplifier has an I_Q of 17 μ A	2Q, 2007	22	SLYT272
Accurately measuring ADC driving-circuit settling time	1Q, 2007	14	SLYT262
Low-cost current-shunt monitor IC revives moving-coil meter design	2Q, 2006	27	SLYT242

Title	Issue	Page	Lit. No.
Amplifiers: Op Amps (Continued)			
High-speed notch filters	1Q, 2006	19	SLYT235
Getting the most out of your instrumentation amplifier design	4Q, 2005	25	SLYT226
So many amplifiers to choose from: Matching amplifiers to applications	3Q, 2005	24	SLYT213
Auto-zero amplifiers ease the design of high-precision circuits	2Q, 2005	19	SLYT204
Active filters using current-feedback amplifiers	3Q, 2004	21	SLYT081
Integrated logarithmic amplifiers for industrial applications	1Q, 2004	28	SLYT088
Op amp stability and input capacitance	1Q, 2004	24	SLYT087
Calculating noise figure in op amps	4Q, 2003	31	SLYT094
Expanding the usability of current-feedback amplifiers	3Q, 2003	23	SLYT099
Video switcher using high-speed op amps	3Q, 2003	20	SLYT098
Analyzing feedback loops containing secondary amplifiers	1Q, 2003	14	SLYT103
RF and IF amplifiers with op amps	1Q, 2003	9	SLYT102
Active output impedance for ADSL line drivers	4Q, 2002	24	SLYT108
FilterPro™ low-pass design tool	3Q, 2002	24	SLYT113
Using high-speed op amps for high-performance RF design, Part 2	3Q, 2002	21	SLYT112
Using high-speed op amps for high-performance RF design, Part 1	2Q, 2002	46	SLYT121
Worst-case design of op amp circuits	2Q, 2002	42	SLYT120
Fully differential amplifier design in high-speed data acquisition systems	2Q, 2002	35	SLYT119
Designing for low distortion with high-speed op amps	July 2001	25	SLYT133
Frequency response errors in voltage feedback op amps	February 2001	48	SLYT146
Pressure transducer-to-ADC application	February 2001	38	SLYT144
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines	February 2001	32	SLYT143
Analysis of fully differential amplifiers	November 2000	48	SLYT157
Thermistor temperature transducer-to-ADC application	November 2000	44	SLYT156
Reducing PCB design costs: From schematic capture to PCB layout	August 2000	48	SLYT167
The PCB is a component of op amp design	August 2000	42	SLYT166
Fully differential amplifiers	August 2000	38	SLYT165
Design of op amp sine wave oscillators	August 2000	33	SLYT164
Using a decompensated op amp for improved performance	May 2000	26	SLYT174
Sensor to ADC — analog interface design	May 2000	22	SLYT173
Matching operational amplifier bandwidth with applications	February 2000	36	SLYT181
Reducing crosstalk of an op amp on a PCB	November 1999	23	SLYT190
Single-supply op amp design	November 1999	20	SLYT189
Low-Power RF			
Selecting antennas for low-power wireless applications	2Q, 2008	20	SLYT296
Using the CC2430 and TIMAC for low-power wireless sensor applications: A power- consumption study	2Q, 2008	17	SLYT295
General Interest			
Introduction to capacitive touch-screen controllers	2Q 2013	29	SLYT513
High-definition haptics: Feel the difference!	3Q, 2012	29	SLYT483
Applying acceleration and deceleration profiles to bipolar stepper motors	3Q, 2012	24	SLYT482
Industrial flow meters/flow transmitters	2Q, 2012	29	SLYT471
Analog linearization of resistance temperature detectors	4Q, 2011	21	SLYT442
Spreadsheet modeling tool helps analyze power- and ground-plane voltage drops to keep core voltages within tolerance	2Q, 2007	29	SLYT273
Analog design tools	2Q, 2002	50	SLYT122
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors	February 2001	52	SLYT147

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A090712

Auto-Track, E2E, FilterPro, Impedance Track, MSP430, OMAP, SWIFT, and TouchPath are trademarks and WEBENCH and DLP are registered trademark of Texas Instruments. The *Bluetooth* word mark and logos are owned by the Bluetooth SIG, Inc., and any use of such marks by Texas Instruments is under license. Celeron is a trademark and StrataFlash is a registered trademark of Intel Corporation. ENERGY STAR is a registered trademark of the U.S. Environmental Protection Agency. I²C Bus is a registered trademark of NXP B.V. Corporation. InfiniBand is a service mark of the InfiniBand Trade Association. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com