

Solving AC dropout recovery in a high-density GaN-optimized PFC converter

Brent McDonald

System and Application Engineer
Power Design Services

Introduction

A loss of power in data center server power-supply units can interrupt everything from entertainment to financial transactions to home security systems. Specifications such as the V2 Power Shelf Specification from the Open Compute Project (OCP) [1] emphasize the need to reduce server downtime with robust AC dropout control algorithms. In addition, the need for cost-effective solutions in data centers to improve power factor correction (PFC) light load and peak efficiency while shrinking passive components is becoming difficult with conventional continuous conduction mode control [2-8].

To address this problem, TI developed a gallium nitride (GaN)-based high-density design using two-phase integrated triangular current mode (iTCM) PFC (Figure 1) [9]. Low-value inductors operating at a high frequency have enabled the high efficiency (>99%) and power density (120 W/in³) of this design. These small inductors present a unique problem to AC dropout recovery in that only a few microseconds of switch on-time can result in over 70 A of switch current. In addition, any delays in timing can also result in significant reverse current, further exacerbating PFC recovery. Keeping the current levels at a safe magnitude and preventing reverse current required the development of a new solution to the AC dropout and recovery problem. This article discusses this solution with lab verification data based on the Variable-Frequency, ZVS, 5-kW, GaN-Based, Two-Phase Totem-Pole PFC Reference Design [10], for which Table 1 lists the primary components and system specifications.

 


Figure 1. iTCM topology with inductor and current envelopes.

Parameters	Value
AC input	90 V-264 V
Line frequency	50-60 Hz
DC output	400 V
Maximum power	5 kW
Holdup time at full load	20 ms
L _g , low-frequency inductor	140 μH
L _b , high-frequency inductor	14 μH
C _b , high-frequency blocking capacitor	1.5 μF
Total harmonic distortion (THD)	OCP v3
Electromagnetic interference (EMI)	European standard (EN) 55022 Class A
Operating frequency	Variable, 75 kHz-1.2 MHz
Microcontroller	TMS320F280049C [11]
High-frequency GaN field-effect transistors (FETs) (S ₁₁ , S ₁₂ , S ₂₂ , S ₂₁)	LMG3526R030 [12]
Low-frequency silicon FETs (S ₃ , S ₄)	IPT60R022S7XTMA1
Dimensions	38 mm ´ 65 mm ´ 263 mm
Power density	120 W/in ³

Table 1. iTCM topology with inductor and current envelopes.

Topology overview

The topology uses two phases operating 180° out of phase with a single DC blocking capacitor, C_b, taking advantage of the ripple current cancellation provided by the two-phase architecture and reducing the root-mean-

square (RMS) current stress in C_b . L_{b1} and L_{b2} are sized to process the high-frequency AC ripple current necessary for TCM operation, removing the DC bias burden required for the inductor used in TCM, as defined in [5]. Using ferrite cores for L_{b1} and L_{b2} ensures low loss in the presence of the high flux swings necessary for zero voltage switching (ZVS). L_{g1} and L_{g2} are larger in value than L_{b1} and L_{b2} (approximately 10 times larger), preventing most of the high-frequency current from flowing into the input source and subsequently improving EMI. In addition, the reduced ripple current in L_{g1} and L_{g2} enables the possible use of lower-cost core materials.

Figure 1 also illustrates the ripple current envelopes for the inductors and switch nodes.

AC dropout technical challenges

The first challenge that I want to highlight is reverse-current generation when the AC input voltage disappears. Since all of the switches in the totem-pole PFC topology are bidirectional, it is essential that the FETs operating as synchronous rectifiers shut off as quickly as possible when removing AC. This shutoff prevents the generation of a negative current that will cause the output voltage to discharge and reduce the available holdup time. **Figure 2** illustrates the path for generating this negative current for the synchronous conduction interval during the positive half cycle. In addition, any substantial delays in turning off the synchronous rectifiers can also result in a large current spike capable of activating overcurrent protection (OCP). For example, if the synchronous rectifier stays on when no input voltage is present, you can solve $V_{dc} = L_{b1} \cdot \frac{dI_1}{dt}$ for the amount of time it takes to generate 70 A of current, namely 2.5 μs . This short time presents a significant problem for the AC dropout detection to identify the problem and stop switching before the system hits OCP or causes damage.

 


Figure 2. Synchronous rectifier S_{21} delayed turnoff V_{dc} discharge path.

The second challenge is resuming operation of the PFC after restoring AC. The central issue of this event comes from the fact that the bypass diodes on the PFC charges the output voltage to the peak of the input sine wave, which occurs most readily at high line when the output voltage has fallen well below this peak value. During these events, the converter has no mechanism to stop the current, making the surge current very large. Improper control of the switches during these events can make things much worse by saturating the inductors, creating OCP events and further discharging the output voltage. The need for a precise control algorithm during this time is again multiplied by the high-frequency operation point of the iTTCM topology with the small-value inductors used for L_{b1} and L_{b2} .

AC dropout solution

In order to precisely determine the presence and absence of the AC input, the solution uses a virtual AC input signal that monitors the integrity of the actual AC input. This virtual signal is generated by measuring the input voltage amplitude, frequency and phase, such that during normal operation it tracks the 50- and 60-Hz component of the actual AC input nearly perfectly. The system can easily recognize the presence and absence of the AC input voltage by comparing the actual input to the virtual input. Any sudden changes in the difference between these two signals indicates an input transient event. It is this transient event that is used to detect both the loss and restoration of the AC input voltage. **Figure 3** illustrates the virtual AC input, along with the actual input during a dropout event.

 


Figure 3. AC input dropout with the virtual AC signal.

Figure 4 illustrates the state machine that governs the dropout and restore process. During startup, the system goes through an initialization cycle (Sync Init) where it determines the RMS input voltage magnitude. It uses a software phase-locked loop (SPLL) to ensure that the phase of $V_{ac,virtual}$ matches $V_{ac,actual}$. Once the SPLL is locked (Sync On), the processor monitors the ratio between $V_{ac,actual}/V_{ac,virtual}$ (see Figure 3). If this ratio is less than the target threshold, then a dropout event is declared and switching stops immediately (Stop State). From here, the system clears any faults that occurred and goes into a standby state (Ready), where it monitors the $V_{ac,actual}/V_{ac,virtual}$ ratio to determine when it goes above the resume threshold. Once the state machine has determined that AC is restored, it resumes switching immediately and resynchronizes the SPLL (Resume State). By using the $V_{ac,actual}/V_{ac,virtual}$ ratio in concert with the SPLL, the algorithm is able to determine the AC dropout and restore times for any input voltage or frequency. In addition, since the algorithm always monitors the ratio $V_{ac,actual}/V_{ac,virtual}$, it is able to respond more quickly than a traditional level-based-solution that detects when the AC input voltage goes to zero. Level-based monitoring for dropout can create delays that can result in large current spikes and significant reverse current.

 


Figure 4. AC dropout and restore state machine.

Results

Figure 5 illustrates the performance of the two-phase iTCM totem-pole PFC with the aforementioned algorithm during an AC dropout and restore event. The AC input voltage is 230 V_{RMS} at 60 Hz and the output voltage is 400 V. The load is 5 kW (400 V, 12.5 A) of constant current with a 20-ms AC dropout event. In order to produce the worst-case stress for the system, AC was removed such that it would return at the peak of the AC line cycle. This is the worst case for inrush current, in that the input bypass diodes will cause significant inrush current into the output capacitors when the AC line peak exceeds V_{OUT} .

The waveform in Figure 5 also provides an image zoomed in on the recovery portion of the event. It is clearly visible that the PFC switch current is well controlled and below the GaN FET OCP limit [12]. Minimized reverse current prevents unnecessary discharge of V_{OUT} . In addition, there is no abnormal behavior from the bypass diode conduction intervals, since the algorithm is able to easily determine whether the input voltage is above or equal to the output voltage.

 


Figure 5. AC dropout and restore performance at 5 kW.

In addition to AC dropout, the design also delivers low THD, high efficiency, high power density and fast load transient response.

If you are interested in more details on this algorithm or other aspects of this design, you can find the full schematics, layout, bill of materials, test results and code for the two-phase totem-pole PFC reference design in reference [10].

References

1. **V2 Power Shelf Specification 6600W @ 12.6V DC (2+1) Redundant**. OPEN Compute Project. Facebook: Menlo Park, California, February 2015.
2. Fernandes, Ryan, and Olivier Trescases. **A Multimode 1-MHz PFC Front End With Digital Peak Current Modulation**. Published in IEEE Transactions on Power Electronics 31, no. 8 (August 2016): pp. 5694-5708. doi: 10.1109/TPEL.2015.2499194.
3. Lim, Shu Fan, and Ashwin M. Khambadkone. **A Multimode Digital Control Scheme for Boost PFC with Higher Efficiency and Power Factor at Light Load**. Published in 2012 Twenty-Seventh Annual IEEE Applied Power Electronics Conference and Exposition (APEC), pp. 291-298. doi: 10.1109/APEC.2012.6165833.
4. Huang, Long, Wenxi Yao, and Zhengyu Lu. **Interleaved Totem-Pole Bridgeless PFC Rectifier with ZVS and Low Input Current Ripple**. Published in 2015 IEEE Energy Conversion Congress and Exposition (ECCE), pp. 166-171. doi: 10.1109/ECCE.2015.7309684.
5. Liu, Zhengyang. 2017. **Characterization and Application of Wide-Band-Gap Devices for High Frequency Power Conversion**. Ph.D. dissertation, Virginia Polytechnic Institute and State University.
6. Kim, J.W., S.M. Choi, and K.T. Kim. **Variable On-Time Control of the Critical Conduction Mode Boost Power Factor Correction Converter to Improve Zero-Crossing Distortion**. Published in 2005 International Conference on Power Electronics and Drives Systems, pp. 1542-1546. doi: 10.1109/PEDS.2005.1619933.
7. Xu, Xiaojun, and Alex Q. Huang. **A Novel Closed Loop Interleaving Strategy of Multiphase Critical Mode Boost PFC Converters**. Published in 2008 Twenty-Third Annual IEEE Applied Power Electronics Conference and Exposition (APEC), pp. 1033-1038. doi: 10.1109/APEC.2008.4522849.
8. Neumayr, D., D. Bortis, E. Hatipoglu, J.W. Kolar, and G. Deboy. **Novel Efficiency-Optimal Frequency Modulation for High Power Density DC/AC Converter Systems**. Published in 2017 IEEE 3rd International Future Energy Electronics Conference and ECCE Asia (IFEEC 2017-ECCE Asia), pp. 834-839. doi: 10.1109/IFEEC.2017.7992148.
9. Rothmund, Daniel, Dominik Bortis, Jonas Huber, Davide Biadene, and Johann W. Kolar. **10 kV SiC-Based Bidirectional Soft-Switching Single-Phase AC/DC Converter Concept for Medium-Voltage Solid-State Transformers**. Published in 2017 IEEE 8th International Symposium on Power Electronics for Distributed Generation Systems (PEDG), pp. 1-8. doi: 10.1109/PEDG.2017.7972488.
10. Texas Instruments. n.d. **Variable-Frequency, ZVS, 5-kW, GaN-Based, Two-Phase Totem-Pole PFC Reference Design**. Texas Instruments reference design No. PMP40988. Accessed Dec. 27, 2022.
11. Texas Instruments. n.d. **C2000™ 32-Bit MCU with 100-MHz, FPU, TMU, 256-kb Flash, CLA, InstaSPIN-FOC™, CLB, PGAs, SDFM**. Accessed Dec. 27, 2022.
12. Texas Instruments. n.d. **Automotive 650-V 30-mΩ GaN FET with Integrated Driver, Protection and Temperature Reporting**. Accessed Dec. 27, 2022.

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated