

Addressing the protection challenges of 48V AI servers using hot-swap controllers

Avishek Pal
Power Switches

Rakesh Panguloori
Power Switches

Introduction

With advancements in artificial intelligence (AI) and machine learning, enterprise servers have become extremely power-hungry as they simultaneously process a large amount of data and storage. The steady-state power rating of each server motherboard has gone up to 5kW or 6kW, in contrast to 1kW or 2 kW for general servers. The form factor remains the same, however, which imposes system design challenges given the increased power density. The load amplitude, slew rate and frequency of transient loads on AI servers have increased three to four times compared to general servers.

Figure 1 shows a typical power distribution in a 48V rack server where the input is protected by the hot-swap circuit - and then distributed to all downstream system loads.

 


Figure 1. Typical block diagram of a 48V rack server power distribution.

In this article, we’ll discuss various challenges that AI-based processors bring into 48V server designs, along with design guidelines and important tips and tricks for the design and layout to achieve a reliable hot-swap solution for the system specifications outlined in [Table 1](#).

Design Parameter	Value
Input voltage range	40V to 60V
Output capacitance	4.2mF
Steady-state thermal design power rating	6kW
Transient power rating	8kW at 400μs
Transient load profile	15% to 100% of the transient power rating with a 10% duty cycle
Load slew rate	>2A/μs
Frequency of transient load	>1kHz

Table 1. Typical system specifications.

Challenges in designing a hot-swap circuit for a 48V AI server

It’s interesting to look at how hot-swap circuit configurations have evolved over the years. A hot-swap solution consists of three main components: a N-channel metal-oxide semiconductor field-effect transistor (MOSFET) that serves as the main power control switch; a sense resistor that measures the current; and the hot-swap controller, which includes a current-sense amplifier completing the loop to control the MOSFET’s pass current.

As shown in [Figure 2](#), you can use a single MOSFET-based hot-swap solution for low-power designs. Fundamentally, the hot-swap controller comes with current- and power-limiting functionalities to limit the inrush and fault currents while ensuring the MOSFET’s safe operating area (SOA). These functionalities are good enough to design low-power (<500W) hot-swap solutions.

 


Figure 2. Traditional power-limiting hot-swap circuit.

 


Figure 3. Hot-swap circuit with GATE slew-rate control.

 


Figure 4. Hot-swap circuit with local discharge path for Cdv/dt.

With the increase in digital load, the system needs a higher output capacitance (>470μF), requiring parallel MOSFETs to support steady-state current and the adoption of output-voltage slew-rate control [1] to keep the MOSFET within its SOA.

In the output-voltage slew-rate control method, capacitor C_{dv/dt} placed across GATE-GND (see [Figure 3](#)) limits the slew-rate of the gate and output voltages, which limits the inrush current. MOSFETs can handle more energy when the power dissipation in them is reduced and spread over longer durations. Therefore, as the output capacitance increases, you need a higher C_{dv/dt}

to reduce both the inrush current and power dissipation in the MOSFET during startup.

A higher C_{dv}/dt interferes with the turnoff process, however, the hot-swap controller has limited pulldown strength. This necessitates a local P-channel N-channel P-channel (PNP)-based discharge circuit for C_{dv}/dt , as shown in **Figure 4**. During startup, C_{dv}/dt controls slew-rate in the same way, but during a turnoff event, the Q1 PNP transistor activates and discharges C_{dv}/dt locally. Diode D1 blocks the discharge of C_{dv}/dt into the GATE pin, which reduces the stress on the GATE pin and also ensures proper operation of the controller.

In AI-powered graphics processing unit applications, the hot-swap solution has to support currents around 150A and must support high-frequency, high slew-rate load transients, which present three new challenges.

Challenge No. 1: Turnoff delay during an output short-circuit

With the increase in load current, more MOSFETs need to be parallel to limit the maximum steady-state MOSFET junction temperature to a safe value (100°C to 125°C). For example, to support a steady-state load current of 150A at an ambient temperature of 70°C, eight Texas Instruments (TI) CSD19536KTT MOSFETs need to be in parallel to limit the steady-state MOSFET junction temperature to 100°C. Paralleled MOSFETs help thermally, but increase the effective capacitance on the GATE pin of the hot-swap controller and impact the turnoff response.

During an output short-circuit, the MOSFETs need to turn off fast enough to prevent further buildup of fault current and avoid damage to the MOSFETs, input power supply, or printed circuit board (PCB). The gate pull-down strength of the TI LM5066I hot-swap controller is limited to 160mA, which is not enough to turn off all eight MOSFETs completely during a short-circuit event, as shown in [Figure 5](#).

 


Figure 5. Short-circuit response of the LM5066I controller with eight MOSFETs.

Challenge No. 2: False gate turn-off during a load transient

Although the local PNP-based discharge circuit for C_{dv}/dt helps reliably turn-off the MOSFETs during an output short-circuit event, it causes a false GATE turn-off in the presence of high-frequency, high slew-rate load transients. During load step-up, the MOSFET source node drops because of the finite input and output impedances of the hot-swap circuit. The voltage drop at the source node gets coupled to the MOSFET gate node through the C_{GS} capacitance of the MOSFET and causes the gate node to drop as well. The MOSFET source node recovers during load step-down. The gate node cannot recover completely to its previous level, because of the limited gate current (20 μA typical) of the LM5066I hot-swap controller. As a result, the hot-swap controller gate continues to drop further in the subsequent load transient cycles developing the base-emitter voltage for Q1. Finally, PNP bipolar junction transistor Q1 turns on, and falsely shuts down the system. **Figure 6** illustrates the whole process, while **Figure 7** shows the corresponding test result.

 


Figure 6. Illustration of a hot-swap circuit for a dynamic load.

 


Figure 7. Response of a hot-swap circuit to a dynamic load.

Challenge No. 3: Parallel resonance during controlled (slow) turn-on

Generally, parallel MOSFETs are more prone to parasitic oscillations than a single MOSFET in the linear region of operation. This is because of the presence of parasitic stray package inductances and capacitances on the drain, source and gate nodes, which form a resonant tank circuit resembling a Colpitts oscillator. Unlike switching regulators with a gate-drive strength of $>2A$, hot-swap controllers with a lower gate-drive strength ($20\mu A$) limit the inrush current during start-up by operating the MOSFETs in the linear region. As a result, the parallel combination of hot-swap MOSFETs is highly susceptible, with more chance of generating sustained oscillations. This phenomenon causes the violation of the MOSFET SOA during a power-into-short fault, leading to MOSFET damage.

Proposed circuit enhancements

Let's discuss circuit enhancements to help solve these three challenges.

Improving the turn-off response

In the proposed solution shown in [Figure 8](#), introducing an external fast pull-down circuit using a PNP transistor (Q_{PD} and R_{PD}) will boost up the turn-off speed. During an output short-circuit event, the gate pull-down current of $160mA$ creates a substantial voltage drop across the R_{PD} resistor and enables fast pull-down of the PNP transistor (Q_{PD}). This in turn shorts the gate-to-source of all parallel MOSFETs, turning off the MOSFETs immediately to quickly disconnect the power path. [Figure 9](#) shows the experimental result for a short-circuit event with a fast pull-down circuit.

Overcoming false turn-off for dynamic loads

In this solution, the hot-swap gate node is decoupled from the MOSFET gate terminal by placing the D_{SS} diode between them, again shown in [Figure 8](#). This modification helps eliminate the reflection of output voltage ripple to the hot-swap controller GATE node and avoids false turn-on of the soft-start PNP transistor, Q_{SS} . Changing the position of the diode does not impact controller behavior during start-up nor any of the fault events. As shown in the test result (see [Figure 10](#)), the system operates continuously even for large load steps from $20A$ to $120A$ at a $1kHz$ frequency.

 


Figure 8. Proposed hot-swap circuit configuration.

 


Figure 9. Output short-circuit response with fast pull-down circuit.

 


Figure 10. Load transient performance for steps from 20A to 120A to 20A at a 1kHz frequency.

Damping parasitic oscillations

Adding a damping resistor (R_{G1} , R_{G2} , R_{G3}) in series with the gate of each MOSFET can eliminate the parasitic oscillations in the system. Usually, we recommend a 10Ω 0603 package resistance, but based on the parasitics, a low value around 1Ω may also help. We suggest testing on your PCB and deciding the value of the damping resistor.

Design guidelines and component selection

Reference [1] iterates a procedure for designing a hot-swap circuit to protect the system and MOSFETs. We recommend reviewing Reference [1] to become familiar with the design.

Feeding the system specifications shown in Table 1 into the [LM5066I design calculator](#) will obtain the values of the current-sense resistor (R_{SNS}), power-limiting resistor (R_{PWR}), fault timer capacitor (C_{TIMER}), soft-start capacitor ($C_{dv/dt}$) and number (N) of selected MOSFETs to parallel. In the [8kW Hot-Swap Reference Design for 48V Artificial Intelligence Servers](#) [2], $R_{SNS} = 330\mu\Omega$, $R_{PWR} = 28.7k\Omega$, $C_{TIMER} = 10nF$, $C_{dv/dt} = 47nF$ and $N = 8$.

Looking at [Figure 8](#), select the R_{PD} resistor using [Equation 1](#):

$$R_{PD} > \frac{V_{BE(sat)}}{I_{GATE(CB)}} \quad (1)$$

where, $V_{BE(sat)}$ is the base-emitter saturation voltage of the Q_{PD} PNP transistor and $I_{GATE(CB)}$ is the power-on reset circuit-breaker sink current in the LM5066I hot-swap controller. The 8kW hot-swap reference design uses an R_{PD} value = 20Ω.

$C_{dv/dt}$ discharge circuit

Figure 8 uses a 100V signal diode for D_{SS} . The diode should handle a few tens of milliamperes of forward current. The 8kW hot-swap reference design uses the BAV16W-7-F from Diodes Inc.

You will have to select R_{SS1} , R_{SS2} and Q_{SS} iteratively so that none of the three components become stressed during turn-off. For Q_{SS} , you can select any standard PNP transistor with collector-emitter (V_{CEO}) and collector-base (V_{BEO}) voltages of >100V_{DC} and a continuous collector current of >200mA. Select the values for R_{SS1} and R_{SS2} and their respective power ratings to limit the current flowing through the Q_{SS} transistor to a safe value. You must use a special high-power resistor for R_{SS2} to manage the transient peak power stress during turn-off. The 8kW hot-swap reference design uses onsemi MMBT5401LT1G for Q_{SS} , with R_{SS1} = 100Ω and R_{SS2} = 499Ω (the Vishay RCS0805499RFKEA).

Input transient voltage suppression (TVS) diodes are required to protect against transient overvoltages during input hot-plug and output short-circuit events. The TI **TVS diode recommendation tool** can help you obtain the part number (voltage and power ratings) of the TVS diode and the number of TVS diodes to parallel. The 8kW hot-swap reference design uses three Littelfuse 8.0SMDJ60A TVS diodes. For a deeper analysis into TVS diode selection, see Reference [3].

You will need output Schottky diodes to protect the output pin of the hot-swap controller against a negative transient in the event of an output short-circuit event. The 8kW hot-swap reference design uses three onsemi FSV20100V Schottky diodes.

Conclusion

The emerging 48V AI servers demand significantly more power, both in peak and steady states, than traditional servers. The high-power consumption along with fast and transient dynamics impose challenges in designing front-end protection using a hot-swap controller and parallel MOSFETs. The challenges include fast turn-off of parallel MOSFETs for real faults while avoiding false turn-off for high-frequency transients from the computational load. The proposed solution in this article eliminates the limitations of legacy hot-swap controllers and enables the design of a reliable input protection solution for a 48V AI server.

References

1. Rogachev, Artem. “**Robust Hot Swap Design.**” Texas Instruments application report, literature No. SLVA673A, April 2014.
2. Texas Instruments. “**8kW Hot-Swap Reference Design for 48V Artificial Intelligence Servers.**” Texas Instruments test report, literature No. PMP23496, August 2024.
3. Hegarty, Timothy. 2011. “TVS Clamping in Hot-Swap Circuits.” Power Electronics Technology, October 2011.

Related Websites

- [LM5066I](#)
- [PMP23496](#)

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2025, Texas Instruments Incorporated