

# ***AN-2218 Precision Current Limiting with the LMP8646 and LM3102***

---

## **ABSTRACT**

This application report discusses how to design the Texas Instruments LMP8646 with the LM3102 voltage regulator and a supercap load application.

---

## **Contents**


1	Overview .....	2
2	Example .....	2

## **List of Figures**

1	SuperCap Application with LM3102 Regulator and LMP8646 Precision Current Limiter .....	2
2	LMP8646 Output Accuracy Equation.....	3
3	SuperCap Application with LM3102 Regulator Plot .....	4

## 1 Overview

The LMP8646 is a precision current limiter used to improve the current limit accuracy of any switching or linear regulator with an available feedback node. Many regulators might have an internal current limiter, but its output accuracy is often as high as 30%. The output accuracy of the LMP8646 can be as low as 3%, making it a preferred current limiter for many regulator applications. The SuperCap application with LM3102 regulator and LMP8646 precision current limiter is shown in Figure 1.

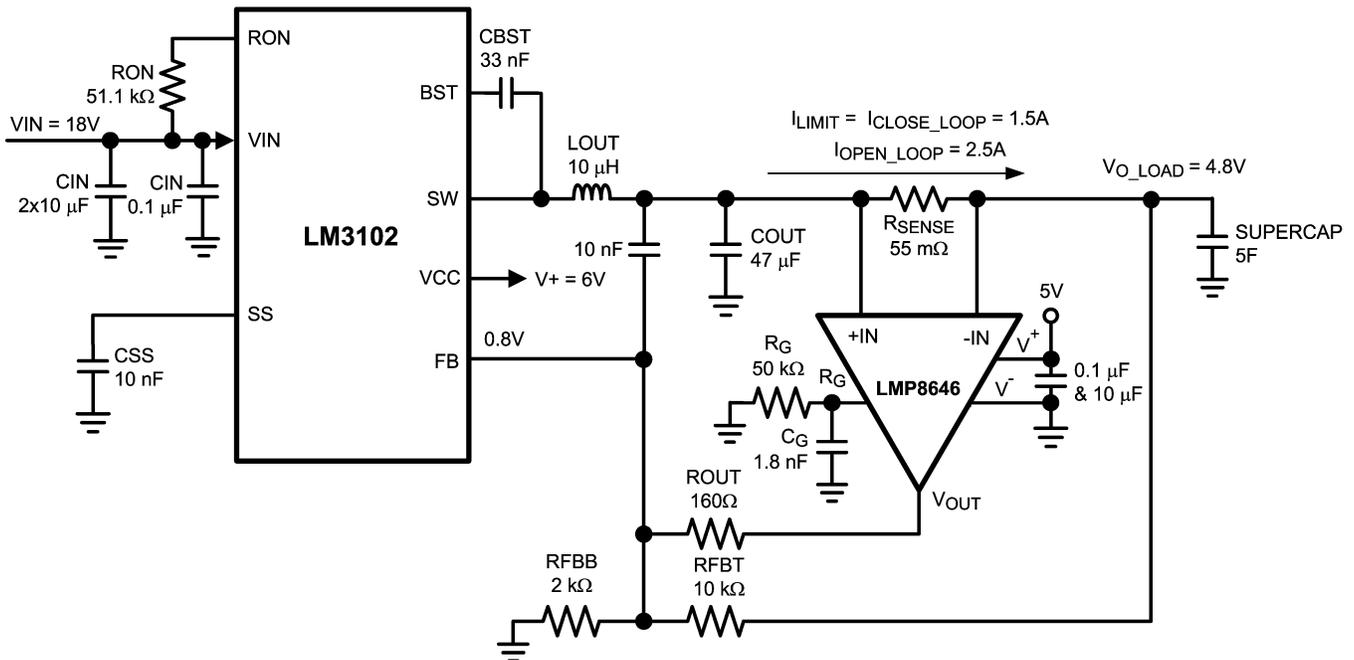

**Figure 1. SuperCap Application with LM3102 Regulator and LMP8646 Precision Current Limiter**

## 2 Example

A supercap application requires a very high capacitive load to be charged. This example assumes the output capacitor is 5F with a limited sense current,  $I_{LIMIT}$ , at 1.5A. The LM3102 provides the current to charge the supercap, and the LMP8646 monitors this current to make sure it does not exceed the desired 1.5A value.

This is done by connecting the LMP8646 output to the feedback pin of the LM3102, as shown in Figure 1. This feedback voltage at the FB pin is compared to a 0.8V internal reference. Any voltage above this 0.8V means the output current is above the desired value of 1.5A, and the LM3102 will reduce its output current to maintain the desired 0.8V at the FB pin. The following steps show the design procedures for this supercap application. In summary, the steps consist of selecting the components for the voltage regulator, integrating the LMP8646 and selecting the proper values for its gain, bandwidth, and output resistor, and adjusting these components to yield the desired performance.

### Step 1: Choose the components for the Regulator.

To select the appropriate components for the LM3102 voltage regulator, see *AN-1646 LM3102 Demonstration Board Reference Design* ([SNVA248](#)).

**Step 2: Step 2: Choose the sense resistor,  $R_{SENSE}$** 

$R_{SENSE}$  sets the voltage  $V_{SENSE}$  between +IN and -IN and has the following equation:

$$R_{SENSE} = V_{OUT} / [(I_{LIMIT}) \times (R_G / 5k\Omega)] \quad (1)$$

In general,  $R_{SENSE}$  depends on the output voltage, limit current, and gain. To choose the appropriate  $R_{SENSE}$  value, see the Selection of the Sense Resistor,  $R_{SENSE}$  section in *LMP8646 Precision Current Limiter (SNOSC63)*. Typically,  $R_{SENSE}$  is a power resistor in the mOhm range. In this example, we will use 55 mOhm.

**Step 3: Choose the gain resistor,  $R_G$ , for LMP8646**

$R_G$  is chosen from the limited sense current. As stated in [Equation 1](#), since  $V_{OUT} = V_{FB} = 0.8V$ , the limited sense current is 1.5A and  $R_{SENSE}$  is 55 mOhm,  $R_G$  can be calculated as:

$$R_G = (V_{OUT} \times 5 \text{ k}\Omega) / (R_{SENSE} \times I_{LIMIT})$$

$$R_G = (0.8 \times 5 \text{ k}\Omega) / (50 \text{ m}\Omega \times 1A) = 50 \text{ k}\Omega \text{ (approximate)} \quad (2)$$

**Step 4: Choose the Bandwidth Capacitance,  $C_G$ .**

The product of  $C_G$  and  $R_G$  determines the bandwidth for the LMP8646. To see the range for the LMP8646 bandwidth and gain, see the Typical Performance Characteristics plots in *LMP8646 Precision Current Limiter (SNOSC63)*. Since each application is very unique, the LMP8646 bandwidth capacitance,  $C_G$ , needs to be adjusted to fit the appropriate application.

Bench data has been collected for the supercap application with the LM3102 regulator, and we found that this application works best for a bandwidth of 500 Hz to 3 kHz. Operating outside of this recommended bandwidth range might create an undesirable load current ringing. We recommend choosing a bandwidth that is in the middle of this range and using the equation:

$$C_G = 1/(2 \times \pi \times R_G \times \text{Bandwidth}) \quad (3)$$

to find  $C_G$ . For example, if the bandwidth is 1.75 kHz and  $R_G$  is 50 kOhm, then  $C_G$  is approximately 1.8 nF.

After selecting an initial  $C_G$  value, capture the plot for  $I_{LIMIT}$  and adjust  $C_G$  until a desired load current plot is obtained.

**Step 5: Calculate the Output Accuracy and Tolerable System Error**

Since the LMP8646 is a precision current limiter, the output current accuracy is extremely important. This accuracy is affected by the system error contributed by the LMP8646 device error and other errors contributed by external resistances, such as  $R_{SENSE}$  and  $R_G$ .

In this application,  $V_{SENSE} = I_{LIMIT} \times R_{SENSE} = 1.5A \times 55 \text{ m}\Omega = 0.0825V$ , and  $R_G = 50 \text{ k}\Omega$ . From the LMP8646 Electrical Characteristics Table, it is known that  $V_{OFFSET} = 1 \text{ mV}$  and  $Gm\_Accuracy = 2\%$ . Using the equations in [Figure 2](#), the output accuracy can be calculated as 3.24%.

$$\text{Output Accuracy} = \left| \frac{V_{OUT\_THEO} - V_{OUT\_CAL}}{V_{OUT\_THEO}} \right| \times 100(\%)$$

$$\text{where } V_{OUT\_THEO} = (V_{SENSE}) \times \frac{R_G}{1/Gm}$$

$$\text{and } V_{OUT\_CALC} = \frac{(V_{SENSE} + V_{OFFSET}) \times R_G}{1/[Gm (1 + Gm\_Accuracy)]}$$

**Figure 2. LMP8646 Output Accuracy Equation**

### Step 6: Choose the Output Resistor, R<sub>OUT</sub>

At startup, the capacitor is not charged yet and thus the output voltage of the LM3102 is very small. Therefore, at startup, the output current is at its maximum (I<sub>MAX</sub>). When the output voltage is at its nominal, then the output current will settle to the desired limited value. Because a large current error is not desired, R<sub>OUT</sub> needs to be chosen to stabilize the loop with minimal initial startup current error. Follow the equations and example below to choose the appropriate value for R<sub>OUT</sub> to minimize this initial error.

Assume that the tolerable current error, I<sub>ERROR</sub>, is 5%, where  $I_{ERROR} = (I_{MAX} - I_{LIMIT})/I_{MAX}$  (%). Therefore, the maximum allowable current is calculated as:

$$I_{MAX} = I_{LIMIT} (1 + I_{ERROR}) = 1.5A \times (1 + 5/100) = 1.575 A.$$

Next, use the following formula to calculate for R<sub>OUT</sub>:

$$R_{OUT} = \frac{(I_{MAX} * R_{SENSE} * Gain - V_{FB})}{\frac{V_{FB}}{R_{FBB}} - \frac{(V_{O\_REG\_MIN} - V_{FB})}{R_{FBT}}} \tag{4}$$

For example, assume the minimum LM3102 output voltage, V<sub>O\_REG\_MIN</sub>, is 0.6V, then R<sub>OUT</sub> can be calculated as:

$$R_{OUT} = [1.575A \times 55 \text{ mOhm} \times (49.9k / 5k) - 0.8] / [(0.8 / 2k) - (0.6 - 0.8) / 10k] = 153.6 \text{ Ohm}.$$

Populate R<sub>OUT</sub> with a resistor that is as close as possible to 153.6 Ohm (this application uses 160 Ohm). If the current exceeds 1.575A at any point in time, then adjust this R<sub>OUT</sub> value to obtain the desired limit current. We recommend that the value for R<sub>OUT</sub> is at least 50 Ohm.

### Step 7: Adjusting the Components

Capture the output current and output voltage plots and adjust the components as necessary. The most common components to adjust are C<sub>G</sub> to decrease the current ripple and R<sub>OUT</sub> to get a low current error. An example output current and voltage plot can be seen in [Figure 3](#).

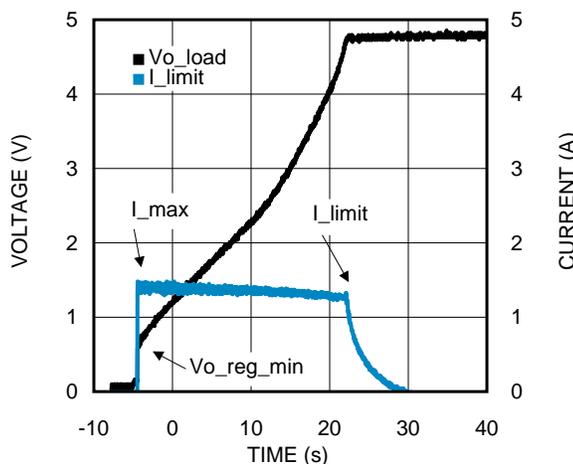


Figure 3. SuperCap Application with LM3102 Regulator Plot

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)