

# Application Report

## AN-31 amplifier circuit collection



### ABSTRACT

This application report provides basic circuits of the Texas Instruments amplifier collection.

### Table of Contents

<b>1 Basic Circuits</b> .....	<b>3</b>
<b>2 Signal Generation</b> .....	<b>15</b>
<b>3 Signal Processing</b> .....	<b>24</b>
<b>4 References</b> .....	<b>41</b>
<b>Revision History</b> .....	<b>41</b>

### List of Figures


Figure 1-1. Inverting Amplifier.....	3
Figure 1-2. Non-Inverting Amplifier.....	3
Figure 1-3. Difference Amplifier.....	4
Figure 1-4. Low-Power Difference Amplifier.....	4
Figure 1-5. Inverting Summing Amplifier.....	5
Figure 1-6. Non-Inverting Summing Amplifier.....	5
Figure 1-7. Inverting Amplifier With High Input Impedance.....	6
Figure 1-8. Two-Stage Inverting Amplifier With High Input Impedance.....	6
Figure 1-9. AC Coupled Non-Inverting Amplifier.....	7
Figure 1-10. Practical Differentiator.....	7
Figure 1-11. Integrator.....	8
Figure 1-12. Current to Voltage Converter (Transimpedance Amplifier).....	8
Figure 1-13. Reference Voltage Generator.....	9
Figure 1-14. Neutralizing Input Capacitance to Optimize Response Time.....	9
Figure 1-15. Threshold Detector for Photodiodes.....	10
Figure 1-16. Double-Ended Limit Detector.....	10
Figure 1-17. Multiple Aperture Window Discriminator.....	11
Figure 1-18. Offset Voltage Adjustment for Inverting Amplifiers.....	12
Figure 1-19. Offset Voltage Adjustment for Non-Inverting Amplifiers.....	12
Figure 1-20. Offset Voltage Adjustment for Voltage Followers.....	13
Figure 1-21. Offset Voltage Adjustment for Difference Amplifiers.....	13
Figure 1-22. Offset Voltage Adjustment for Inverting Amplifiers With Source Resistance.....	14
Figure 2-1. Sine Wave Generator With Low Component Count.....	15
Figure 2-2. Sine Wave Generator.....	15
Figure 2-3. Free-Running Multivibrator.....	16
Figure 2-4. Function Generator.....	16
Figure 2-5. Pulse Width Modulator.....	17
Figure 2-6. Improved Howland Current Pump.....	18
Figure 2-7. Wien Bridge Oscillator With Automatic Gain Control.....	18
Figure 2-8. Positive Output Voltage Reference.....	19
Figure 2-9. Buffered Positive Voltage Reference.....	19
Figure 2-10. Negative Output Voltage Reference.....	20
Figure 2-11. Buffered Negative Voltage Reference.....	20
Figure 2-12. Current Sink.....	21
Figure 2-13. Current Source.....	21
Figure 2-14. Voltage-to-Current Converter With BJT Output.....	22
Figure 2-15. Voltage-to-Current Converter With Darlington Pair Output.....	22
Figure 2-16. Voltage-to-Current Converter With MOSFET Output.....	23
Figure 3-1. Instrumentation Amplifier.....	24

Figure 3-2. Variable Gain Instrumentation Amplifier.....	25
Figure 3-3. Instrumentation Amplifier With $\pm 100$ -V Common Mode Range.....	25
Figure 3-4. Instrumentation Amplifier With $\pm 10$ -V Common Mode Range.....	26
Figure 3-5. High Input Impedance Instrumentation Amplifier.....	26
Figure 3-6. Bridge Amplifier With Temperature Sensitivity.....	27
Figure 3-7. Precision Diode.....	27
Figure 3-8. Precision Clamp.....	27
Figure 3-9. Fast Half Wave Rectifier.....	28
Figure 3-10. AC to DC Converter.....	28
Figure 3-11. Peak Detector.....	29
Figure 3-12. Absolute Value Amplifier.....	29
Figure 3-13. Sample and Hold I.....	30
Figure 3-14. Sample and Hold II.....	30
Figure 3-15. Adjustable Q Notch Filter.....	31
Figure 3-16. Easily Tuned Notch Filter.....	32
Figure 3-17. Sallen-Key Two-Stage Bandpass Filter.....	32
Figure 3-18. Two-Stage Capacitance Multiplier.....	33
Figure 3-19. Simulated Inductor.....	33
Figure 3-20. Capacitance Multiplier.....	34
Figure 3-21. High Pass Sallen-Key Active Filter.....	34
Figure 3-22. Low Pass Sallen-Key Active Filter.....	35
Figure 3-23. Current Monitor.....	35
Figure 3-24. Saturating Servo Preamplifier With Rate Feedback.....	36
Figure 3-25. Power Booster.....	36
Figure 3-26. Fast Zero Crossing Detector.....	37
Figure 3-27. Amplifier for Piezoelectric Transducer.....	37
Figure 3-28. Temperature Probe.....	38
Figure 3-29. Photodiode Amplifier I.....	38
Figure 3-30. Photodiode Amplifier II.....	39
Figure 3-31. High Input Impedance AC Follower.....	39
Figure 3-32. Multiplier/Divider.....	40

## Trademarks

All other trademarks are the property of their respective owners.

## 1 Basic Circuits

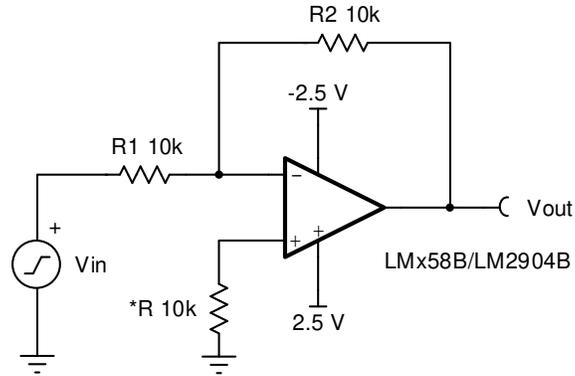


$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

\* R Optional to Protect LM358 & LM324

Devices from Transient Current Spikes

**Figure 1-1. Inverting Amplifier**

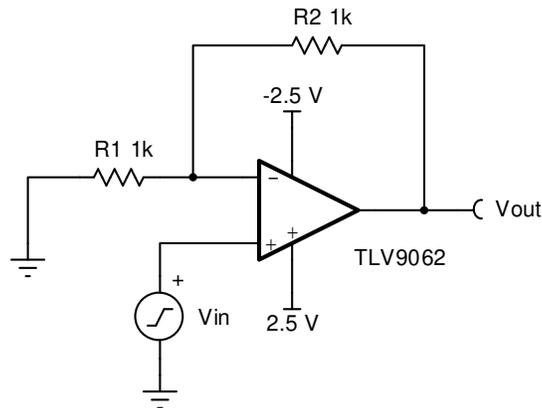
See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#). To learn more about \*R and how to protect LM358/LM2904 devices from transient current spikes at the input, see [23].



$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

**Figure 1-2. Non-Inverting Amplifier**

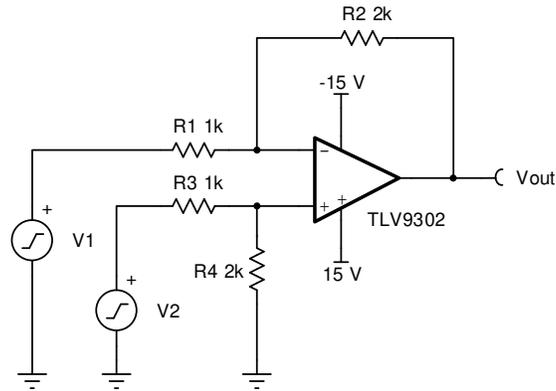See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \left( \frac{R_4}{R_3 + R_4} \right) \left( 1 + \frac{R_2}{R_1} \right) V_2 - \frac{R_2}{R_1} V_1$$

For  $R_1 = R_3$  and  $R_2 = R_4$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

**Figure 1-3. Difference Amplifier**

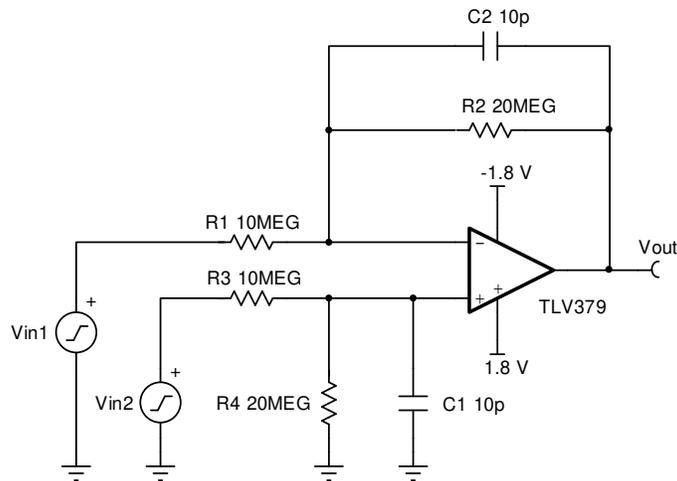See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = \left( \frac{R_4}{R_3 + R_4} \right) \left( 1 + \frac{R_2}{R_1} \right) V_2 - \frac{R_2}{R_1} V_1$$


For  $R_1 = R_3$  and  $R_2 = R_4$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

$$f_{cutoff} = \frac{1}{2\pi C_2 R_2}$$

**Figure 1-4. Low-Power Difference Amplifier**

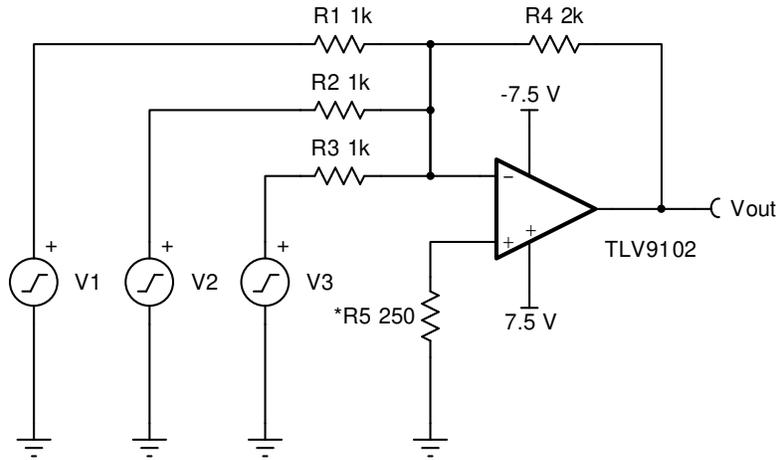See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = -R_4 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

\* R<sub>5</sub> Optional for Input Bias Current Cancellation

**Figure 1-5. Inverting Summing Amplifier**

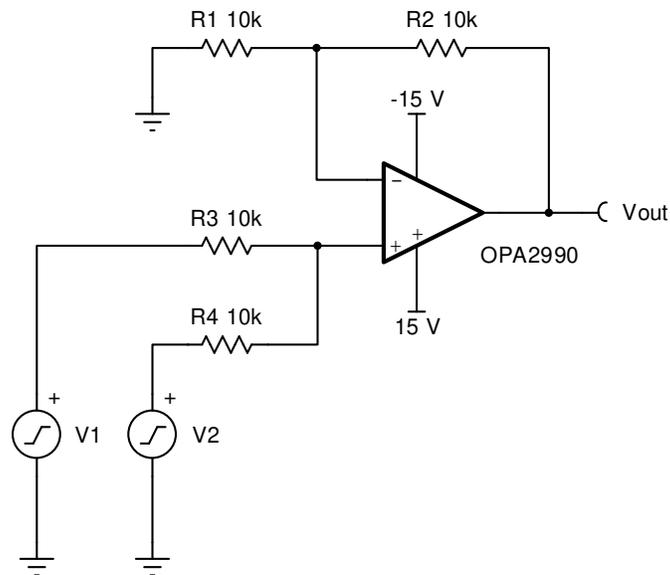See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \left( 1 + \frac{R_2}{R_1} \right) \left( V_1 \frac{R_4}{R_3 + R_4} + V_2 \frac{R_3}{R_3 + R_4} \right)$$

$$V_{out} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) (V_1 + V_2) \text{ if } R_3 = R_4$$

**Figure 1-6. Non-Inverting Summing Amplifier**

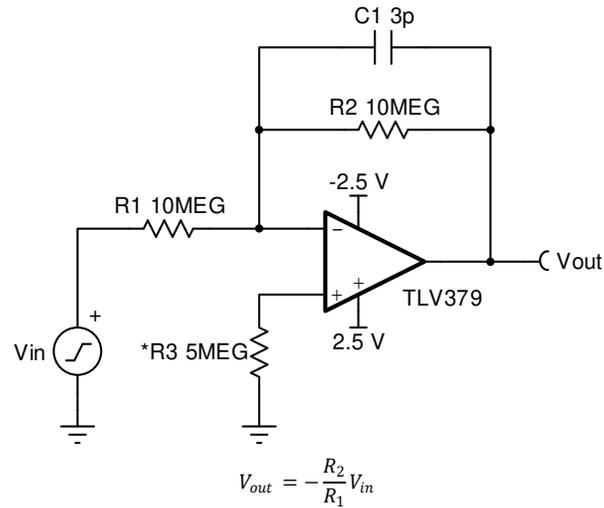
See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



\* R<sub>3</sub> Optional for Input Bias Current Cancellation


**Figure 1-7. Inverting Amplifier With High Input Impedance**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

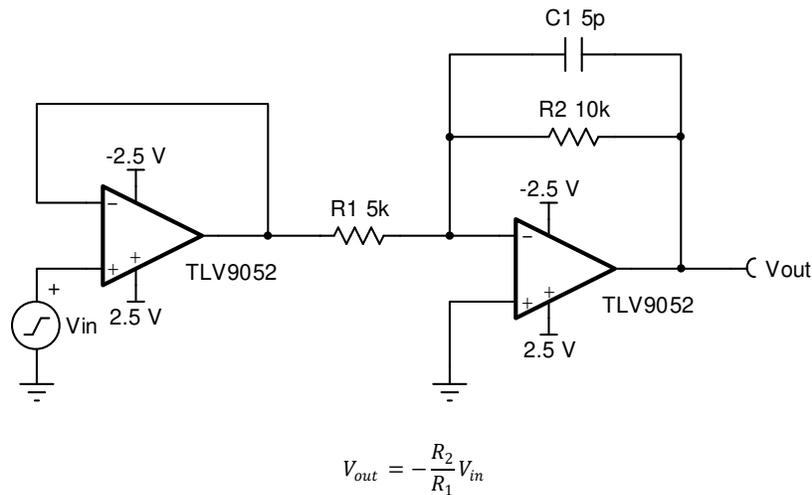

**Figure 1-8. Two-Stage Inverting Amplifier With High Input Impedance**

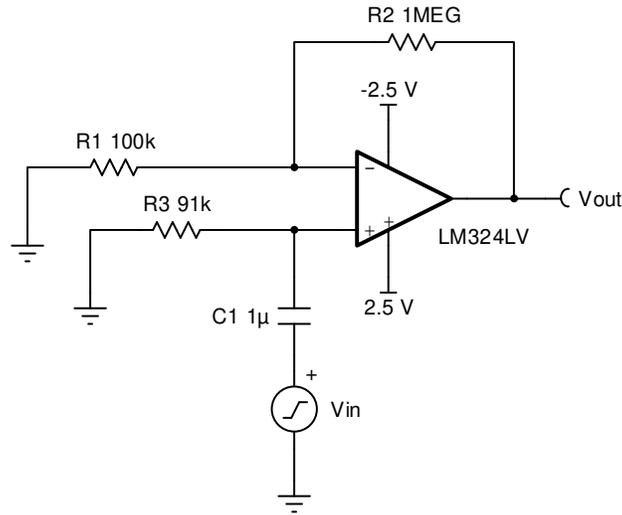Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$R_3 = R_1 || R_2 \text{ for CMRR}$$

$$f_{cutoff\ low} = \frac{1}{2\pi \times C_1 \times R_3}$$

**Figure 1-9. AC Coupled Non-Inverting Amplifier**

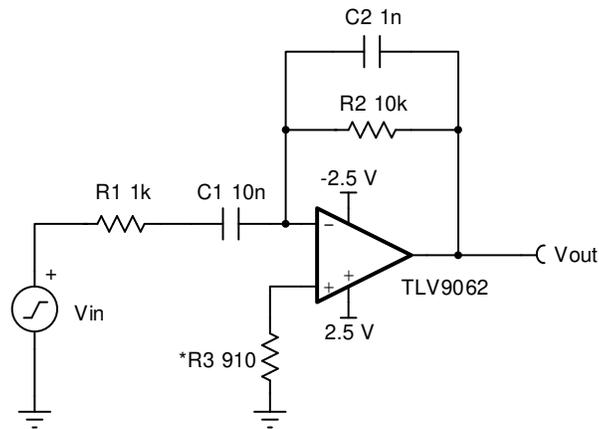See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = -\frac{dV_{in}}{dt}$$

$$f_c = \frac{1}{2\pi R_2 C_1} V_{in}$$


$$f_h = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi R_2 C_2}$$

$$f_c \ll f_h \ll f_{unity\ gain}$$

\* R<sub>3</sub> Optional for Input Bias Current Cancellation

**Figure 1-10. Practical Differentiator**

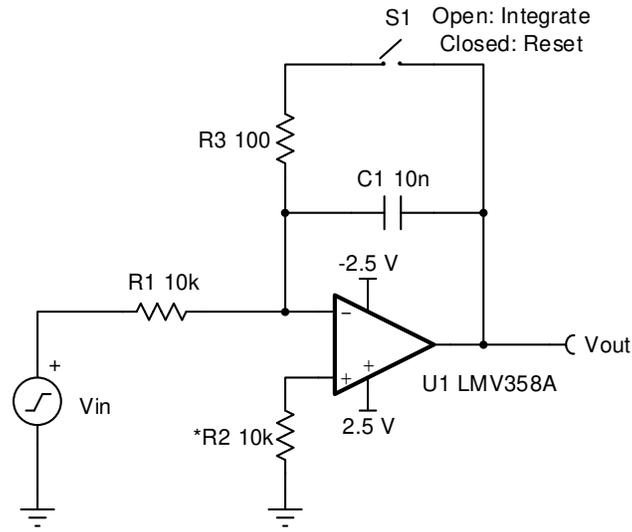See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = -\frac{1}{R_1 C_1} \int_{t_1}^{t_2} V_{in} dt$$


$$f_c = \frac{1}{2\pi R_1 C_1}$$

$$R_1 = R_2$$

\* R<sub>2</sub> Optional for Input Bias Current Cancellation

**Figure 1-11. Integrator**

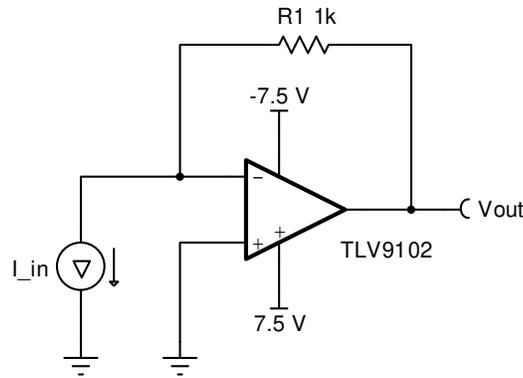
See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = I_{in} R_1$$


**Figure 1-12. Current to Voltage Converter (Transimpedance Amplifier)**

See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

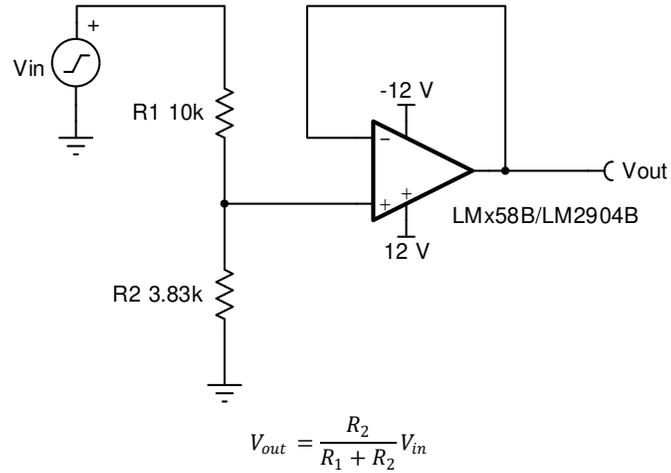


**Figure 1-13. Reference Voltage Generator**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

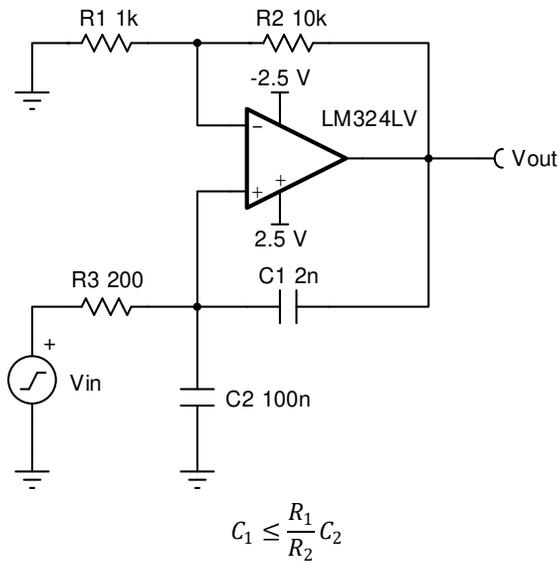


**Figure 1-14. Neutralizing Input Capacitance to Optimize Response Time**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

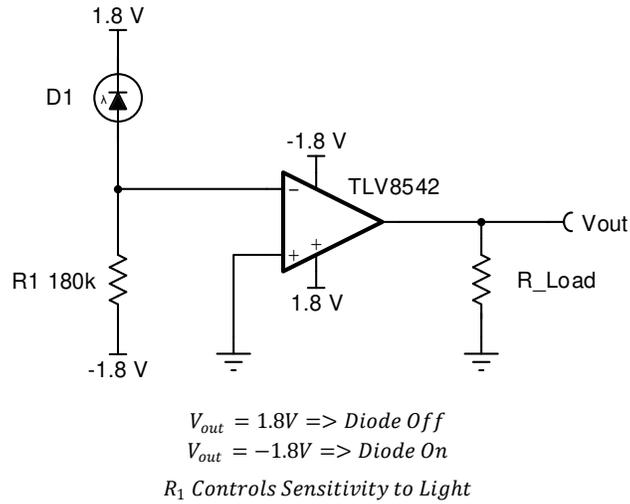


**Figure 1-15. Threshold Detector for Photodiodes**

For more information on modeling photodiodes, see [8]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

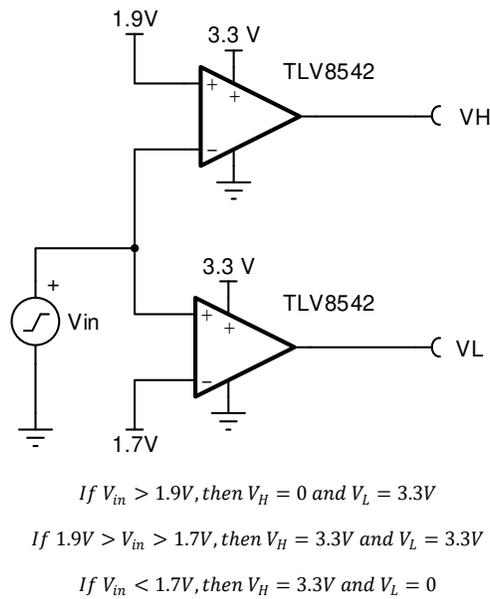

**Figure 1-16. Double-Ended Limit Detector**

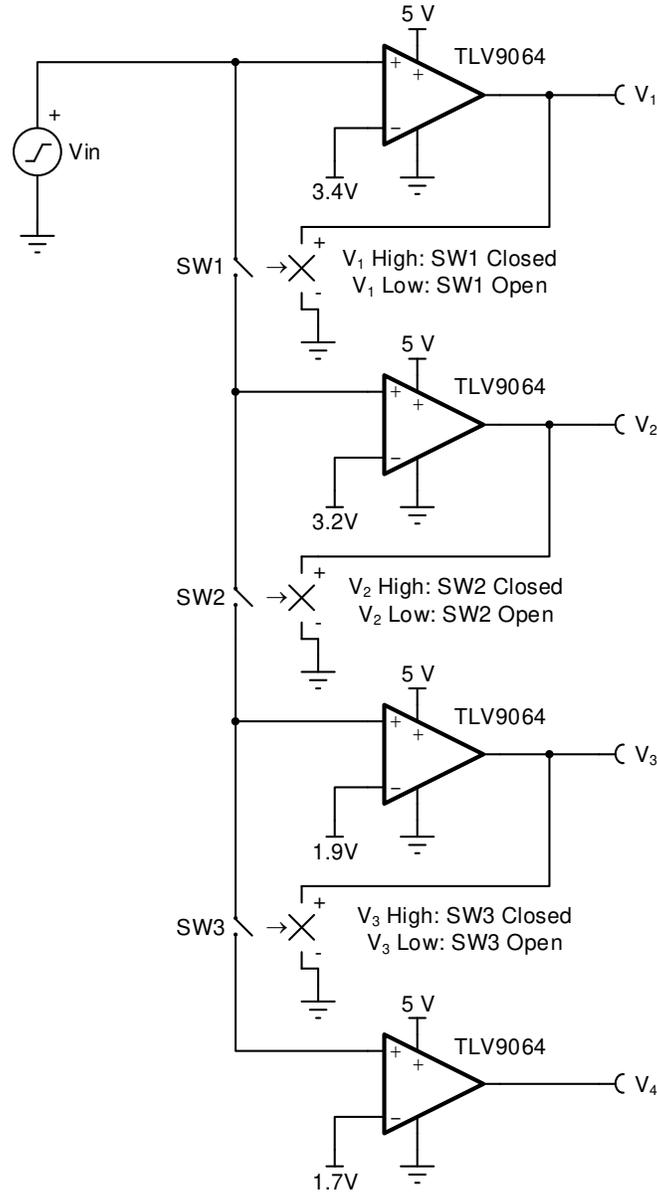
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$\begin{aligned}
 V_{in} > 3.4V &\rightarrow V_1 = 1, V_2 = 1, V_3 = 1, V_4 = 1 \\
 3.4V > V_{in} > 3.2V &\rightarrow V_1 = 0, V_2 = 1, V_3 = 1, V_4 = 1 \\
 3.2V > V_{in} > 1.9V &\rightarrow V_1 = 0, V_2 = 0, V_3 = 1, V_4 = 1 \\
 1.9V > V_{in} > 1.7V &\rightarrow V_1 = 0, V_2 = 0, V_3 = 0, V_4 = 1 \\
 1.7V > V_{in} &\rightarrow V_1 = 0, V_2 = 0, V_3 = 0, V_4 = 0
 \end{aligned}$$

**Figure 1-17. Multiple Aperture Window Discriminator**

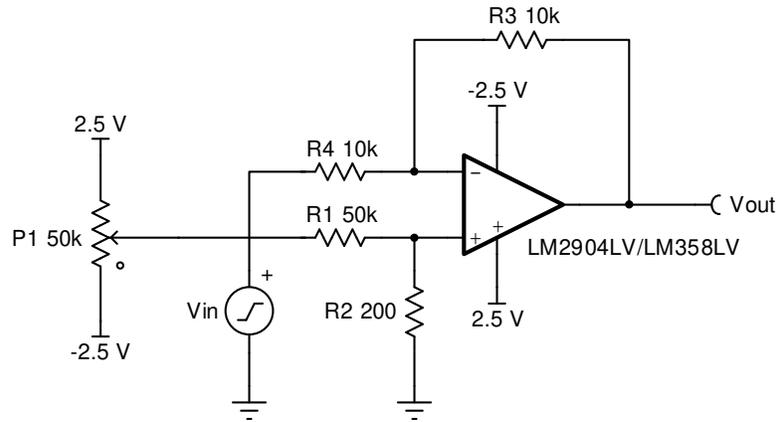Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$\text{Offset Range} = V_{\text{supply}} \left( \frac{R_2}{R_1} \right)$$

$$V_{\text{out}} = \left( -\frac{R_3}{R_1} \right) V_{\text{in}}$$

$$R_1 \gg R_2$$

**Figure 1-18. Offset Voltage Adjustment for Inverting Amplifiers**

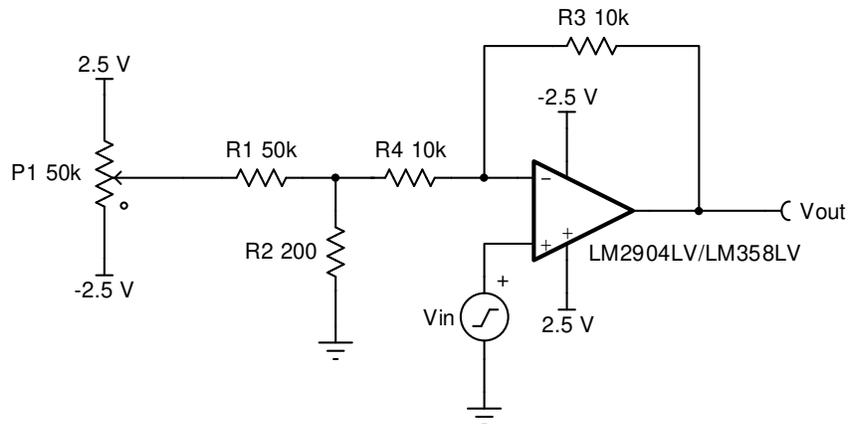Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$\text{Offset Range} = V_{\text{supply}} \left( \frac{R_2}{R_1} \right)$$

$$V_{\text{out}} = \left( 1 + \frac{R_3}{R_2 + R_4} \right) V_{\text{in}}$$

$$R_1 \gg R_2 \text{ and } R_4 \gg R_2$$

**Figure 1-19. Offset Voltage Adjustment for Non-Inverting Amplifiers**

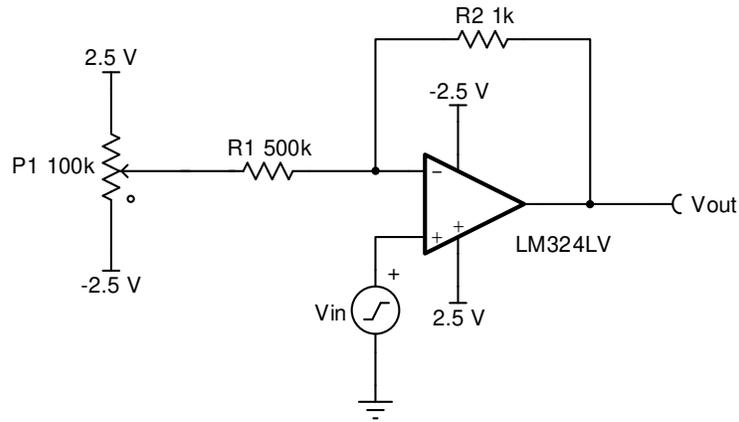Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$\text{Offset Range} = V_{\text{supply}} \left( \frac{R_2}{R_1} \right)$$

$$V_{\text{out}} \approx V_{\text{in}}$$

$$R_1 \gg R_2$$

**Figure 1-20. Offset Voltage Adjustment for Voltage Followers**

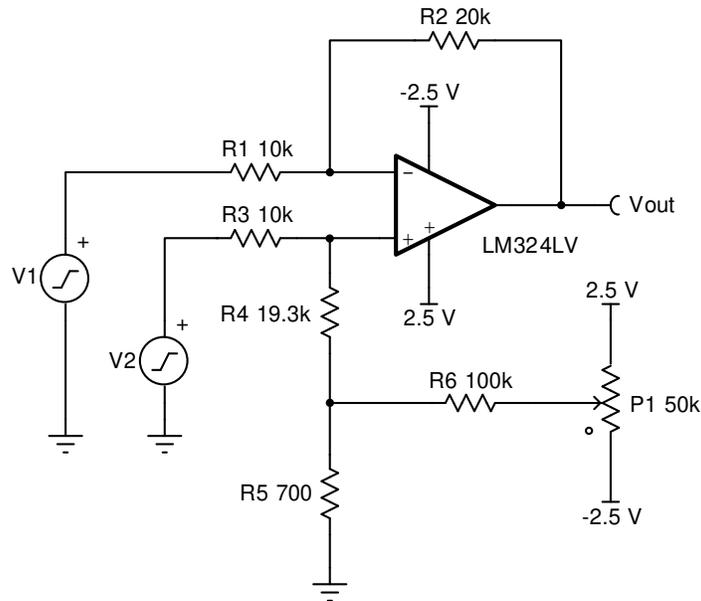Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_2 = R_4 + R_5$$

$$R_1 = R_3$$


$$\text{Offset Range} = V_{\text{supply}} \left( \frac{R_5}{R_5 + R_6} \right) \left( \frac{R_3}{R_3 + R_4} \right)$$

$$V_{\text{out}} = \left( \frac{R_2}{R_1} \right) (V_2 - V_1)$$

$$R_5 \ll \text{Offset Equivalent Resistance}$$

**Figure 1-21. Offset Voltage Adjustment for Difference Amplifiers**

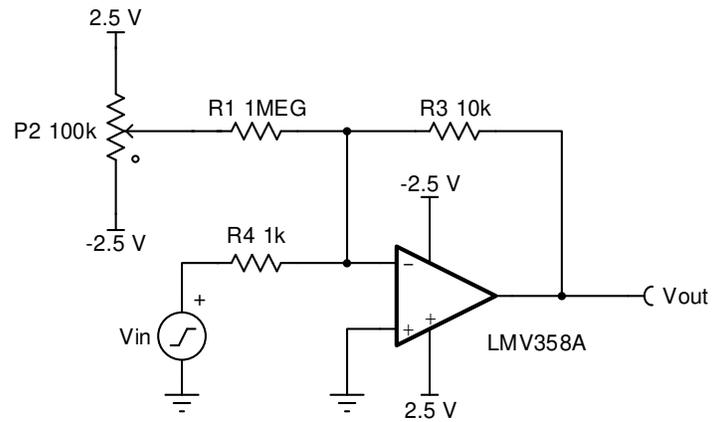Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_3 || R_4 \leq 10k\Omega$$


$$\text{Offset Range} = V_{\text{supply}} \left( \frac{R_3 || R_4}{R_1} \right)$$

$$V_{\text{out}} = \left( -\frac{R_3}{R_4} \right) V_{\text{in}}$$

**Figure 1-22. Offset Voltage Adjustment for Inverting Amplifiers With Source Resistance**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

## 2 Signal Generation

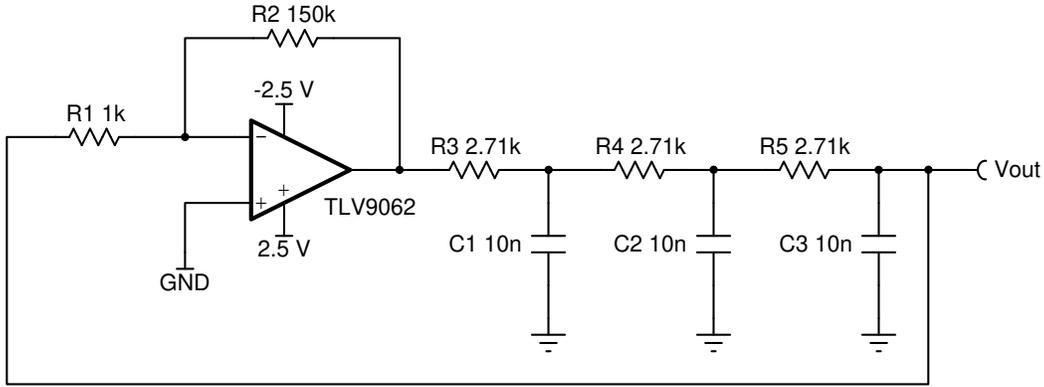


$$\frac{R_2}{R_1} \gg 8$$

Let  $R = R_3, R_4, R_5$  and  $C = C_1, C_2, C_3$

$$f_{oscillation} \approx \frac{\tan(60^\circ)}{2\pi RC}$$

**Figure 2-1. Sine Wave Generator With Low Component Count**

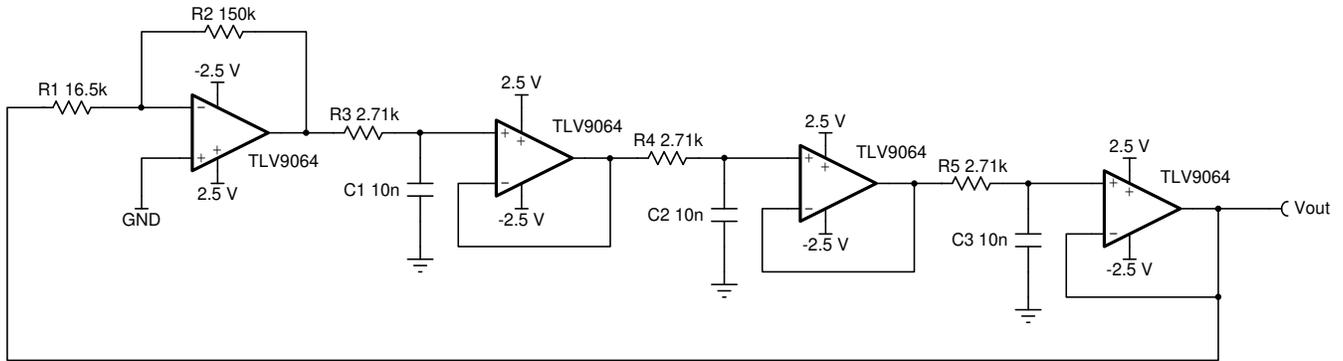For more information on this configuration, also known as a phase-shift oscillator, see [9] and [10]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$8 \leq \frac{R_2}{R_1} \leq 10$$

Let  $R = R_3, R_4, R_5$  and  $C = C_1, C_2, C_3$

$$f_{oscillation} = \frac{\tan(60^\circ)}{2\pi RC}$$


**Figure 2-2. Sine Wave Generator**

For more information on this configuration, also known as a buffered phase-shift oscillator, see [9] and [10]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

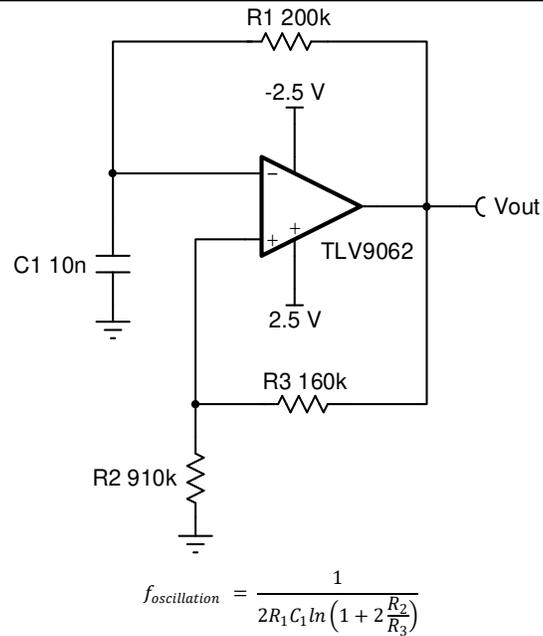


**Figure 2-3. Free-Running Multivibrator**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

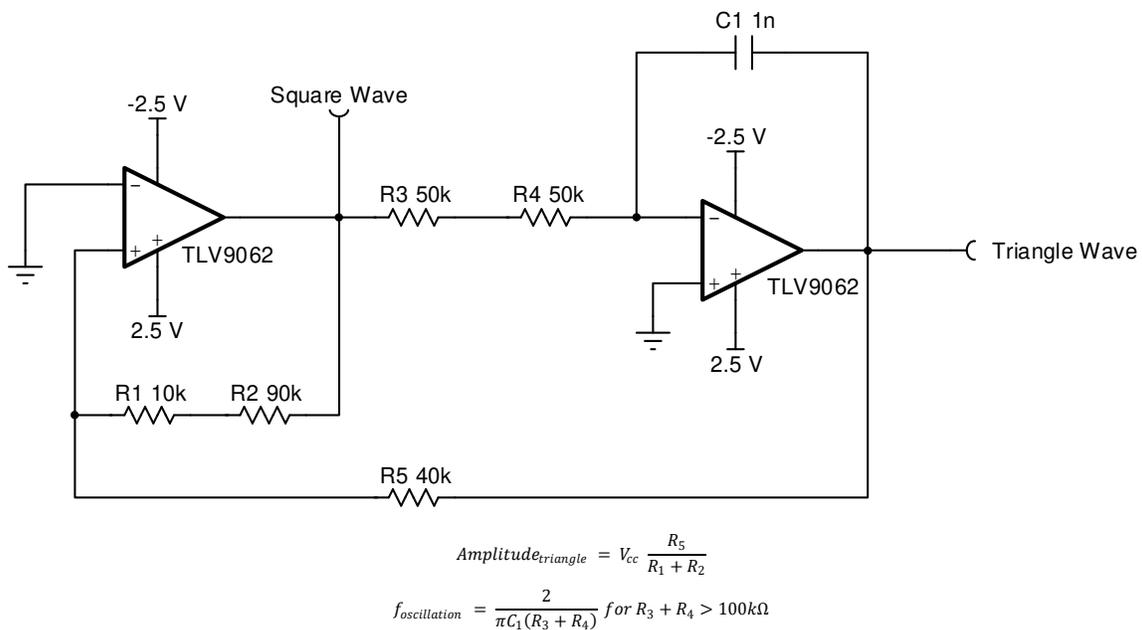

**Figure 2-4. Function Generator**

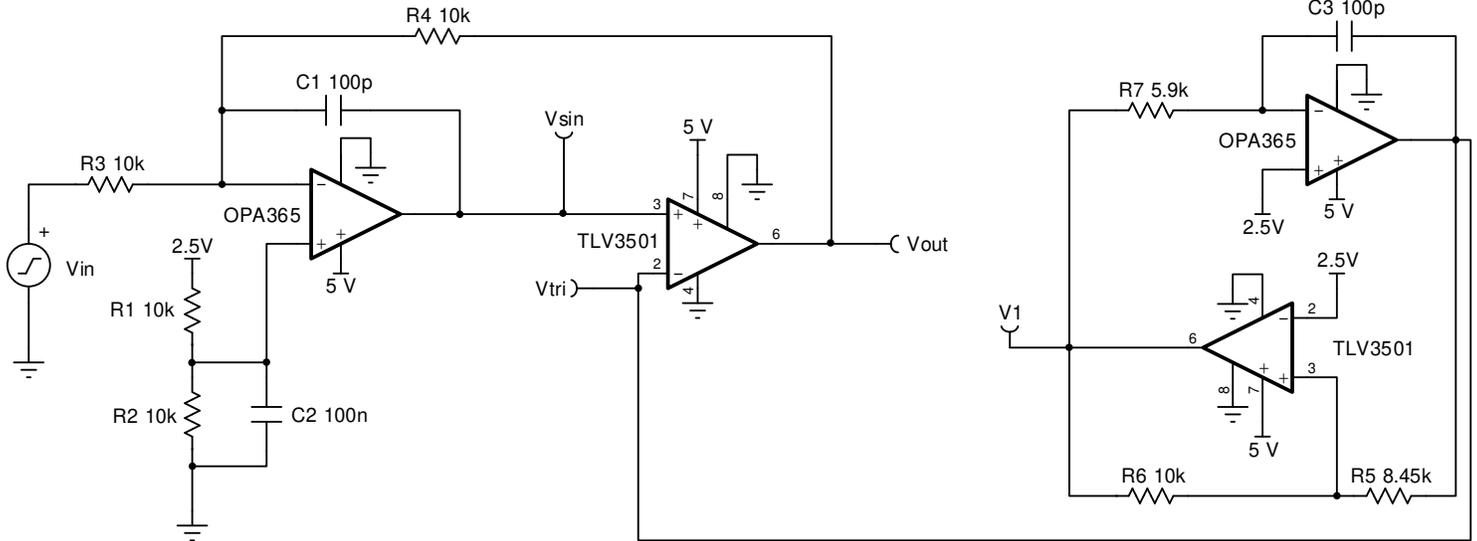See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_1 = R_2 = R_3 = R_4$$

$$V_{tri} > |V_i|$$

$$\frac{R_5}{R_6} = \frac{|V_{tri}|}{|V_1|} \text{ for } V_1 = V_{ref}$$


$$f_{oscillation} = \frac{R_6}{4 \times R_7 \times R_5 \times C_3}$$

$$C_1 > \frac{1}{2\pi \times R_4 \times f_{oscillation}}$$

$$C_2 = \frac{1}{2\pi \times f_{noise\ filter} \times (R_1 || R_2)}$$

**Figure 2-5. Pulse Width Modulator**

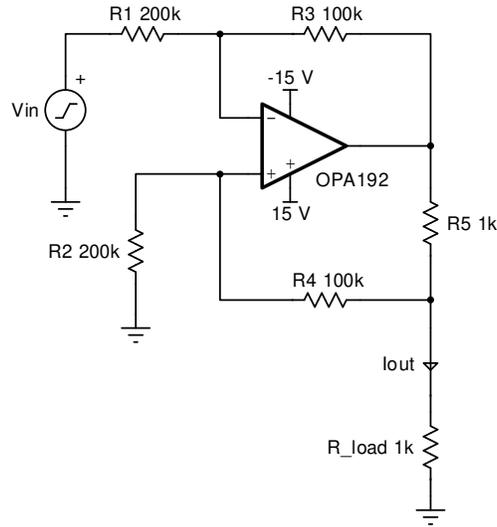See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = -\frac{R_3 V_{in}}{R_1 R_5}$$

$$R_3 = R_4 + R_5$$

$$R_1 = R_2$$

**Figure 2-6. Improved Howland Current Pump**

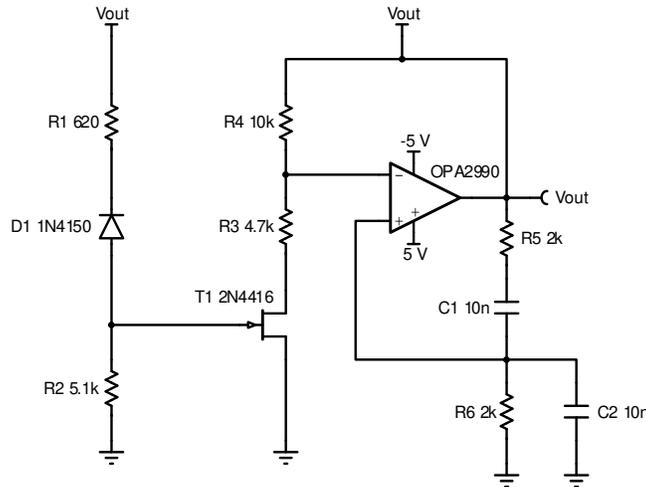For an in-depth dive into this configuration, see our [11]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$f_{oscillation} = \frac{1}{2\pi C_1 R_5}$$

$$\text{Set Gain} = 3.1$$


$$\text{Gain} = \frac{R_3 + R_4}{R_4}$$

$$R_5 = R_6$$

$$C_1 = C_2$$

**Figure 2-7. Wien Bridge Oscillator With Automatic Gain Control**

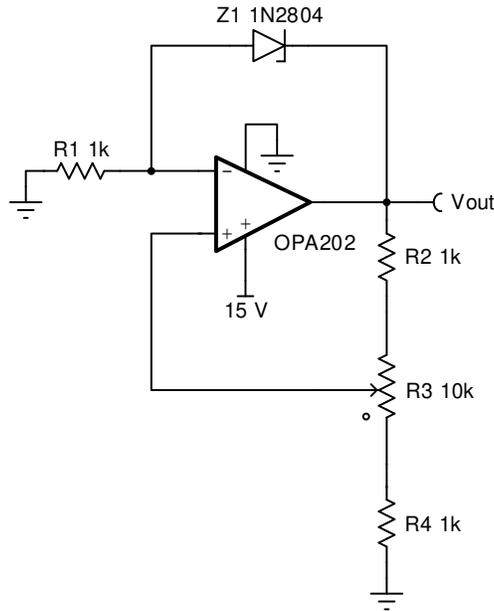Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$7.58V \leq V_{out} \leq 13.93V$$

$R_1$  controls  $V_{out,max}$

$R_2, R_4,$  &  $V_{zener}$  control  $V_{out,min}$

**Figure 2-8. Positive Output Voltage Reference**

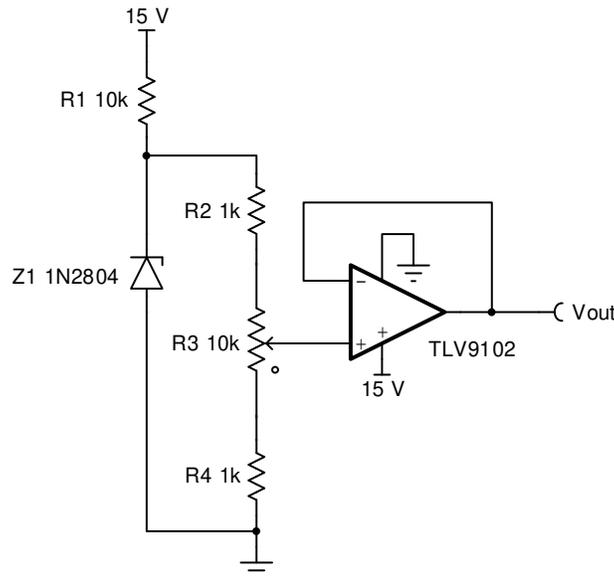See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$500mV \leq V_{out} \leq 5.5V$$

Decreasing  $R_2$  &  $R_4$  increases  $V_{out}$  range

$V_{zener}$  adjusts  $V_{out}$  range

**Figure 2-9. Buffered Positive Voltage Reference**

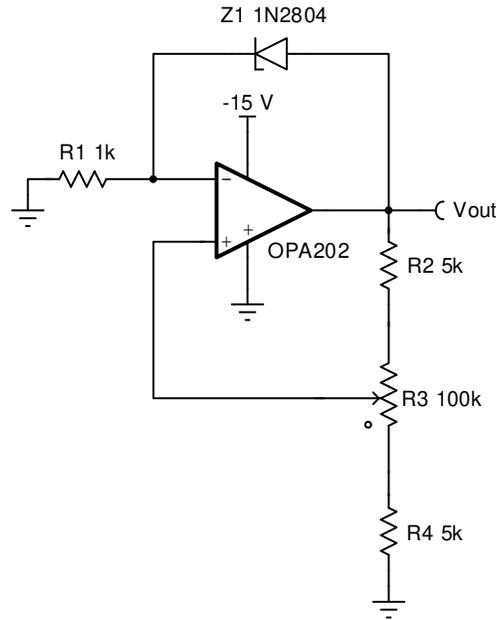See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$-13.9V \leq V_{out} \leq -7.6V$$

*Decreasing  $R_2$  and  $R_4$  increases  $V_{out}$  range*

*$V_{zener}$  adjusts  $V_{out}$  range*

**Figure 2-10. Negative Output Voltage Reference**

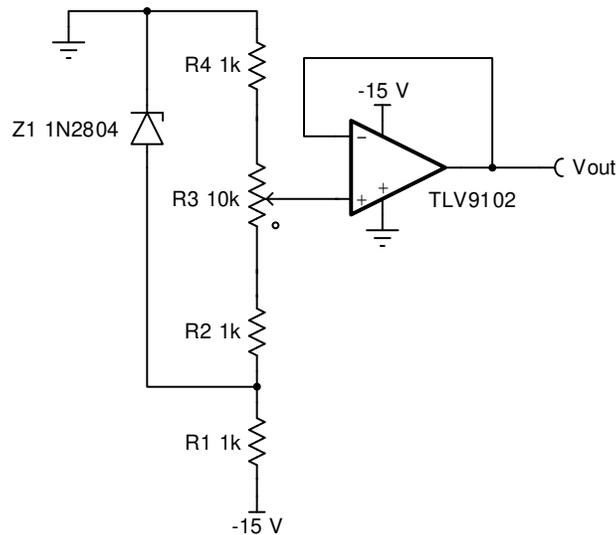See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$-5.5V \leq V_{out} \leq -500mV$$

*Decreasing  $R_2$  &  $R_4$  increases  $V_{out}$  range*

*$V_{zener}$  adjusts  $V_{out}$  range*

**Figure 2-11. Buffered Negative Voltage Reference**

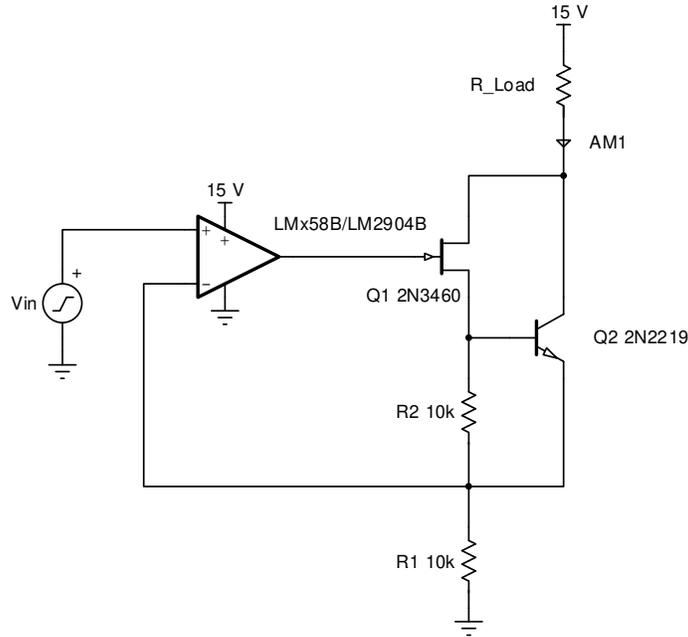See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_o = \frac{V_{in}}{R_1}$$

$$V_{in} \geq 0V$$

Ensure  $R_1 \gg R_{Load}$

**Figure 2-12. Current Sink**

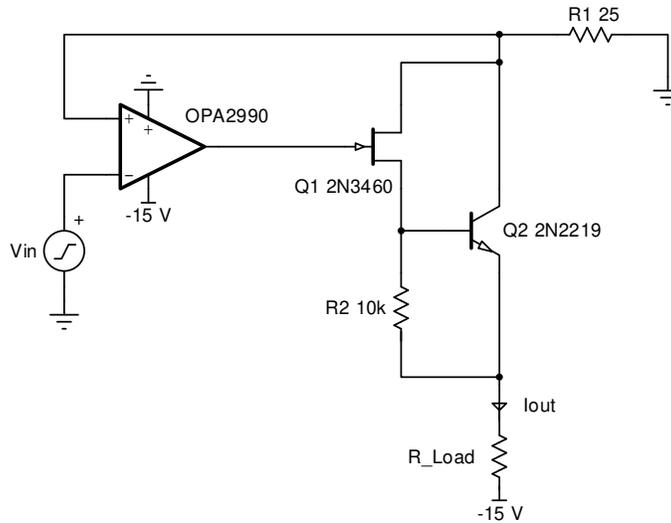See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = \frac{V_{out}}{R_1}$$

$$V_{in} < 0$$

**Figure 2-13. Current Source**

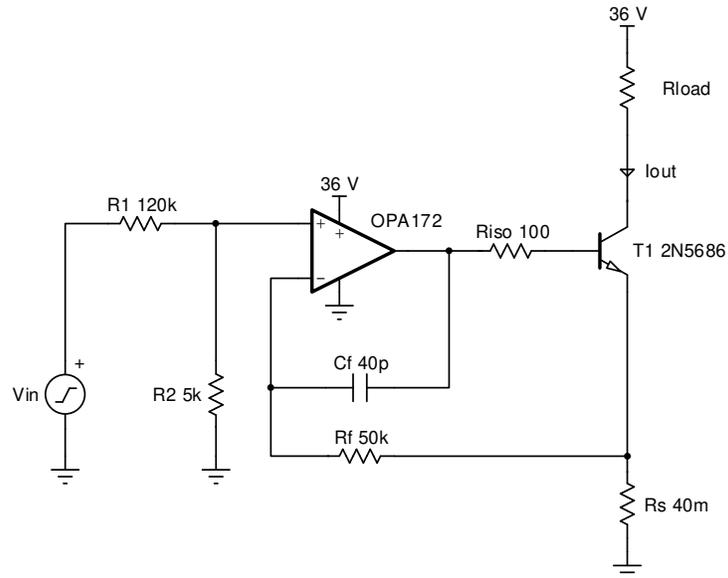See [2] for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = V_{in} \frac{R_2}{R_s(R_1 + R_2)}$$

$$R_s = \frac{V_{in,max}}{I_{out,max}}$$

**Figure 2-14. Voltage-to-Current Converter With BJT Output**

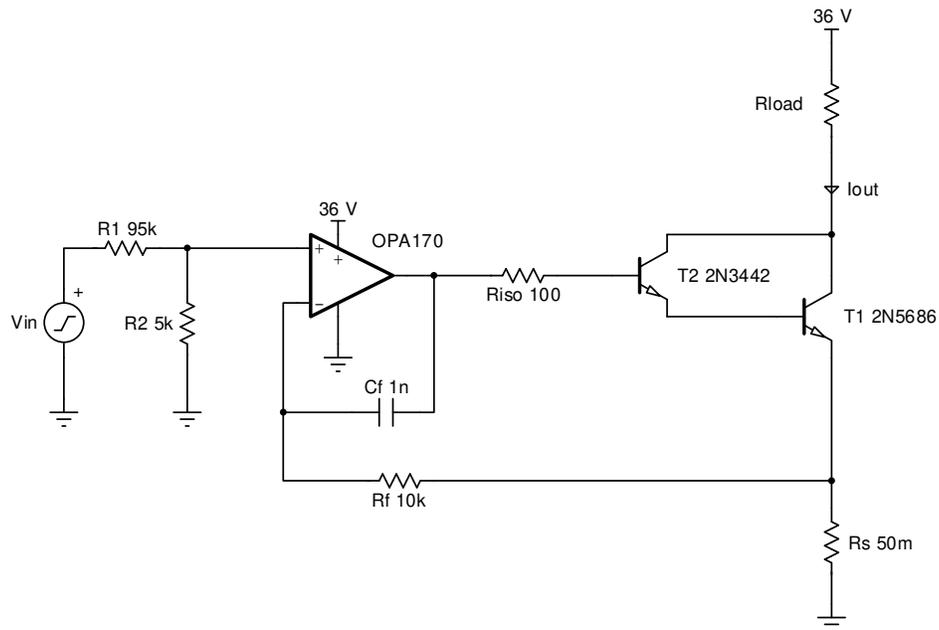Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = V_{in} \frac{R_2}{R_s(R_1 + R_2)}$$

$$R_s = \frac{V_{in,max}}{I_{out,max}}$$

**Figure 2-15. Voltage-to-Current Converter With Darlington Pair Output**

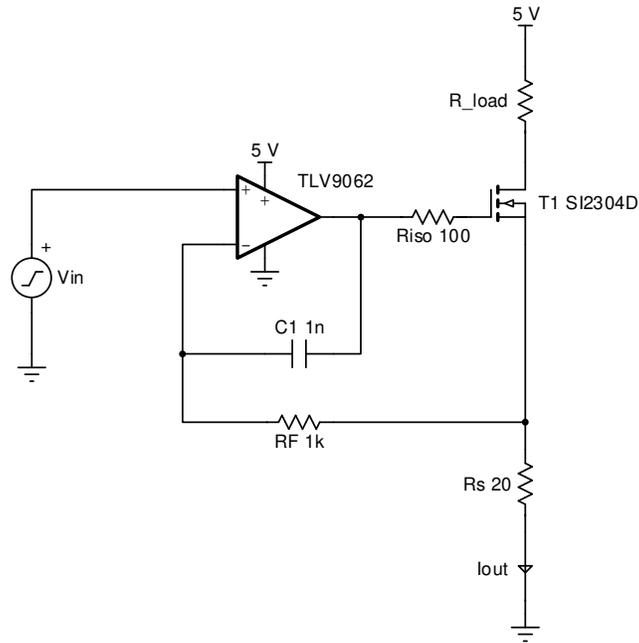Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$I_{out} = \frac{V_{in}}{R_s}$$

$$R_s = \frac{V_{in,max}}{I_{out,max}}$$

**Figure 2-16. Voltage-to-Current Converter With MOSFET Output**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

### 3 Signal Processing

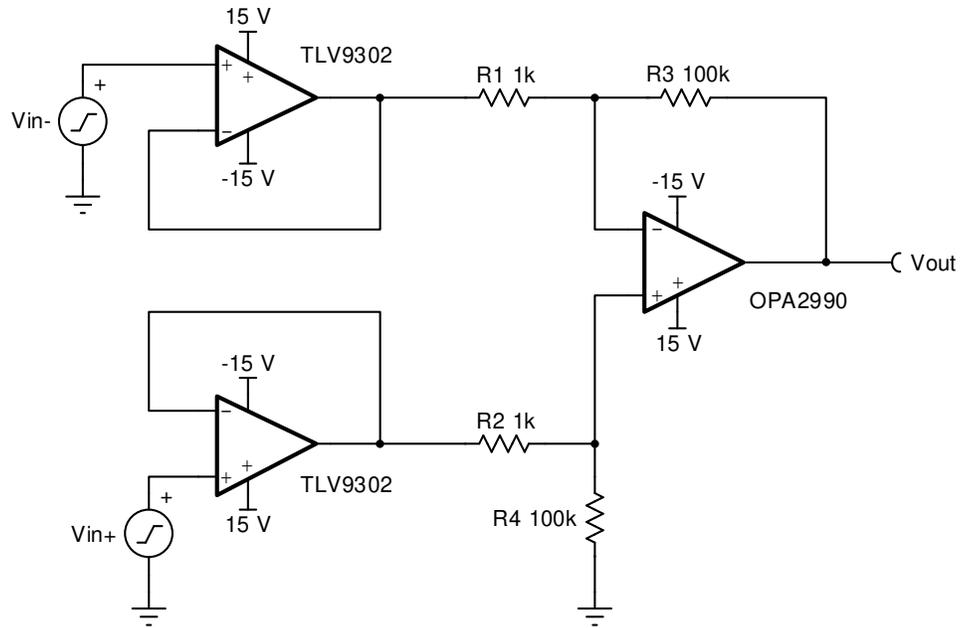


$$V_{out} = \frac{R_3}{R_1} (V_{in+} - V_{in-})$$

$$\frac{R_3}{R_1} = \frac{R_4}{R_2}$$

**Figure 3-1. Instrumentation Amplifier**

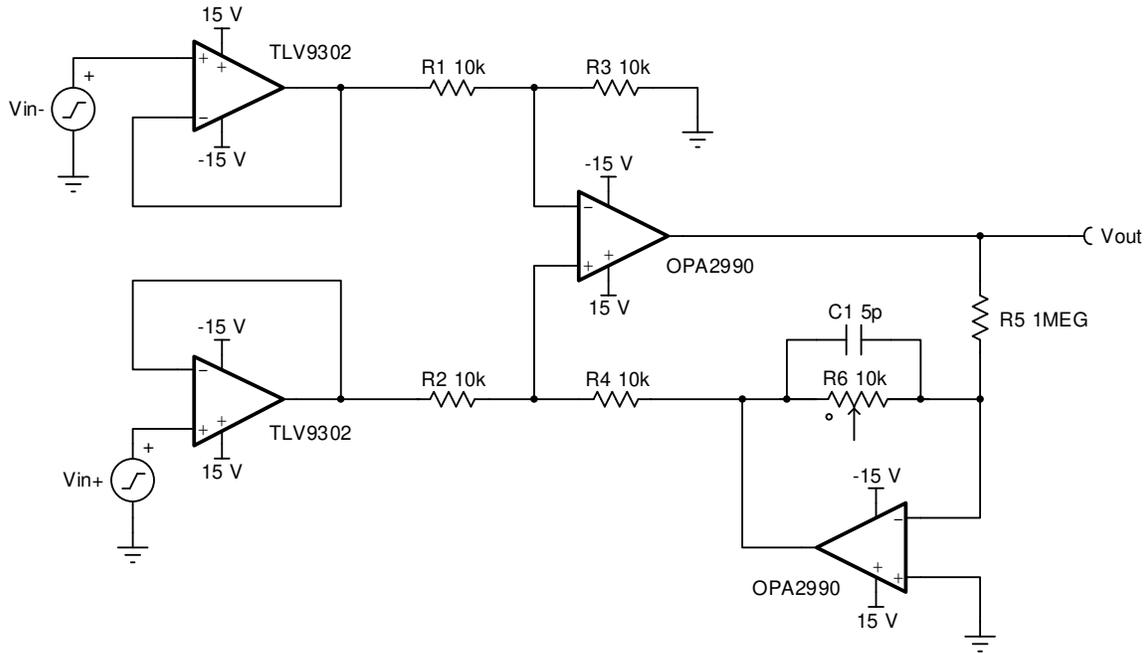Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \frac{10^{-4} R_6 R_3}{R_1} (V_{in+} - V_{in-})$$

$$\frac{R_3}{R_1} = \frac{R_4}{R_2}$$

Figure 3-2. Variable Gain Instrumentation Amplifier

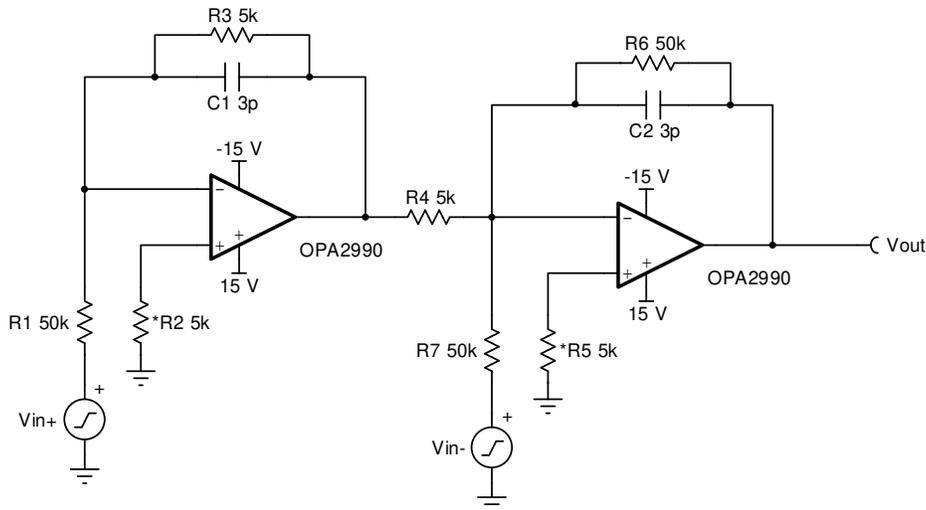Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_2 = R_3 = R_4 = R_5$$


$$R_1 = R_6 = 10R_3$$

$$V_{out} = \left(\frac{R_7}{R_6}\right) V_{in}$$

\* R<sub>2</sub> and R<sub>5</sub> Optional for Input Bias Current Cancellation

Figure 3-3. Instrumentation Amplifier With ±100-V Common Mode Range

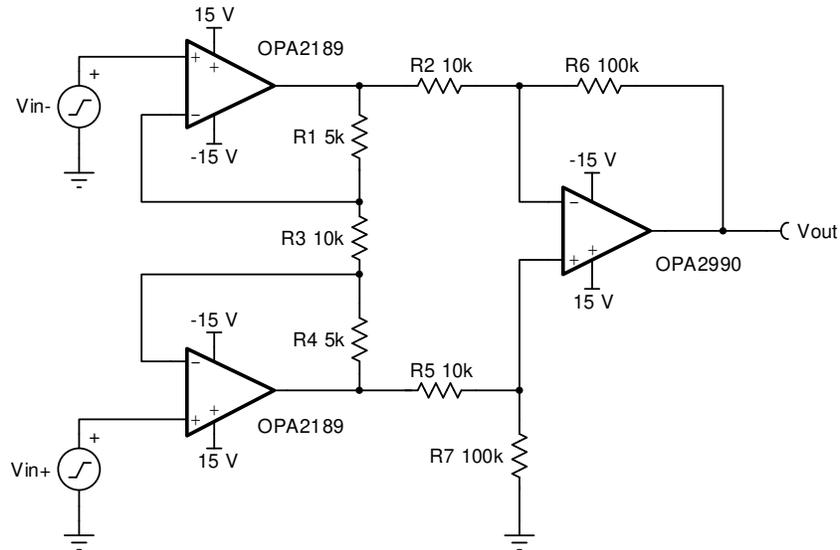
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$\begin{aligned}
 R_1 &= R_4 \\
 R_2 &= R_5 \\
 R_6 &= R_7 \\
 V_{out} &= \frac{R_6}{R_2} \left( 1 + \frac{2R_1}{R_3} \right) V_{in}
 \end{aligned}$$

**Figure 3-4. Instrumentation Amplifier With  $\pm 10$ -V Common Mode Range**

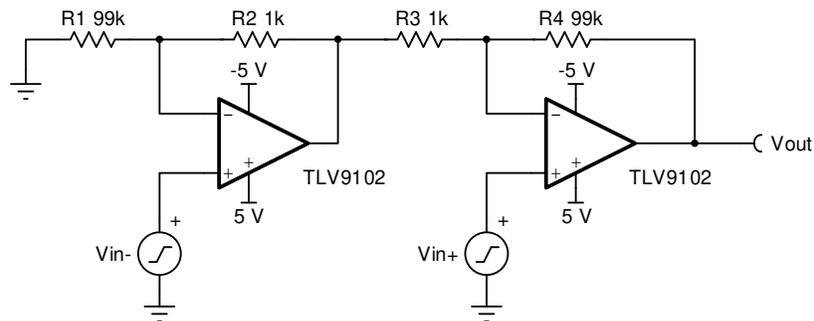
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$\begin{aligned}
 R_1 &= R_4 \text{ \& } R_2 = R_3 \\
 V_{out} &= \left( 1 + \frac{R_1}{R_2} \right) V_{in}
 \end{aligned}$$


**Figure 3-5. High Input Impedance Instrumentation Amplifier**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

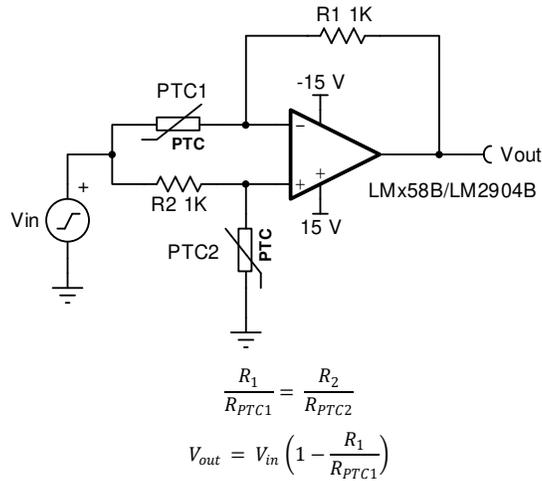


**Figure 3-6. Bridge Amplifier With Temperature Sensitivity**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

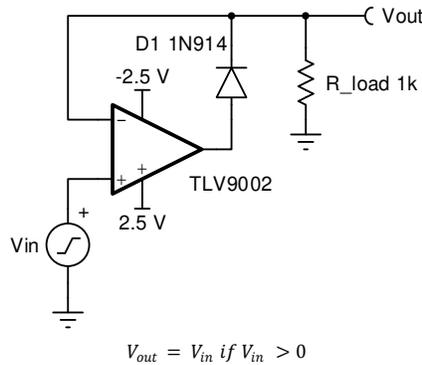


**Figure 3-7. Precision Diode**

For more information on this configuration, see [12]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

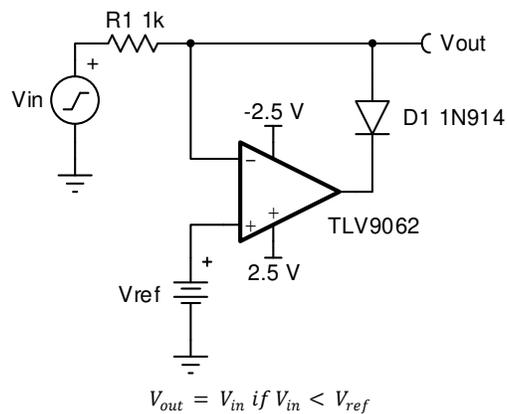

**Figure 3-8. Precision Clamp**

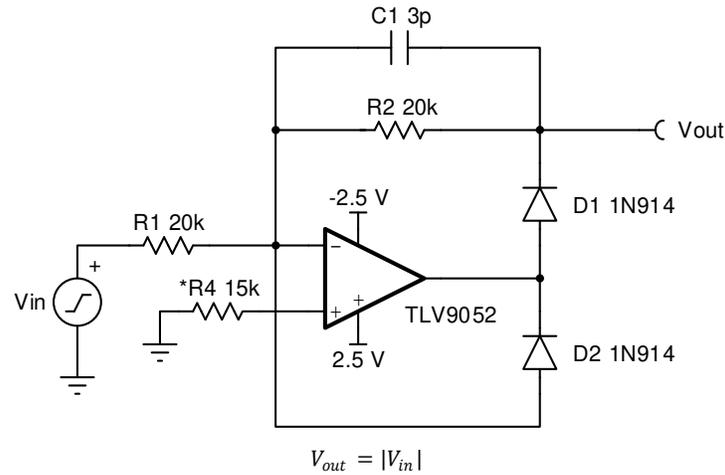For more information on this configuration, see [12]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = |V_{in}|$$

\*  $R_4$  Optional for Input Bias Current Cancellation

**Figure 3-9. Fast Half Wave Rectifier**

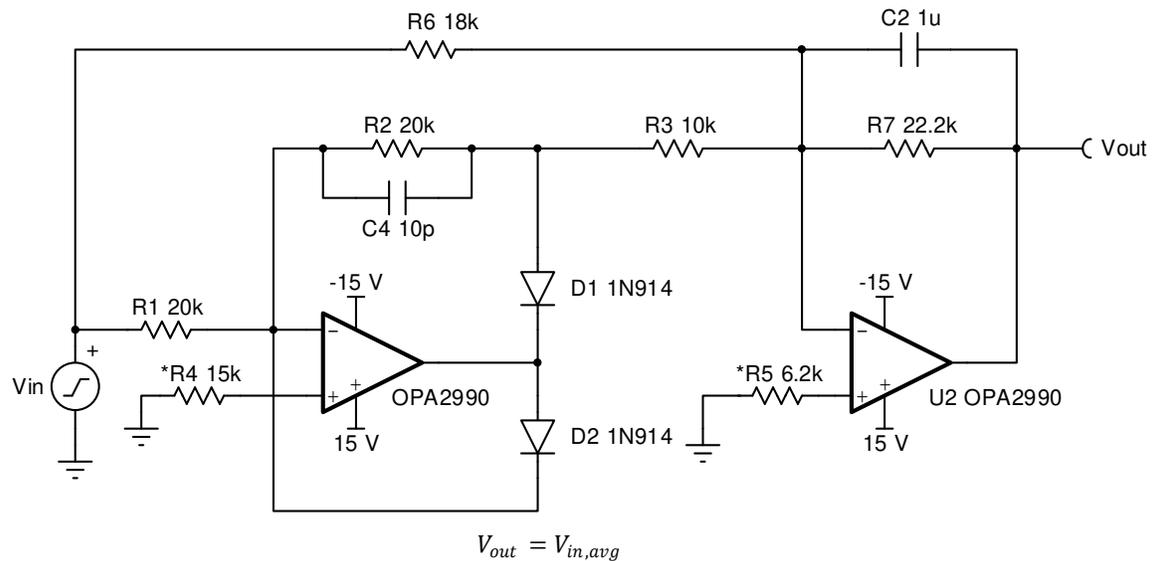For more information on this configuration, see [12]. See [Analog engineer's circuit cookbook: amplifiers](#) for more information. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = V_{in,avg}$$


$$0 < V_{in} < V_{cc} - V_{D1}$$

Ensure Op Amps Remain in Linear Range

\*  $R_4$  and  $R_5$  Optional for Input Bias Current Cancellation

**Figure 3-10. AC to DC Converter**

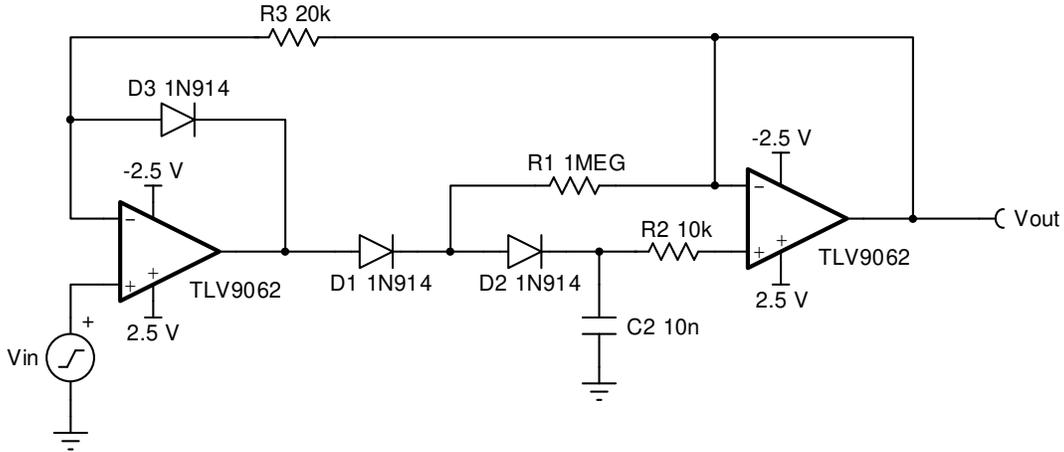
For more information on this configuration, see [12]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = V_{peak}$$

**Figure 3-11. Peak Detector**

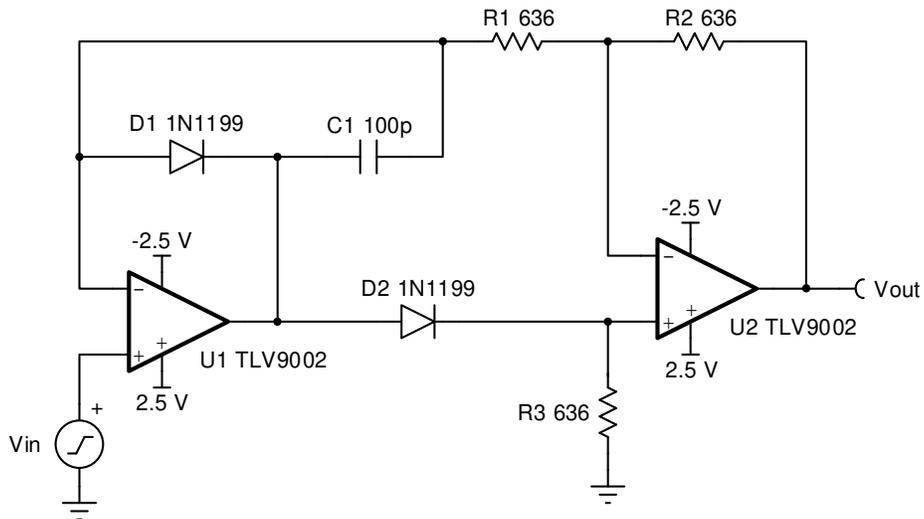Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = |V_{in}|$$

$$R_2 = R_1$$

$$\frac{GBW_{U2}}{4} = \frac{1}{2\pi R_1 C_1}$$

**Figure 3-12. Absolute Value Amplifier**

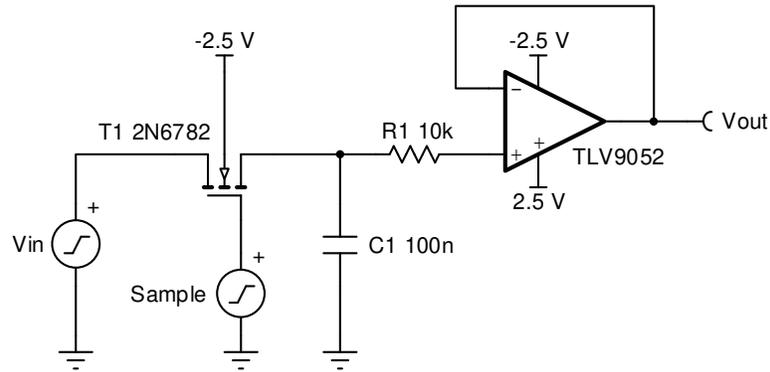For more information on this circuit, see [13]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$t_{\text{sample}} \propto C_1$$

$$\text{Droop Rate} \propto \frac{1}{C_1}$$

**Figure 3-13. Sample and Hold I**

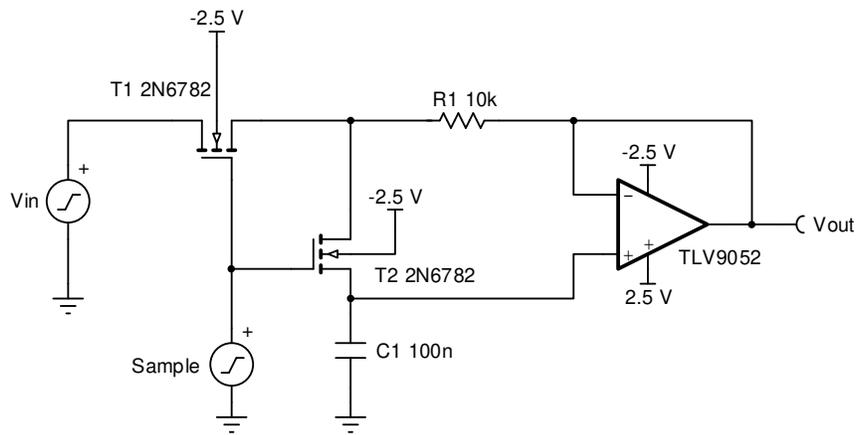For more information on this circuit, see [14]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$t_{\text{sample}} \propto C_1$$

$$\text{Droop Rate} \propto \frac{1}{C_1}$$

**Figure 3-14. Sample and Hold II**

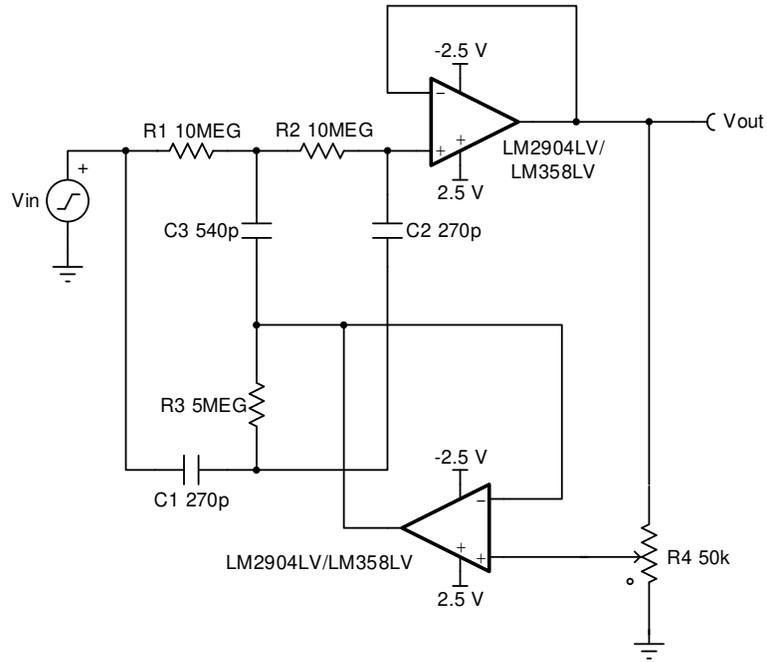For more information on this circuit, see [14]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$f_o = \frac{1}{2\pi R_1 C_1}$$

$$R_1 = R_2 = 2R_3$$


$$2C_1 = 2C_2 = C_3$$

$$0.25 < Q_{network} < 10$$

*Increasing Potentiometer Setting Increases  $Q_{network}$*


**Figure 3-15. Adjustable Q Notch Filter**

For more information on this configuration, see [15] and [16]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

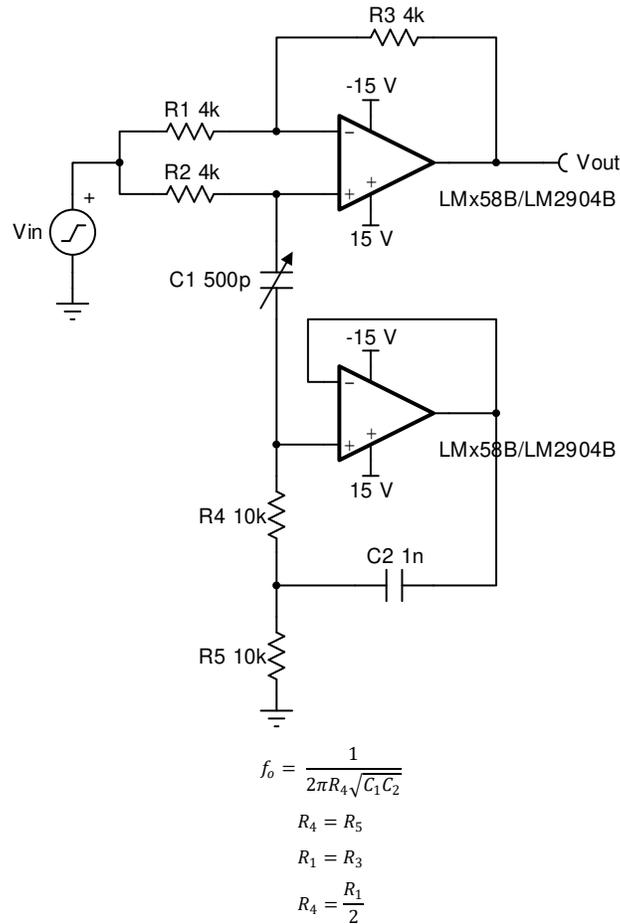


**Figure 3-16. Easily Tuned Notch Filter**

For more information on this configuration, see [15] and [16]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

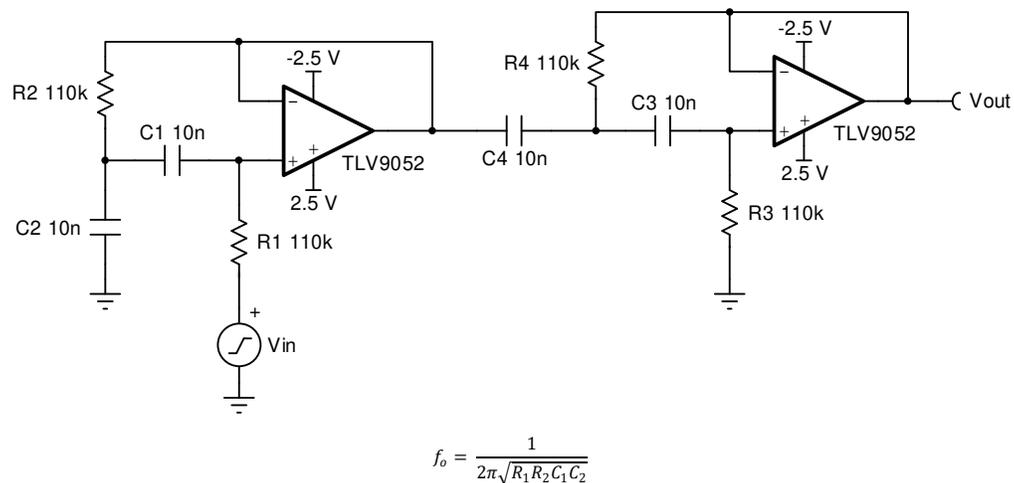


**Figure 3-17. Sallen-Key Two-Stage Bandpass Filter**

For more information on this configuration, see [17]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

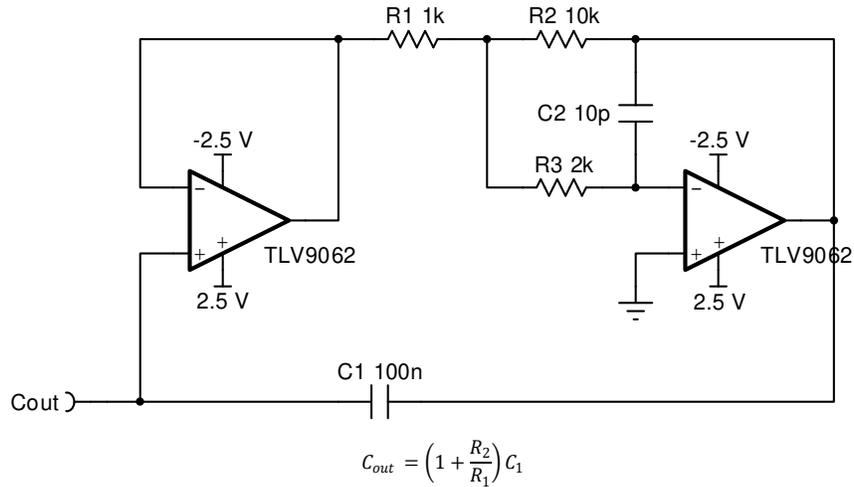


**Figure 3-18. Two-Stage Capacitance Multiplier**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).

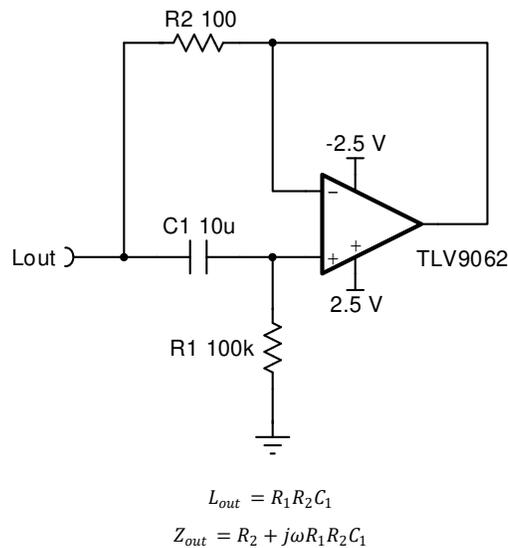

**Figure 3-19. Simulated Inductor**

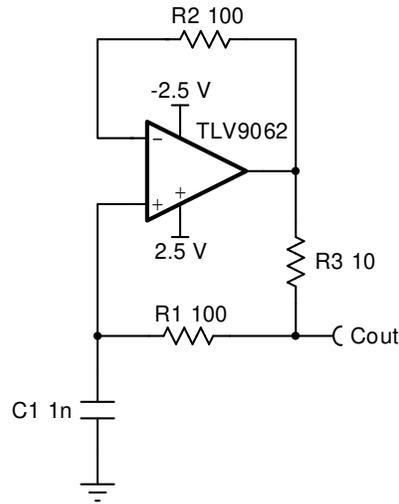For more information on this configuration, see [19]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$C_{out} \approx \frac{R_1}{R_3} C_1$$

$$C_1 \geq 100 \times C_{in \text{ amplifier}}$$

$$R_{source} \gg R_3$$

**Figure 3-20. Capacitance Multiplier**

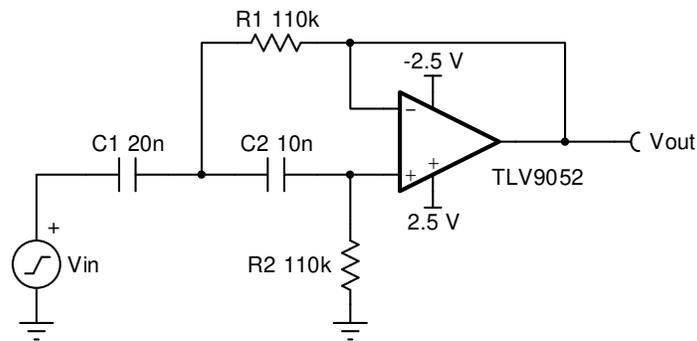Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_2 = mR_1$$

$$C_2 = nC_1$$


$$f_c = \frac{1}{2\pi RC\sqrt{mn}}$$

$$Q = \frac{\sqrt{mn}}{m+1}$$

Choose  $m$  and  $n$  for desired  $f_c$  and  $Q$

**Figure 3-21. High Pass Sallen-Key Active Filter**

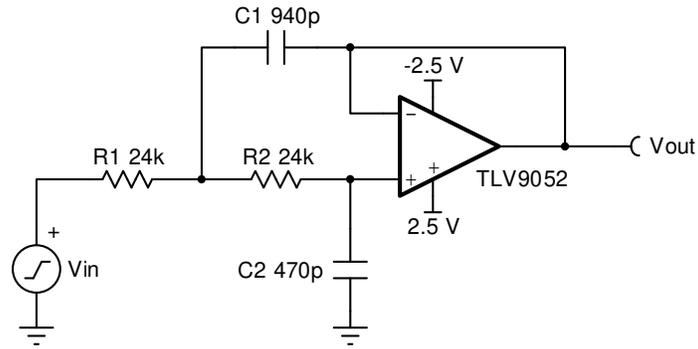For more information on this configuration, see [17]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$R_1 = mR_2$$

$$C_1 = nC_2$$


$$f_c = \frac{1}{2\pi RC\sqrt{mn}}$$

$$Q = \frac{\sqrt{mn}}{m + 1}$$

Choose  $m$  and  $n$  for desired  $f_c$  and  $Q$

**Figure 3-22. Low Pass Sallen-Key Active Filter**

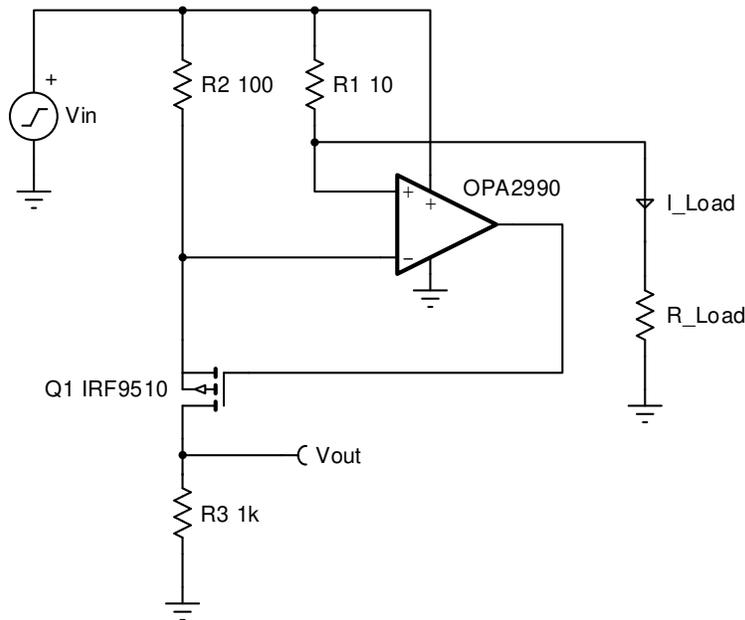
For more information on this configuration, see [17] and [18]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = \frac{R_1 R_3}{R_2} I_L$$

**Figure 3-23. Current Monitor**

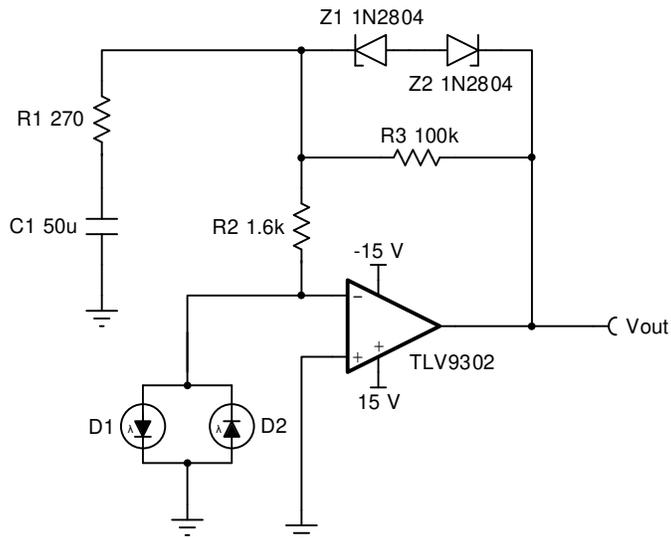Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = \frac{0.1V}{\mu A} \text{ from } D1, D2$$

Linear Range through 60μA

**Figure 3-24. Saturating Servo Preamplifier With Rate Feedback**

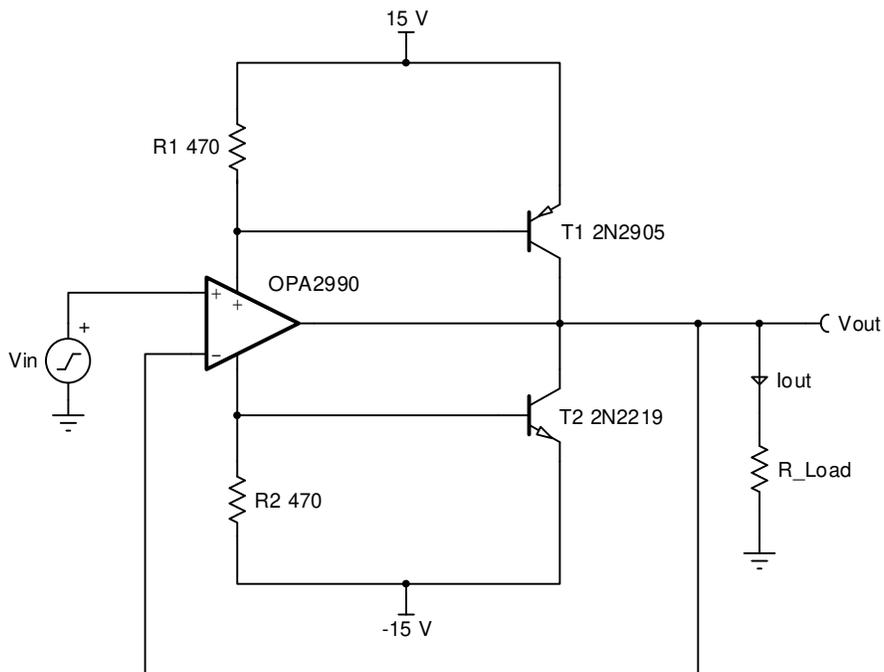For more information on modeling photodiodes, see [8]. More information on this configuration can be found in [20]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = V_{in}$$

$Q_1$  and  $Q_2$  Increase  $I_{out}$

**Figure 3-25. Power Booster**

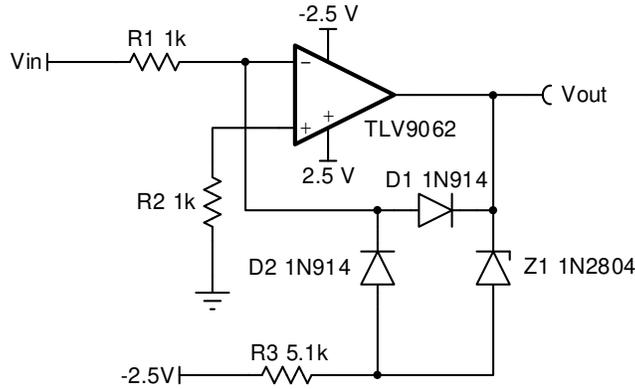
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



*Time to Detect Falling, Zero Crossing Reduced by ~65%  
 Versus Using Amplifier as Comparator*

**Figure 3-26. Fast Zero Crossing Detector**

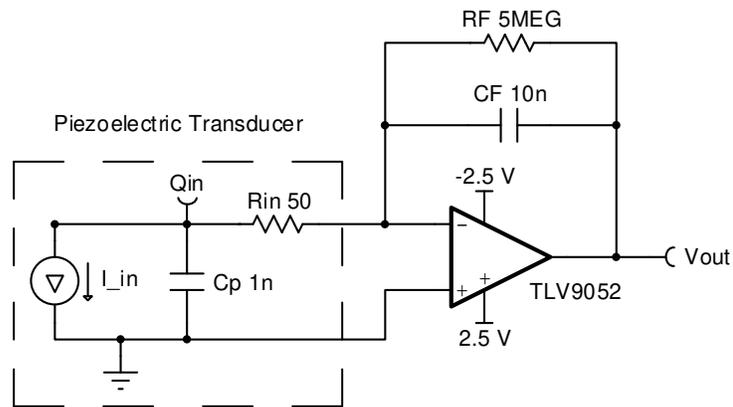Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$Gain = \frac{V_{out}}{Q_{in}} = \frac{1}{C_F}$$

$$f_{LPF} = \frac{1}{2\pi R_F C_F}$$

$$f_{HPF} = \frac{1}{2\pi R_{in} C_{in}}$$

**Figure 3-27. Amplifier for Piezoelectric Transducer**

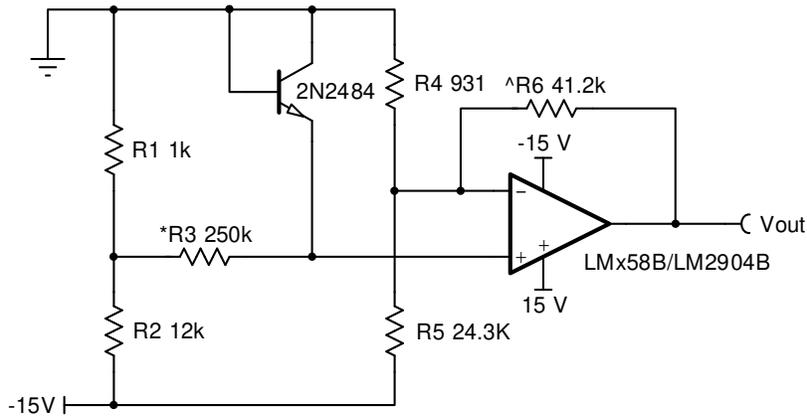For more information on this configuration, see [21] and [22]. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).




$$V_{out} = 103.9mV/^{\circ}C - 383mV$$

\* Value Can Be Changed for 0V at 0°C

^ Value Can Be Changed for 100mV/°C

**Figure 3-28. Temperature Probe**

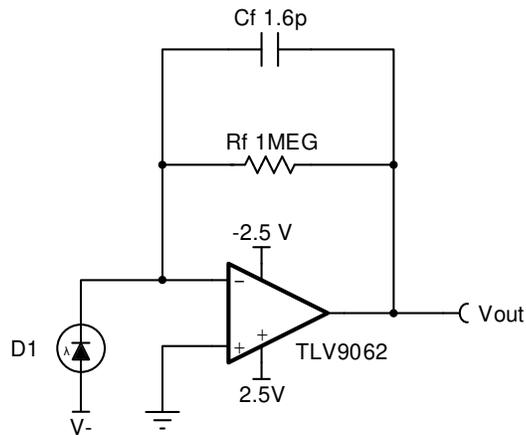
Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = R_f I_D$$

**Figure 3-29. Photodiode Amplifier I**

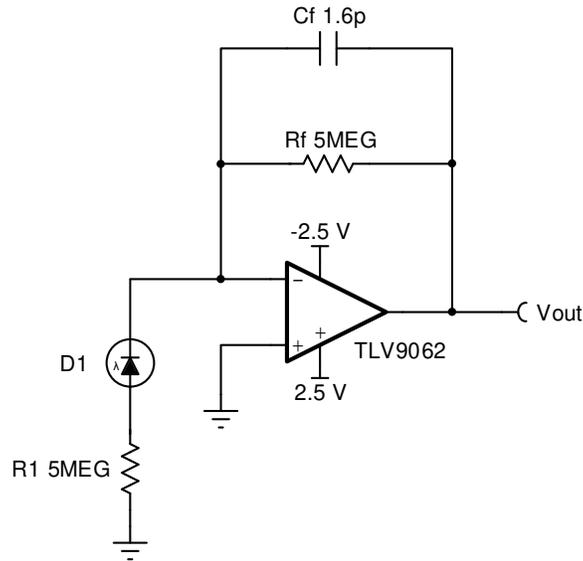
For more information on modeling photodiodes, see [8]. See [Analog engineer's circuit cookbook: amplifiers](#) or [2] for more information on this circuit. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = 5V/\mu A \times \frac{R_f}{R_1}$$

**Figure 3-30. Photodiode Amplifier II**

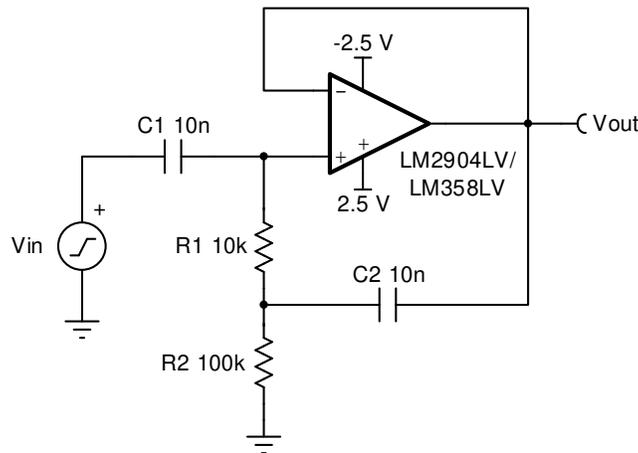For more information on modeling photodiodes, see [8]. See [Analog engineer's circuit cookbook: amplifiers](#) for more information on this circuit. Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



$$V_{out} = \frac{(R_1 + R_2)C_1s + C_1C_2R_1R_2s^2}{1 + (R_1 + R_2)C_1s + C_1C_2R_1R_2s^2} V_{in}$$

**Figure 3-31. High Input Impedance AC Follower**

Simulate this design by downloading [TINA-TI](#) and the [schematic](#).



## 4 References

1. To learn more about the design of many of these and other amplifier configurations, consult our [Analog engineer's circuit cookbook on amplifiers](#).
2. Alternatively, more information on several of these circuits can be found in our app note entitled, [AN-20 an applications guide for op amps](#).
3. To learn more about the characteristics of amplifiers, common techniques used in amplifier circuit design, and a variety of other amplifier topics, consult our [Texas Instruments Precision Labs video series on amplifiers](#).
4. For specific questions regarding your design, [reach out to our engineers via e2e](#), our online forum.
5. For a handy reference guide for your analog designs, check out the [Analog Engineer's Pocket Reference Guide](#) available for free in pdf form.
6. Use our [Analog Engineer's Calculator](#) to help crunch design equations.
7. Check out our [Amplifier's Product Page](#) to quickly sort through our products and find the amplifier(s) that best fit your needs.
8. For more information on modeling photodiodes including the model used in this design, see the [1 MHz, single-supply, photodiode amplifier reference design](#).
9. For more information on sine-wave oscillators, check out TI's app note on the [Sine-wave oscillator](#).
10. Alternatively, see our note on the [Design of op amp sine wave generators](#).
11. For more on the Howland Current Pump, see [AN-1515 a comprehensive study of the Howland current pump](#).
12. For more information on the Precision Diode, Precision Clamp, Half Wave Rectifier, and AC to DC Converter circuits, see our [LB-8 precision AC/DC converters](#) application note.
13. More information on the Absolute Value Amplifier can be found in our app note on [Precision absolute value circuits](#).
14. To learn more about Sample-and-Hold configurations, see our application note on the [Specifications and architectures of sample-and-hold amplifiers](#).
15. For more information on Q Notch Filters, see our [LB-5 high Q Notch filter](#) on the subject.
16. Further analysis of notch filters can be found in our app note on [High-speed notch filters](#).
17. For more information on Sallen-Key filter design, see our [Analysis of the Sallen-Key architecture](#) application note on the subject.
18. For more information on Low Pass Sallen-Key filter design, see our [Active low-pass filter design](#) application note.
19. More information on simulated inductors can be found in our application note entitled, [An audio circuit collection, part 3](#).
20. More information on a variety of circuits can be found in our [AN-4 monolithic op amp—the universal linear component](#) application note.
21. To learn more about the theory behind, design of, and simulation of piezoelectric transducers and their amplifiers, see this [Signal conditioning piezoelectric sensors](#) application note.
22. Additional information on piezoelectric transducers can be found in our analog applications journal entry, [Signal conditioning for piezoelectric sensors](#), on the subject.
23. For more information on the LM324/LM358 device family and how to properly connect unused inputs, see [Application design guidelines for LM324/LM358 devices](#).

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Revision C (March 2019) to Revision D (October 2020)</b>	<b>Page</b>
• Changed TINA-TI hyperlinks throughout document.....	3
• Changed Figure 2-3 Free-Running Multivibrator equation.....	15

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2020, Texas Instruments Incorporated