

# LMH6643

*Lower System Cost Solution for Transmitting Video*



Literature Number: SNOA810

# Application Brief

## Lower System Cost Solution for Transmitting Video

Application Brief 116

John Bittner

There are many types of video systems that require the source of a video signal to be located several hundred feet from a video display. A good example of this is a video surveillance system where the camera and display are located at opposite ends of a building. Traditionally, this type of closed-circuit video system would use coaxial cable to transmit the camera's video signal to the display. However, in many cases it would be better to transmit this signal on twisted-pair wire, which is smaller, lighter, and costs 80% less than coaxial cable.

Figure 1 is the block diagram of a system that transmits NTSC video on twisted-pair wire. This system was designed and tested to transmit video on 1,000 feet of inexpensive 24-gauge wire (CAT-3). Even though the signal is transmitted on 1,000 feet of wire, this system provides good quality color video at the display. Both the video driver and receiver use the LMH6643 dual op amp, which has the necessary high-speed AC characteristics for this application.

Advertisement

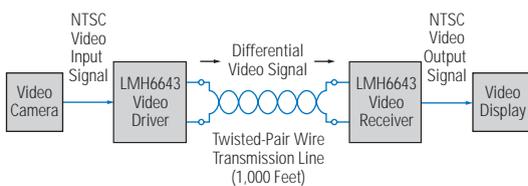


Figure 1: Block Diagram of Twisted-Pair Video System

A detailed schematic of the video driver is shown in Figure 2. It is a simple, low cost circuit that converts the single-ended input signal from a camera into a differential signal that drives the twisted-pair line. The input receives an NTSC composite video signal with 1 V<sub>pp</sub> amplitude, and the output drives the twisted-pair with a 2 V<sub>pp</sub> differential signal. A 50Ω source resistor is in series with the outputs of both op amps, matching the video driver output resistance to the twisted-pair characteristic impedance. The LMH6643 has a typical gain-bandwidth of 130 MHz, slew rate of 130 V/μs, differential gain of 0.01%, and differential phase of 0.01 degrees. These specifications are more than adequate for transmitting consumer grade video. In addition, the LMH6643 can supply a maximum output current of ±75 mA, so it can easily drive the 100Ω impedance of the twisted-pair line.

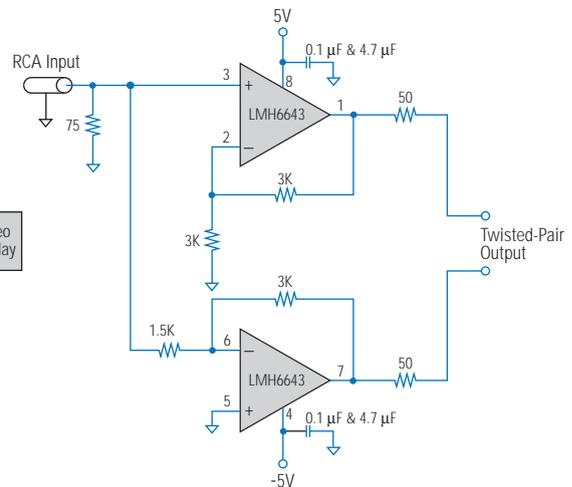


Figure 2: Twisted-Pair Video Driver

In the video receiver circuit of *Figure 3*, the differential input signal from the twisted-pair is converted into a  $1 V_{pp}$  single-ended output signal. Op amp 1 performs the differential to single-ended conversion, and op amp 2 compensates for attenuation of the video signal due to the 1,000 feet of twisted-pair wire. In the circuit of op amp 2, R2 is adjusted so that the overall gain of the system is unity (gain of the last op amp is greater than one in order to compensate for signal loss in the twisted-pair). C1 and R1 provide a zero-pole function that compensates for attenuation of higher frequency signals in the twisted-pair. The proper values for R1, C1, and R2 can be set by transmitting a  $1 V_{pp}$  square wave with a frequency of about 300 kHz, and adjusting these components for an optimized square wave at the output. This can be done with the following procedure: first, adjust R2 so that the square wave at the receiver output has an amplitude of  $1 V_{pp}$  (with the output driving a  $75\Omega$  load). Next, set C1 and R1 to optimize the risetime/falltime and damping of this square wave. In the demonstration circuit that transmits video on 1,000 feet of wire, R1 = 3.9K, C1 = 68 pF, and R2 = 3.6K.

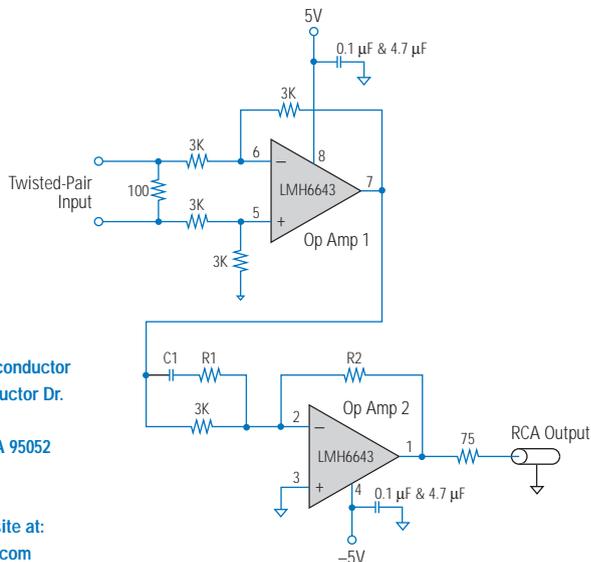


Figure 3: Twisted-Pair Video Receiver

Like the video driver, the receiver also consists of a simple and low-cost circuit. As a result, overall system cost of the twisted-pair wire, video driver and receiver is probably one of the lowest cost solutions for transmitting video on a closed-circuit system.

*Figure 4* shows the response of this system when transmitting a square wave. Trace 1 is the input signal and trace 2 is the output. The transitions of the output signal have rise and fall times of 160 ns with about 5% of overshoot. Note that 1,000 feet of twisted-pair wire delays the input signal by 1.4  $\mu$ s. Differential gain and phase of the system was measured with an HP3577A Network Analyzer. A  $0.55 V_{pp}$  sine wave test signal was applied to the input, and the gain and phase were measured at 3.58 MHz (NTSC reference frequency). When the DC offset of the test signal changed from 0 to 1V, the gain changed  $-0.028$  dB (differential gain), and phase changed 0.23 degrees (differential phase).

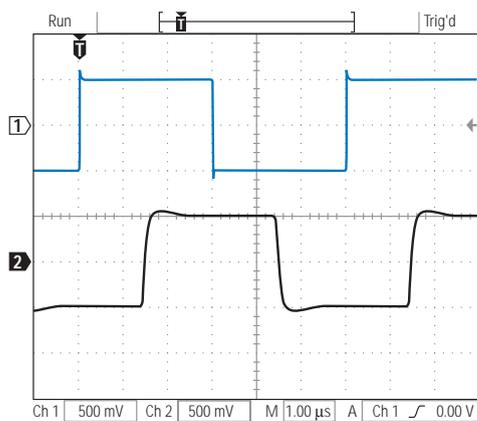


Figure 4: System Square Wave Response  
Ch1: Input, Ch2: Output

National Semiconductor  
2900 Semiconductor Dr.  
PO Box 58090  
Santa Clara, CA 95052  
1-800-272-9959

Visit our Web site at:  
[www.national.com](http://www.national.com)

For more information,  
send email to:  
[newfeedback@nsc.com](mailto:newfeedback@nsc.com)

#### Additional Information

[www.national.com/pf/LM/LMH6643.html](http://www.national.com/pf/LM/LMH6643.html)  
[amplifiers.national.com](http://amplifiers.national.com)

Visit **The National Edge**, our online technical journal for an archive of Application Briefs and other interesting information.  
[edge.national.com](http://edge.national.com)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated