

**LMV831,LMV832,LMV834,LMV851,LMV852,
LMV854,LMV861,LMV862**

EMI-Hardened Operational Amplifiers for Robust Circuit Design



Literature Number: SNOA817

As the number of electronic devices in the world continues to increase, the issue of Electronic Interference (EMI) between these devices becomes a greater challenge.

In response to the growing need for ICs that are resistant to electromagnetic waves, National has developed several op amp families that are hardened to EMI. The LMV851/52/54 low-power CMOS op amps have 8 MHz gain bandwidth, while the LMV861/62 and LMV831/32/34 series have a gain bandwidth of 30 MHz and 3 MHz, respectively.

The effect of EMI can be demonstrated in a setup where a cell phone introduces interference in a pressure sensor application as seen in *Figure 1*. When the cell phone is called, the application will detect the RF signal transmitted by the cell phone. As a result, the output of Op Amp 2 will show a voltage shift. The magnitude of this unwanted voltage shift depends, among other factors, on the EMI robustness of the op amps.

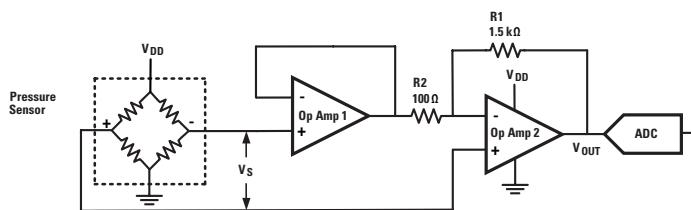


Figure 1. Pressure Sensor Application

The experiment is performed with a typical standard dual op amp and with the LMV852 dual EMI-hardened op amp. The resulting voltage shift on the output of Op Amp 2 is depicted in *Figure 2*, where the cell phone is placed a couple of centimeters above the application.

The difference between the two types of op amps is clearly visible. The typical standard dual op amp has an output voltage shift (disturbing signal) larger than 1V as a result of the RF signal transmitted by the cell phone. The LMV852 EMI-hardened op amp does not show any significant disturbances.

The op amp can play an important role in making designs significantly more EMI hardened. This is because the EMI robustness between op amps differs and the op amp is often the component where a disturbing RF signal

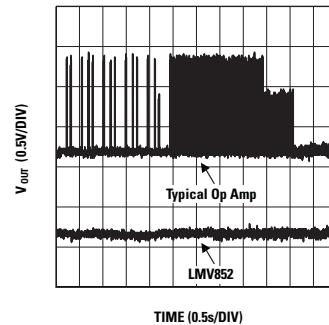


Figure 2. Comparing EMI Robustness

arrives on a PCB. Relatively long connections, to sensors for instance, can easily pick up disturbances and carry them to the op amp. An EMI-robust part will hardly detect the signal and will prevent the detected signal from propagating to the connected circuitry on the PCB. This ensures a proper functioning device.

EMI and Op Amps

To understand the sensitivity of an op amp to EMI, it is important to know how interference arrives at an op amp. Disturbing RF signals can potentially arrive either conductively via the op amp pins or through the air coupling into the IC directly. Since the dimensions of an op-amp IC are relatively small compared to the wavelength of the disturbing RF signals, interference will dominantly arrive through conduction (refer to application note AN-1698). The op amp will receive hardly any disturbances itself. The RF signals interfering with the op amp are thus dominantly received by the PCB and wiring connected to the op amp pins. As a result, RF voltages on the pins of the op amp can be used to represent interference.

RF signals interfere with op amps via the non-linearity of the op amp circuitry. This non-linearity results in the detection of out-of-band signals. The resulting effect is that the amplitude modulation of the out-of-band signal is down converted into the base band.

This base band can easily overlap with the band of the op-amp circuit. As an example, *Figure 3* depicts a typical output signal of a unity-gain-connected op amp in the presence of an interfering RF signal. Clearly, the output voltage varies in the rhythm of the on-off keying of the RF carrier.

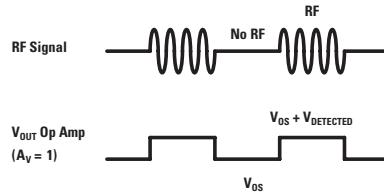


Figure 3. Offset Voltage Variation due to an Interfering RF Signal

The resulting voltage shift for the EMI-hardened op amp series is considerably smaller than for typical op amps which demonstrates the robustness to EMI.

EMI Rejection Ratio (EMIRR) Parameter

To identify EMI-hardened op amps, a parameter is needed that quantitatively describes the EMI performance of op amps. Therefore, the EMI Rejection Ratio (EMIRR) is introduced. This parameter describes the resulting input-referred offset voltage shift of an op amp as a result of an applied RF carrier (interference) with a certain frequency and level. The definition of EMIRR is given by:

$$\text{EMIRR}_{V_{\text{RF_PEAK}}} = 20 \log \left(\frac{V_{\text{RF_PEAK}}}{\Delta V_{\text{OS}}} \right)$$

in which $V_{\text{RF_PEAK}}$ is the amplitude of the applied unmodulated RF signal (V) and ΔV_{OS} is the resulting input-referred offset voltage shift (V). The offset voltage shift generally depends quadratically on the applied RF level, and therefore, the RF level at which the EMIRR is determined should be specified. The chosen standard level for the RF signal is 100 mV_p. Application note AN-1698 addresses the conversion of EMIRR values measured at signal levels other than 100 mV_p. The interpretation of the EMIRR parameter is straightforward. When two op amps have an EMIRR which differs by 20 dB, the resulting error signals when used in identical configurations differs by 20 dB as well. Thus, a higher EMIRR number means a more robust op amp.

Measuring EMIRR

Each of the op amp pins can be tested separately for EMIRR. The measurement on the IN+ pin is discussed here since it is generally the most sensitive pin together with the IN- pin. For testing the IN+ pin, the op amp is connected in a unity-gain configuration. Applying the RF signal is straightforward as it can be connected directly to the IN+ pin. The circuit diagram is shown in *Figure 4*.

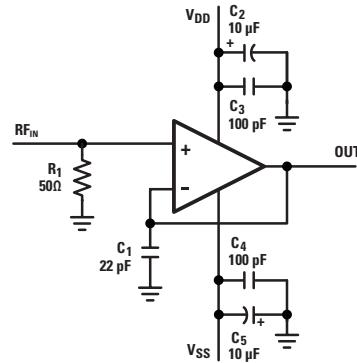


Figure 4. Circuit for Coupling the RF Signal to IN+

For determining the EMIRR, two measurements are needed: one is measuring the DC output level when the RF signal is off; and the other is measuring the DC output level when the RF signal is switched on. The difference of the two DC levels is the output voltage shift as a result of the RF signal. As the op amp is in the unity-gain configuration, the input-referred offset voltage shift corresponds one-to-one to the measured output voltage shift. By knowing the applied RF signal and the input-referred offset shift, the EMIRR can be calculated.

Conclusion

Designing EMI-robust circuits requires careful selection of the op amp used in the circuit, since its EMI robustness can vary substantially. The selection can be made based on the op amp's EMIRR, which quantitatively describes the EMI performance of op amps. ■

To learn more about EMI-hardened amplifiers, visit: national.com/amplifiers

References:

AN-1698 *A Specification for EMI-Hardened Operational Amplifiers*

National Semiconductor
2900 Semiconductor Drive
Santa Clara, CA 95051
1 800 272 9959

Mailing Address:
PO Box 58090
Santa Clara, CA 95052



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated