
AN-776 20 Watt Simple Switcher Forward Converter

ABSTRACT

This application note provides information about the 20-watt simple switcher forward converter.

Contents

1	Overview	2
2	Transformer Design	2
3	Output Filter—Inductor	4
4	Output Filter—Capacitor	4
5	Snubber Circuit	5
6	Other Components	5

List of Figures

1	Basic Forward Converter.....	3
2	5V, 4 A Forward Converter Circuit Schematic	6
3	Switch Current.....	6
4	Switch Voltage.....	7
5	Inductor Current.....	7
6	Output Ripple Voltage	8
7	Load Step Response	8

List of Tables

1	Design Specifications.....	2
---	----------------------------	---

1 Overview

A 20W, 5V at 4A, step-down regulator can be developed using the LM2577 Simple Switcher IC in a forward converter topology. This design allows the LM2577 IC to be used in step-down voltage applications at output power levels greater than the 1 A LM2575 and 3 A LM2576 buck regulators. In addition, the forward converter can easily provide galvanic isolation between input and output.

The design specifications are shown in [Table 1](#).

Table 1. Design Specifications

V_i Range	20V–24V
V_o	5V
$I_{o(max)}$	4A
ΔV_o	20 mV

With the input and output conditions identified, the design procedure begins with the transformer design, followed by the output filter and snubber circuit design.

2 Transformer Design

- Using the maximum switch voltage, input voltage, and snubber voltage, the transformer's primary-to-clamp windings turns ratio is calculated:

$$V_{SW} \geq V_{imax} + V_{imax} (N_p/N_c) + V_{snubber} \quad (1)$$

$$N_p/N_c \leq (V_{SW} - V_{imax} - V_{snubber})/V_{imax} \quad (2)$$

$$N_p/N_c \leq (60V - 24V - 5V)/24V = 1.29 \quad (3)$$

$$\Delta \text{ let } N_p/N_c = 1.25 \quad (4)$$

The $V_{snubber}$ voltage is an estimate of the voltage spike caused by the transformer's primary leakage inductance.

- The duty cycle, t_{on}/T , of the switch is determined by the volt-second balance of the primary winding.

During t_{on} :

$$V_i = L_p (\Delta i/T_{ON}) \rightarrow \Delta i = (V_i/L_p) t_{on}$$

During t_{off} :

$$V_i = (N_p/N_c) L_p (\Delta i/t_{off}) \rightarrow \Delta i = (N_p/N_c) (V_i/L_p) t_{off}$$

Setting Δi 's equal;

$$(V_i/L_p) t_{on} = (N_p/N_c) (V_i/L_p) t_{off}$$

$$t_{on}/t_{off} = N_p/N_c$$

$$\text{Since } D = t_{on}/T = t_{on}/(t_{on} + t_{OFF})$$

$$\text{max. duty cycle} = D_{max} = (N_p/N_c) / [(N_p/N_c) + 1]$$

$$D_{max} = (1.25) / (1.25 + 1) = 0.56 \text{ (56\%)}$$

- The output voltage equations of a forward converter provides the transformer's secondary-to-primary turns ratio:

$$V_o + V_{diode} \leq V_{imin} \times D_{max} (N_s/N_p)$$

$$N_s/N_p \geq (V_o + V_{diode}) / (V_{imin} \times D_{max})$$

$$N_s/N_p \geq (5.5V) / (20V)(56\%) = 0.49$$

$$\Delta \text{ let } N_s/N_p = 0.5$$

- Calculate transformer's primary inductance by finding the maximum magnetizing current (Δi_{Lp}) that does not allow the maximum switch current to exceed its 3 A limit (capital I for DC current, Δi for AC current, and lower case i for total current):

$$i_{sw} = i_{pri} = i_{Lo} + \Delta i_{Lp} \quad (5)$$

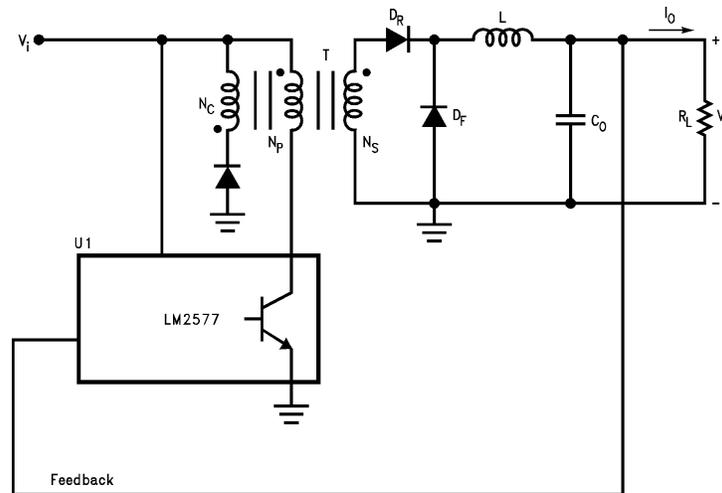


Figure 1. Basic Forward Converter

where i_{L_o} , is the reflected secondary current and Δi_{L_p} is the primary inductance current.

$$i_{L_o'} = i_{L_o}(N_s/N_p) \quad (i_{L_o} \text{ reflected to primary})$$

$$i_{L_o} = I_{L_o} \pm \Delta i_{L_o}/2 \tag{6}$$

$$\Delta i_{L_o} \text{ is the output inductor's ripple current} \tag{7}$$

$$I_{L_o} = I_o \text{ (the load current)} \tag{8}$$


$$i_{L_o'} = (I_o \pm \Delta i_{L_o}/2)(N_s/N_p) \tag{9}$$

$$i_{L_o'(pk)} = (I_{o(max)} + \Delta i_{L_o}/2)(N_s/N_p) \tag{10}$$

$$i_{sw} = I_{sw} + \Delta i_{sw} \tag{11}$$

$$i_{sw(pk)} = i_{L_o'(pk)} + \Delta i_{L_p(pk)} \tag{12}$$
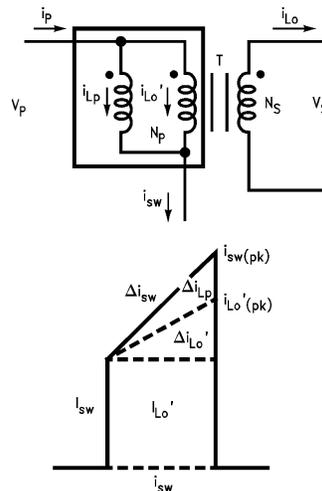
$$i_{sw(pk)} = (I_{o(max)} + \Delta i_{L_o}/2)(N_s/N_p) + \Delta i_{L_p(pk)} \tag{13}$$



Using standard inductors, a good practical value to set the output inductor current (Δi_{L_o}) to is 30% of the maximum load current (I_o). Thus;

$$i_{sw(pk)} = (I_{o(max)} + 0.15\Delta i_{L_o})(N_s/N_p) + \Delta i_{L_p(pk)} \tag{14}$$

$$\Delta i_{L_p(pk)} = i_{sw(pk)} - (I_{o(max)} + 0.15\Delta i_{L_o})(N_s/N_p) \tag{15}$$

$$\Delta i_{L_p(pk)} = 3A - (4A + 0.15 \times 4A)(0.5) = 0.7A \tag{16}$$

$$L_p = V_{pri} \times \Delta t/\Delta i = (V_i - V_{sat})(t_{on}/\Delta i_{L_p(pk)}) \tag{17}$$

$$= (V_{i(max)} - V_{sat})(D_{max}/(\Delta i_{L_p(pk)} \times f)) \tag{18}$$

$$= (24V - 0.8V)(0.56/0.7 \times 52 \text{ kHz}) \tag{19}$$

$$L_p = 357 \mu\text{H} \quad (20)$$

$$\Delta \text{let } L_p = 350 \mu\text{H} \quad (21)$$

3 Output Filter—Inductor

The first component calculated in the design is the output inductor, using the current-to-voltage relationship of an inductor:

$$V_L = L_o (\Delta i_{L_o} / t_{on}) \quad (22)$$

Choosing an inductor ripple current value of $0.3I_o$ and a maximum output current of 4A:

$$\Delta i_{L_o} = 0.3 (4\text{A}) = 1.2\text{A} \quad (23)$$

During t_{on} :

$$V_L = V_s - V_D - V_o \text{ [where } V_s = (V_i - V_{sat})(N_s/N_p)\text{]} \quad (24)$$

Thus,


$$[(V_i - V_{sat})(N_s/N_p) - V_d - V_o] = L_o (\Delta i_{L_o} / D) f$$

$$L_o = [(V_i - V_{sat})(N_s/N_p) - V_d - V_o] \times D / \Delta i_{L_o} \times f$$

$$L_o = [(24\text{V} - 0.8\text{V})(0.5) - 0.5\text{V} - 5\text{V}] 56\% / 1.2\text{A} \times 52 \text{ kHz}$$

$$L_o = 55 \mu\text{H}$$
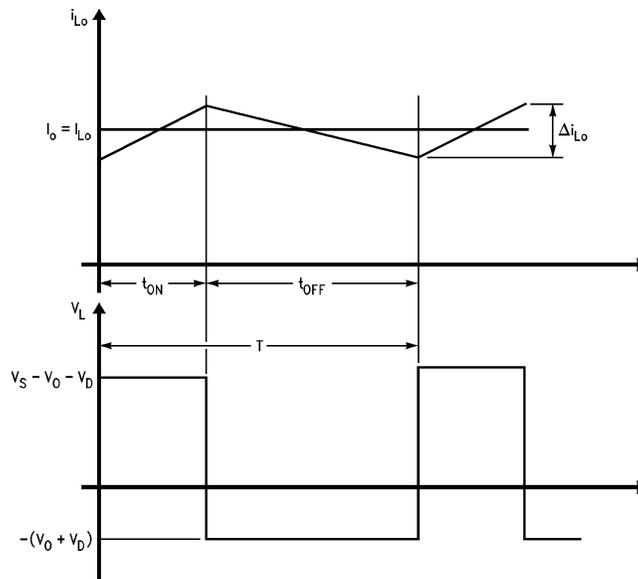
$$\Delta \text{let } L_o = 60 \mu\text{H}$$



4 Output Filter—Capacitor

Since the output capacitor's current is equal to inductor's ripple current, the output capacitor's value can be found using the inductor's ripple current. Starting with the current-voltage relationship, the output capacitance is calculated:

$$\Delta V_o = 1/C_o \int i dt$$

$$= \Delta i_{L_o} / 4C_o (TR/2)$$

$$= (\Delta i_{L_o} \cdot T) / 8C_o$$

$$C_o = (\Delta i_{L_o} \cdot T) / 8\Delta V_o$$

However, the equivalent series resistance (ESR) of the capacitor multiplied by the inductor's ripple current creates a parasitic output ripple voltage equal to:

$$\Delta V_o = \text{ESR}_{co} \cdot \Delta i_{L_o} = \text{ESR}_{co} \cdot 0.3 I_o \quad (25)$$

This parasitic voltage is usually much larger than the inherent ripple voltage. Hence, the output capacitor parameter of interest, when calculating the output ripple voltage, is the equivalent series resistance (the capacitance of the output capacitor will be determined by the frequency response analysis). Using a standard-grade capacitor with ESR of 0.05Ω produces a total output ripple voltage of:

$$\Delta V_o = 0.05\Omega \cdot 1.2A \approx 60 \text{ mV} \quad (26)$$

To get output ripple voltage of 20 mV or less (as was part of the design specs) requires a capacitor with ESR of less than 17 mΩ.

5 Snubber Circuit

A snubber circuit (C_S , R_S , D_S) is added to reduce the voltage spike at the switch, which is caused by the transformer's leakage inductance. It is designed as follows: when the switch is off,

$$V_R = V_{CE} - V_{IN} - V_D \quad (27)$$

$$V_{LL} = V_D + V_R - V_{IN}(N_p/N_c) \quad (28)$$

Substituting for V_R , the voltage across the leakage inductance, V_{LL} , is,

$$V_{LL} = V_{CE} - V_{IN}(1 + N_p/N_c) \quad (29)$$

Using the current-voltage relationship of inductors,

$$t_s = I_{PRI}(L_L/V_{LL}) \quad (30)$$

Substituting for V_{LL} ,

$$t_s = I_{PRI} L_L / (V_{CE} - V_{IN}(1 + N_p/N_c)) \quad (31)$$

Calculating for the average leakage inductance current, $I_{LL(AVE)}$,

$$I_{LL(AVE)} = I_{PRI(MAX)} (t_s)/2T \quad (32)$$

$$= I_{PRI(MAX)}^2 L_L f / 2(V_{CE} - V_{IN}(1 + N_p/N_c)) \quad (33)$$

Solving for the snubber resistor;

$$R_S = V_R / I_{LL(AVE)} \quad (34)$$

Substituting $I_{LL(AVE)}$ and V_R results in,

$$R_S = 2 (V_{CE} - V_{IN}(1 + N_p/N_c)) X \quad (35)$$

$$(V_{CE} - V_{IN} - V_D) / (L_L (I_{PRI(MAX)})^2 f) \quad (36)$$

Choosing L_L to equal 10% of L_p ,

$$R_S = 2 (65V - 24V - 1V) X (65V - 24V(2.25)) / \quad (37)$$

$$(7 \mu\text{H} (3A)^2 52 \text{ kHz}) \quad (38)$$

$$= 268.9\Omega \approx 270\Omega \quad (39)$$

Using the current-voltage relationship of capacitors,

$$\Delta V_R = (T - t_s) I_C / C_S = (T - t_s) V_R / R_S C_S \approx V_R / R_S C_S f \quad (40)$$

The capacitor C_S equates to,

$$C_S = V_R / R_S f \Delta V_R \quad (41)$$

$$C_S = 40V / (270\Omega)(52 \text{ kHz}) 10V = 0.28 \mu\text{F} \approx 0.33 \mu\text{F} \quad (42)$$

The snubber diode has a current rating of 1A peak and a reverse voltage rating of 30V.



6 Other Components

Diodes, D_R and D_F , used in the secondary are 5A, 30V Schottky diodes. The same diode type is used for D_C , however a lower current diode could have been used.

A compensation network of R_C and C_C optimizes the regulator's stability and transient response and provides a soft-start function for a well-controlled power-up.


The finished circuit is shown below.

Figure 2. 5V, 4 A Forward Converter Circuit Schematic

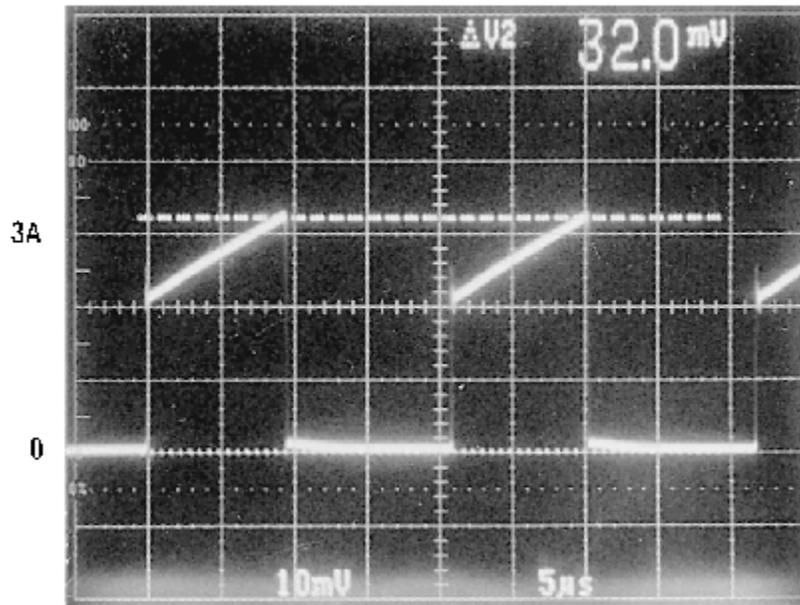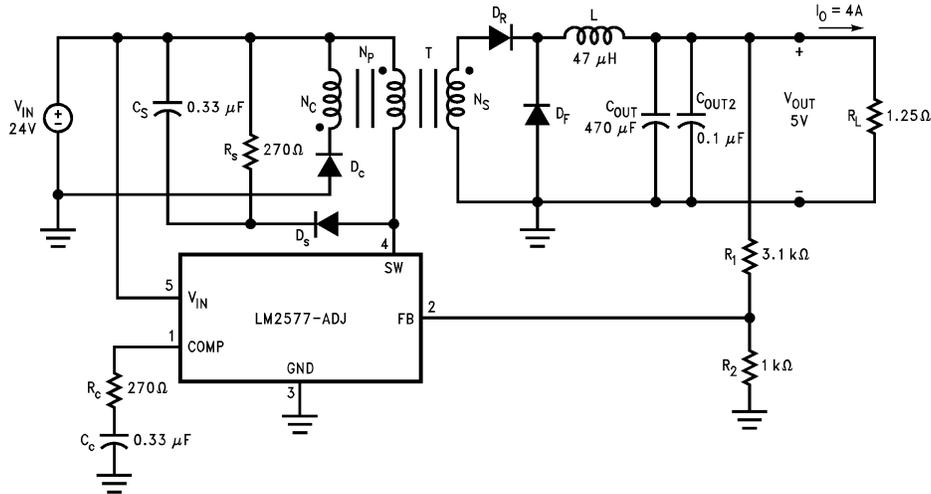


Vertical: 1 A/div
Horizontal: 5 μs/div

Figure 3. Switch Current

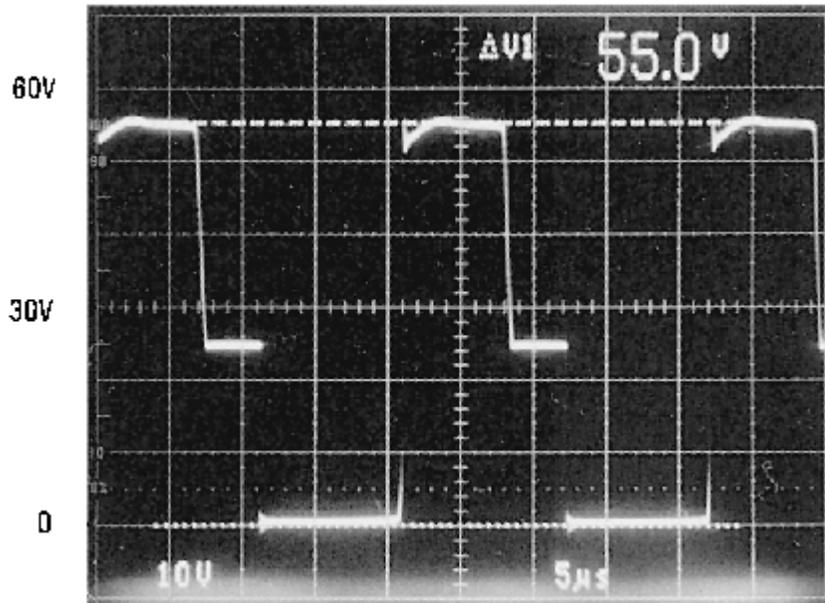


Vertical: 10 V/div
Horizontal: 5 µs/div

Figure 4. Switch Voltage

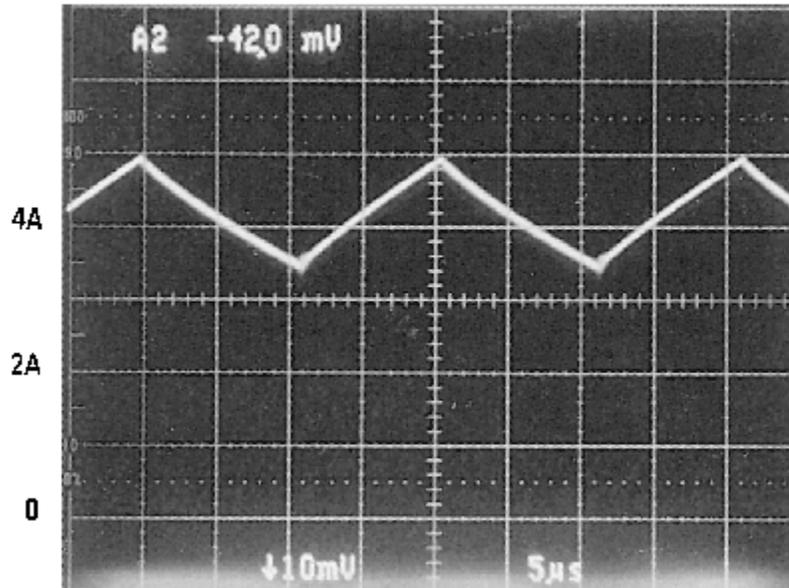


Vertical: 1 A/div
Horizontal: 5 µs/div

Figure 5. Inductor Current

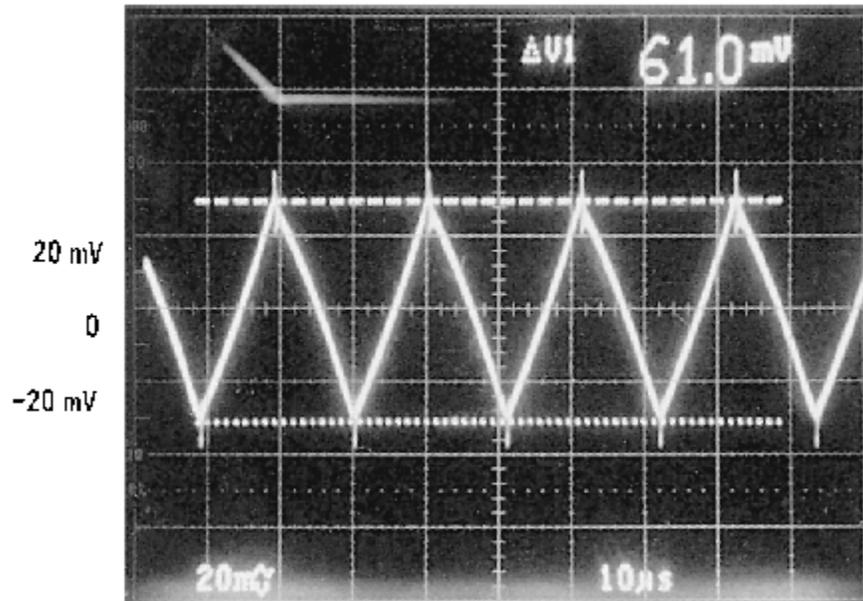

Vertical: 20 mV/div
Horizontal: 10 μs/div

Figure 6. Output Ripple Voltage

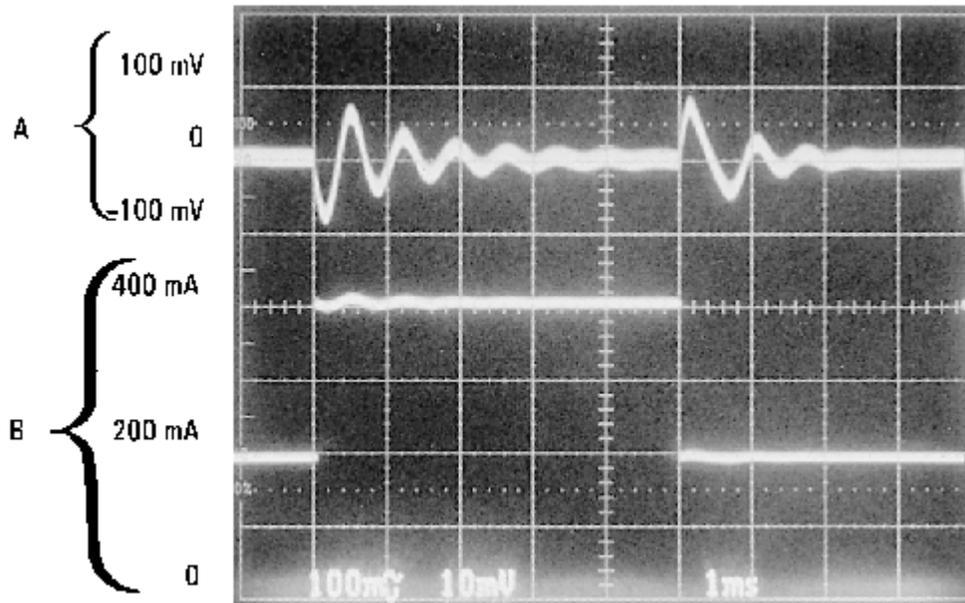

A: Output Voltage Change, 100 mV/div
B: Output Current, 200 mA/div
Horizontal: 10 ms/div

Figure 7. Load Step Response

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com