

AN-1471 LM3489 Demonstration Board

1 Introduction

The LM3489 is a high efficiency PFET switching regulator controller that can be used to quickly and easily develop a small, cost effective, switching buck regulator for a wide range of applications. The hysteretic control architecture provides for simple design without any control loop stability concerns using a wide variety of external components. The PFET architecture also allows for low component count as well as ultra-low dropout, and 100% duty cycle operation. Another benefit is high efficiency operation at light loads without an increase in output ripple. A dedicated Enable Pin (enabled if left unconnected) provides a shutdown mode drawing only 7 μ A.

The current limit protection can be implemented by measuring the voltage across the PFET's $R_{DS(ON)}$, thus, eliminating the need for a sense resistor. The cycle-by-cycle current limit can be adjusted with a single resistor, ensuring safe operation over a range of output currents.

This LM3489 demonstration board provides a 3.3 V output with 500 mA nominal load capability (maximum 1A) from a wide input voltage range of 7 V to 28 V. The reference design is optimized for overall conversion efficiency. This document contains the demo board schematic, PCB layout, Bill of Materials (BOM) and typical operating waveforms are provided for reference.

2 Evaluation Board Schematic

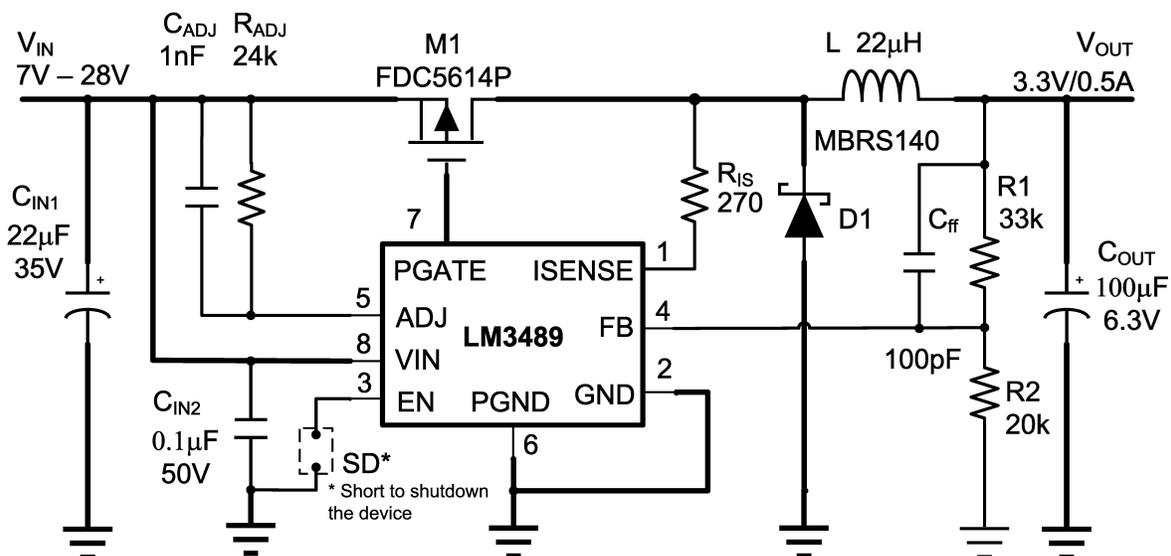


Figure 1. LM3489 Evaluation Board Schematic

Table 1. Bill of Materials (BOM)

Label	Description	Manufacturer
CIN1	Tantalum Capacitor 22µF 35V EEJL1VD226R	Panasonic
	Tantalum Capacitor 22µF 35V 293D226X0035E	Vishay
CIN2	0603 Ceramic Chip Capacitor 0.1µF 50V ECJ1VB1H104K	Panasonic
COUT	Low ESR Capacitor, POSCAP 100µF 6.3V 6TPC100M	Sanyo
CADJ	0603 Ceramic Chip 1nF 50V ECJ1VB1H102K	Panasonic
	0603 Ceramic Chip 1nF 50V VJ0805A102KXAA	Vishay
Cff	0805 Ceramic Chip 100pF 50V ECJ1VC1H101J	Panasonic
	0805 Ceramic Chip 100pF 50V VJ0805A101KXAA	Vishay
D1	Schottky Diode 1A 40V MBRS140T3	ON Semiconductor
	Schottky Diode 1A 40V CMSH1-40	Central Semi
L	Inductor 22µH LQH66SN220M03L	Murata
M1	P-channel MOSFET 60V FDC5614P	Fairchild
R1	0805 Chip Resistor 33kΩ CRCW08053302F	Vishay
	0805 Chip Resistor 33kΩ ERJ3GEYF333	Panasonic
R2	0805 Chip Resistor 20kΩ CRCW08052002F	Vishay
	0805 Chip Resistor 20kΩ ERJ3GEYF203	Panasonic
RADJ	0603 Chip Resistor 24kΩ CRCW08052402F	Vishay
	0603 Chip Resistor 24kΩ ERJ3GEYF243	Panasonic
RIS	0603 Chip Resistor 270Ω CRCW08052700F	Vishay
	0603 Chip Resistor 270Ω ERJ3GEYF271	Panasonic
U1	Buck Controller With ENABLE PIN LM3489	Texas Instruments

3 Demonstration Board PCB Layout

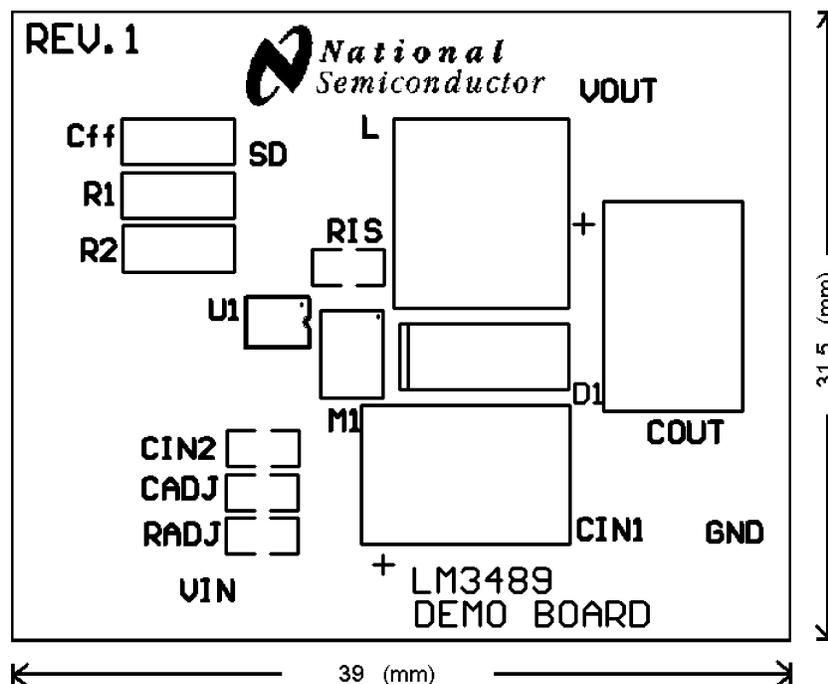


Figure 2. LM3489 Demonstration Board PCB Top Overlay

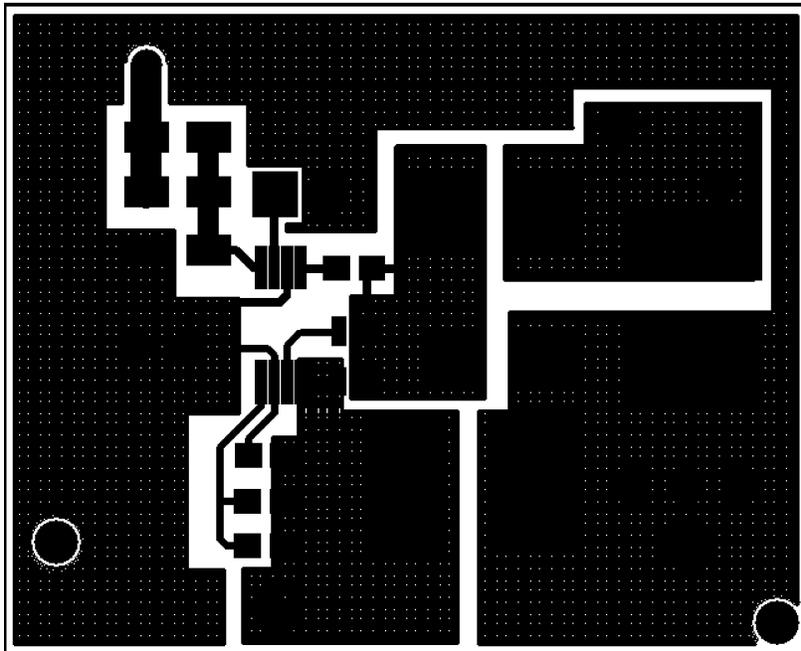


Figure 3. LM3489 Demonstration Board PCB Top Layer Layout

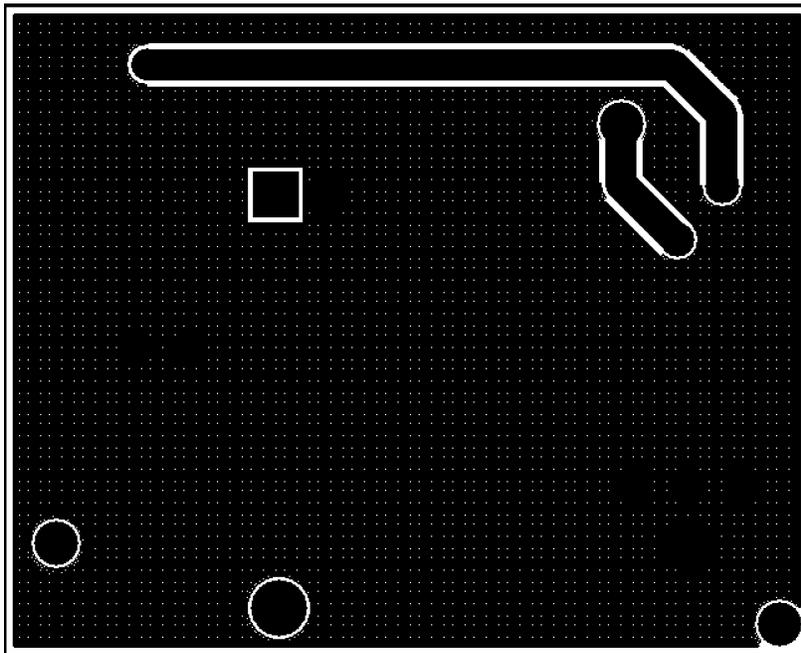


Figure 4. LM3489 Demonstration Board PCB Bottom Layer Layout


4 Demonstration Board Quick Setup Procedures

Step	Description	Notes
1	Connect power supply to VIN terminals	V _{IN} range 7 V to 28V
2	Connect load to the VOUT terminals	I _{OUT} range 0A to 500 mA
3	SD jumper should left open for normal operation -Short this jumper to shutdown	
4	Set V _{IN} = 12V, with no load applied, check V _{OUT} with voltmeter	3.3 V ±100 mV
5	Apply 500 mA load and check V _{OUT} again	3.3 V ±100 mV
6	Short output terminals and check short circuit current with an ammeter	Nominal 1.4A
7	Short SD jumper to check for shutdown function	

5 Demonstration Board Performance Characteristic

Description	Symbol	Condition	Min	Typical	Max	Unit
Input Voltage	V _{IN}		7	12	28	V
Output Voltage	V _{OUT}		3.2	3.3	3.4	V
Output Current	I _{OUT}		0	0.5	1	A
Output Voltage Ripple	V _{OUT(Ripple)}	20 MHz Bandwidth limit	-	-	40	mV _{P-P}
Output Voltage Regulation	ΔV _{OUT}	All V _{IN} and I _{OUT} conditions	1.5		1.5	%
Efficiency		V _{IN} = 7 V V _{IN} = 28 V (I _{OUT} = 100 mA to 500 mA)	88 73		90 80	%
Output Short Current Limit	I _{LIM-SC}			1.4		A

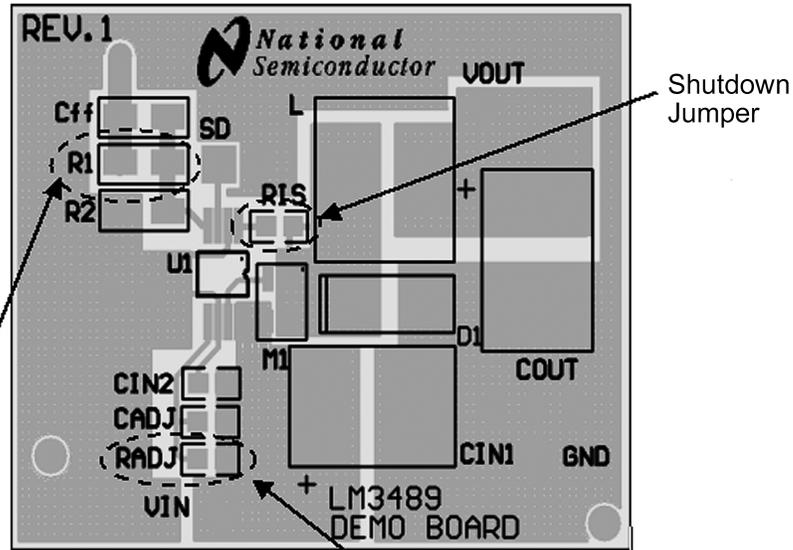6 Output Voltage and Current Limit Setting



Output Voltage setting

Find the value of R1 by :

Assume R2 = 20kΩ

$$R1 = \left(\frac{V_{OUT}}{1.239} - 1 \right) \times 20k\Omega$$





Current Limit setting





Find the value of R_{ADJ} by :

$$R_{ADJ} = \frac{R_{DS(on),M1} \times I_{IND_PEAK}}{3 \times 10^{-6}} \Omega$$

7 Typical Performance and Waveforms

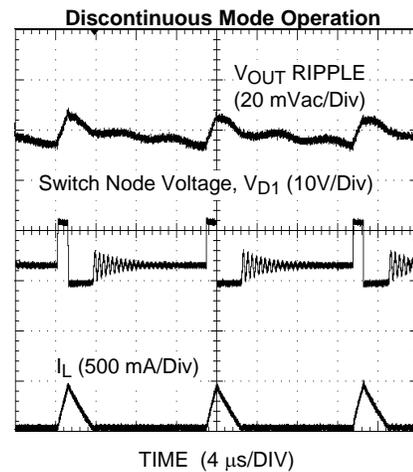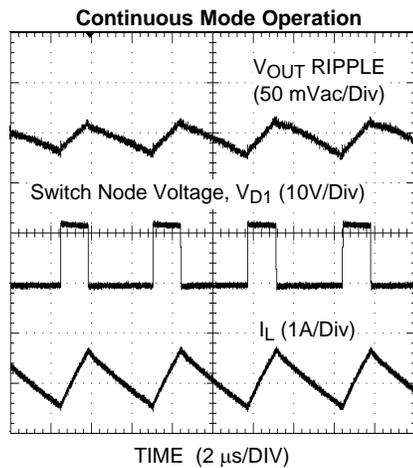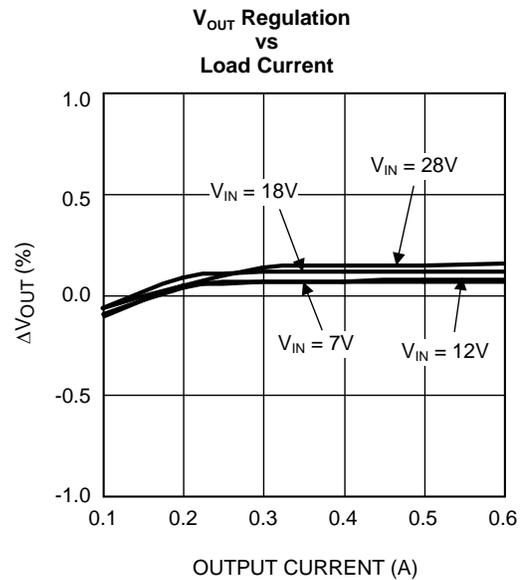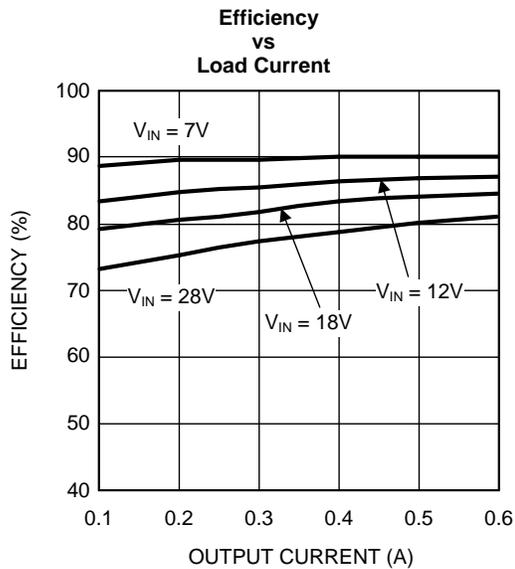All curves taken at $V_{IN} = 12\text{ V}$ with the demonstration board for $V_{OUT} = 3.3\text{ V}$. $T_J = 25^\circ\text{C}$, unless otherwise specified.



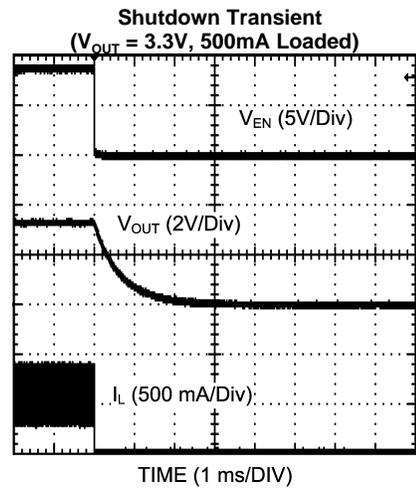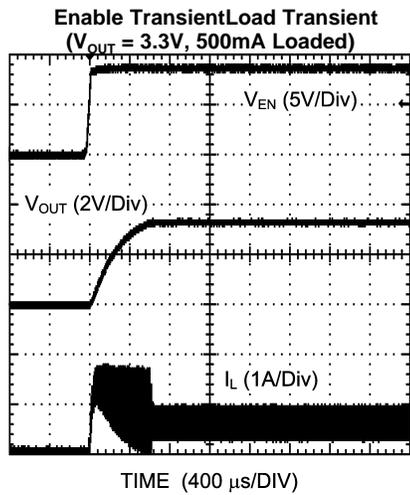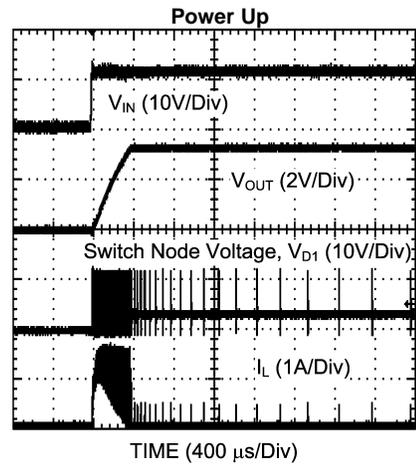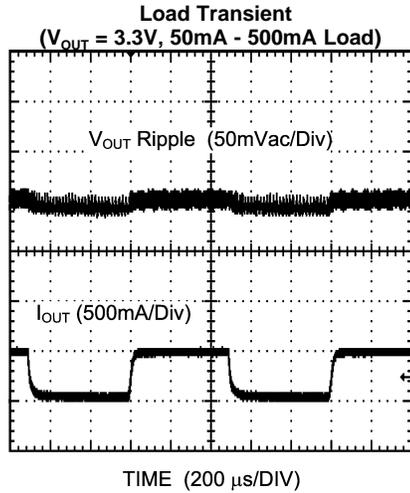

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com