

AN-2112 LM25117 Evaluation Board

1 Introduction

The LM25117 evaluation board provides the design engineer with a fully functional synchronous buck converter based on Emulated Current Mode Control to evaluate the LM25117 controller IC. The evaluation board provides 3.3V output with a 9A current capability in addition with average output current information. The input voltage ranges from 6V to 36V.

2 Performance of the Evaluation Board

- Input Voltage Range: 6V to 36V
- Output Voltage: 3.3V
- Output Current: 9A
- Nominal Switching Frequency: 230 kHz
- Synchronous Buck Operation: Yes
- Diode Emulation Mode: Yes
- Hiccup Mode Overload Protection: Yes
- External VCC Sourcing: No
- Current Monitor Output: Yes

3 Powering and Loading Consideration

3.1 Proper Board Connection

When applying power to the LM25117 evaluation board certain precautions need to be followed. A misconnection can damage the assembly.

The input connection is made to the J1 (VIN+) and J2 (VIN-) connectors. The load is connected to the J3 (VOUT+) and J4 (VOUT-). Be sure to choose the correct connector and wire size when attaching the source power supply and the load. The average output current can be monitored at J5. Use RCA jack to remotely sense the current monitor output. TP5 is directly connected to UVLO and can be used as an input of the remote shutdown signal.

3.2 Source Power

The power supply and cabling must present low impedance to the evaluation board. Insufficient cabling or a high impedance power supply will droop during power supply application with the evaluation board inrush current. If large enough, this droop will cause a chattering condition upon power up. During power down, this insufficient cabling or a high impedance power supply will overshoot, results in a non-monotonic decay on the output.

An additional external bulk input capacitor may be required unless the output voltage droop/overshoot of the source power supply is less than 0.5V.

3.3 Loading

When using an electronic load, it is strongly recommended to power up the evaluation board at light load and then slowly increase the load. If it is desired to power up the evaluation board at maximum load, resistor bank must be used. In general, electronic load is best suited for monitoring steady state waveforms.

3.4 Air Flow

Prolonged operation with high input voltage at full power will cause the MOSFETs to overheat. A fan with a minimum of 200LFM should be always provided.

3.4.1 Quick Start-up Procedure

1. Set the power supply current limit to at least 11A. Connect the power supply to J1 and J2.
2. Connect the load with a 9A capacity between J3 and J4.
3. Set input voltage to 6V and turn it on.
4. Measure the output voltage. The output should be regulated at 3.3V.
5. Slowly increase the load current while monitoring the output voltage. The output should remain in regulation up to full load current.
6. Slowly sweep the input voltage from 6V to 36V while monitoring the output voltage. The output should remain in regulation.


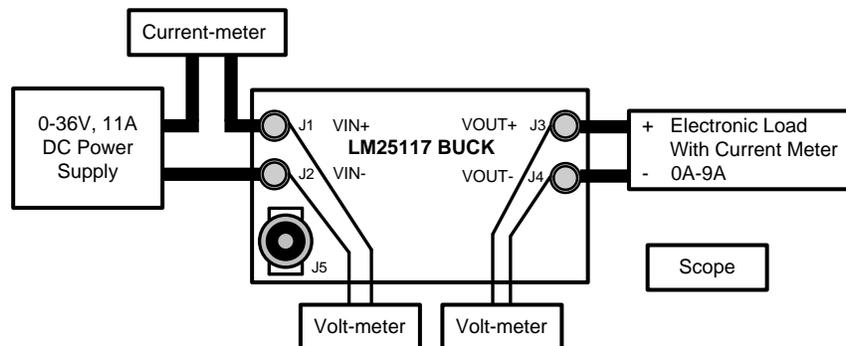


Figure 1. Typical Evaluation Setup

3.5 Waveforms

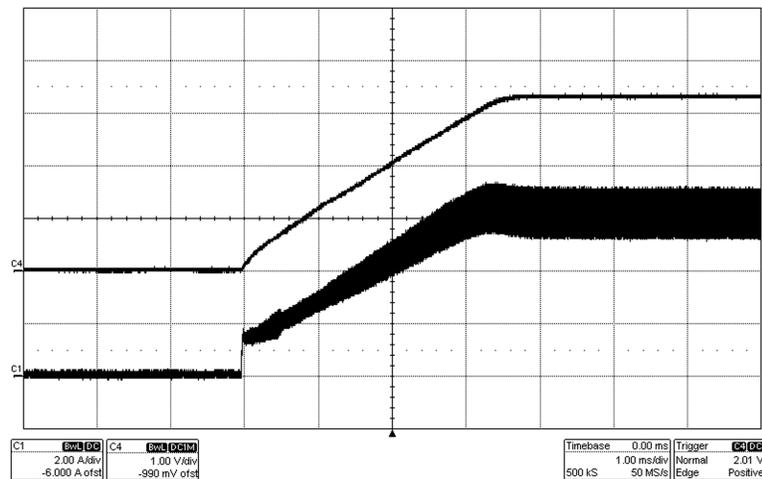3.5.1 Soft Start

When applying power to the LM25117 evaluation board a certain sequence of events occurs. Soft-start capacitor and other components allow for a linear increase in output voltage. [Figure 2](#) shows the output voltage during a typical start-up with a load of 0.5Ω



Conditions:

Input Voltage = 24VDC
 0.5Ω Load on the output


Traces:

Top Trace: Output Voltage, Volt/div = 1V
 Bottom Trace: Inductor Current, Amp/div=2A
 Horizontal Resolution = 1ms/div

Figure 2. Start-Up with Resistive Load

3.5.2 Load Transient

Figure 3 shows the transient response for a load of change from 2A to 6.5A. The upper waveform shows output voltage droop and overshoot during the sudden change in output current shown by the lower waveform.

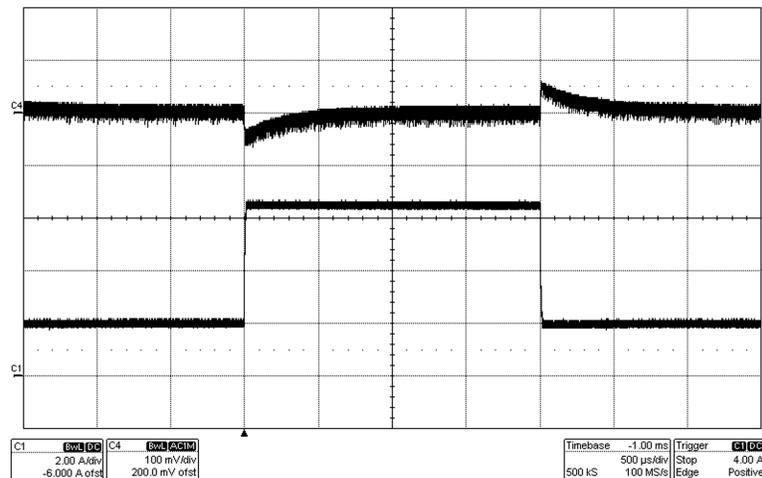

Conditions:

Input Voltage = 24VDC
 Output Current 2A to 6.5A


Traces:

Top Trace: Output Voltage
 Volt/div = 100mV, AC coupled
 Bottom Trace: Load Current, Amp/div = 2A
 Horizontal Resolution = 0.5ms/div

Figure 3. Load Transient Response

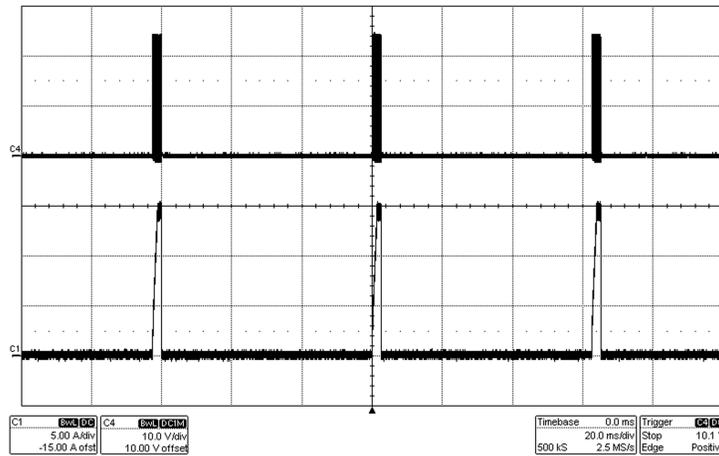3.5.3 Overload Protection

The evaluation board is configured with hiccup mode overload protection. The restart time can be programmed by C20 restart capacitor. Figure 4 shows hiccup mode operation in the event of an output short.



Conditions:

Input Voltage = 24VDC

Output Short

Traces:

Top Trace: SW Voltage Volt/div = 10V


Bottom Trace: Inductor Current, Amp/div = 5A

Horizontal Resolution = 20ms/div

Figure 4. Short Circuit

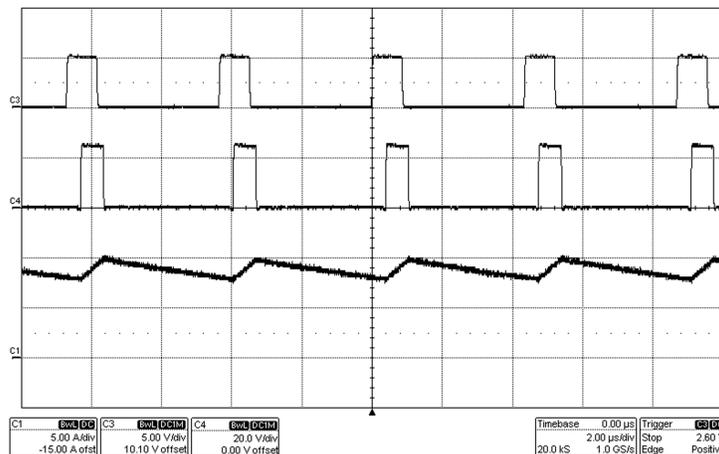3.5.4 External Clock Synchronization

A TP3 (SYNC) test point has been provided on the evaluation board in order to synchronize the internal oscillator to the external clock. Figure 5 shows the synchronized switching operation.



Conditions:

Input Voltage = 24VDC

Load Current = 9A

Traces:

Top Trace: SYNC pulse, 20% duty cycle, Volt/div = 5V

Middle Trace: SW voltage, Volt/div = 20V


Bottom Trace: Inductor Current, Amp/div = 5A

Horizontal Resolution = 2μs/div

Figure 5. Clock Synchronization

3.5.5 Shutdown

Figure 6 shows the shutdown procedure by powering off the source power. When UVLO pin voltage is less than 1.26V, the switching stops and soft-start capacitor is discharged by internal switches.

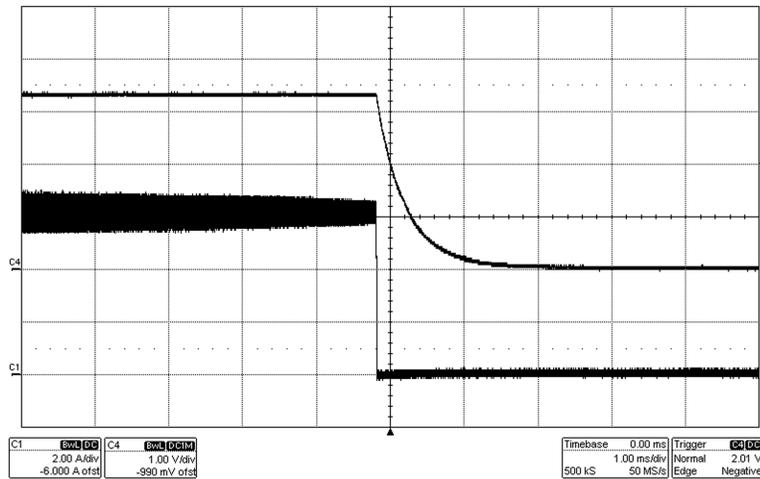

Conditions:

Input Voltage = 24VDC
0.5Ω Load on the Output

Traces:

Top Trace: Output Voltage, Volt/div = 1V
Bottom Trace: Inductor Current, Amp/div = 2A
Horizontal Resolution = 1ms/div

Figure 6. Shutdown

3.6 Performance Characteristics

Figure 7 shows the efficiency curves. During the efficiency measurement, monitor the current into and out of the evaluation board and monitor the voltage directly at the input and output terminals of the evaluation board.

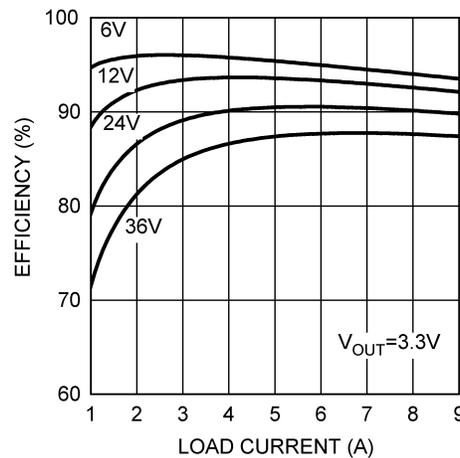


Figure 7. Typical Efficiency vs Load Current

3.7 Board Configuration

3.7.1 Loop Response

TP6 and TP7 have been provided in order to measure the loop transfer function. Refer to AN-1889([SNVA364](#)) for detail information about the loop transfer function measurement.


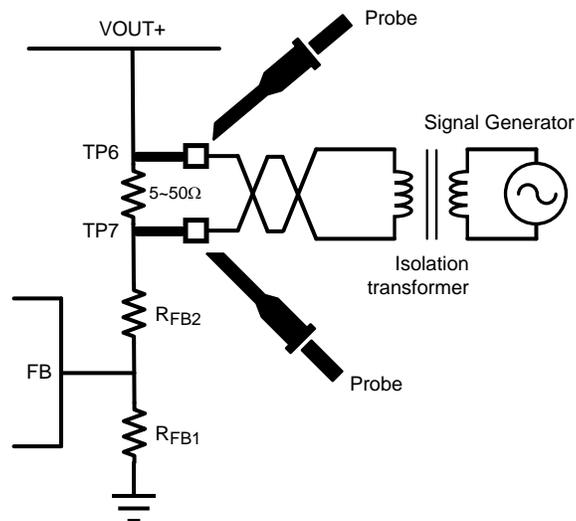


Figure 8. Loop Response Measurement Setup


3.8 Evaluation Board Schematic

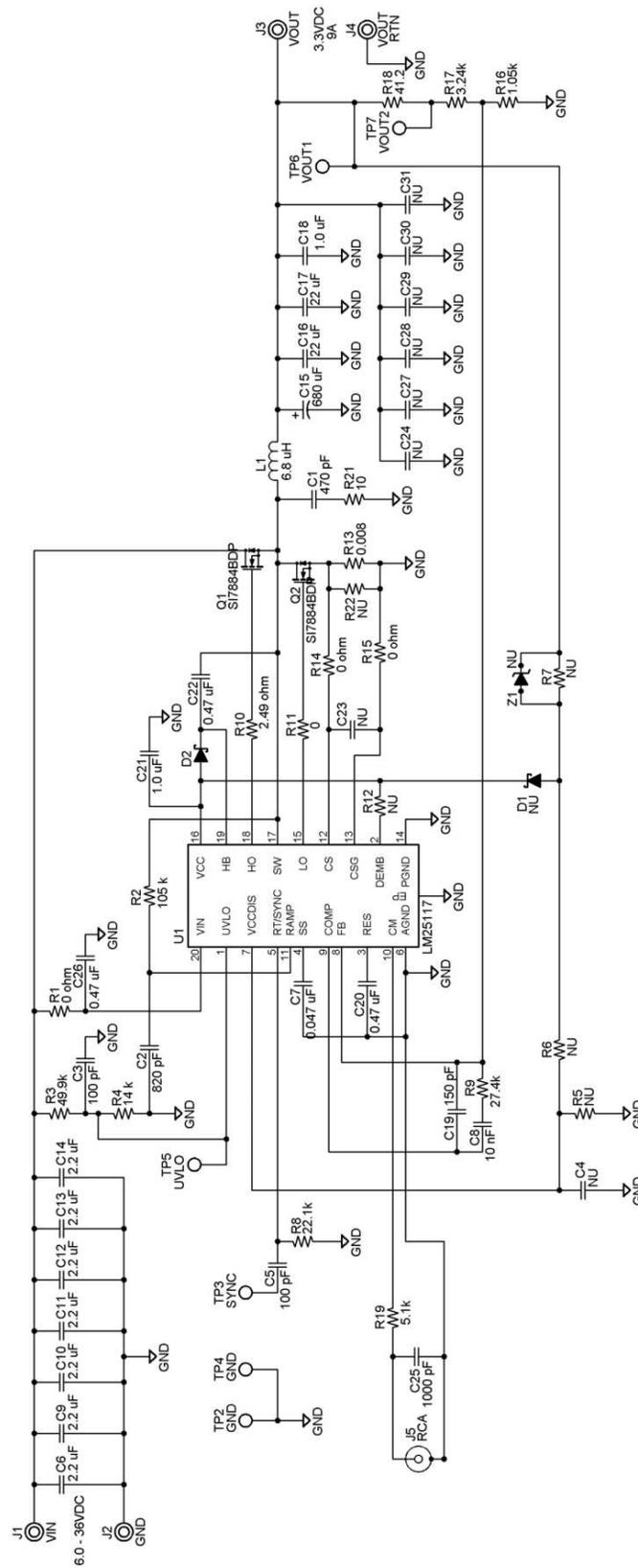

3.9 Bill of Materials


Part	Value	Package	Part Number	Manufacturer
C1	470pF, 100V, C0G	0805	C2012C0G2A471J	TDK
C2	820pF, 50V, C0G	0603	C1608C0G1H821J	TDK
C3, C5	100pF, 50V, C0G	0603	C1608C0G1H101J	TDK
C4, C23	NU	0603		
C6, C9, C10, C11, C12, C13, C14	2.2μF, 50V, X7R	1210	C3225X7R1H225K	TDK
C7	0.047μF, 16V, X7R	0603	C1608X7R1C473K	TDK
C8	0.01μF, 25V, C0G	0603	C1608C0G1E103J	TDK
C15	680μF, 6.3V, 10mΩ	Φ10	APXA6R3ARA681MJC0 G	UNITED CHEMICON
C16, C17	22μF, 16V, X7R	2220	C5750X7R1C226M	TDK
C18, C21	1μF, 16V, X7R	0603	C1608X7R1C105K	TDK
C19	150pF, 50V, C0G	0603	C1608C0G1H151J	TDK
C20, C22	0.47μF, 25V, X7R	0603	GRM188R71E474KA12	MURATA
C24, C27, C28, C29, C30, C31	NU	2220		
C25	1000pF, 50V, X7R	0603	C1608X7R1H102K	TDK
C26	0.47μF, 50V, X7R	0805	GRM21BR71H474KA88L	MURATA
R1	0 ohm	0805	MCR10EZPJ000	ROHM
R2	105k, 1%	0805	CRCW0805105KFKEA	VISHAY
R3	49.9k, 1%	0805	CRCW080549K9FKEA	VISHAY
R4	14k, 1%	0603	CRCW060314K0FKEA	VISHAY
R5, R6, R7, R12	NU	0603		
R11, R14, R15	0 ohm	0603	MCR03EZPJ000	ROHM
R8	22.1k, 1%	0603	CRCW060322K1FKEA	VISHAY
R9	27.4k, 1%	0603	CRCW060327K4FKEA	VISHAY
R10	2.49 ohm, 1%	0603	CRCW06032R49FKEA	VISHAY
R13	0.008 ohm, 1W, 1%	0815	RL3720WT-R008-F	SUSUMU
R16	1.05k ohm, 1%	0603	CRCW06031K05FKEA	VISHAY
R17	3.24k, 1%	0603	CRCW06033K24FKEA	VISHAY
R18	41.2 ohm, 1%	0805	CRCW080541R2FKEA	VISHAY
R19	5.1k, 5%	0603	CRCW06035K10JNEA	VISHAY
R21	10 ohm, 1%	2010	CRCW201010R0FKEF	VISHAY
R22	NU	1206		
D1	NU	PowerDI323		
D2	60V, 1A	SOD123F	PMEG6010CEH	NXP
Z1	NU	SOT89		
L1	6.8μH, 18.5A / 27A	18.2x18.3	7443556680	WE
Q1, Q2	40V, 58A	PowerPAK SO-8	SI7884BDP	VISHAY
U1		HTSSOP-20	LM25117	Texas Instruments
J1, J2, J3, J4	Terminal-Turret		1509	KEYSTONE
J5	RCA Jack, Blue		RCJ-025	CUI
TP2, TP3, TP4, TP5, TP6, TP7	Test Point		1040	KEYSTONE

3.10 PC Board Layout

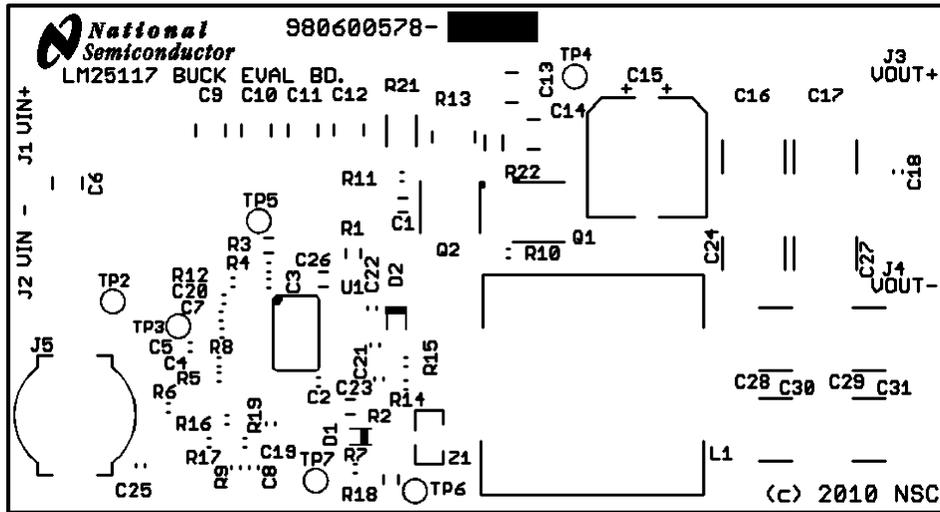


BOTTOM SILKSCREEN (.BPL) LAYER AS VIEWED FROM TOP

880600578-001

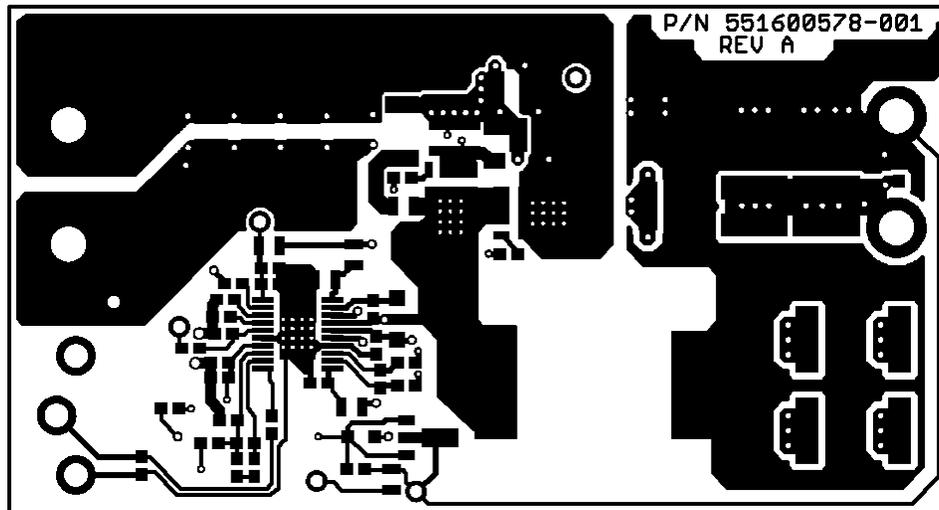


TOP (.CMP) LAYER AS VIEWED FROM TOP

880600578-001

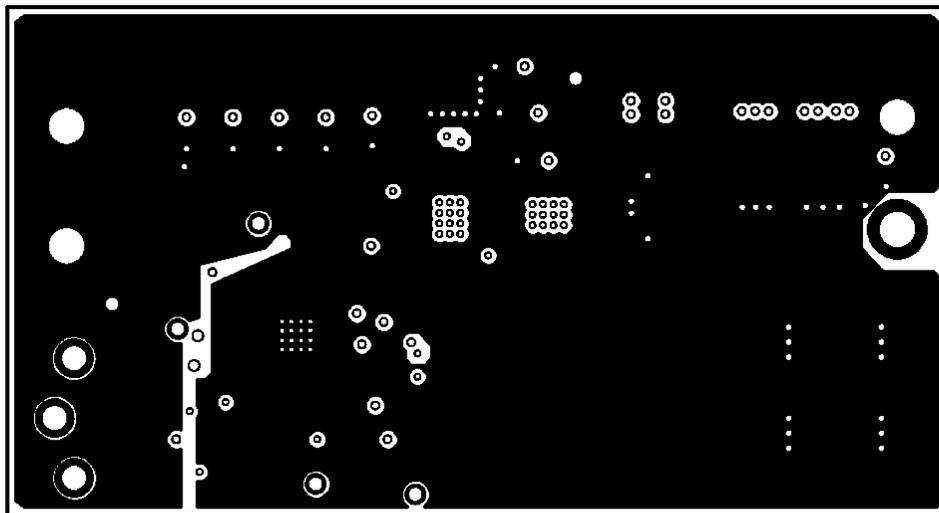


LAYER 2 (.LY2) AS VIEWED FROM TOP

880600578-001

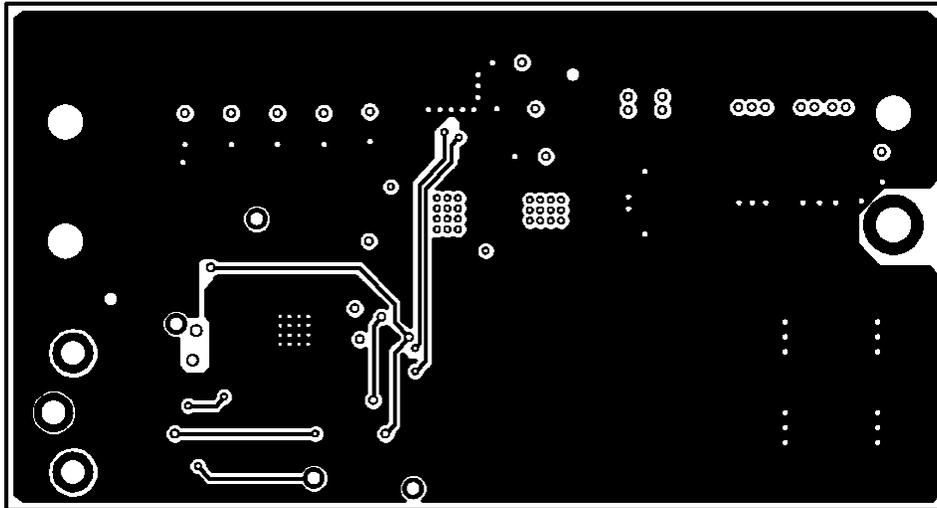

LAYER 3 (.LY3) AS VIEWED FROM TOP

880600578-001

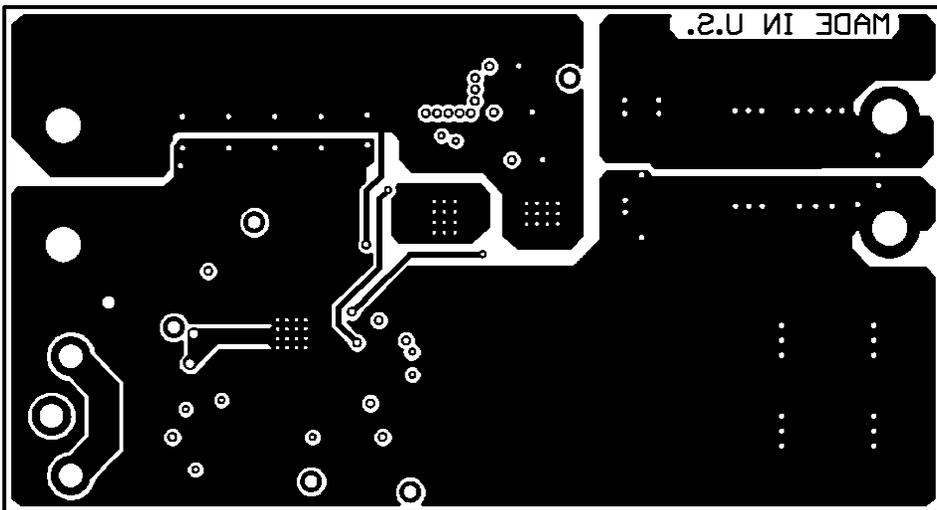

BOTTOM (.SOL) LAYER AS VIEWED FROM TOP

880600578-001

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com