

Using the LM3643/4/8 in an Inductorless and/or Simplified PCB Routing Configuration

1 Introduction

The LM3643, LM3644 and LM3648 are a family of high-power LED flash drivers designed to be a lighting source in many applications ranging from a mobile-phone, front-facing "selfie" flash to a flashlight/torch on a handheld point-of-sale (POS) terminal. While each device is highly configurable, there are designs where the full feature set may not be needed or where the fine pitch of the device (0.4 mm) could be prohibitive. To help highlight these auxiliary use cases, this application note discusses how to use the LM3643/4/8 family of devices, without an inductor, for applications that do not require the DC-DC boost converter, as well as a use case where the LM3643/4/8 family can be placed on a PCB without the use of micro vias for the center bumps.


2 No Inductor Use Case

For lighting applications that always have an input voltage higher than the LED forward voltage, the inductor for the DC-DC converter on the LM3643/4/8 parts can removed from the bill of materials (BOM) with little, or no, impact on the light quality. In many cases, the inductor is the largest passive component in the flash-driver solution, and its removal can shrink the overall printed circuit board footprint dramatically while lowering the overall BOM cost. There are a few key system-related items that must be evaluated before removing the inductor from the BOM.

2.1 Maximum Allowed LED Forward Voltage

To determine whether or not the inductor can be used for a given application, confirm that the maximum LED forward voltage at the target current is less than minimum supply voltage minus the voltage drops across the LM3643/4/8. Find the maximum LED voltage for a given current and input voltage using a simple equation:

$$V_{\text{IN MIN}} = (I_{\text{LEDTOTAL}} \times R_{\text{PMOS}}) + V_{\text{LED}} + V_{\text{HR}} \tag{1}$$

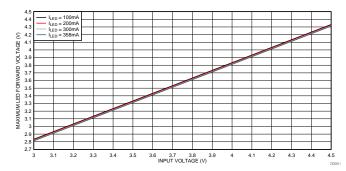



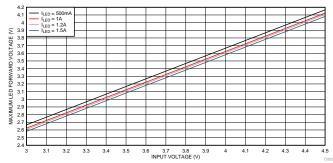


Figure 2. Maximum LED Voltage in Flash Mode



No Inductor Use Case www.ti.com

NOTE: When operating the devices at high current, careful PCB layout must be observed to manage the thermal dissipation across the device. At higher input voltages, the power dissipated across the device can be high causing the maximum on-chip temperature to reach or exceed the maximum operating junction temperature highlighted in the data sheet. To mitigate this self heating, shorted current pulses might be required to avoid exceeding the maximum junction temperature as well as to prevent the on-chip thermal shutdown.

In the LM3643/4/8 devices, the R_{PMOS} value is equal to 86 $m\Omega$ and V_{HR} is 158 mV in torch and 290 mV in flash mode. As V_{IN} drops, V_{HR} drops as well. If V_{IN} drops enough to violate the V_{HR} requirement for regulation, the LED current decreases. In Figure 3, V_{IN} starts at 4.5 V and drops to below 3 V when trying to deliver 500 mA. As V_{IN} drops below V_{LED} + V_{HR} , the LED current starts to decay linearly as the current source is no longer able to regulate. As V_{IN} increases, the LED current returns to regulation.

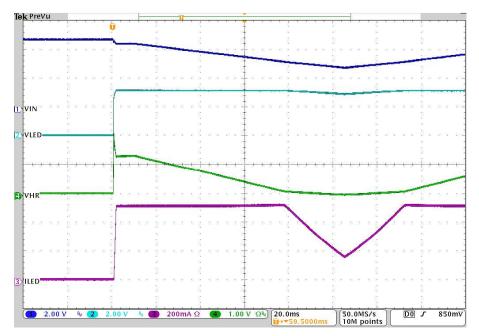


Figure 3. Effect of Low Headroom on Flash Current

2.2 Schematic

To operate the LM3643/4/8 devices without an inductor, the IN and SW pin must be shorted on the PCB. This provides the power path to the current source/s.

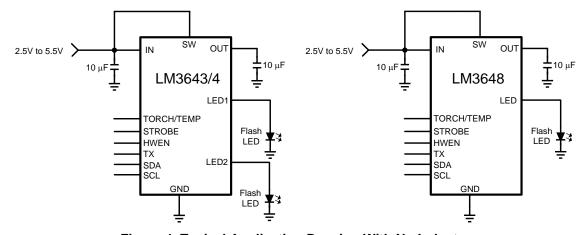


Figure 4. Typical Application Drawing With No Inductor



2.2.1 I2C Configuration

To prevent the NMOS of the boost DC-DC from turning on, it is imperative to set the boost mode bit in the Boost Configuration Register (Bit2 in Register 0x07) to a 1. This forces the device to be in pass mode, while allowing the current source/s to still turn on.

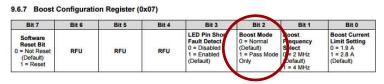



Figure 5. Boost Mode Bit Setting

3 Layout Without Micro Vias

Because the LM3643/4/8 has 12 bumps in a 4×3 bump array, two of the center bumps require the use of fine-pitch micro vias to route the traces to the outer perimeter of the device on a different PCB layer. In some designs, the use of micro vias is not an option due to cost or lack of a manufacturing flow that allows for micro vias. In these instances, the LM3643/4/8 family of devices can still be used with the omission of certain functions. By omitting the TX function, the HWEN center pin can easily be routed to the outer edge of the device by using a simple PCB trace. The STROBE functionality can be preserved as well by omitting the use of the TORCH/TEMP functionality.

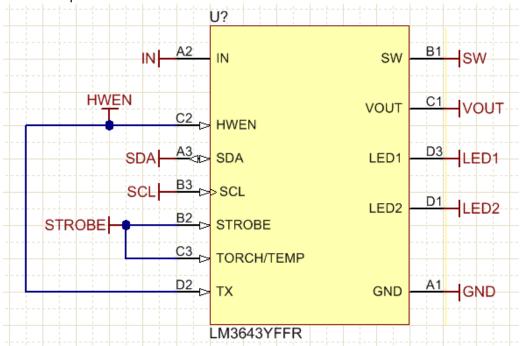3.1 Schematic

By connecting the HWEN and TX pins together, as well as connecting the STROBE and TORCH/TEMP pins together, the LM3643/4/8 devices can be routed and controlled without the need of micro vias in the center bumps.





3.2 Layout

The PCB trace to bring the HWEN pin out to the perimeter is very straightforward. It requires only a trace to route from the C2 bump through the outer D2 bump as shown in Figure 6. To connect route the B2 STROBE pin to the outside bump, a diagonal trace to the C3 bump is required. This connection requires a PCB manufacturing process that can tolerate narrow trace to bump clearances due to the diagonal routing. If the clearance constraint required to route the STROBE trace is too narrow, the STROBE functionality can still be enabled via I2C commands.

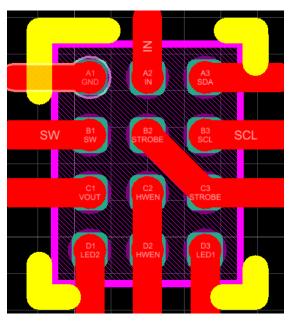


Figure 6. PCB Layout

3.3 I2C Register Settings

To ensure that the LM3643/4/8 does not create a false TX or TORCH/TEMP event, the pin-enable bits for these functions must be disabled via I2C. Bit 7 and Bit 4 in register 0x01 must be set to logic 0 to disable the pin functionality.

9.6.1 Enable Register (0x01)

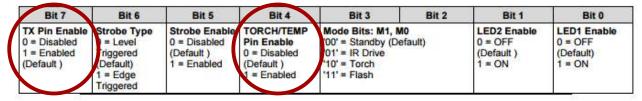


Figure 7. Enable Register Information

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

| Products | Applications |
|----------|--------------|
| Tiouucis | Applications |

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive **Amplifiers** amplifier.ti.com Communications and Telecom www.ti.com/communications **Data Converters** dataconverter.ti.com Computers and Peripherals www.ti.com/computers **DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps DSP dsp.ti.com **Energy and Lighting** www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical Logic Security www.ti.com/security logic.ti.com

Power Mgmt power.ti.com Space, Avionics and Defense www.ti.com/space-avionics-defense

Microcontrollers microcontroller.ti.com Video and Imaging www.ti.com/video

RFID www.ti-rfid.com

OMAP Applications Processors www.ti.com/omap TI E2E Community e2e.ti.com

Wireless Connectivity www.ti.com/wirelessconnectivity