

# Simple Backlight Driver Dimming Performance

Matthew Lin

## ABSTRACT

The [TPS61158](#), [TPS61160/61](#), [TPS61162A/63A](#), [TPS61165](#), and [TPS61169](#) (hereafter "TPS611xx") are simple backlight drivers commonly used in smartphones and tablets. These devices support PWM dimming with an input voltage as low as 2.7 V. This application note discusses the requirements for using the TPS611xx parts at the lowest performance specifications for PWM dimming.

## Contents

1	Minimum PWM On-Time Requirement .....	2
2	Minimum Performance Specifications.....	2
3	TPS61162A/3A Special Cases.....	3

## List of Figures

1	Low Duty-Cycle Behavior.....	2
2	Internal Low-Pass Filter to Error Amplifier.....	3
3	Offset Voltage Model .....	3
4	TPS61162A/TPS61163A Error Amplifier Block Diagram.....	3
5	Hysteresis.....	4
6	Incrementation Effects on Resolution .....	4

## List of Tables

1	Typical Voltage Offset.....	3
---	-----------------------------	---

## Trademarks

EasyScale is a trademark of Texas Instruments.

## 1 Minimum PWM On-Time Requirement

All devices mentioned except for the [TPS61169](#) are equipped with both PWM dimming and EasyScale™ 1-wire control interface; the TPS61169 only has PWM dimming. All devices with 1-wire control have a minimum PWM input on time of 50 ns. For pulse widths below 50 ns, or equivalently a 0.5% duty cycle at the maximum frequency, 100 kHz, the internal-glitch rejection on the PWM (or CTRL) input can randomly detect or ignore logic pulses. As a result, going below 50 ns can inadvertently trigger the device to enter 1-wire mode. To ensure proper detected logic levels, keep the pulse width above 50 ns. When 1-wire control is randomly activated, the default current output is maximum current, causing the device to output inconsistent output current. Because the TPS61169 does not have 1-wire control, at lower input voltages—the device does not stop outputting current unless the PWM signal is 0 V. *Any pulse width greater than 50 ns at any frequency within the range of each chip, respectively, outputs a stable and steady current.*

## 2 Minimum Performance Specifications

The 100-kHz PWM frequency and 3.3-V input voltage was used to test each device. The maximum current for all the devices was set to 20 mA.

### 2.1 Linearity

These devices maintain their linearity as low as 1% duty cycle at all frequencies in range.

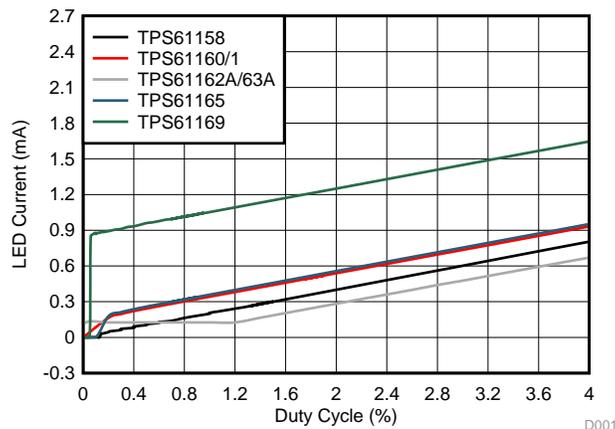


Figure 1. Low Duty-Cycle Behavior

### 2.2 Internal Low Pass Filter to Error Amplifier

All devices mentioned have an internal low-pass filter on the control pin. The output of the low-pass filter is connected to the error amplifier as a DC-reference voltage for the FB pin regulation. Though a PWM signal is used to control the LED current, the LED current has a varying DC current that is proportional to PWM input duty cycle. Using this low pass filter eliminates any audible noise due to the output voltage ripple at the PWM frequency and also allows the regulation voltage to be independent of the PWM logic voltage, which often has large variations. [Figure 2](#) shows the internal low-pass filter and error amplifier schematic.

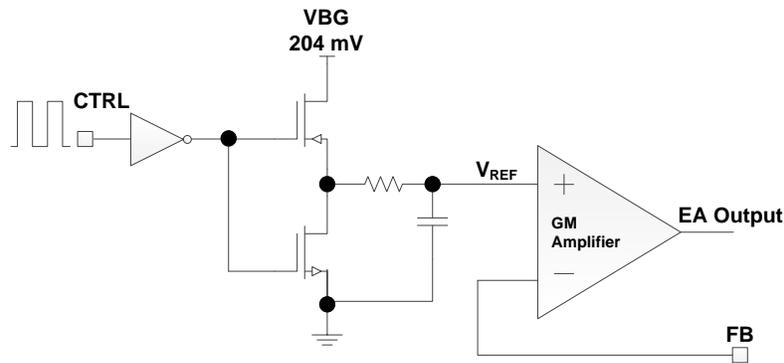


Figure 2. Internal Low-Pass Filter to Error Amplifier

### 2.3 Offset Voltage in Error Amplifier

Offset voltage is a non-zero value of a differential input created when the inputs of the GM amplifier are not exactly matched. It can be modeled as shown in Figure 3.

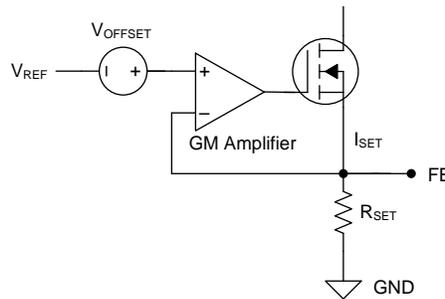


Figure 3. Offset Voltage Model

Table 1. Typical Voltage Offset

Device	TPS61158	TPS61160/61	TPS61162A/63A	TPS61165	TPS61169
Voltage offset (mV)	0.039	0.68	1.27	0.83	8.6

### 3 TPS61162A/3A Special Cases

The TPS61162A/63A are the only devices listed in Table 1 that use a 9-bit ADC to convert the low-pass filtered PWM signal-to-digital current values. Figure 4 is the block diagram of the front end before the error amplifier. This creates special cases as described below.

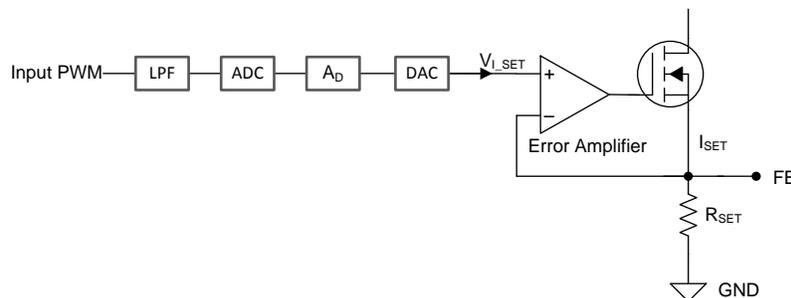


Figure 4. TPS61162A/TPS61163A Error Amplifier Block Diagram

### 3.1 Hysteresis

Hysteresis is the system dependence on the history of the previous current. It prevents any PWM jitter from feeding through to the LED current by preventing duty-cycle-to-LED current changes until the duty cycle overcomes 2 LSBs after a change in direction.

The minimum current the TPS61162A/TPS61163A can supply is  $3 \times I_{\text{FULL SCALE}} / 512$  and supplies this current as soon as a measurable PWM signal is detected. Furthermore, when using the device at either maximum or minimum ADC values to output  $3 \times I_{\text{FULL SCALE}} / 512$  or  $I_{\text{FULL SCALE}}$ , the hysteresis holds these values for longer, typically about 3 LSBs, as opposed the 2 LSBs of hysteresis in the intermediate steps (see Figure 5).

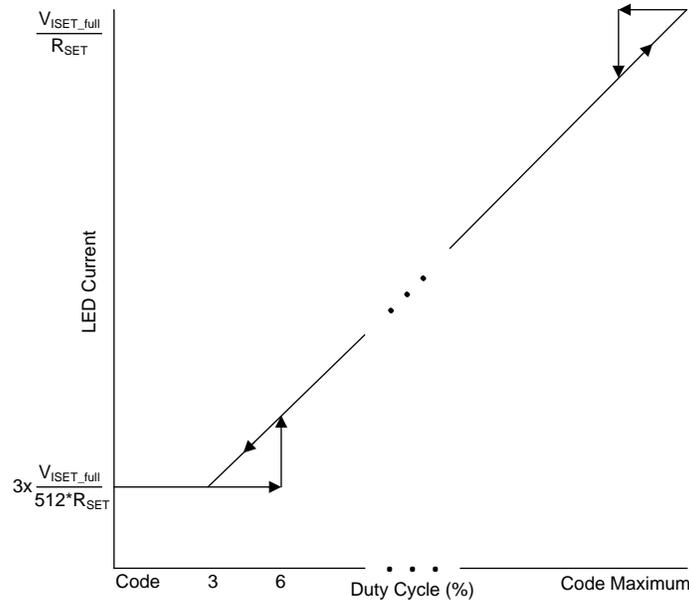


Figure 5. Hysteresis

### 3.2 Resolution

The TPS61162A/63A has a 9-bit ADC, which provides for a minimum of  $I_{\text{FULL SCALE}} / 512$  increment in LED current. Any PWM signal with greater than 9-bit resolution steps still results in 9-bit incremented current steps.



Figure 6. Incrementation Effects on Resolution

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated