

Using the LP8860-Q1 for Low EMI Automotive Designs

Cecilia Reyes

ABSTRACT

The LP8860-Q1 device is an automotive high-efficiency, four-channel LED driver with a boost controller typically used in automotive backlight applications such as infotainment and instrument clusters. Automotive electronics must comply with EMI regulations, and CISPR 25 standards are normally followed for measurements. This application note depicts the impact of various component and device register level changes on conducted EMI emissions. Measurement plots shown in [Section 4](#) of this application note were taken at an external compliance laboratory and provide a good idea for the level of conducted emission from the LP8860 EMI EVM. Note that measurements shown in other sections of this application note were taken in an in-house measurement setup, which is not fully calibrated to standard requirements. These measurements taken from the in-house setup are useful for gaining insight into how various changes may impact EMI but they should not be used for drawing any conclusions about absolute level of conducted emissions.

Contents

1	Test Setup and Conditions	3
2	Overview of Tests.....	5
3	Results for Conducted EMI Testing and Variations	5
4	Conducted Emissions Measurements at External Compliance Laboratory	18
5	Summary	19

List of Figures

1	Top Layer of PCB Layout of LP8860-Q1 EMI Test Board	3
2	Top View of LP8860-Q1 EMI Test Board.....	3
3	Schematic of LP8860-Q1 EMI Test Board	3
4	Schematic of LP8860-Q1 EMI Test Board	4
5	Boost Section of LP8860-Q1 EMI Test Board	5
6	Low Frequency: $f_{sw} = 2.2$ MHz.....	5
7	Low Frequency: $f_{sw} = 300$ kHz.....	5
8	High Frequency: $f_{sw} = 2.2$ MHz	5
9	High Frequency: $f_{sw} = 300$ kHz	5
10	Circuit With Boost Input Filter: Pi Filter	7
11	Low Frequency: Pi Filter Used	7
12	Low Frequency: Bypassed Pi Filter	7
13	High Frequency: Pi Filter Used	7
14	High Frequency: Bypassed Pi Filter.....	7
15	Circuit With Boost Input Filter: CM Choke.....	8
16	Low Frequency: Used CM Choke	8
17	Low Frequency: Bypassed CM Choke.....	8
18	High Frequency: Used CM Choke.....	8
19	High Frequency: Bypassed CM Choke	8
20	Circuit With Boost Input Filter: Ferrite Bead.....	9
21	Low Frequency: Used Ferrite Bead	9

22	Low Frequency: Bypassed Ferrite Bead.....	9
23	High Frequency: Used Ferrite Bead.....	9
24	High Frequency: Bypassed Ferrite Bead.....	9
25	Circuit Using Snubbers.....	10
26	Low Frequency: Populated Snubber on GD of SW FET.....	10
27	Low Frequency: Unpopulated Snubber on GD of SW FET.....	10
28	High Frequency: Populated Snubber on GD of SW FET.....	10
29	Low Frequency: Unpopulated Snubber on GD of SW FET.....	10
30	Low Frequency: Used Snubber on SW Node.....	11
31	Low Frequency: Removed Snubber on SW Node.....	11
32	High Frequency: Used Snubber on SW Node.....	11
33	High Frequency: Removed Snubber on SW Node.....	11
34	Circuit With Capacitors Between Boost Out and LED Drive.....	12
35	Low Frequency: No Capacitors.....	12
36	Low Frequency: Capacitors between Boost OUT and LED Drivers.....	12
37	High Frequency: No Capacitors.....	12
38	High Frequency: Capacitors Between Boost OUT and LED Drivers.....	12
39	Circuit With Capacitors Between LED Drivers and GND.....	13
40	Low Frequency: No Capacitors.....	13
41	Low Frequency: Capacitors between LED Drivers and GND.....	13
42	High Frequency: No Capacitors.....	13
43	High Frequency: Capacitors between LED Drivers and GND.....	13
44	Low Frequency: Spread Spectrum Disabled.....	14
45	Low Frequency: Spread Spectrum Enabled.....	14
46	High Frequency: Spread Spectrum Disabled.....	14
47	High Frequency: Spread Spectrum Enabled.....	14
48	Low Frequency: 120 mA.....	15
49	Low Frequency: 80 mA.....	15
50	High Frequency: 120 mA.....	15
51	High Frequency: 80 mA.....	15
52	Low Frequency: 100% Brightness.....	16
53	Low Frequency: 10% Brightness.....	16
54	High Frequency: 100% Brightness.....	16
55	High Frequency: 10% Brightness.....	16
56	Low Frequency: $V_{IN} = 12\text{ V}$	17
57	Low Frequency: $V_{IN} = 9\text{ V}$	17
58	High Frequency: $V_{IN} = 12\text{ V}$	17
59	High Frequency: $V_{IN} = 9\text{ V}$	17
60	Conducted Emissions for 2.2-MHz Line.....	18
61	Conducted Emissions for 2.2-MHz Return.....	18
62	Conducted Emissions for 400-kHz Line.....	19
63	Conducted Emissions for 400-kHz Return.....	19

Trademarks

All trademarks are the property of their respective owners.

1 Test Setup and Conditions

1.1 EVM Layout and Schematic

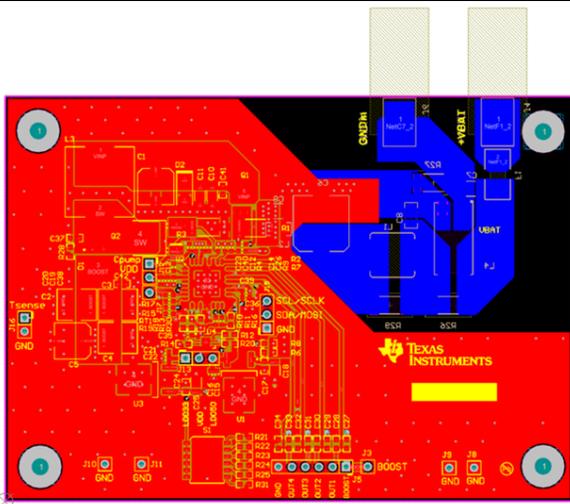


Figure 1. Top Layer of PCB Layout of LP8860-Q1 EMI Test Board

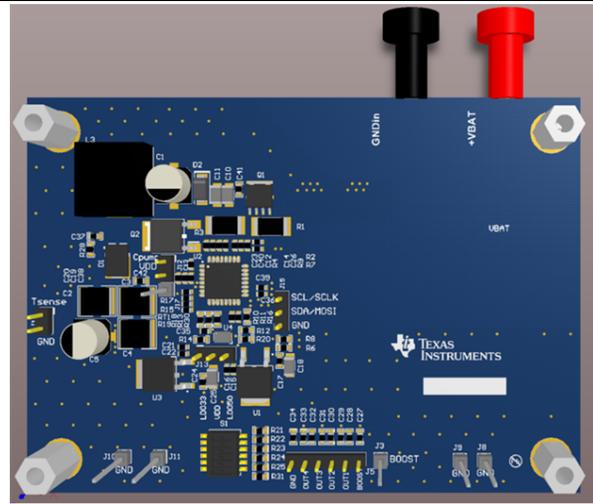


Figure 2. Top View of LP8860-Q1 EMI Test Board

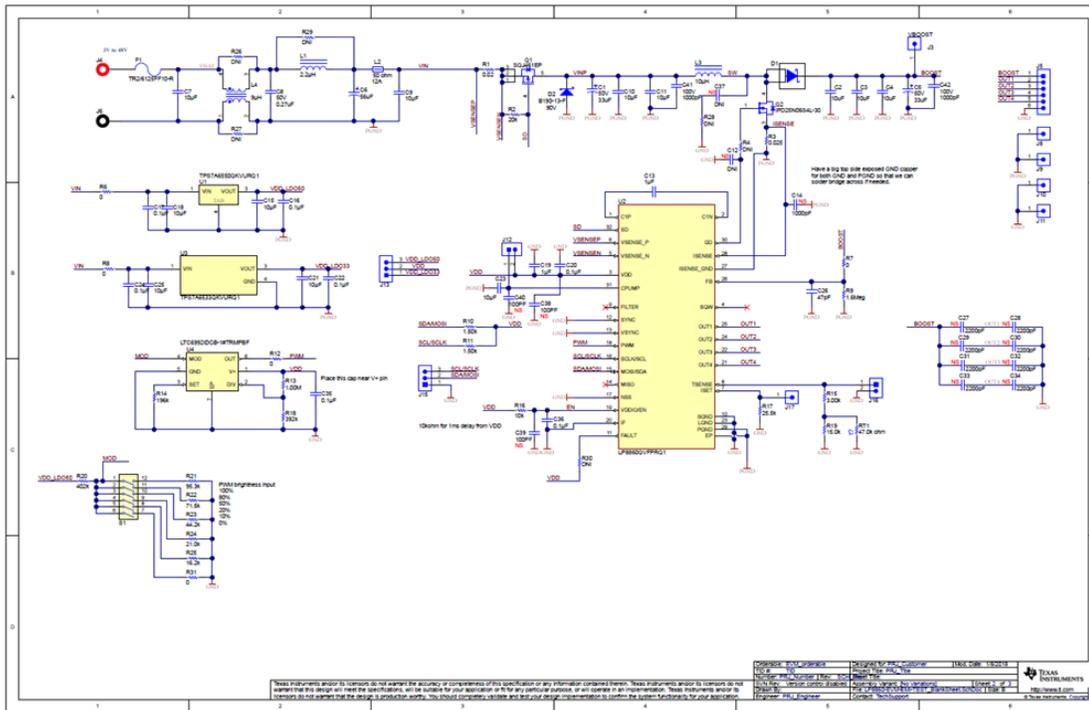


Figure 3. Schematic of LP8860-Q1 EMI Test Board

1.2 Diagram of Test Setup

Under CISPR 25 Standards, the setup in Figure 4 was prepared for the LP8860-Q1 EMI test board.

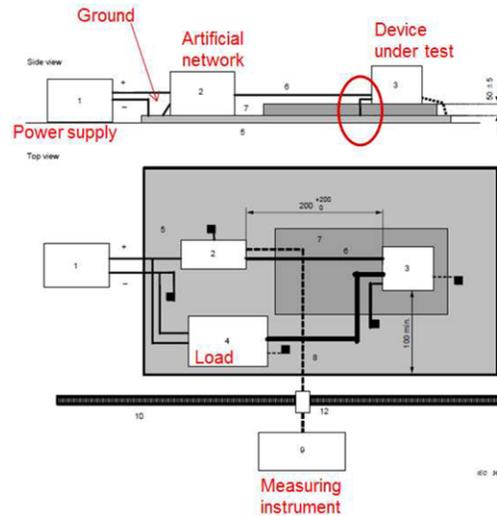


Figure 4. Schematic of LP8860-Q1 EMI Test Board

1.3 Equipment and Testing Conditions

The default conditions for the LP8860-Q1 EVM defined below were used in an internal debugging chamber.

- Equipment : Rhode and Schwarz Spectrum Analyzer
- Frequency ranges measured
 - Low frequency: 150 kHz to 30 MHz
 - High frequency: 30 MHz to 108 MHz
- Default setting parameters
 - $V_{IN} = 12\text{ V}$
 - $V_{OUT} = 36\text{ V}$, 11 LEDs
 - Switching frequency: 2.2 MHz
 - LED channels: 4
 - LED current per string: 120 mA
 - Boost input filters (pi filter, common mode choke, and ferrite bead) used
 - Snubbers used
 - Spread spectrum disabled
 - Charge pump enabled

2 Overview of Tests

VARIATIONS	DETAILS
Boost switching frequency	300 kHz and default: 2.2 MHz (boost inductor, boost input capacitance and boost output capacitance were adjusted to correct values for SW frequency)
Boost input filter : Pi filter	Use or bypass
Boost input filter : Common mode choke	Use or bypass
Boost input filter : Ferrite bead	Use or bypass
Snubber on gate drive of SW FET, R4, C12	Use or not, Default : 5 Ω + 220 pF
Snubber on SW node, R28, C37	Use or not, Default : 5 Ω + 220 pF
Capacitors between boost out and LED drivers	Use 220 pF or not
Capacitors between LED drivers and GND	Use 220 pF or not
Spread spectrum	Enabled or not
LED current per string	120 mA, 80 mA
Dimming	100%, 10%
V_{IN}	12 V or 9 V

3 Results for Conducted EMI Testing and Variations

3.1 Boost Switching Frequency

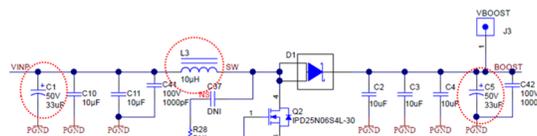


Figure 5. Boost Section of LP8860-Q1 EMI Test Board

Changing the boost switching frequency generally has the impact of moving the EMI peaks at that specific switching frequency and its harmonics to a different frequency range. If the application permits, changing the switching frequency can be an effective tool to move EMI peaks from the lower limit range to possibly a higher limit range. In addition, board parasitic and circuit element resonances may impact EMI behavior when switching frequency is changed and can possibly provide better EMI results. Changing the switching frequency can also help in avoiding system level interference with other components in the system.

Boost inductor, boost input capacitance and boost output capacitance were adjusted accordingly for the specified switching frequency. For the 300 kHz switching frequency, a 22- μ H inductor with all input and output capacitors populated. For the 2.2-MHz switching frequency, a 10- μ H inductor was used and C1 (33 μ F) and C5 (33 μ F) were both removed.

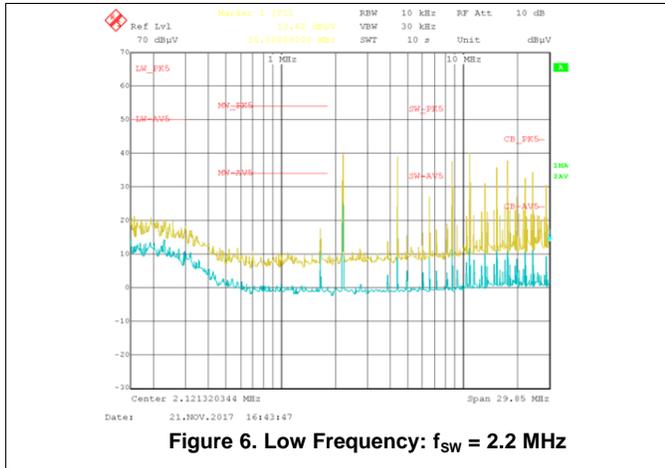


Figure 6. Low Frequency: $f_{SW} = 2.2 \text{ MHz}$

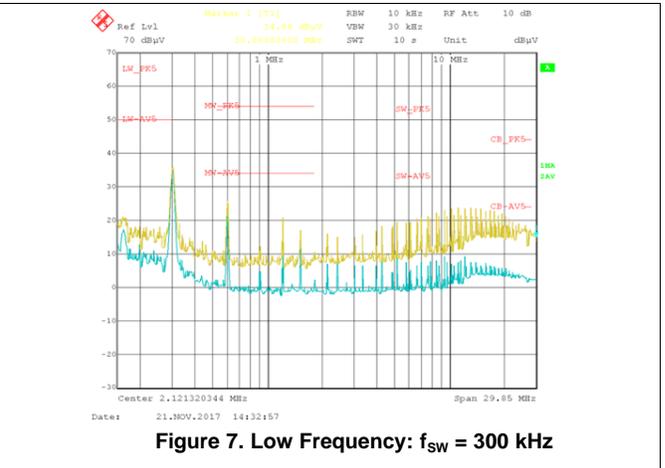


Figure 7. Low Frequency: $f_{SW} = 300 \text{ kHz}$

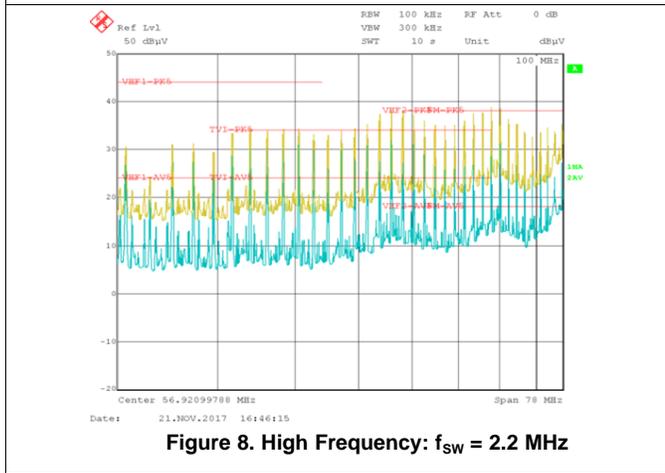


Figure 8. High Frequency: $f_{SW} = 2.2 \text{ MHz}$

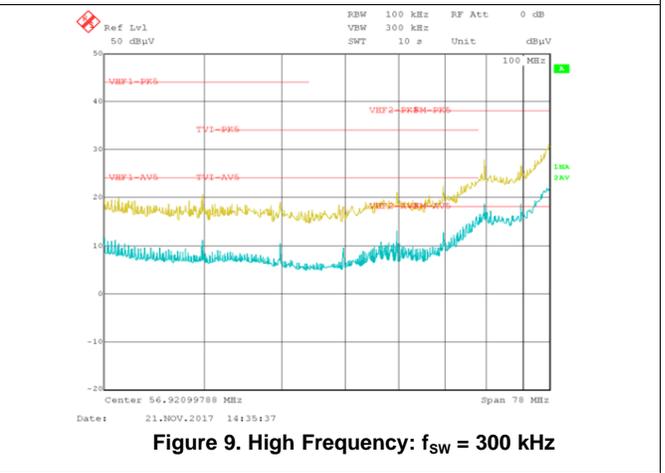


Figure 9. High Frequency: $f_{SW} = 300 \text{ kHz}$

3.2 Boost Input Filter: Pi Filter

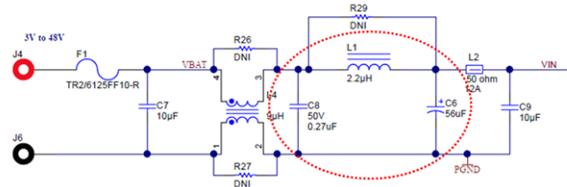


Figure 10. Circuit With Boost Input Filter: Pi Filter

The Pi filter is placed at the boost input of the EVM. The filter uses a 2.2- μ H inductor in between a 0.27- μ F capacitor at the input and 56- μ F capacitor at the output. Small and large capacitors were selected for this pi filter to reject both high and low frequencies thus reducing EMI as shown in the following test results. Values of these components can be appropriately changed to achieve EMI reduction at any given frequency of interest. See [AN-2162 Simple Success With Conducted EMI From DC-DC Converters](#) for filter component selection.

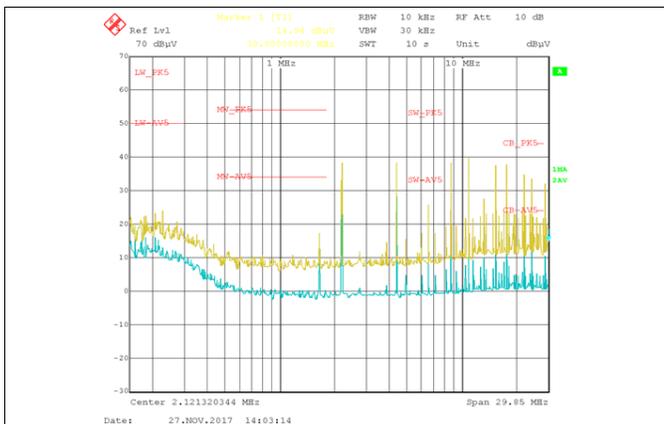


Figure 11. Low Frequency: Pi Filter Used

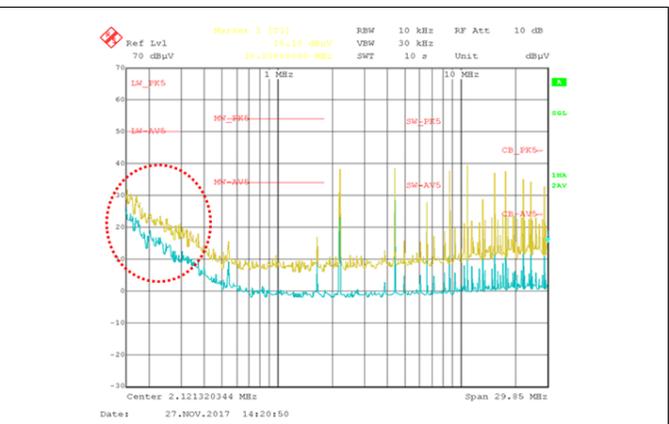


Figure 12. Low Frequency: Bypassed Pi Filter

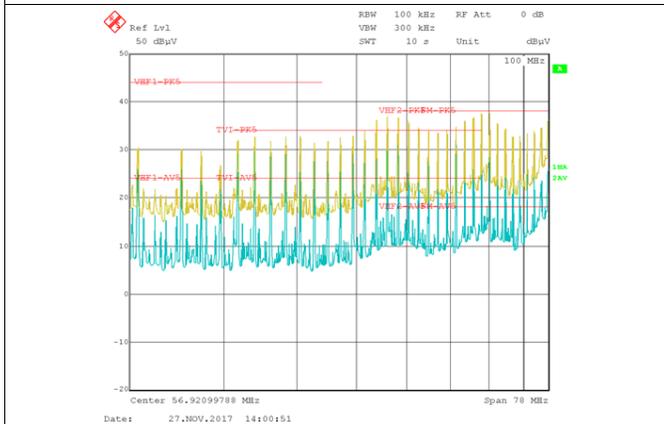


Figure 13. High Frequency: Pi Filter Used

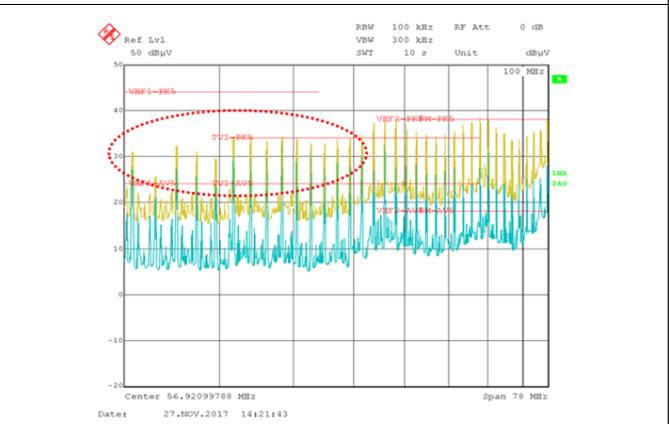


Figure 14. High Frequency: Bypassed Pi Filter

3.3 Boost Input Filter: CM Choke

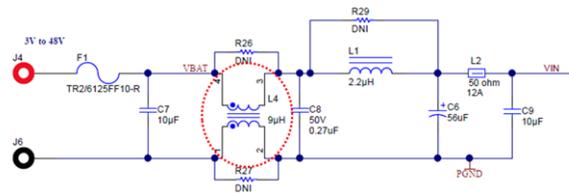


Figure 15. Circuit With Boost Input Filter: CM Choke

Due to the switching mechanism of boost converter circuits, the coupling of high-frequency currents to both line and neutral signal paths is a common scenario. For this reason, employing a common-mode choke at input/output terminals of the system can provide significant reduction in conducted noise. A common-mode choke has both line and neutral windings wound on a common ferrite core, which helps in presenting higher impedance to noise currents compared to inductors wound on separate cores. Various common-mode chokes are available and present high impedance at different frequencies. Consult data sheet impedance graphs to choose an appropriate component for a particular need. This EVM uses a 9- μH inductance common-mode choke in its design which is placed at the input of the power supply to the boost converter. The following results show a significant difference with and without the common-mode choke.

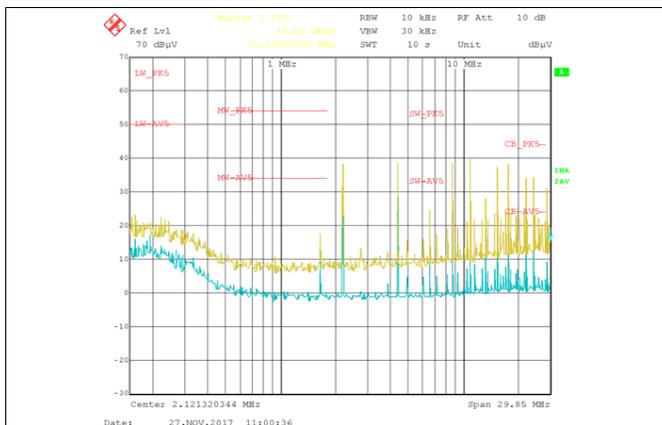


Figure 16. Low Frequency: Used CM Choke

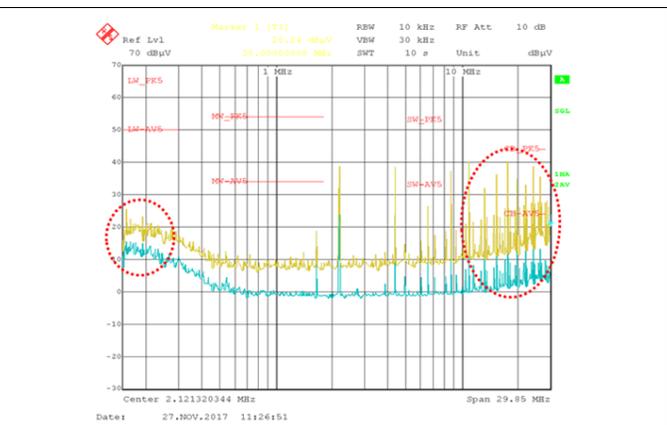


Figure 17. Low Frequency: Bypassed CM Choke

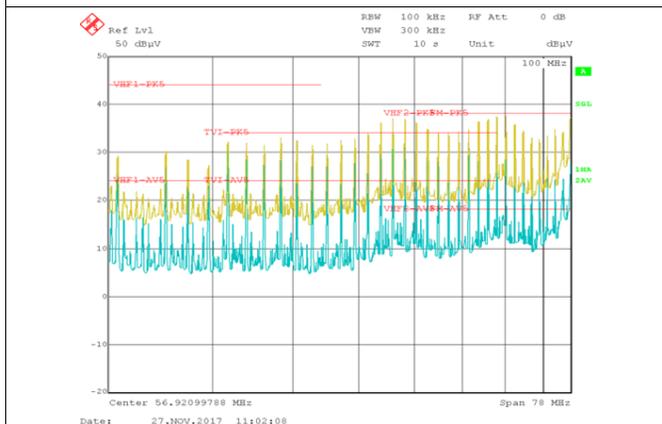


Figure 18. High Frequency: Used CM Choke

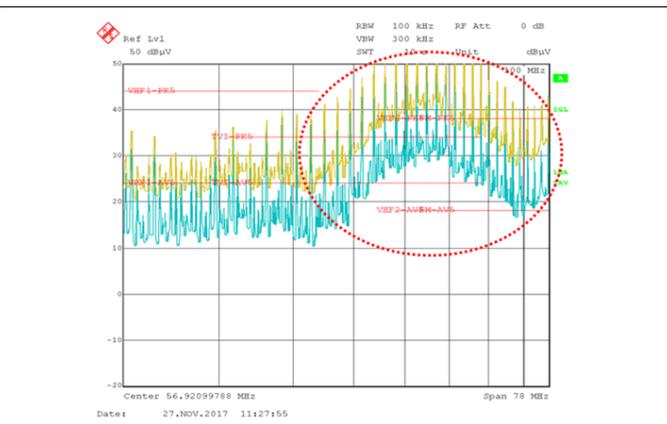


Figure 19. High Frequency: Bypassed CM Choke

3.4 Boost Input Filter: Ferrite Bead

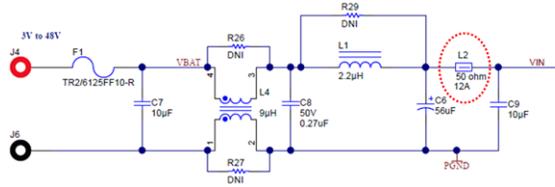


Figure 20. Circuit With Boost Input Filter: Ferrite Bead

A ferrite-bead filter is placed in series with the power supply of the boost converter to provide additional attenuation to noise. Similar to a common-mode choke, many different ferrite bead components are available to address various frequency ranges. Consult component data sheets to select the appropriate component for application needs. In addition to appropriate impedance characteristics, check the current-handling capability of the ferrite bead to ensure adequacy for a particular application.

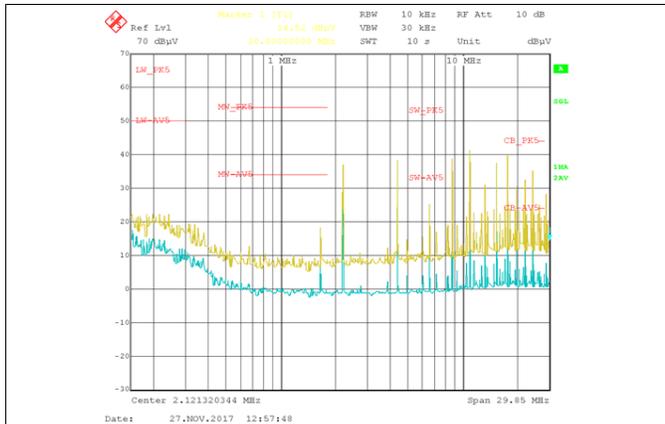


Figure 21. Low Frequency: Used Ferrite Bead

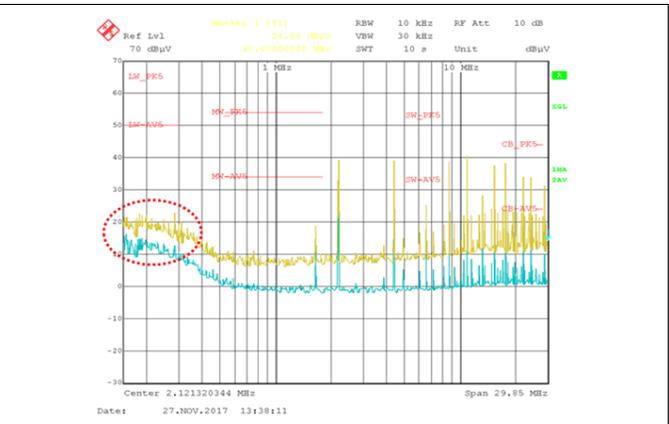


Figure 22. Low Frequency: Bypassed Ferrite Bead

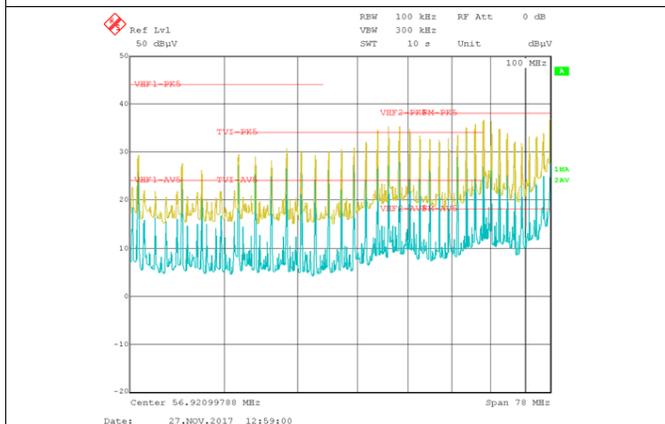


Figure 23. High Frequency: Used Ferrite Bead

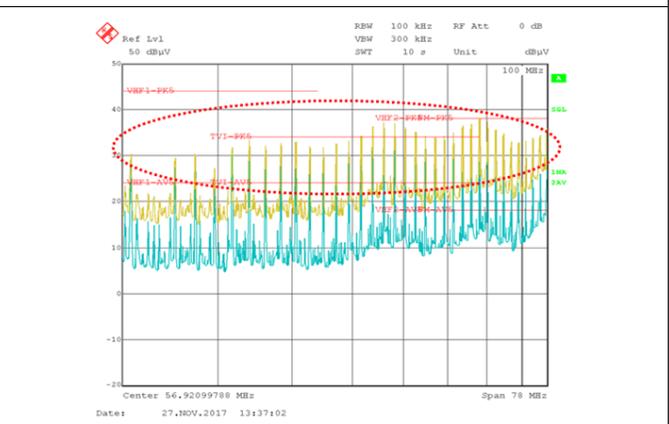


Figure 24. High Frequency: Bypassed Ferrite Bead

3.5 Snubbers


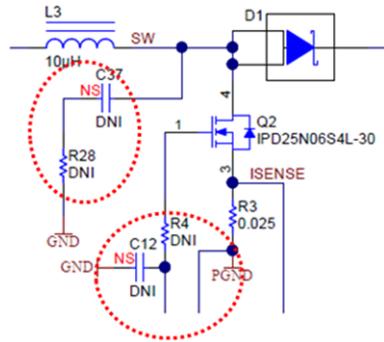
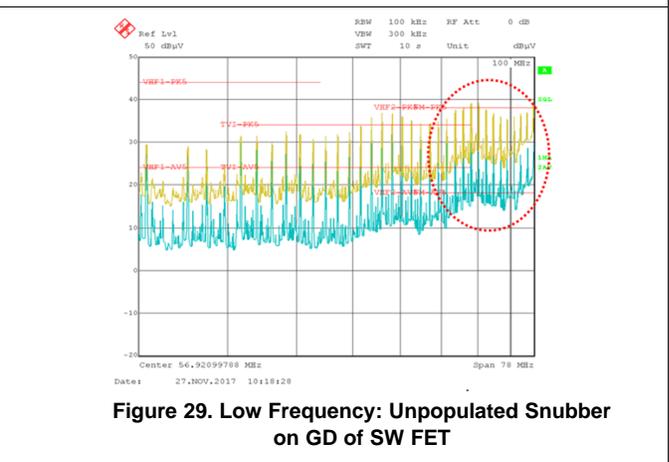
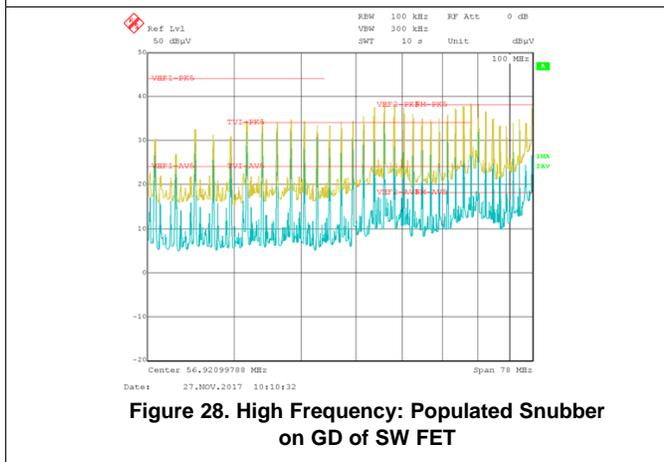
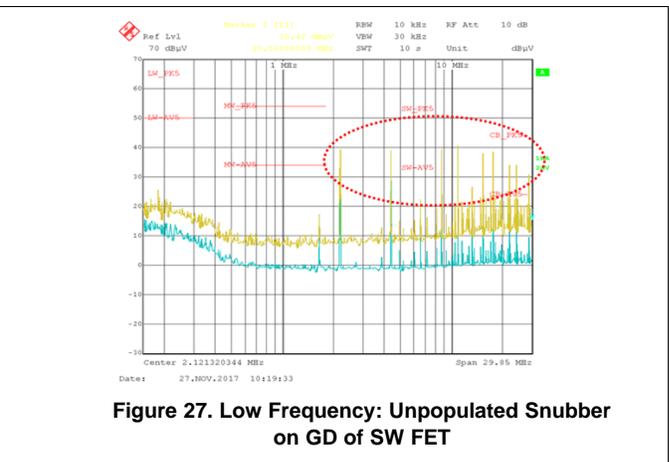


Figure 25. Circuit Using Snubbers





Snubbers on fast switching nodes can be used to reduce rise/fall times of the signal and can be an effective tool to reduce EMI. Choose values carefully so that rise and fall times are not excessively slowed. Slower rise/fall times can lead to higher power dissipation in the switching device, thereby reducing overall efficiency. They are also a concern for thermal and heat dissipation.

This EVM uses two snubbers. A 5-Ω resistor, 220-pF capacitor (R4 and C12) are placed on the gate driver of the switching FET while a second 5-Ω resistor, 220-pF capacitor (R28 and C37) are placed on the switching node of the boost.

3.5.1 On-Gate Drive of Switching FET

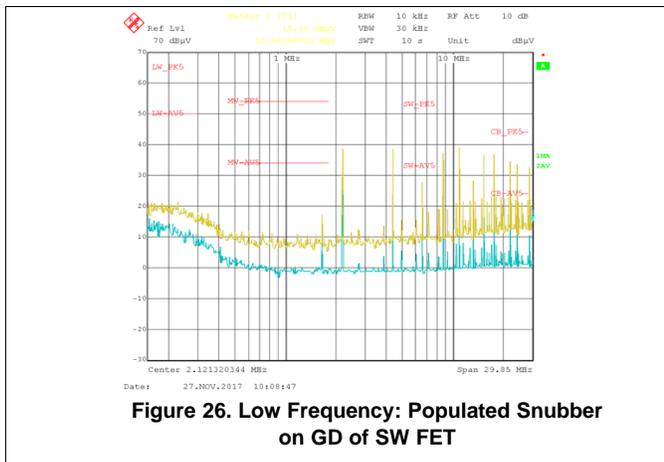

3.5.2 Snubber on SW Node

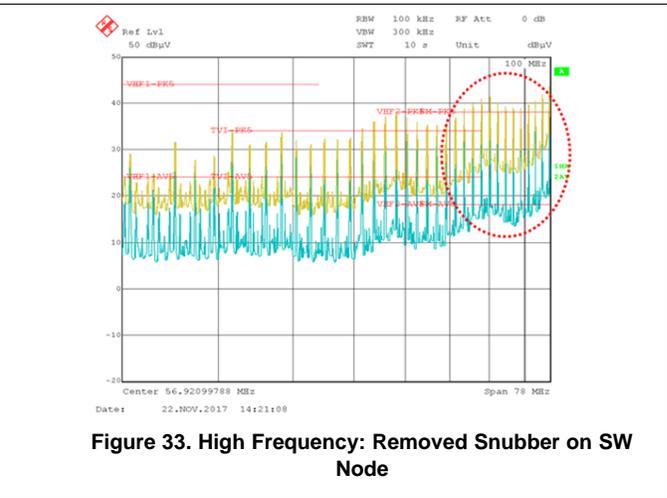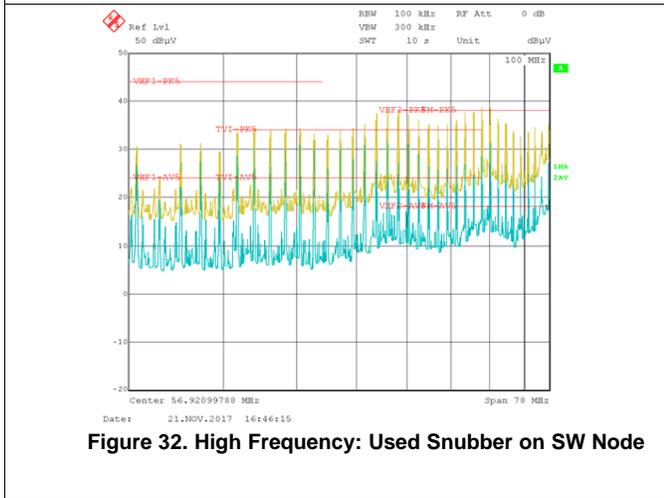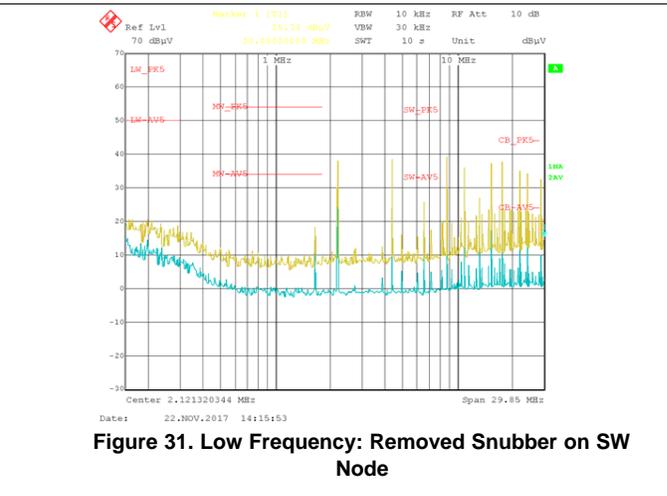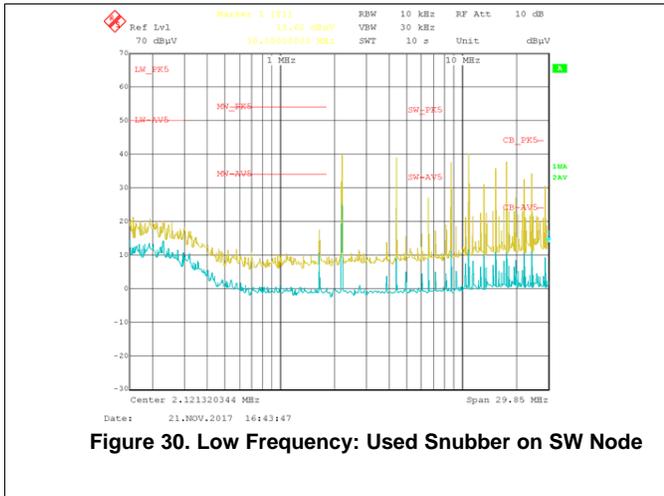

3.6 Capacitors Between Boost Out and LED Drive

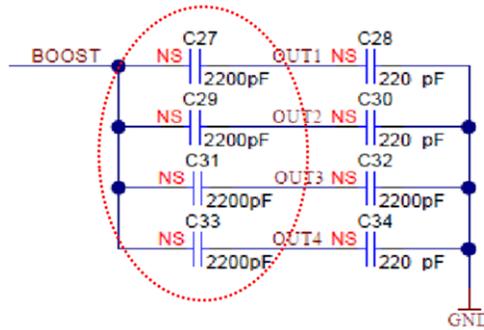


Figure 34. Circuit With Capacitors Between Boost Out and LED Drive

This variation includes 2.2-nF capacitors placed in between the boost and output of LED drivers. The capacitors provide protection in the case of a short at the boost output and prevent ESD damage. While this option is available for protection in the case of an accidental short between boost output and current sinks, it generally increases the EMI and is not recommended from a purely EMI perspective.

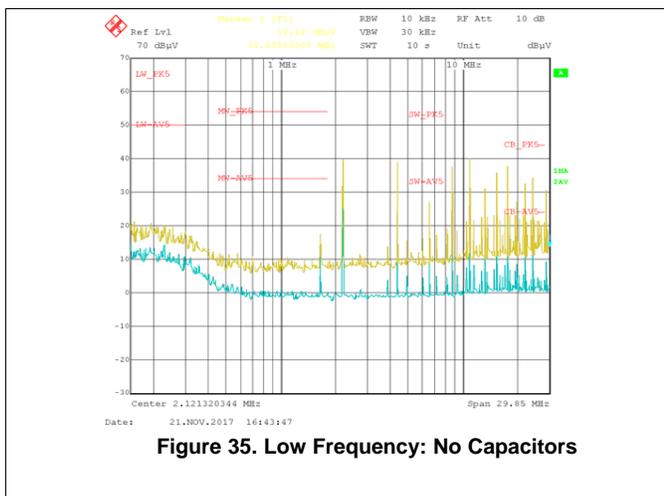


Figure 35. Low Frequency: No Capacitors

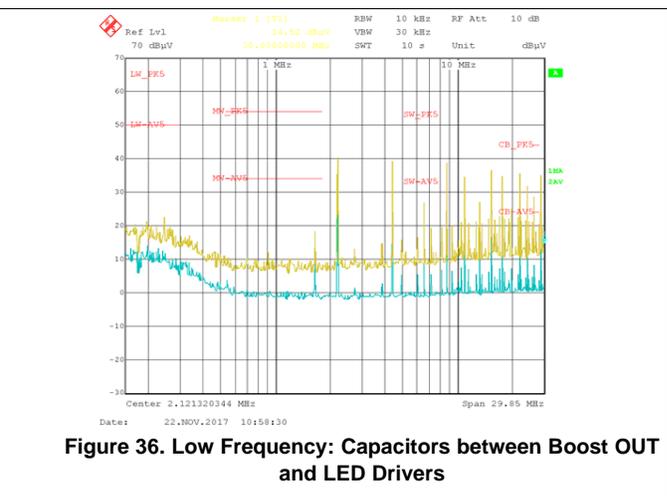


Figure 36. Low Frequency: Capacitors between Boost OUT and LED Drivers

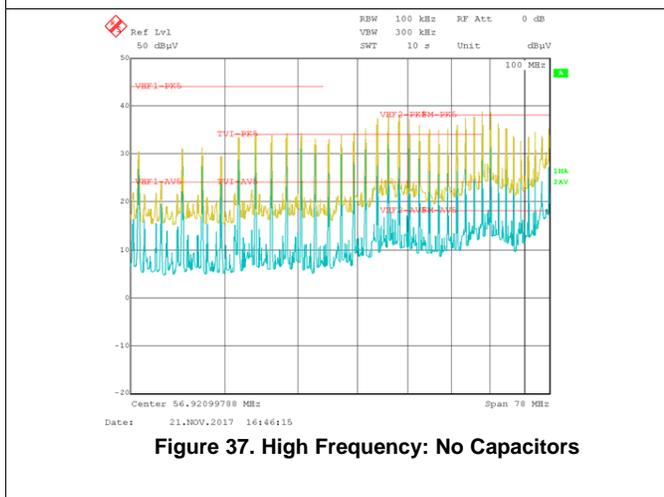


Figure 37. High Frequency: No Capacitors

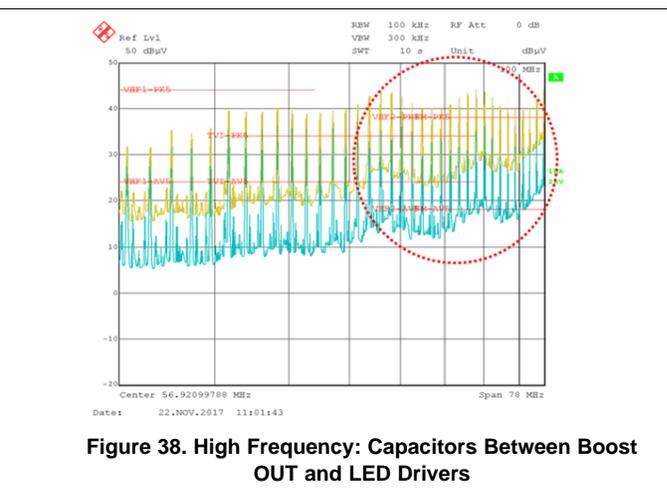


Figure 38. High Frequency: Capacitors Between Boost OUT and LED Drivers

3.7 Capacitors Between LED Drivers and GND

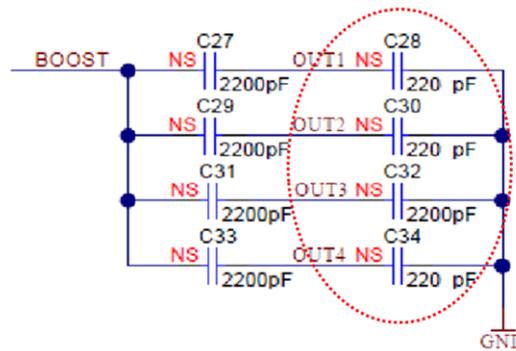


Figure 39. Circuit With Capacitors Between LED Drivers and GND

This variation includes 220-pF capacitors connected between LED driver inputs and ground. These capacitors are used to slow down LED current edge and lower its ripple to achieve accurate current control. By using these capacitors, EMI levels can be attenuated; however, take care not to excessively slow down the LED current rise time. The rise time defines the minimum current pulse width and limits the highest achievable dimming ratio.

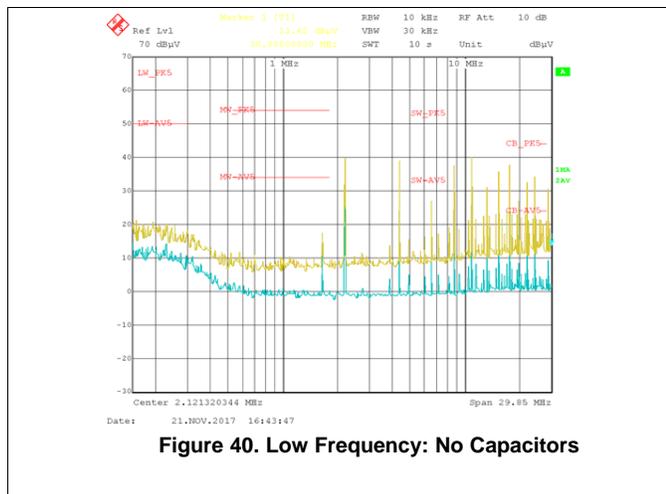


Figure 40. Low Frequency: No Capacitors

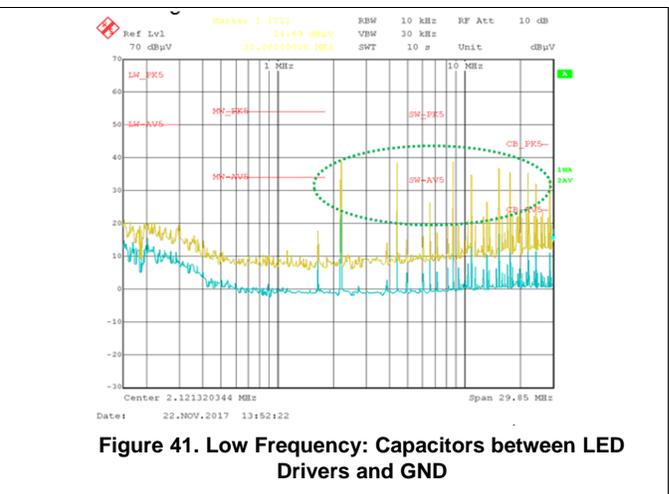


Figure 41. Low Frequency: Capacitors between LED Drivers and GND

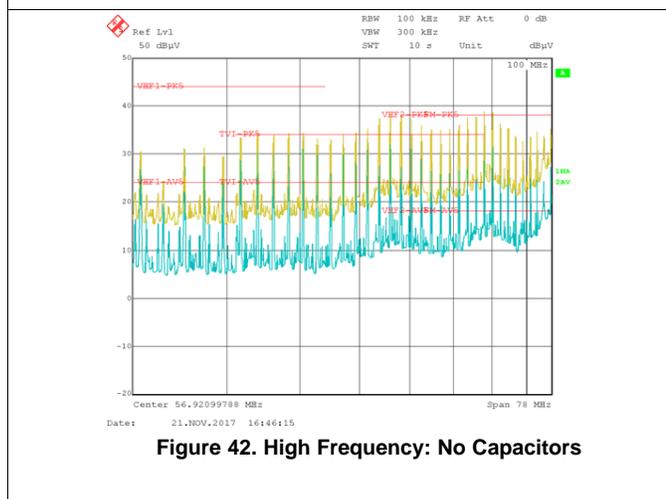


Figure 42. High Frequency: No Capacitors


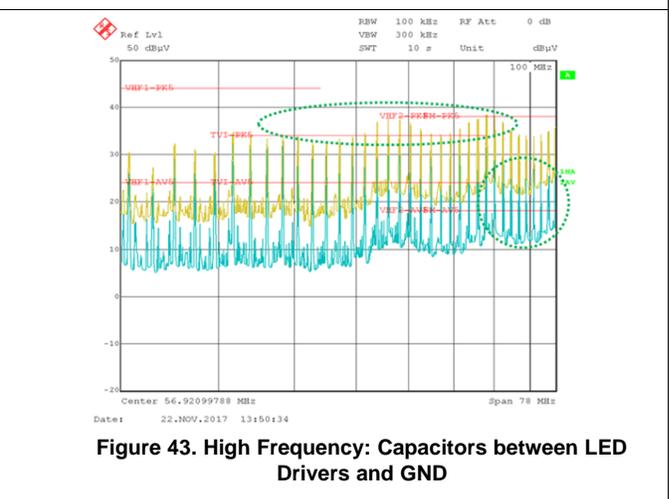
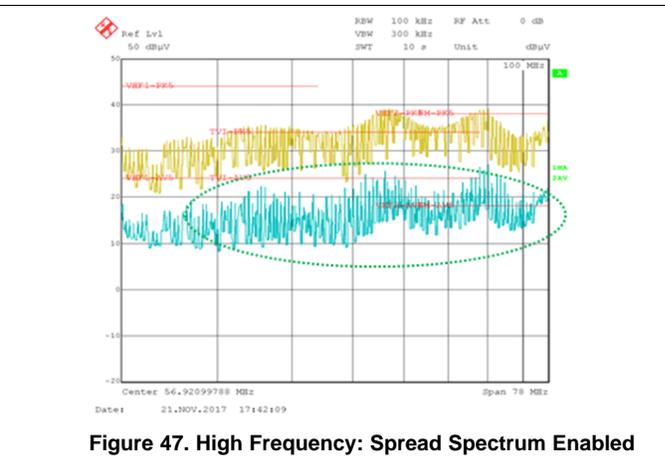
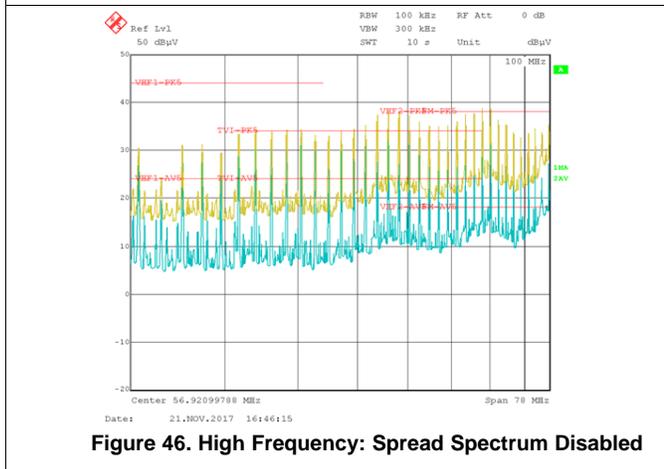
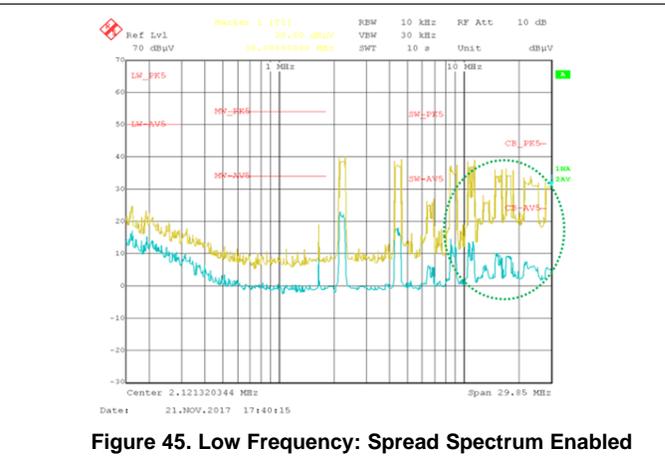


Figure 43. High Frequency: Capacitors between LED Drivers and GND

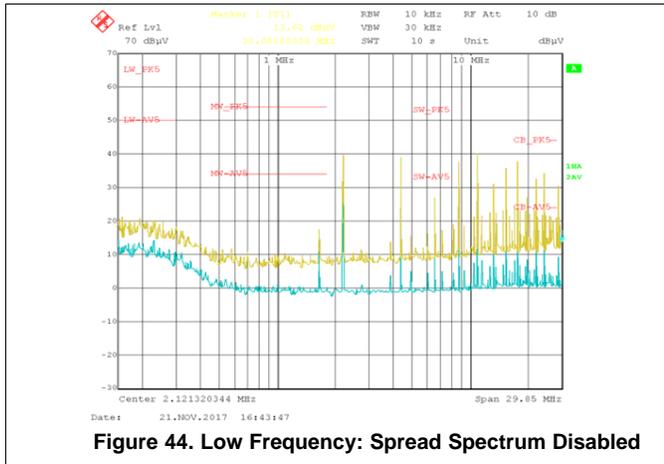3.8 Spread Spectrum: On or Off

The LP8860-Q1 EVM has a feature for dithering or spreading the switching frequency in a wider bandwidth. Spreading the energy of the switching frequency over a wider bandwidth has the impact of reducing the peak energy at one frequency. This reduces the spikes at the switching frequency and its harmonics, which in turn generally reduces EMI. When enabled, the test results revealed that the EMI from the average measurements over high frequencies were significantly reduced.



3.9 LED Current per String

LED current on all strings was reduced from its maximum 120 mA to 80 mA. The results show EMI reduction in the higher frequencies range.

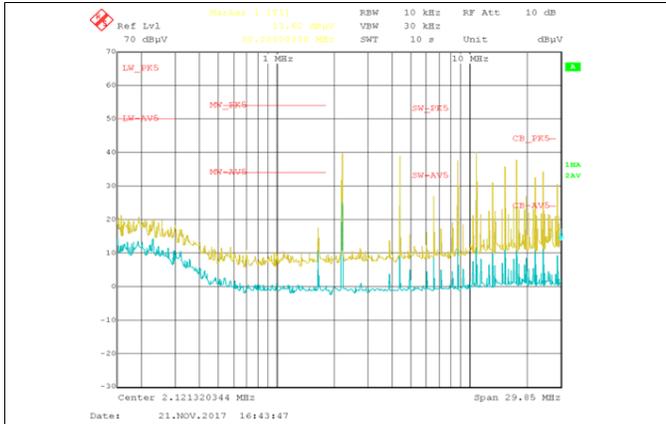


Figure 48. Low Frequency: 120 mA

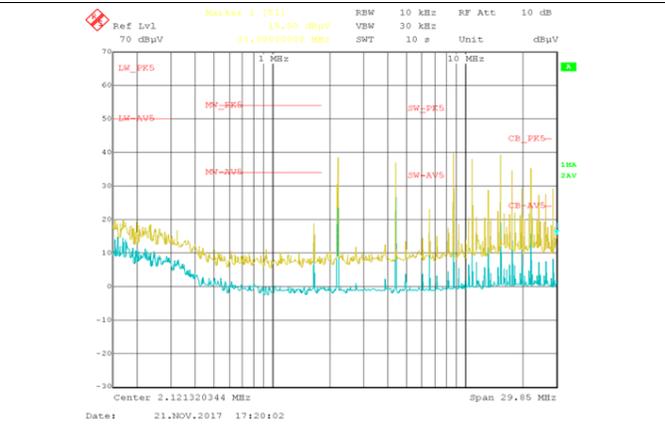


Figure 49. Low Frequency: 80 mA

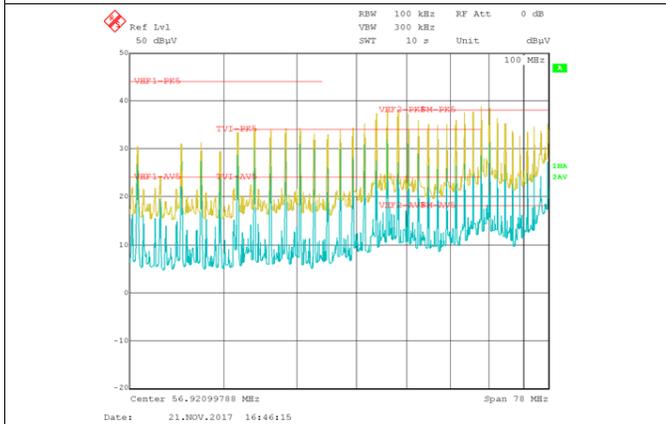


Figure 50. High Frequency: 120 mA

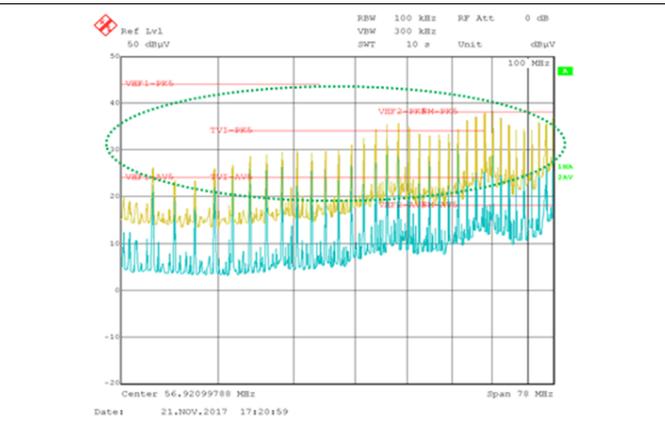


Figure 51. High Frequency: 80 mA

3.10 Dimming

Dimming was reduced from 100% to 10% by varying the PWM duty cycle to show its large impact on EMI on the LP8860-Q1 EMI test board. As expected, due to LED current being on all the time and not switching at 100% PWM duty cycle, EMI levels are generally lower.

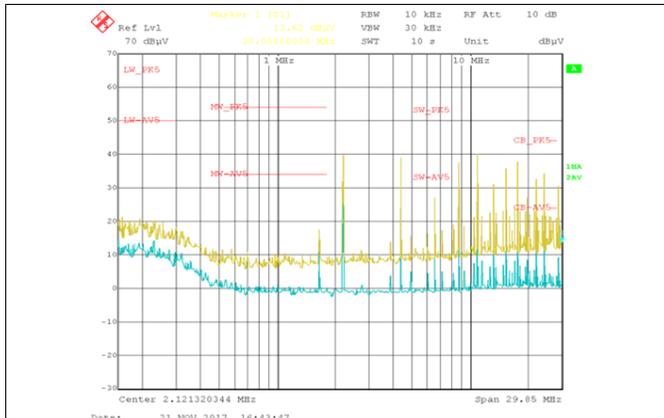


Figure 52. Low Frequency: 100% Brightness

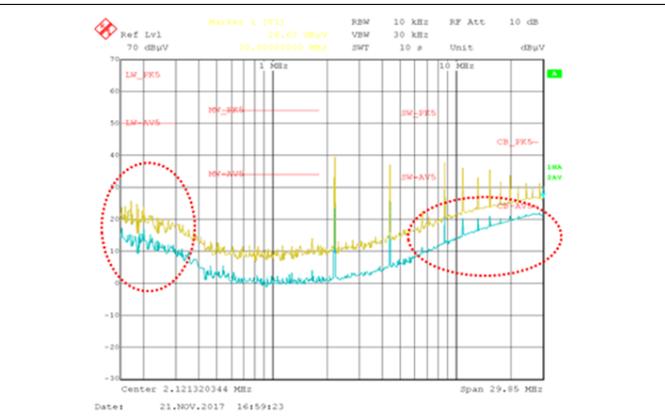


Figure 53. Low Frequency: 10% Brightness

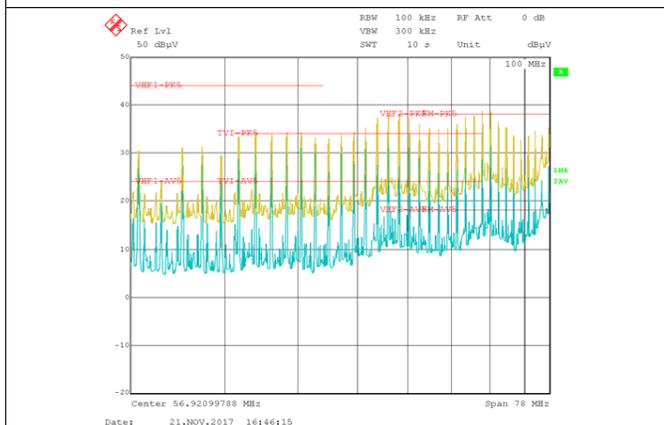


Figure 54. High Frequency: 100% Brightness

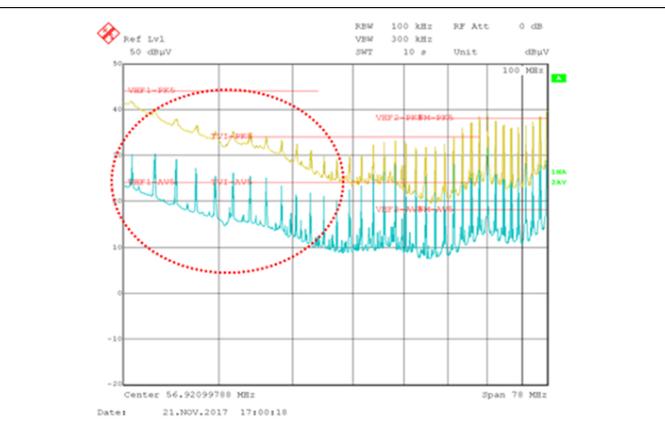


Figure 55. High Frequency: 10% Brightness

3.11 Input Voltage (V_{IN})

The input voltage was reduced from 12 V to 9 V to observe the effects on EMI. As the input voltage decreased, the switching current increased resulting in increased EMI.

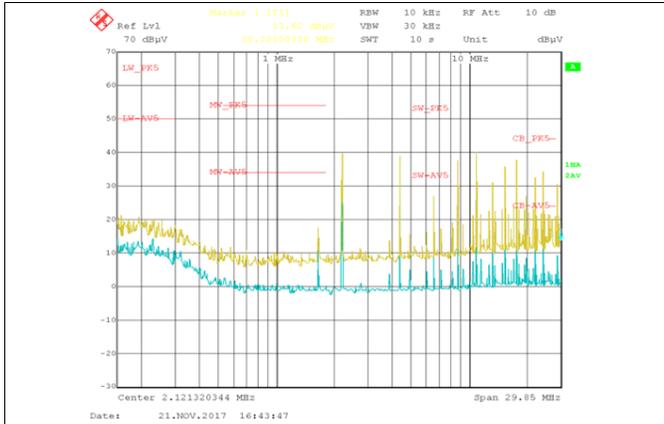


Figure 56. Low Frequency: $V_{IN} = 12\text{ V}$

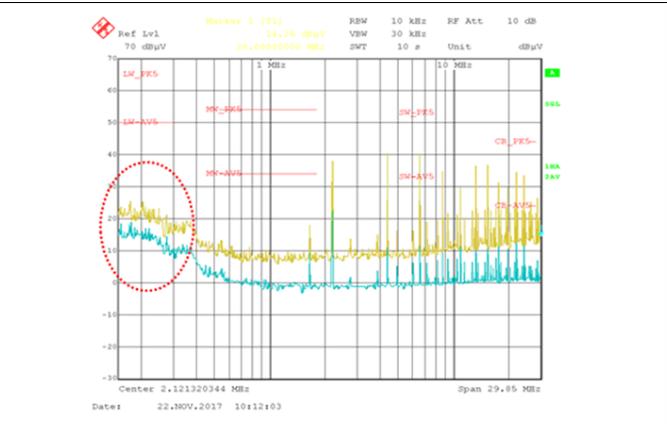


Figure 57. Low Frequency: $V_{IN} = 9\text{ V}$

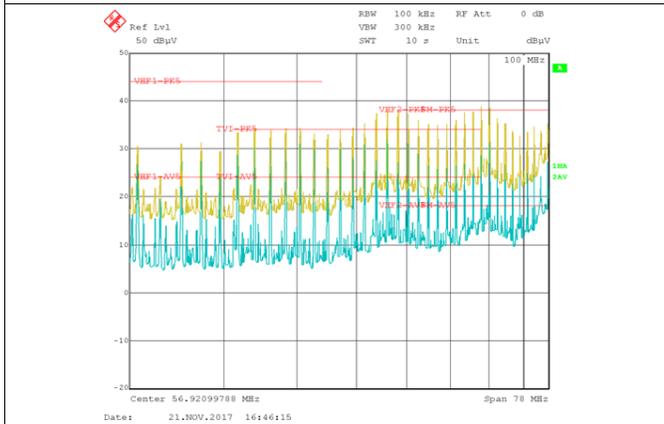


Figure 58. High Frequency: $V_{IN} = 12\text{ V}$

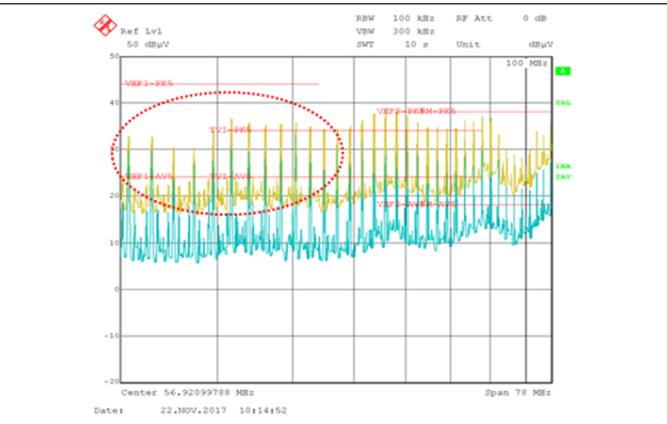


Figure 59. High Frequency: $V_{IN} = 9\text{ V}$

4 Conducted Emissions Measurements at External Compliance Laboratory

The following plots show the results of conducted emissions testing performed at an external compliance laboratory. These results provide good indication that with proper design techniques, EMI compliance success can be achieved with the LP8860-Q1 device.

Test conditions for this testing are as follows:

2.2-MHz EEPROM Configurations:

- Switching frequency : 2.2MHz
- 2x charge pump enabled
- Spread spectrum disabled
- V_{DD} : 3.3 V
- 4 LED strings, 10 LEDs/string
- Maximum LED current per channel : 120 mA
- Brightness control : PWM input pin
- PWM dimming frequency : 4.883 KHz
- Internal 5MHz oscillator used

400-kHz EEPROM Configuration

- Switching frequency : 400 KHz
- 2x charge pump enabled
- Spread spectrum enabled
- V_{DD} : 3.3V
- 4 LED strings, 10 LEDs/string
- Maximum LED current per channel : 120 mA
- Brightness control : PWM input pin
- PWM dimming frequency : 4.883 KHz
- Internal 5-MHz oscillator used

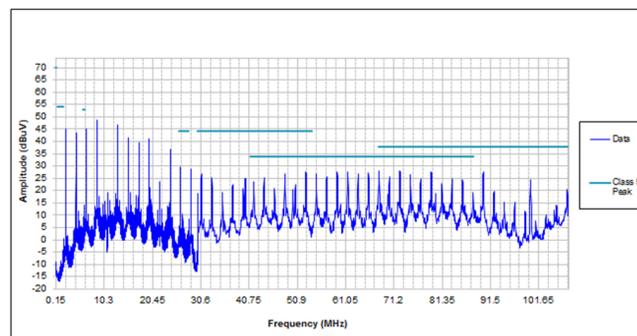


Figure 60. Conducted Emissions for 2.2-MHz Line

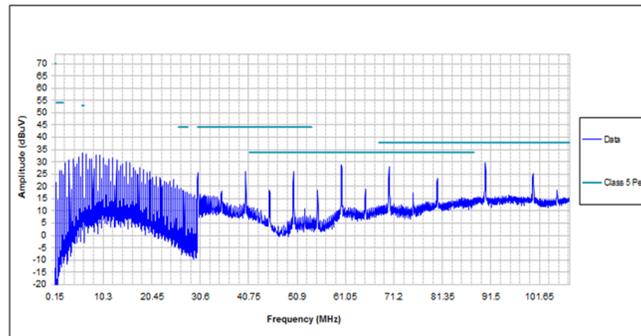


Figure 61. Conducted Emissions for 2.2-MHz Return

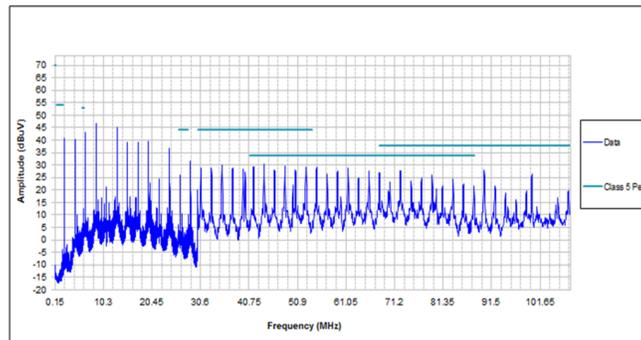


Figure 62. Conducted Emissions for 400-kHz Line

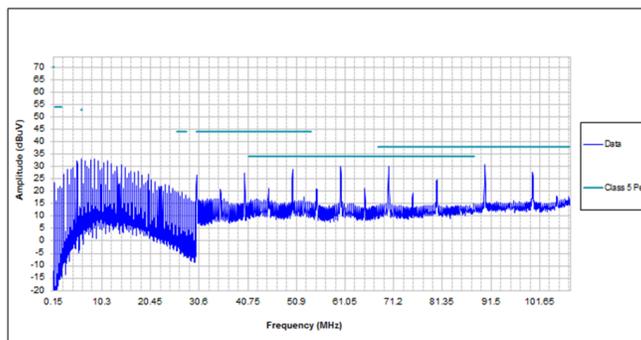


Figure 63. Conducted Emissions for 400-kHz Return

5 Summary

This application note compiles EMI measurements taken under varying board conditions to show relative impact of the changes. This should aid system designers in coming up with appropriate tradeoffs to achieve high performing emissions compliant backlight designs. As pointed out in various sections of this document, care should be taken and impacts should be well understood when implementing EMI solutions so as not to cause performance or system reliability issues. The setup of these measurements is not calibrated and absolute readings of the emissions plot are not meaningful. The collected data should be used as reference to see the relative impact of board level changes on conducted emissions.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated