

# User's Guide

## AM26x Hardware Design Guidelines



### ABSTRACT

The AM26x Hardware Design Guidelines is an essential document for hardware designers creating PCB systems based on the AM26x family of MCU devices. This document serves to integrate device-specific schematic and PCB layout recommendations by utilizing hardware design examples from the various AM263x, AM263Px, and AM261x evaluation modules (EVMs). The AM26x EVMs include the following hardware platforms:

**Table 1-1. AM26x Evaluation Module (EVM) Platforms**

Device Family	Hardware Platform		
	LaunchPad	ControlCARD	System on Module (SOM)
AM263x	<a href="#">LP-AM263</a>	<a href="#">TMDSCNCD263</a>	
AM263Px	<a href="#">LP-AM263P</a>	<a href="#">TMDSCNCD263P</a>	
AM261x	<a href="#">LP-AM261</a>		<a href="#">AM261-SOM-EVM</a>

In general, AM26x LaunchPads are lower-cost, entry-level evaluation platforms, while ControlCARDs and SOMs are meant for engineers designing complex systems with higher I/O requirements.

Additional collateral documents and tools can be found in [Section 16](#).

### Table of Contents

<b>1 Introduction</b>	<b>5</b>
<b>2 Power</b>	<b>10</b>
2.1 Discrete DC-DC Power Solution	11
2.2 Integrated PMIC Power Solution	13
2.3 Power Decoupling and Filtering	16
2.4 Estimated Power Consumption	21
2.5 Power Distribution Network	21
2.6 eFuse Power	28
<b>3 Clocking</b>	<b>30</b>
3.1 Crystal and Oscillator Input Options	30
3.2 Output Clock Generation	32
3.3 Crystal Selection and Shunt Capacitance	32
3.4 Crystal Placement and Routing	32
<b>4 Resets</b>	<b>33</b>
<b>5 Bootstrapping</b>	<b>37</b>
5.1 SOP Signal Implementation	37
<b>6 OSPI and QSPI Memory Implementation</b>	<b>42</b>
6.1 ROM OSPI and QSPI Boot Requirements	46
6.2 Additional OSPI and QSPI References	51
<b>7 Debug Interfaces</b>	<b>52</b>
7.1 JTAG Emulators and Trace	52
7.2 UART	54
<b>8 USB</b>	<b>54</b>
8.1 USB Device Mode	56
8.2 USB Host Mode	57
<b>9 Multiplexed Peripherals</b>	<b>58</b>
<b>10 Digital Peripherals</b>	<b>58</b>
10.1 General Digital Peripheral Routing Guidelines	58

10.2 Trace Length Matching.....	58
<b>11 Analog Peripherals.....</b>	<b>59</b>
11.1 General Analog Peripheral Routing Guidelines.....	59
<b>12 Layer Stackup.....</b>	<b>60</b>
12.1 Key Stackup Features.....	62
<b>13 Vias.....</b>	<b>65</b>
<b>14 BGA Power Fan-Out and Decoupling Placement.....</b>	<b>65</b>
14.1 Ground Return .....	66
14.2 1.2V Core Digital Power.....	69
14.3 3.3V Digital and Analog Power.....	74
14.4 1.8V Digital and Analog Power.....	80
<b>15 Summary.....</b>	<b>85</b>
<b>16 References.....</b>	<b>85</b>
<b>17 Revision History.....</b>	<b>86</b>

## List of Figures

Figure 1-1. Typical AM26x System Block Diagram with Discrete Power (Based on LP-AM263 Launchpad Design).....	6
Figure 1-2. Typical AM26x System Block Diagram with PMIC Power (Based on TMDSCNCD263P controlCard Design).....	7
Figure 1-3. Typical AM261x System Block Diagram with PMIC Power (Based on LP-AM261 Design).....	8
Figure 2-1. AM263x DC-DC Regulator Example Design.....	11
Figure 2-2. AM263x LP-AM263 Schematic Excerpt 1.2V Core Power Implementation .....	12
Figure 2-3. AM263x LP-AM263 Schematic Excerpt 3.3V System Digital, Analog I/O Power Implementation .....	12
Figure 2-4. AM263x LP-AM263 Schematic Excerpt – Power Good Implementation (see PORz Reset Implementation) .....	13
Figure 2-5. AM263Px TMDSCNCD263P PMIC Implementation.....	14
Figure 2-6. LP-AM261 PMIC Implementation.....	15
Figure 2-7. AM263x LaunchPad Excerpt – 1.2V Power Decoupling Schematic .....	18
Figure 2-8. AM263x LaunchPad Excerpt – 3.3V Digital I/O and Analog I/O Decoupling and Filtering Schematic .....	18
Figure 2-9. AM263x LaunchPad Excerpt – 1.8V Digital I/O and Analog I/O Decoupling and Filtering Schematic.....	19
Figure 2-10. AM263x LaunchPad Excerpt – ADC and DAC VREF Decoupling Schematic.....	20
Figure 2-11. AM263Px controlCard Excerpt – additional VREFHI_G3 and VREFLO_G3 connections.....	20
Figure 2-12. AM26x PDN Requirements – Example Diagram.....	22
Figure 2-13. AM263x LaunchPad PDN Simulations – 1.2V Core Power Simulation Domain .....	24
Figure 2-14. AM263x LaunchPad PDN Simulations – 1.2V Core Power Simulated Z11.....	25
Figure 2-15. AM263x LaunchPad PDN Simulations – 3.3V Digital and Analog I/O Power Simulation Domain (A).....	26
Figure 2-16. AM263x LaunchPad PDN Simulations – 3.3V Digital and Analog I/O Power Simulation Domain (layer 8, bottom).....	26
Figure 2-17. AM263x LaunchPad PDN Simulations – 3.3V Digital I/O Power Simulated Z11.....	27
Figure 2-18. AM263x LaunchPad PDN Simulations – 3.3V Analog I/O Power Simulated Z11 .....	27
Figure 2-19. AM26x eFuse VPP - External Power Supply Implementation .....	28
Figure 2-20. AM263Px/AM261x eFuse VPP - Internal Analog LDO Implementation.....	29
Figure 3-1. Excerpt From AM263x Control Card Schematics (for full crystal and oscillator input requirements).....	30
Figure 3-2. Excerpt From AM263x controlCard Schematics - Oscillator Clock Source and Clock Distributor.....	31
Figure 3-3. Excerpt From AM263x LaunchPad Layout – CLKOUT0 and EXT_REFCLK0 Output .....	32
Figure 3-4. Excerpt From AM263x Launchpad Layout - Crystal Layout and Ground Ring Structure.....	32
Figure 4-1. Excerpt From AM263x Launchpad Schematic – PORz Generation.....	33
Figure 4-2. Excerpt from AM263Px controlCARD Schematic- PORz Generation.....	34
Figure 4-3. Excerpt from AM261x LaunchPad Schematic - PORz Generation.....	34
Figure 4-4. Excerpt From AM263x Control Card Schematic – PORz and WARMRSTn Pinout.....	35
Figure 4-5. Excerpt From AM263x Control Card Schematic – WARMRSTn Push-Button Open-Drain Driver.....	36
Figure 5-1. Excerpt From AM263x Launchpad Schematic – SOP[3:0] Functional and SOP Paths.....	37
Figure 5-2. Excerpt From AM263x Launchpad Layout – All SOP[3:0] Functional and SOP Paths .....	38
Figure 5-3. Excerpt From AM263x Launchpad Layout – Highlighting SOP0/QSPI_D0 Path and SOP Isolation Resistor.....	38
Figure 5-4. LP-AM261 SOP Isolation Resistors.....	39
Figure 5-5. LP-AM261 SOP Isolation Mux.....	39
Figure 5-6. LP-AM261 PORz SOP Driver RC Delay.....	39
Figure 5-7. LP-AM261 SOP State Driver.....	40
Figure 5-8. LP-AM261 SOP Isolation Mux Output Enable Generation.....	40
Figure 5-9. LP-AM261 SOP Isolation - Layout.....	41
Figure 6-1. Example AM263x QSPI Controller and NOR Flash Memory Schematic .....	42
Figure 6-2. Example AM263Px OSPI Controller and NOR Flash Memory Schematic .....	43
Figure 6-3. Excerpt From LP-AM263 Launchpad Layout – Highlighting SOP0/QSPI_D0 Path and SOP Isolation Resistor....	44
Figure 6-4. AM26x QSPI - Routing Rules Diagram.....	45

Figure 6-5. AM263Px. AM261x OSPI - Routing Rules Diagram.....	45
Figure 6-6. AM263Px OSPI Reset Scheme.....	48
Figure 6-7. Resetting OSPI Flash Using PORz or WARMRESETn.....	49
Figure 6-8. Resetting OSPI Flash Using OSPI0_RESET_OUT0 and PORz, WARMRESETn.....	50
Figure 6-9. Resetting OSPI Flash using Buffered GPIO61 and PORz, WARMRESETn.....	51
Figure 7-1. Example MIPI-60 JTAG and 16-bit Trace Implementation .....	53
Figure 8-1. USB 2.0 Micro-AB Port Showing Critical Signals - LP-AM261.....	54
Figure 8-2. USB ESD Suppression - LP-AM261.....	55
Figure 8-3. USB Routing Example.....	56
Figure 8-4. USB Host Mode Power Switch - LP-AM261.....	57
Figure 8-5. TPS2051B Layout Example - LP-AM261.....	57
Figure 11-1. AM263P Resolver ADC System .....	59
Figure 12-1. LP-AM263 Stackup .....	60
Figure 12-2. LP-AM261 Stackup.....	61
Figure 12-3. AM261x ZFG/ZNC PCB System Stackup.....	61
Figure 14-1. AM263x controlCARD Excerpt – Ground Return Vias Under AM263x BGA Layer 1 and Layer 2.....	66
Figure 14-2. AM263x controlCARD Excerpt – Ground Return Vias Under AM263x BGA Layer 10.....	67
Figure 14-3. AM261x ZFG Routing Study - Ground Return Vias on Layer 1.....	68
Figure 14-4. AM261x ZNC Routing Study - Ground Return Vias on Layer 1.....	68
Figure 14-5. AM263x controlCARD Excerpt – 1.2V Core Power Output, Power Plane Vias and BGA Vias.....	69
Figure 14-6. AM263x controlCARD Excerpt – 1.2V Core Power Plane, Layer 5.....	70
Figure 14-7. AM263x controlCARD Excerpt – 1.2V Core Power Decoupling Mounting, Layer 10 .....	70
Figure 14-8. AM263x controlCARD Excerpt – 1.2V Core Power Decoupling Mounting, Layer 10 .....	71
Figure 14-9. AM261x LaunchPad Excerpt – 1.2V Core Power Output, Power Plane Vias and BGA Vias.....	72
Figure 14-10. AM261x LaunchPad Excerpt – 1.2V Core Power Plane, Layer 4.....	72
Figure 14-11. AM261x LaunchPad Excerpt – 1.2V Core Power Decoupling Mounting, Layer 6.....	73
Figure 14-12. AM263x controlCARD Excerpt – 3.3V Digital and Analog Power Planes on Layer 5 and Layer 6 .....	75
Figure 14-13. AM263x controlCARD Excerpt – 3.3V Digital I/O and Analog I/O BGA Pinout and Regulator Output.....	75
Figure 14-14. AM263x controlCARD Excerpt – Common 3.3V Plane Transition Vias.....	76
Figure 14-15. AM263x controlCARD Excerpt – 3.3V Digital and Analog Planes Layer 6 .....	76
Figure 14-16. AM263x controlCARD Excerpt – 3.3V Digital and Analog Power Decoupling Mounting, Layer 10 .....	76
Figure 14-17. AM261x LaunchPad Excerpt – 3.3V Digital and Analog Power Planes on Layer 3 and Layer 4.....	77
Figure 14-18. AM261x LaunchPad Excerpt – 3.3V Digital I/O BGA Pinout and PMIC Output.....	78
Figure 14-19. AM261x LaunchPad Excerpt - 3.3V Analog IO BGA Pinout.....	78
Figure 14-20. AM261x LaunchPad Excerpt – 3.3V Digital Plane on Layer 3 .....	79
Figure 14-21. AM261x LaunchPad Excerpt – 3.3V Digital Power Decoupling Mounting, Layer 6.....	79
Figure 14-22. AM263x controlCARD Excerpt – 1.8V Digital Power Via Fan-Out and Plane Routing Layer 6.....	80
Figure 14-23. AM263x controlCARD Excerpt – 1.8V Digital Power Decoupling on Layer 10.....	81
Figure 14-24. AM263x controlCARD Excerpt – 1.8V Analog Power Via Fan-Out and Plane Routing Layer 6.....	81
Figure 14-25. AM263x controlCARD Excerpt – 1.8V Analog Power Decoupling on Layer 10.....	82
Figure 14-26. AM261x LaunchPad Excerpt – 1.8V Digital Power Via Fan-Out and Plane Routing - Layer 3.....	83
Figure 14-27. AM261x LaunchPad Excerpt – 1.8V Digital Power Decoupling on Layer 6.....	83
Figure 14-28. AM261x LaunchPad Excerpt – 1.8V Analog Power Via Fan-Out and Plane Routing - Layer 4.....	84
Figure 14-29. AM261x LaunchPad Excerpt – 1.8V Analog Power Decoupling on Layer 6.....	84

## List of Tables

Table 1-1. AM26x Evaluation Module (EVM) Platforms.....	1
Table 1-1. Acronyms Used in This Document.....	9
Table 2-1. AM26x Core Voltage Requirements.....	10
Table 2-2. AM26x IO Voltage Requirements.....	10
Table 2-3. AM26x PMICs.....	13
Table 2-4. TPS6538600QDCARQ1 Configuration for AM26x Devices.....	14
Table 2-5. TPS65036x Configuration on LP-AM261.....	15
Table 2-6. TPS65036x Variants for AM261x.....	15
Table 2-7. AM263x, AM263Px, AM261x-ZCZ Recommended Decoupling per Power Net.....	16
Table 2-8. AM261x (all other packages) Recommended Decoupling per Power Net.....	17
Table 2-9. AM26x ADC/DAC VREF Decoupling.....	20
Table 2-10. Estimated Peak Power Consumption - Automotive-grade AM26x, R5F = 400MHz, 150°C Junction Temperature.....	21
Table 2-11. Estimated Peak Power Consumption - Industrial-grade AM261x, R5F = 500MHz, 125°C Junction Temperature.....	21
Table 2-12. AM26x Transient Current Model – Use-case Conditions .....	22

Table 2-13. AM26x Transient Current Model – Resulting PDN Requirements .....	23
Table 5-1. SOP and Functional Mode Signal Mapping.....	37
Table 6-1. AM261x ZFG, ZEJ, ZNC Flash Power Nets.....	43
Table 6-2. AM26x QSPI – Recommended Routing Rules.....	46
Table 6-3. AM263Px, AM261x OSPI – Recommended Routing Rules.....	46
Table 6-4. AM263x QSPI Pins Configured in Boot ROM.....	47
Table 6-5. AM263Px OSPI Pins Configured in Boot ROM.....	47
Table 6-6. AM263Px-SIP Package OSPI Pins Configured in Boot ROM.....	48
Table 6-7. AM261x ZCZ Package OSPI Pins Configured in Boot ROM.....	49
Table 6-8. AM261x ZFG, ZEJ, ZNC Package OSPI Pins Configured in Boot ROM.....	49
Table 6-9. OSPI0_RESET_OUT0 Pin Options.....	50
Table 10-1. AM26x Digital Peripherals - Trace Length Matching.....	58
Table 12-1. AM261x Package Sizes.....	60
Table 12-2. Stackup Features by Package Size.....	62
Table 12-3. 6-Layer PCB: Layer Utilization.....	62
Table 12-4. AM263x, AM263Px, AM261x ZCZ Package, 6-Layer PCB: Controlled Impedance Planning Options .....	62
Table 12-5. 4-Layer PCB: Layer Utilization.....	63
Table 12-6. AM261x ZFG Package, 4-Layer PCB: Controlled Impedance Planning Options .....	63
Table 12-7. AM261x ZNC Package, 4-Layer PCB: Controlled Impedance Planning Options .....	64
Table 13-1. AM26x EVM Via Types.....	65
Table 14-1. BGA Attribute Sections by Device Package.....	65

## Trademarks

Sitara™ and LaunchPad™ are trademarks of Texas Instruments.

Arm® and Cortex® are registered trademarks of Arm Limited (or its subsidiaries) in the US and/or elsewhere.

All trademarks are the property of their respective owners.



## 1 Introduction

The AM263x, AM263Px, and AM261x devices are single, dual, or quad-core Arm® Cortex®-R5F based MCUs in the Sitara™ MCU family intended for industrial and automotive motion control applications.

---

### Note

In this document, AM26x refers to the TI Sitara™ MCU family of high-performance microcontrollers. This includes the AM263x, AM263Px, and AM261x devices. Device-specific references are denoted by the full general product number (AM263x, AM263Px, AM261x), while general device information are denoted by AM26x.


---

A typical AM26x design with a discrete power design is shown in [Figure 1-1](#). This diagram is excerpted from the AM263x LaunchPad™ (LP-AM263) system block diagram.

A typical AM26x design with a Power Management Integrated Circuit (PMIC)-based power design is shown in [Figure 1-2](#). This diagram is excerpted from the AM263Px controlCard (TMDSCNCD263P) system block diagram.

A typical AM261x design with a smaller footprint PMIC is shown in [Figure 1-3](#). This diagram is taken from the AM261x LaunchPad (LP-AM261) system block diagram.

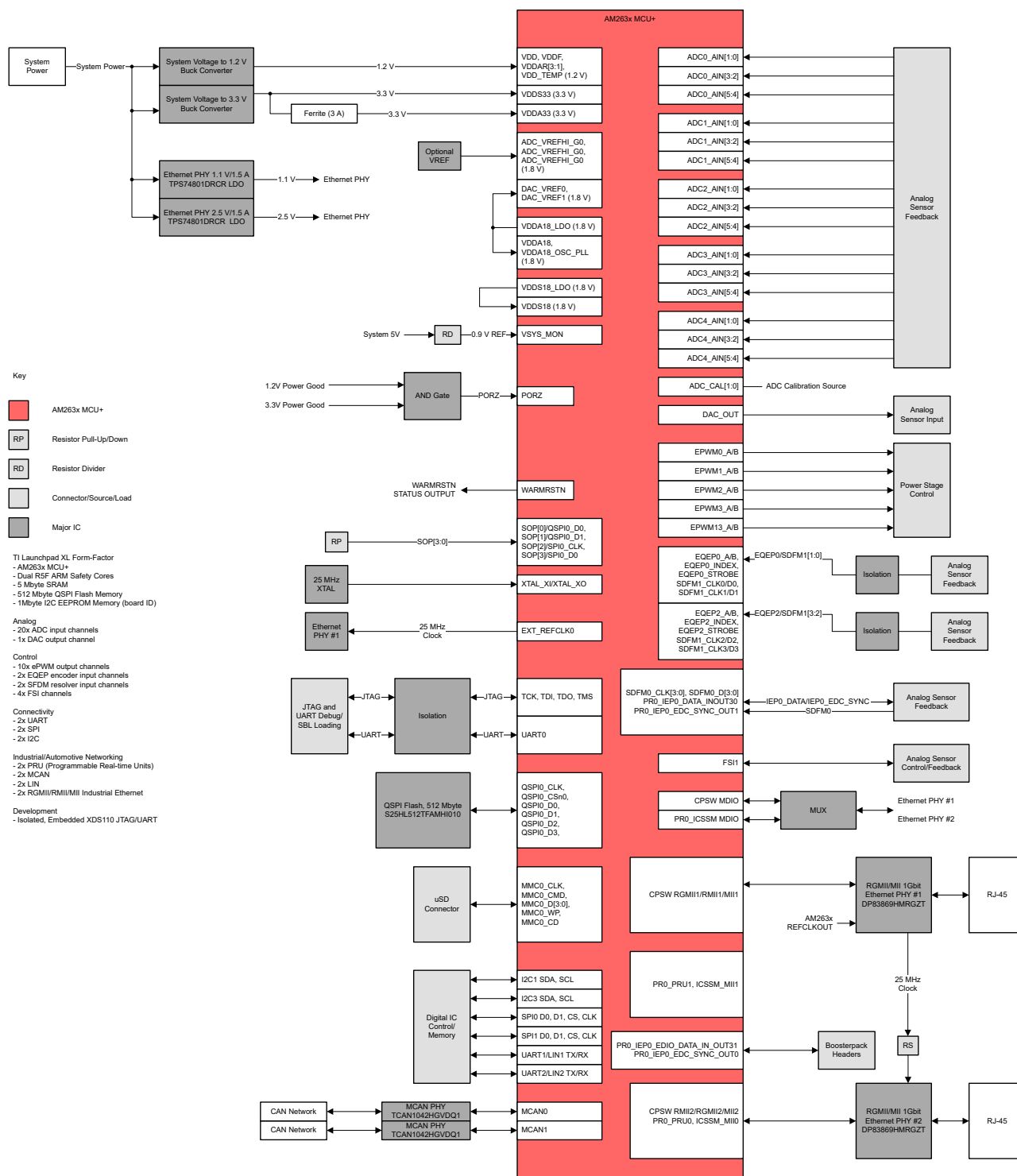As seen in the following block diagrams, the AM26x devices offer designers a wide range of digital connectivity, control and analog sensor feedback options with multiple power design options supported.




### Note

The current requirement for the *System Voltage to 1.2V Buck Converter* for AM263x, AM263Px is 3A. For AM261x, the current limit is 2A.

**Figure 1-1. Typical AM26x System Block Diagram with Discrete Power (Based on LP-AM263 Launchpad Design)**



**Figure 1-2. Typical AM26x System Block Diagram with PMIC Power (Based on TMDSCNCD263P controlCard Design)**

 

This document must be referenced along with the other key AM26x collateral references. See [Section 16](#) for a complete list of supplementary documents for the AM26x MCU devices.

**Table 1-1. Acronyms Used in This Document**

Acronym	Description
EVM	Evaluation Module. Referencing TI PCB assemblies such as the AM263x controlCard (TMDSCNCD263) or AM263x LaunchPad (LP-AM263).
PDN	Power Distribution Network. The active and passive components providing regulated power to a load such as the AM263x MCU power pins.
EMI	Electromagnetic Interference
PI	Power Integrity
SI	Signal Integrity
BOM	Bill of Materials
PMIC	Power Management Integrated Circuit
SOM	System on Module
LP	LaunchPad
SoC	System on a Chip

## 2 Power

### AM26x Device Power Rails

AM26x devices have two main device power nets: The core voltage rail, and the IO voltage rail. [Table 2-1](#) details the core voltage requirements for AM26x devices. [Table 2-2](#) details the IO voltage requirements for AM26x devices.

**Table 2-1. AM26x Core Voltage Requirements**

Device	Core Voltage	Associated Core Power Nets
AM263x	1.2V	VDD_CORE
		VDDAR
AM263Px	1.2V	VDD_CORE
		VDDAR
AM261x (Automotive-grade, 400MHz)	1.2V	VDD_CORE
		VDDAR
AM261x (Industrial-grade, 400MHz OR 500MHz)	1.25V	VDD_CORE
		VDDAR

#### Note

AM261x core voltage differs depending on the microcontroller Orderable Part Number (OPN). Industrial-grade AM261xAO... devices require 1.25V for the core supply for operation at 500MHz or 400MHz. Automotive-grade AM261xAL...Q1 and AM261xAP...Q1 devices require 1.2V for the core supply for operation at 400MHz or 200MHz. For more details on the AM261x OPNs, refer to the [AM261x Sitara™ Microcontroller data sheet](#).

**Table 2-2. AM26x IO Voltage Requirements**

Device	IO Voltage	Associated Power Nets
AM263x	3.3V	VDDS33
		VDDA33
AM263Px	3.3V	VDDS33
		VDDA33
AM261x (Industrial & Automotive-grade)	3.3V	VDDSHV_A
		VDDSHV_B
		VDDSHV_C
		VDDSHV_F
		VDDSHV_G
		VDDSHV_D
	3.3V or 1.8V	VDDSHV_E
		VDDSHV_E

#### Note

AM261x power nets VDDSHV\_D and VDDSHV\_E can be either 3.3V or 1.8V, depending on what voltage level external flash is used. For more information, refer to [Section 6](#).

Different power topologies, such as discrete supplies or Power Management ICs (PMICs) can be used to supply an AM26x system. The following sections detail the different types of topologies used.



## 2.1 Discrete DC-DC Power Solution

The AM263x LaunchPad and AM263x controlCard EVM designs both integrate a set of buck-converter, DC-DC regulators that are useful as a reference power design for some systems. This design consists of a pair of TPS62913 buck-converter regulators for the AM26x MCU core, system digital and analog I/O power, and a set of TPS74801 LDO for powering paired industrial Ethernet PHY.

Current and transient requirements of the DC-DC closed-loop and passive power plane and decoupling network are taken from the power consumption and transient loading tables: [Table 2-12](#) and [Table 2-13](#). Many DC-DC regulators can be matched to fit within these requirements and the maximum power consumption.

TI also recommends to use the power-good generation circuits available on these and similar DC-DC regulators to drive the power on reset (PORZ) into the AM26x.

### Note

For AM263x, AM263Px, and Automotive-grade AM261x devices, the core voltage (VDD) requirement is 1.2V. For Industrial-grade AM261x devices, the core voltage (VDD) requirement is 1.25V.



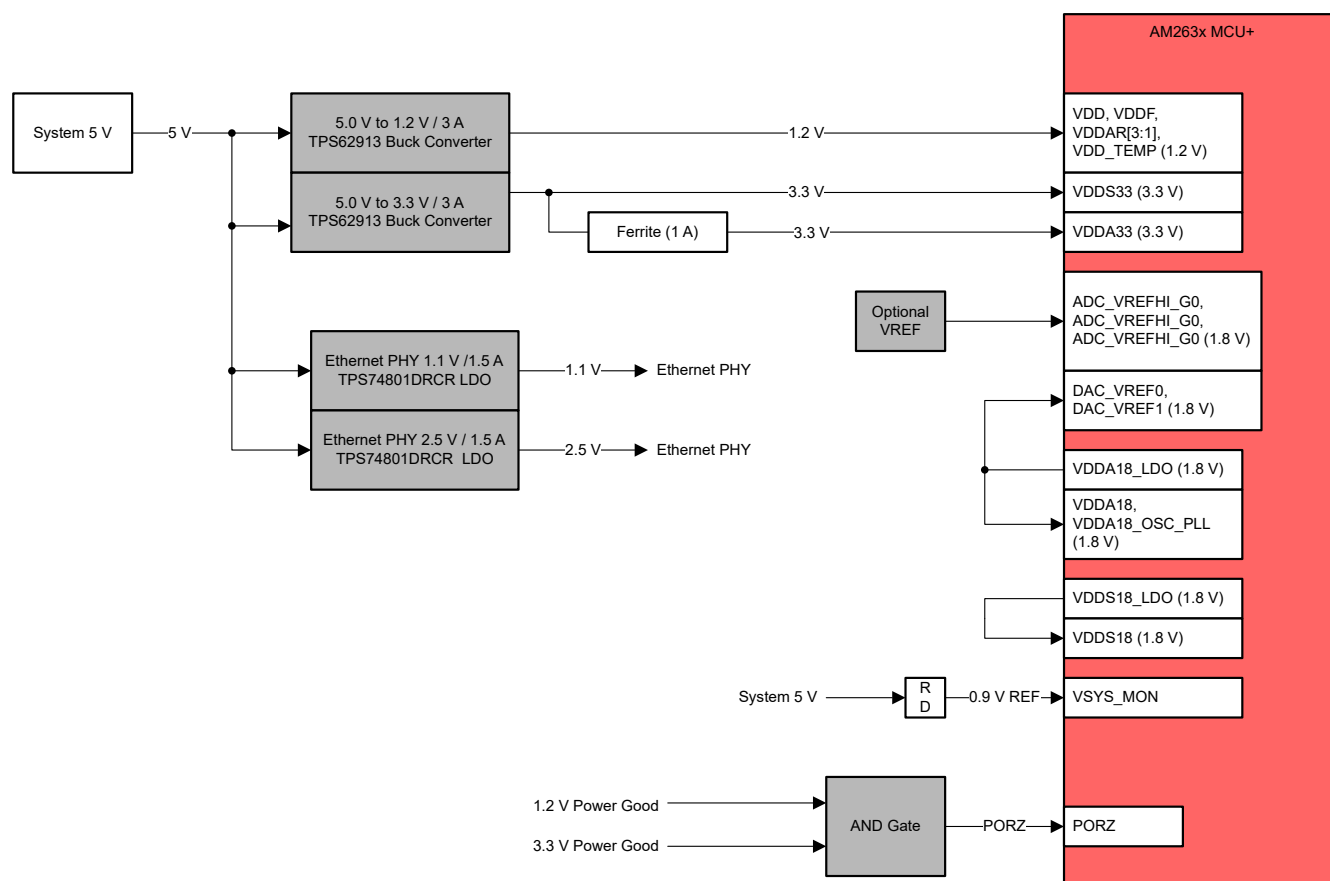



Figure 2-1. AM263x DC-DC Regulator Example Design

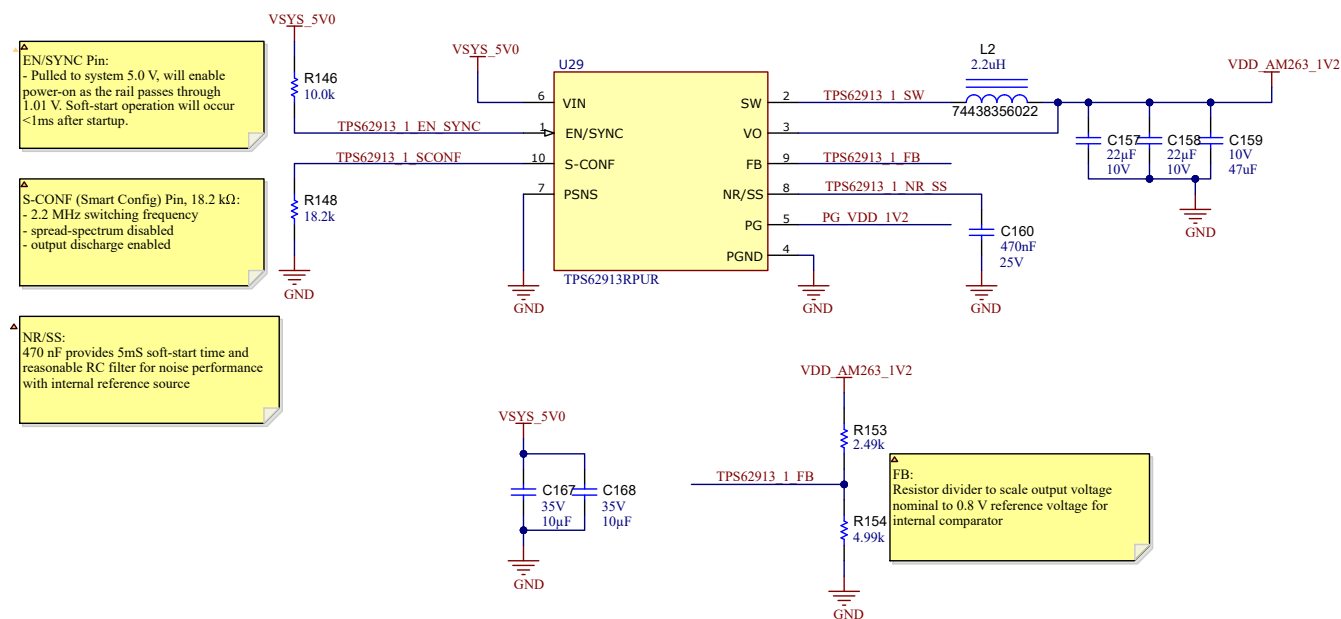

**Figure 2-2. AM263x LP-AM263 Schematic Excerpt 1.2V Core Power Implementation**

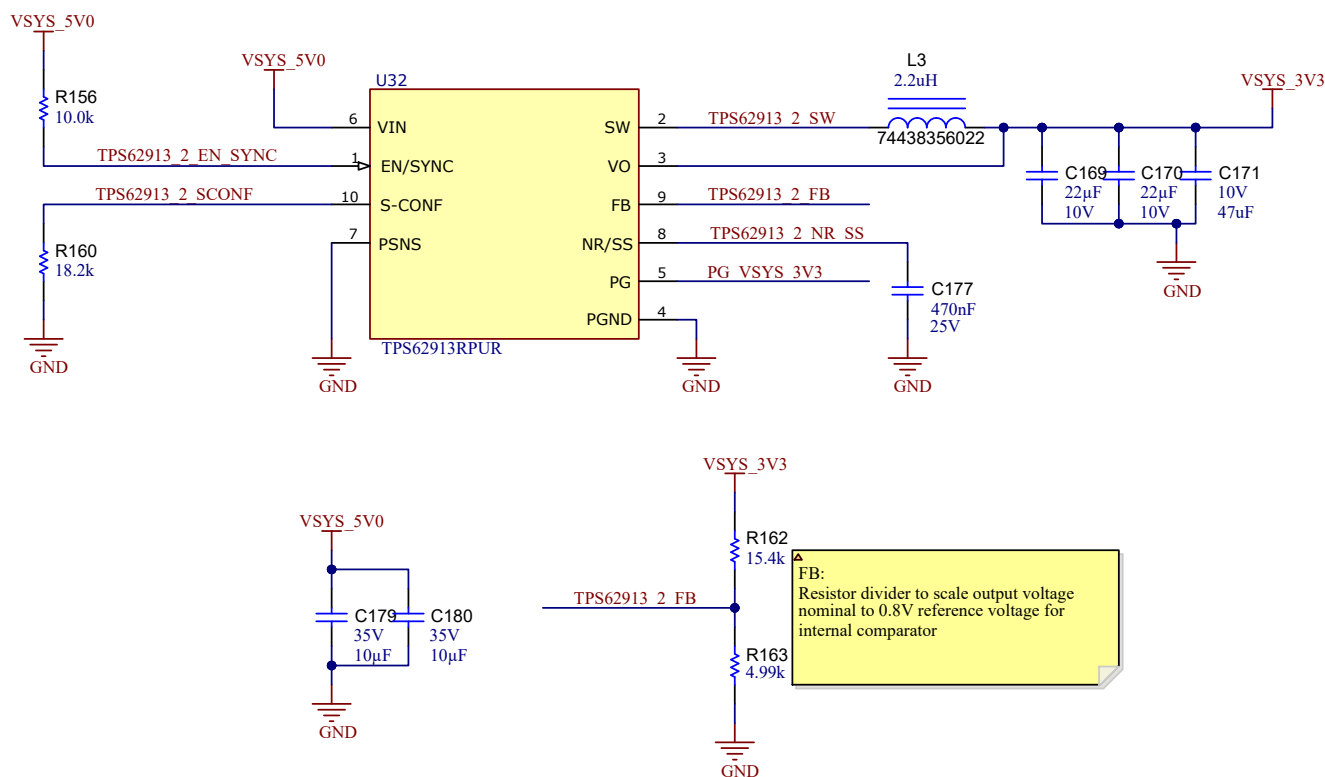

**Figure 2-3. AM263x LP-AM263 Schematic Excerpt 3.3V System Digital, Analog I/O Power Implementation**

 

**Figure 2-4. AM263x LP-AM263 Schematic Excerpt – Power Good Implementation (see PORz Reset Implementation)**

## 2.2 Integrated PMIC Power Solution

A PMIC-based power tree allows for a more streamlined, single-chip design for controlling the power rails in an AM26x system. Several Texas Instruments PMICs are recommended for use with AM26x MCUs, and are detailed in the table below:

**Table 2-3. AM26x PMICs**

PMIC Orderable Part Number	AM26x Target Device	TI EVM / Reference Design Example
TPS6538600QDCARQ1 + TPS6290x-Q1 <sup>(1)</sup>	AM263x	
• TPS62903x-Q1 = 3A supply for AM263x/ AM263Px	AM263Px	AM263Px controlCARD (TMDSCNCD263P)
• TPS62902x-Q1 = 2A supply for AM261x	AM261x	AM261x controlSOM (AM261-SOM-EVM)
TPS65036x <sup>(2)</sup>	AM261x	AM261x LaunchPad (LP-AM261)
TPS65219x	AM263Px	
TPS65214x	AM261x	

- (1) TPS6290x-Q1 is required to supply the 1.2V (AM263x, AM263Px, Automotive-grade AM261x) / 1.25V (Industrial-grade AM261x) core voltage to the AM26x device. The correct orderable part number to supply 3A for AM263x and AM263Px and 2A for AM261x is required.
- (2) There are multiple orderable part numbers of this PMIC associated with AM261x. See [Table 2-6](#) for additional details.


### Using TPS653860 with AM26x

The AM263Px controlCard EVM and AM261x controlSOM EVM designs make use of a multirail power supply for microcontrollers in safety-relevant applications (TPS6538600QDCARQ1). The PMIC integrates **four** supply rails to power the MCU, CAN, and other on-board peripherals.

#### Note

This implementation requires a separate TPS62902QRYTQ1 (3A for AM263x/AM263Px) / TPS62902QRYTQ1 (2A for AM261x) buck converter to supply the AM26x core voltage

The NRES output of the PMIC needs to be used to help drive the PORz reset input to the AM263x, AM263Px, or AM261x device to make sure the power on sequencing of the power rails is complete before releasing the MCU from reset.

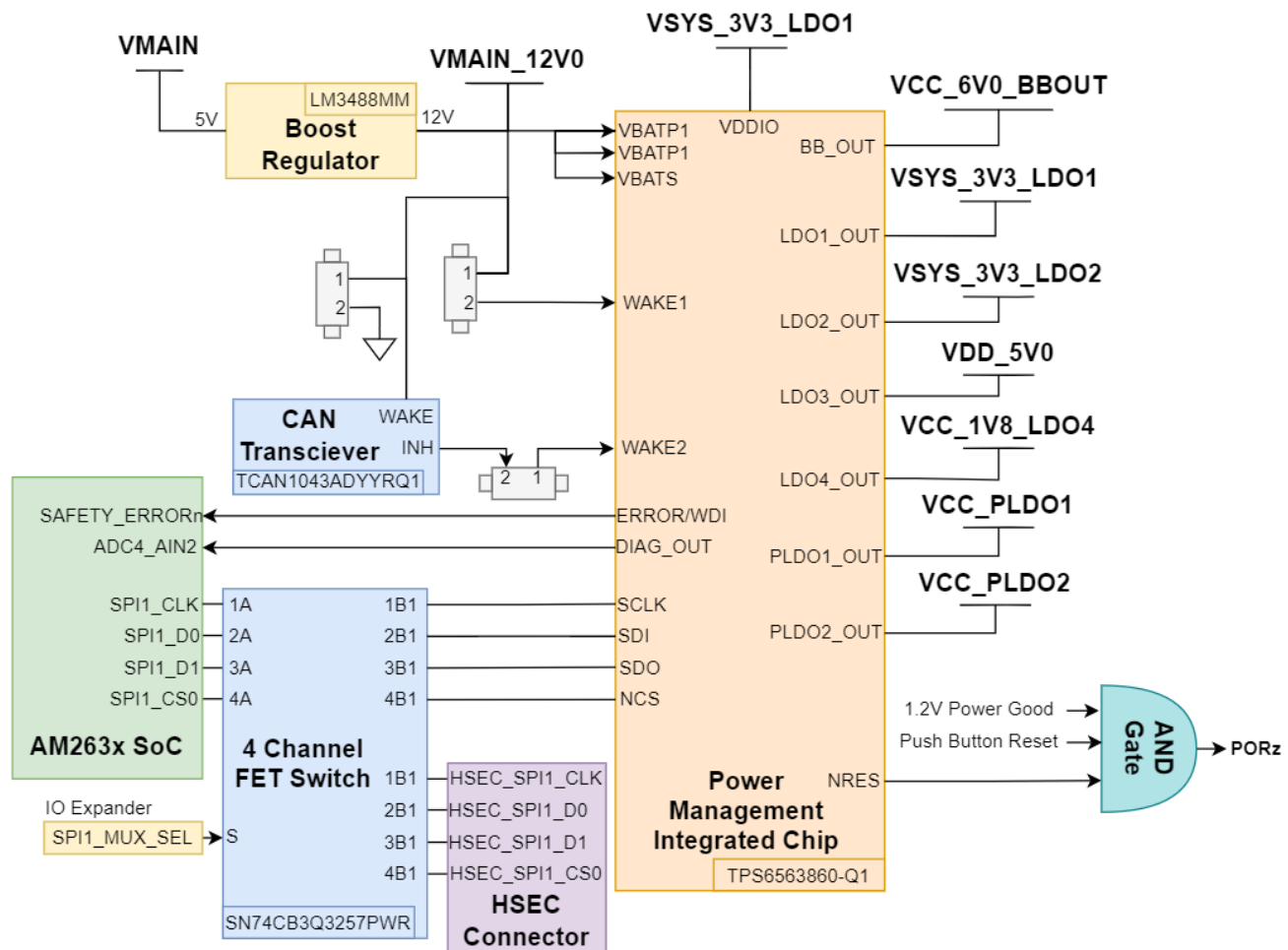

**Figure 2-5. AM263Px TMDSCNCD263P PMIC Implementation**

**Table 2-4. TPS6538600QDCARQ1 Configuration for AM26x Devices**

Output Power Rail	Voltage	Purpose	Enabled at Power-On?
BB_OUT	6V	Power input to separate 1.2V/1.25V regulator for AM26x VDD/VDDAR supply	✓
LDO1_OUT	3.3V	AM26x IO voltage supply	✓
LDO2_OUT	3.3V	System IO and peripheral hardware voltage supply	✓
LDO3_OUT	5V	System supply and peripheral hardware voltage	
LDO4_OUT	1.8V	ADC voltage refrence supply	
PLDO1_OUT	CONFIGURABLE		
PLDO2_OUT	CONFIGURABLE		

#### Note

SPI writes to the PMIC internal registers are required to enable power rails that do not come up by default at power-on.

#### Using TPS650360x with AM261x

The AM261x LaunchPad EVM design makes use of the smaller-package, lower-cost TPS65036x PMIC. This PMIC integrates four supply rails to power the MCU and other on-board peripherals.

### Note

This PMIC can output 1.2V or 1.25V at 2A, which meets the VDD CORE supply requirements of the AM261x MCU. AM263x and AM263Px require 1.2V at 3A, so this PMIC must not be used to power these devices.

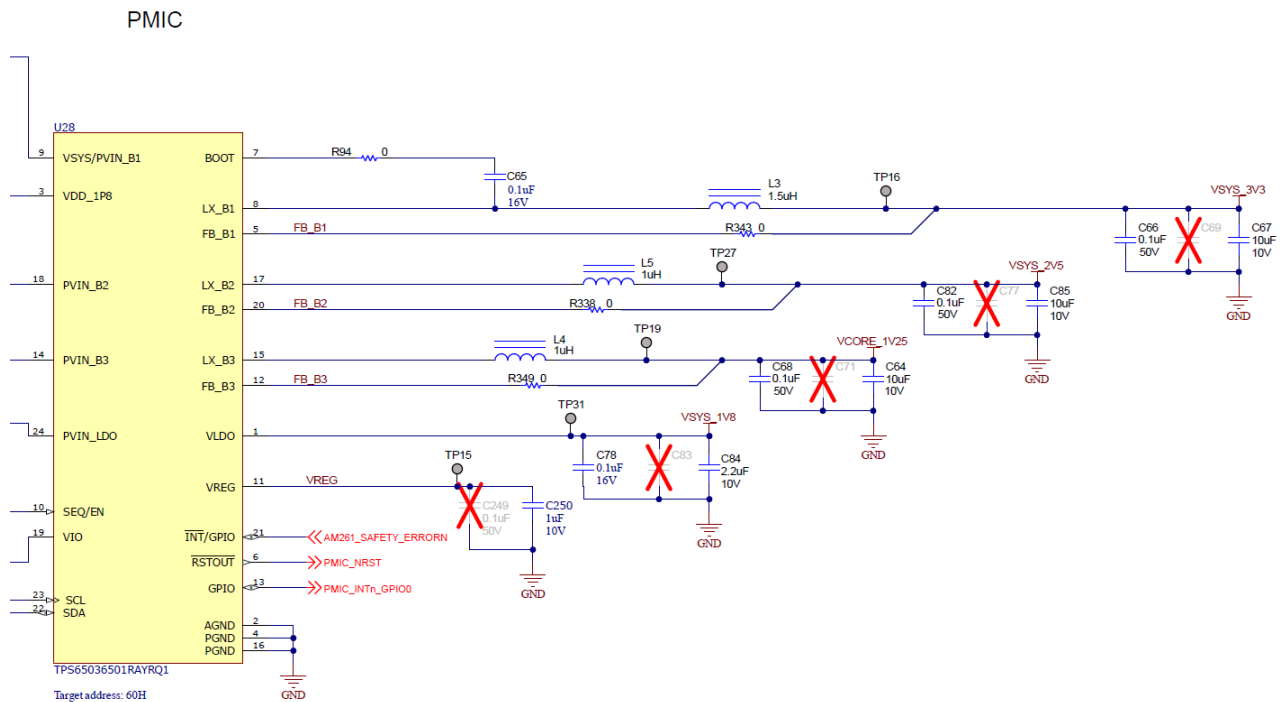


Figure 2-6. LP-AM261 PMIC Implementation

Table 2-5. TPS65036x Configuration on LP-AM261

Output Power Rail	Voltage	Purpose	Enabled at Power-On?
BUCK1	3.3V	AM261x IO voltage and peripheral supply	✓
BUCK2	2.5V	System Ethernet PHY supply	✓
BUCK3	1.25V (500MHz Industrial-grade AM261x)	AM261x core voltage supply	✓
LDO	1.8V	Flash IO voltage supply	✓

There are several variants of this PMIC depending on what supply voltages and features are required for an AM261x system.

Table 2-6. TPS65036x Variants for AM261x

Orderable Part Number	BUCK1	BUCK2	BUCK3	LDO	WD Enabled
TPS65036501RAYRQ1	3.3V	2.5V	1.25V (for Industrial-grade AM261x)	1.8V (for 1.8V IO external flash)	YES
TPS65036601RAYRQ1	3.3V	2.5V	1.2V (for Automotive-grade AM261x)	1.8V (for 1.8V IO external flash)	YES
PTPS65036605RAYRQ1	5V	3.3V	1.25V (for Industrial-grade AM261x)	1.8V or 3.3V	YES
TPS65036608RAYRQ1	3.3V	1.8V	1.25V (for Industrial-grade AM261x)	BYPASS	YES

### Note

*Watchdog Enabled* refers to the PMIC's watchdog Long Window Timer, a 12 minute timer that stops the PMIC, MCU operation from hanging if the system is idle for 12 minutes or longer. This feature is relevant for applications where safety is a priority. When the Watchdog is enabled, the PMIC asserts a reset if left idle for 12 minutes.

For the TPS650360x variants with the Watchdog enabled, this can be disabled via an I2C write to the PMIC registers, or by connecting the GPIO pin (pin 13) to the VDD\_1P8 pin (pin 3) or any other supply that comes up **before** the PMIC ramps. If the watchdog is to be disabled using this hardware method, then the power supply pulling the GPIO pin high **must** ramp before the PMIC turns on. This way, the internal bit to disable the PMIC is set before the PMIC powers on.

The nRSTOUT output of the PMIC must be used to help drive the PORz reset input to the AM261x device to make sure the power on sequencing of the power rails is complete before releasing the MCU from reset. For more information, see [Figure 4-3](#).

## 2.3 Power Decoupling and Filtering

[Table 2-7](#) describes the initial BGA decoupling and power filtering required for the ZCZ package of the AM263x, AM263Px, and AM261x microcontrollers. These decoupling capacitor quantities and sizes were based on the initial simulation feedback of the Control Card EVM PCB and AM263x package with the transient use-cases shown in [Table 2-12](#). [Table 2-8](#) describes the BGA decoupling and power filtering required for the ZFG, ZNC, and ZEJ packages of the AM261x MCU. These packages support 3.3V and 1.8V flash IO on the OSPI/QSPI peripherals, and thus have slightly different device power rails compared to the ZCZ package devices, which only support 3.3V flash IO on the OSPI peripherals. Variation in overall power pin counts also account for differences in decoupling on the AM261x ZFG/ZNC/ZEJ packages.

The decoupling network presented in the sections below and in the AM263x EVM schematics and layouts are reasonable starting points for any AM263x, AM263Px, or AM261x PCB design. However, due to specific PCB routing differences and the resulting plane capacitance and decoupling mounting inductances and other parasitics, TI highly recommends that designers simulate and measure the specific power distribution network performance. Simulations and measurements are usually done with target application software active, and intended operating environment conditions applied to the system.

**Table 2-7. AM263x, AM263Px, AM261x-ZCZ Recommended Decoupling per Power Net**

Device Supply	Quantity	Comment	Part #	Manufacturer
VDD_CORE	17	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
	3	3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
VDDAR[3:1]	2	3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	3	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDS18_LDO	1	3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDS18	4	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA18_LDO	1	4.7uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA18	2	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA18_OSC_PLL LC filter	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
	1	Ferrite bead	BLM18EG121SN1D	Murata
VDDS33	7	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
	1	3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
VDDA33	3	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
	1	3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	1	Ferrite bead	BLM18EG121SN1D	Murata




**Table 2-7. AM263x, AM263Px, AM261x-ZCZ Recommended Decoupling per Power Net (continued)**

Device Supply	Quantity	Comment	Part #	Manufacturer
System 3.3V Power LC filter	1	3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata


**Table 2-8. AM261x (all other packages) Recommended Decoupling per Power Net**

Device Supply	Package or Quantity			Comment	Part #	Manufacturer
	ZFG	ZEJ	ZNC			
VDD_CORE	13	12	18	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
		3		3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
VDDAR[3:2]		2		3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
		2		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDD518_LDO		1		3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDD518		1		3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	7	8	8	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA18_LDO		1		4.7uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	2	1	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA18_USB		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA18		2		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA18_OSC_PLL LC filter		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
		1		Ferrite bead	BLM18EG121SN1D	Murata
VDDSHV_D	1	2	2	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
		1		3.3uF, 0603, X5R	C1608X5R1A335K080AC	Murata
VDDSHV_E		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
		1		3.3uF, 0603, X5R	C1608X5R1A335K080AC	Murata
VDDSHV_A	6	5	6	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
		3		3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
VDDSHV_B		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDSHV_C		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDSHV_F		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDSHV_G	N/A	2	N/A	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
VDDA33		2		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
		1		3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
		1		Ferrite bead	BLM18EG121SN1D	Murata
System 3.3V Power LC filter		1		3.3uF, 0603, X5R	C1608X5R1A335K080AC	TDK
		1		0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata

## VDD 1V2 Core Digital

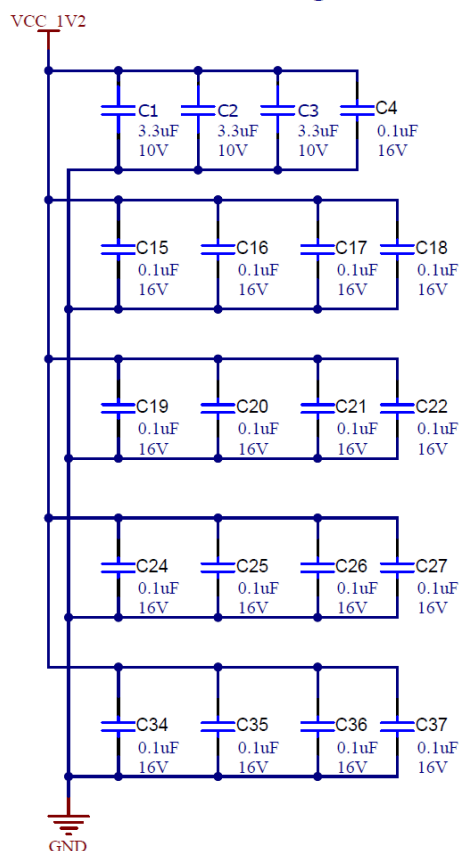

## VDDAR[3:1] 1V2 SRAM Array

 

## VDD\_F 1V2


 


Figure 2-7. AM263x LaunchPad Excerpt – 1.2V Power Decoupling Schematic

### VDDS 3V3 Digital

 

### VDDA 3V3 Analog



 


Figure 2-8. AM263x LaunchPad Excerpt – 3.3V Digital I/O and Analog I/O Decoupling and Filtering Schematic

### VDDS 1V8 Digital

 

### VDDA 1V8 Analog

 

**Figure 2-9. AM263x LaunchPad Excerpt – 1.8V Digital I/O and Analog I/O Decoupling and Filtering Schematic**


### 2.3.1 ADC/DAC Voltage Reference Decoupling

The ADC and DAC voltage reference pins on AM26x devices also require specific decoupling. The requirements are outlined in the table below.


**Table 2-9. AM26x ADC/DAC VREF Decoupling**

ADC VREF	Quantity	Comment	Part #	Manufacturer
ADC_VREFHI_G[1:0]	1	4.7uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	2	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
ADC_VREFHI_G[2]	1	4.7uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
ADC_VREFHI_G[3] <sup>(1)</sup>	1	4.7uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
DAC_VREF[0]	1	4.7uF, 0603, X5R	C1608X5R1A335K080AC	TDK
	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata
DAC_VREF[1] <sup>(2)</sup>	1	0.1uF, 0201, X5R	GRM033R61A104KE15D	Murata

- (1) The AM263Px Sensor Package (ZCZ\_S) has additional set of ADC reference voltages, ADC\_VREFHI\_G3 and ADC\_VREFLO\_G3.  
(2) AM263x and AM263Px have an additional DAC reference voltage, DAC\_VREF1. An additional 0.1uF decoupling capacitor must be used at this pin.

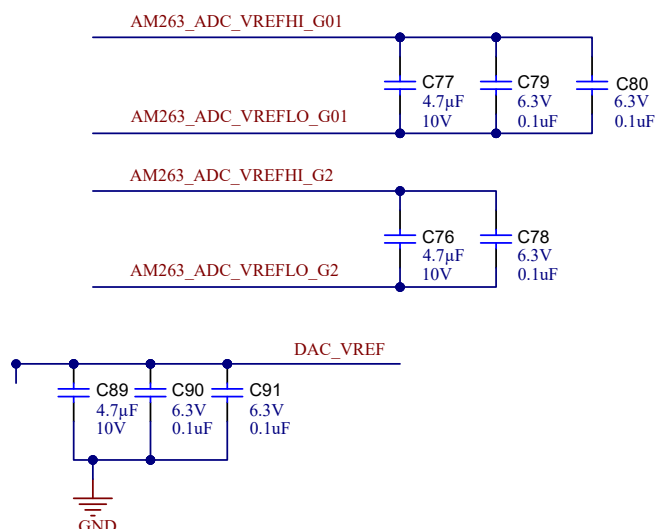

**Figure 2-10. AM263x LaunchPad Excerpt – ADC and DAC VREF Decoupling Schematic**

 

**Figure 2-11. AM263Px controlCard Excerpt – additional VREFHI\_G3 and VREFLO\_G3 connections**

## 2.4 Estimated Power Consumption

This section outlines the latest estimates of the AM263x, AM263Px, and AM261x peak power consumption on a per device power net basis. These values can change as more power modeling and characterization is performed. This data can be used to scale peak DC-DC conversion power margin, perform IR drop analysis of the PCB layout, and help with thermal loading analysis.

These estimates are based on initial power simulations of the device when operating at 150°C junction temperature. For the latest characterized, peak power numbers, see the specific AM26x device data sheet.

A use-case based power estimation tool (PET) is also provided for the AM26x MCUs. These tools can help further bound the peak power based on specific core and peripheral utilization duty-cycle. The device-specific PET can be downloaded from the AM263x, AM263Px, and AM261x product pages.

**Table 2-10. Estimated Peak Power Consumption - Automotive-grade AM26x, R5F = 400MHz, 150°C Junction Temperature**

Device Supply Name	Nominal Voltage (V)	AM263x Peak Current (mA)	AM263Px Peak Current (mA)	AM261x Peak Current (mA)		Supply Description
VDD + VDDARn	1.2	2500	2800	1750		Digital core power
VDDS33	3.3	200	200	3.3V IOs only <sup>(1)</sup>	200	3.3V digital I/O power
				1.8V and 3.3V IOs <sup>(2)</sup>	120	
VDDA33	3.3	100	200	100		3.3V analog I/O power

(1) When all IOs are operating in the 3.3V domain

(2) When OSPI0 and OSPI1 IOs are operating in the 1.8V domain

**Table 2-11. Estimated Peak Power Consumption - Industrial-grade AM261x, R5F = 500MHz, 125°C Junction Temperature**

Device Supply Name	Nominal Voltage (V)	AM261x Peak Current (mA)		Supply Description
VDD + VDDARn	1.25	1500		Digital core power
VDDS33	3.3	3.3V IOs only <sup>(1)</sup>	200	3.3V digital I/O power
		1.8V and 3.3V IOs <sup>(2)</sup>	120	
VDDA33	3.3	100		3.3V analog I/O power


(1) When all IOs are operating in the 3.3V domain

(2) When OSPI0 and OSPI1 IOs are operating in the 1.8V domain

## 2.5 Power Distribution Network

This section outlines the latest estimates of the AM26x transient current requirements on a per net basis. These values can change as more power modeling and characterization is performed.

These transient use-case values were used to constrain the PDN design of the AM26x EVMs (controlCards, LaunchPads, and controlSOM) by creating a set of minimum/maximum operating frequency and PDN impedance ( $Z_{max}$ ) target limits. These limits were based on the magnitude and slew-rate of simulated transient current use-cases. The use-cases were used to estimate the PDN bandwidth needed to adequately decouple the resulting transient event. Additional z-parameter simulation of the EVM PDN was used to verify that the power plane design and decoupling placement and component values meet the defined limits. This is summarized in [Figure 2-12](#).

 

**Figure 2-12. AM26x PDN Requirements – Example Diagram**

**Table 2-12. AM26x Transient Current Model – Use-case Conditions**

Transient Case	Net Name	Nominal Voltage (V)	DC IR Budget (%)	AC Ripple Budget (%)	Idle Current (mA)	Peak Current (mA)	Idle to Peak Slew Rate (ns)	Comment
VDDBASELINE1	VDD	1.2	2.5	2.5	0	2402	2.5	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle.
VDDXTAL_PLL1	VDD	1.2	2.5	2.5	42	875	10	XTAL to PLL turn-on transient
VDD WFI1	VDD	1.2	2.5	2.5	750	1117	12.5	4x RF5 WFI event transient
VDDS33BASELINE1	VDDS33	3.3	2.5	2.5	0	84	2.5	Baseline, simple transient model assuming 0 to peak transition in a single R5F clock cycle
VDDA33BASELINE1	VDDA33	3.3	2.5	2.5	0	34	2.5	Baseline, simple transient model assuming 0 to peak transition in a single R5F clock cycle
VDDS18LDOBASELINE1	VDDS18LDO	1.8	2.5	2.5	0	01	2.5	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle
VDDA18LDOBASELINE1	VDDA18LDO	1.8	2.5	2.5	0	66	2.5	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle



**Table 2-13. AM26x Transient Current Model – Resulting PDN Requirements**

Transient Case	Net Name	Fmax (MHz)	Current Step(mA)	PCB DC Tolerance (mV)	PCB AC Tolerance (mV)	PCB Target DC IR(mΩ)	PCB Target AC Zmax(mΩ)	Comment
VDD BASELINE1	VDD	200	2402	30	30	12	12	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle.
VDD XTAL_PLL1	VDD	50	833	30	30	36	36	XTAL to PLL turn-on transient.
VDD WFI1	VDD	40	367	30	30	82	82	4x RF5 WFI event transient.
VDDS33 BASELINE1	VDDS33	200	84	83	83	982	982	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle.
VDDA33 BASELINE1	VDDA33	200	34	83	83	2419	2419	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle.
VDDS18LDO BASELINE1	VDDS18LDO	200	1	45	45	45	45	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle.
VDDA18LDO BASELINE1	VDDA18LDO	200	66	45	45	682	682	Baseline, simple transient model assuming 0 to peak transition in minimal 1 R5F clock cycle.

### 2.5.1 Simulations


The following simulated PDN z-parameter performance was extracted from the AM263x LaunchPad and controlCard layouts using Ansys SI wave. Wide-band s-parameter models of each of the selected capacitors were taken from the manufacturer. Simulations capture only 25°C (room temperature) PCB and capacitor model performance.

#### 2.5.1.1 Core Digital Power 1.2V


Z11 simulations were performed on the 1.2V core digital power net of the AM263x LaunchPad EVM to verify transient power margin. The simulation domain included the:

- AM263x BGA (UI) 1.2V digital and GND return fan-out
- Internal PCB 1.2V and GND return planes
- Decoupling placed on the 1.2V power net,
- U29 buck regulator output LC filter up to switch node

These simulations were done iteratively with multiple capacitor BOM changes made between each iteration. Each iteration was characterized primarily by the maximum and minimum frequency bandwidth below Ztarget (see above sections) and the BOM selection changed to maximize bandwidth and maximum Ztarget margin. Only the initial and final chosen BOM iterations are shown in [Figure 2-13](#) and [Figure 2-14](#).

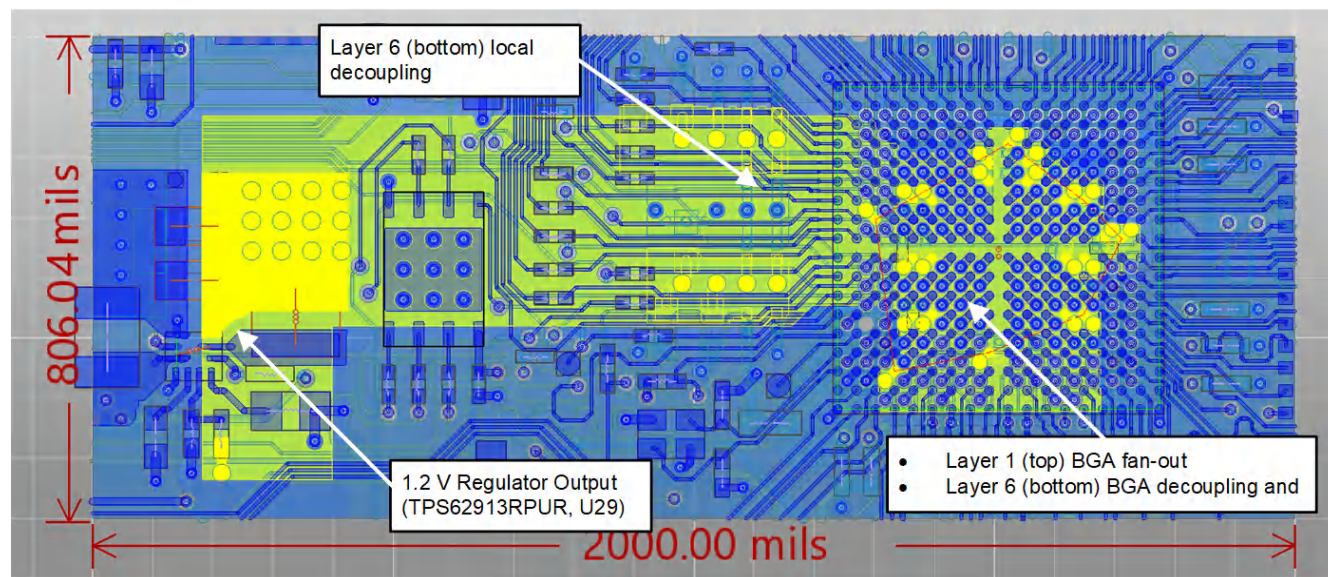

**Figure 2-13. AM263x LaunchPad PDN Simulations – 1.2V Core Power Simulation Domain**

 

**Figure 2-14. AM263x LaunchPad PDN Simulations – 1.2V Core Power Simulated Z11**

- AM263x LaunchPad PDN Simulations – 1.2V Core Power Simulated Z11
  - This resulted in the marker (m2) point of 5.5mΩ
  - $Z_{\text{target}}$  requirement of 36mΩ maintained from 50KHz to 63MHz
  - Major difference in BOM was replacing all 0.1μF BGA and local decoupling capacitors with 1.0μF capacitors - this entirely removed the 10MHz resonant point in the PDN impedance spectrum


### 2.5.1.2 Digital and Analog I/O Power 3.3V

Z11 simulations were performed on the 3.3V digital and analog power net of the controlCard EVM to verify transient power margin. The simulation domain included the:


- AM263x BGA (U1) 3.3V power and ground return BGA and fan-out
- Internal power and ground return routing layers
- Regulator output

Initial runs of these simulations showed that no BOM changes were needed to meet the maximum and minimum frequency bandwidth below Ztarget (see above sections). Only the initial simulation with the final chosen BOM iterations are shown below.

The simulations were divided between the VDDS33 digital 3.3V plane and decoupling network and the VDDA33 analog 3.3V traces and decoupling local to the design. The difference between these simulations is the FL18 ferrite bead element that was used to separate these two decoupling performance simulations.

 

**Figure 2-15. AM263x LaunchPad PDN Simulations – 3.3V Digital and Analog I/O Power Simulation Domain (A)**

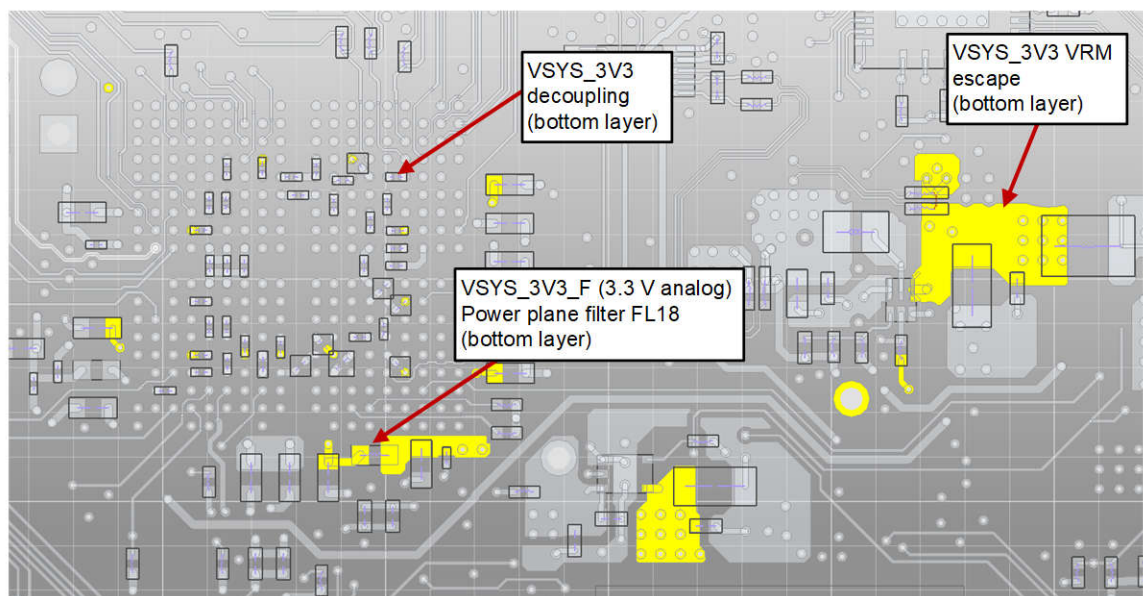

**Figure 2-16. AM263x LaunchPad PDN Simulations – 3.3V Digital and Analog I/O Power Simulation Domain (layer 8, bottom)**



 


Figure 2-17. AM263x LaunchPad PDN Simulations – 3.3V Digital I/O Power Simulated Z11

 


Figure 2-18. AM263x LaunchPad PDN Simulations – 3.3V Analog I/O Power Simulated Z11

## 2.6 eFuse Power

The AM26x MCUs have a one-time programmable eFuse memory that can be utilized for storing customer cryptographic keys and other information specific to individual devices. These e-Fuse memory locations can only be programmed when the target device eFuse power pin (VPP), is powered by a 1.7V nominal output voltage, 100mA peak current supply. This 1.7V VPP power supply can be on-board, off-board or sourced from the AM26x devices' internal 1.8V LDO, re-programmed to the required 1.7V/100mA supply.

The eFuse programming typically follows one or both of the following scenarios:


- **Factory programming** – eFuse memory programmed during post assembly test of the AM26x system.
- **Field programming** – eFuse memory is programmed after the device has left the factory and is installed in the end-equipment.

If the factory programming scenario is required for a product, then implementing the VPP power supply off-board reduces the number of components required to be placed on the PCB assembly. The VPP supply is only be used during this programming sequence, so keeping this hardware on the board is not an efficient use of PCB floor plan area, BOM cost, or test time.

However, if the eFuse memory must be programmed outside the factory environment, the VPP power must either be supplied from an onboard component or from an attached accessory board that can supply this power as needed.

### External VPP Supply

The specific placement of the VPP supply and implementation depend on how the eFuse memory is utilized by the designer. The implementation must follow the diagram shown in [Figure 2-19](#)

 


**Figure 2-19. AM26x eFuse VPP - External Power Supply Implementation**

On the AM263x controlCARD design, the VPP supply is populated on the board to enable convenient eFuse programming for customers experimenting with this process. On the controlCARD, the TLV75801PDRVR LDO (U66) is used to drop down the 3.3V system I/O voltage to the VPP 1.7V.

### On-Chip VPP Supply

The AM263Px and AM261x MCUs have the option to source VPP internally using the 1.8V Analog LDO (ANALDO). The ANALDO must be overwritten to provide 1.7V during eFuse programming, then reverted back to normal operation.



 

**Figure 2-20. AM263Px/AM261x eFuse VPP - Internal Analog LDO Implementation**

For the full VPP electrical requirements and eFuse programming sequence, see the *VPP Specifications for One-Time Programmable (OTP) eFuses* section in the device-specific AM26x Technical Reference Manual.


## 3 Clocking

### 3.1 Crystal and Oscillator Input Options

The AM26x XTAL\_XI and XTAL\_XO clock input can be sourced from either an attached crystal or a single-ended oscillator output.

#### Crystal Clocking Mode


The attached crystal needs to be a fundamental mode crystal operating at 25MHz. The crystal requires shunt capacitors, with capacitance ranging from 12pF-24pF. Figure 3-1 shows an example of the AM26x being clocked in crystal mode.

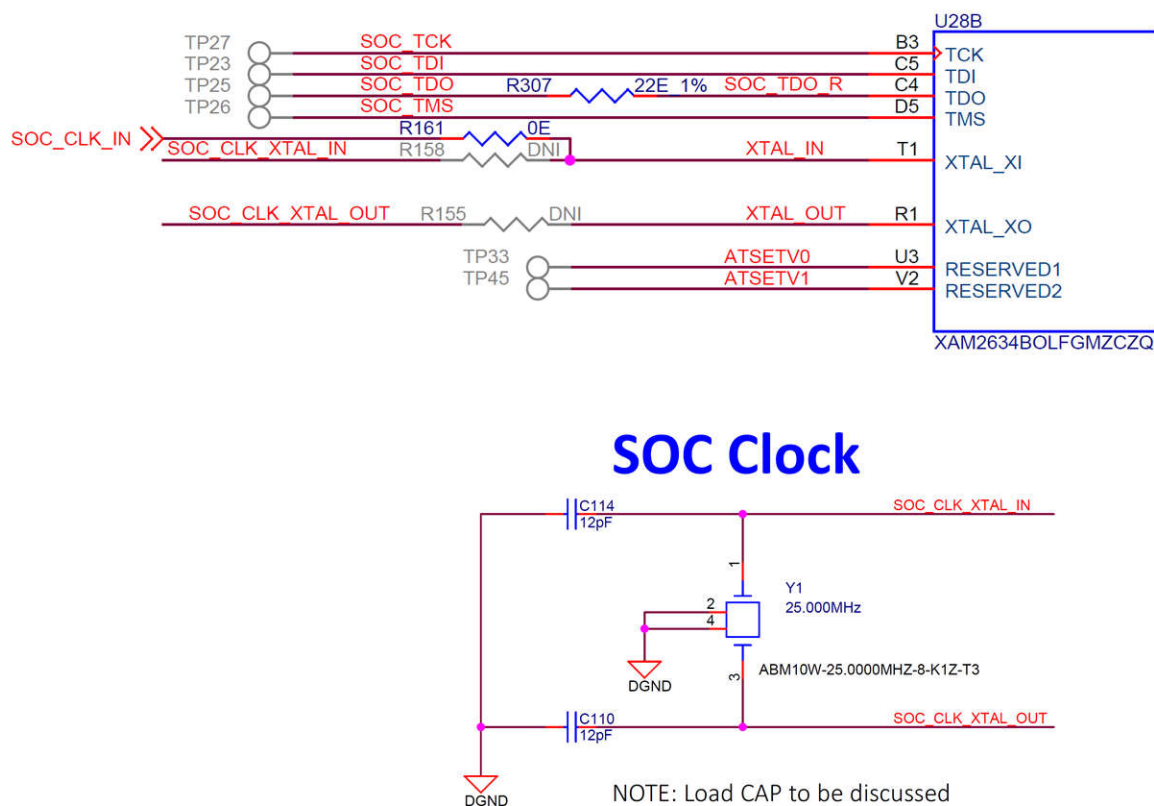

**Figure 3-1. Excerpt From AM263x Control Card Schematics (for full crystal and oscillator input requirements)**

## Oscillator Clocking Mode

If operating from a single-ended oscillator output, then the XTAL\_XI pin needs to be connected to the oscillator and the XTAL\_XO pin must be left floating, unconnected on the PCB. In oscillator input mode, the XTAL\_XI pin can be tied to either a 1.8V square wave or sine wave oscillator. For full oscillator input requirements, see the device specific AM26x data sheet. Figure 3-2 shows an example of an AM26x clock tree using a clock distributor and buffer circuit.

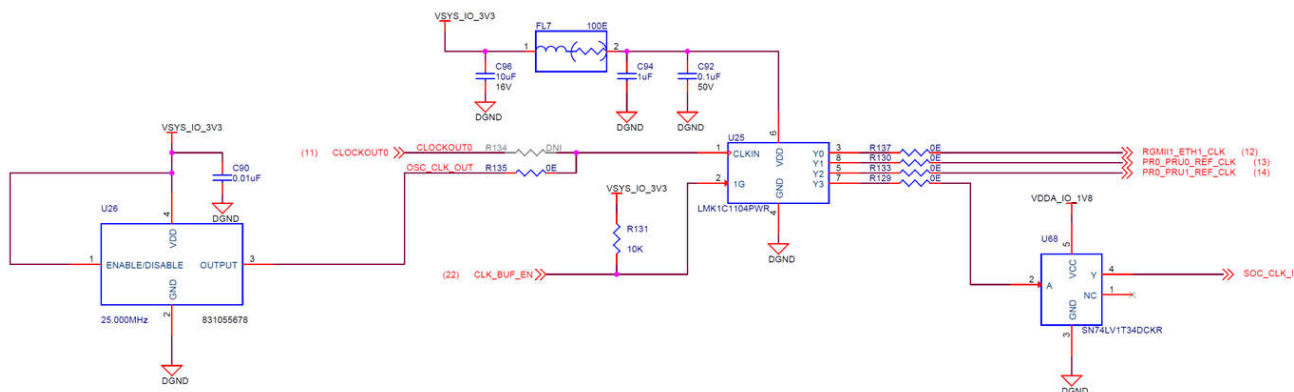

**Figure 3-2. Excerpt From AM263x controlCard Schematics - Oscillator Clock Source and Clock Distributor**

In the case of the AM263x Control Card, an onboard ABM10W-25.0000MHZ-8-K1Z-T3 25MHz crystal provides crystal mode clocking. Alternatively, an LMK1C1104PWR clock distributor circuit and SN74LV1T34 buffer provide the 1.8V square-wave clock to the XTAL\_XI pin. The LMK1C1104PWR is also used to provide a clock source to the onboard Ethernet PHY.

### 3.2 Output Clock Generation

The AM26x devices include two output clock sources, CLKOUT0 and CLKOUT1. These are intended to be used to clock attached peripheral IC such as Industrial/Automotive Ethernet PHYs. This can save on BOM cost and additional IC placement and routing space. The AM263x and AM263Px Launchpads include an optional path for the CLKOUT0 (pin M2) signal to clock the onboard DP83869HMRGZT Ethernet PHY. The AM261x LaunchPad includes an optional path for the CLKOUT1 pin signal to clock an Ethernet PHY via the Ethernet Add-on Board Connector. Unused CLKOUT pins can be left unconnected on the PCB.

The AM26x devices include one external reference clock source, EXT\_REFCLK0. This pin is intended to be used as an external reference clock input to the device clock generator PLL circuits. Unused EXT\_REFCLK pins can be left unconnected on the PCB. For more information on EXT\_REFCLK0, see the device-specific Technical Reference Manual.

 


Figure 3-3. Excerpt From AM263x LaunchPad Layout – CLKOUT0 and EXT\_REFCLK0 Output

### 3.3 Crystal Selection and Shunt Capacitance

In crystal operating mode, the AM26x can be interfaced to a wide variety of compatible crystals. Based on PCB parasitic capacitance and crystal selected, the additional load capacitance needs to be modified to achieve the best start-up stability and frequency accuracy.

For full crystal loading tolerances, see the device-specific AM26x data sheet.

### 3.4 Crystal Placement and Routing

Crystal oscillator input needs to be placed as close as possible to the AM26x XTAL\_XI/XO with minimal length traces between crystal and MCU pads. A ground ring shorted to the local VSS plane needs to be placed adjacent and between the XTAL\_XI and XTAL\_XO traces to help prevent coupling from adjacent signals onto the clock higher impedance crystal input paths.

 


Figure 3-4. Excerpt From AM263x Launchpad Layout - Crystal Layout and Ground Ring Structure

## 4 Resets

The AM26x MCUs have two hardware reset sources:

- **PORz:** Power on reset (logic low enable) pin
  - Must be driven from the power-good circuits of the associated VDD 1.2V core and VDDS33 3.3V I/O regulators or PMIC reset signal
  - For a valid reset the PORz signal must transition from logic low to logic high only after the VDD 1.2V core and VDDS33 3.3V I/O regulators are stable at the nominal values. For power-on-reset timing requirements, see the device-specific data sheet.
- **WARMRSTn:** Warm reset (logic low enable) input and reset status output pin
  - At power-on, the default configuration sets this pin as open-drain output, which outputs the reset status of the device.
  - When the device enters reset, this signal is driven logic low.
  - When the device is fully out of reset, this signal is driven logic high.

### PORz

The PORz is intended to be kept at logic low at initial startup of the system. Once each regulator sourcing the AM26x power pins has been verified to be operating at nominal output voltage, then the PORz signal can be brought up to logic high. This action starts the MCU boot ROM execution, beginning with sampling of the SOP pins.

#### PORz - Discrete Power Tree Implementation

The AM263x LaunchPad implementation utilizes a single SN74LVC1G11 AND gate which takes the open-drain output power-good signals from the onboard DC-DC regulators and an optional push-button reset switch as inputs to the AND gate. A weak pull-down resistor is recommended on the PORz signal to keep the signal at logic low before system startup. PORz must be forced low if either VDD 1.2V or VDDS33 3.3V rail power goes below the nominal operating range.

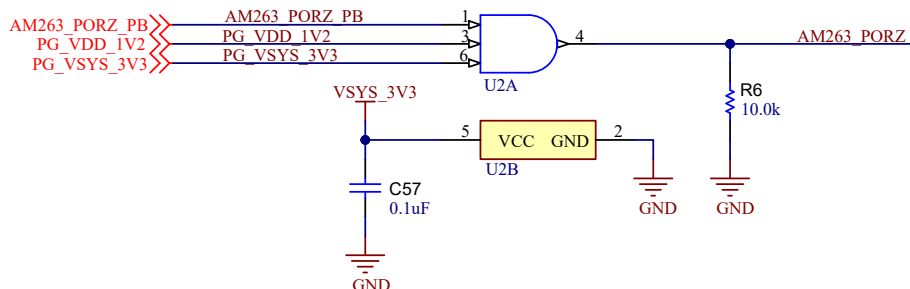


Figure 4-1. Excerpt From AM263x Launchpad Schematic – PORz Generation

## PORz - PMIC Based Power Design Implementation

For AM26x systems that utilize a PMIC-based power design, the PORz logic is slightly more complex. On the AM263Px controlCARD, the open-drain output power-good signal from the 1.2V regulator, the optional push-button reset switch, and the nRST signal from the PMIC are inputs to a SN74LVC1G11 AND gate. The output of the 3-input AND gate is connected to the input of a 2-input SN74LVC1G08 AND gate, with the other input being the output of a voltage divider of the system input voltage (5V) divided down to 0.88V. The output of the SN74LVC1G08 is connected to the AM26x PORz. The SN74LVC1G08 low-level input voltage is 0.8V, so the AND gate outputs a logic 0 if the input voltage drops below 0.8V, thus triggering a reset.

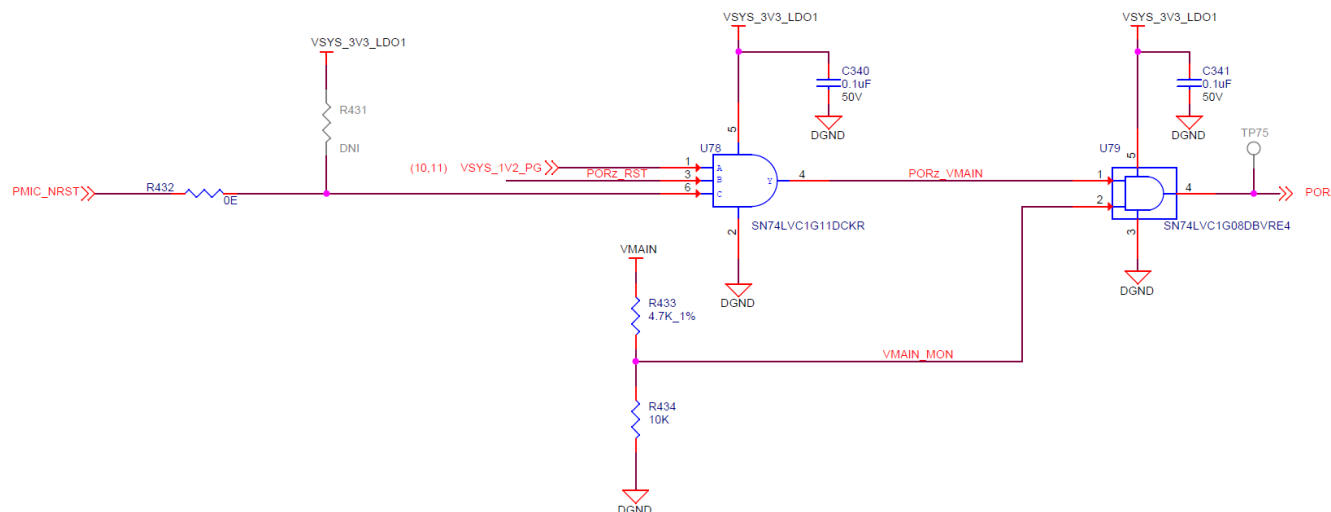


Figure 4-2. Excerpt from AM263Px controlCARD Schematic- PORz Generation

For AM261x system designs that use a single PMIC power design, such as TPS650360, the PORz generation is sourced from the PMIC nRSTOUT signal ANDed with a reset pushbutton. This is a simple and valid design that involves less redundancy and components.

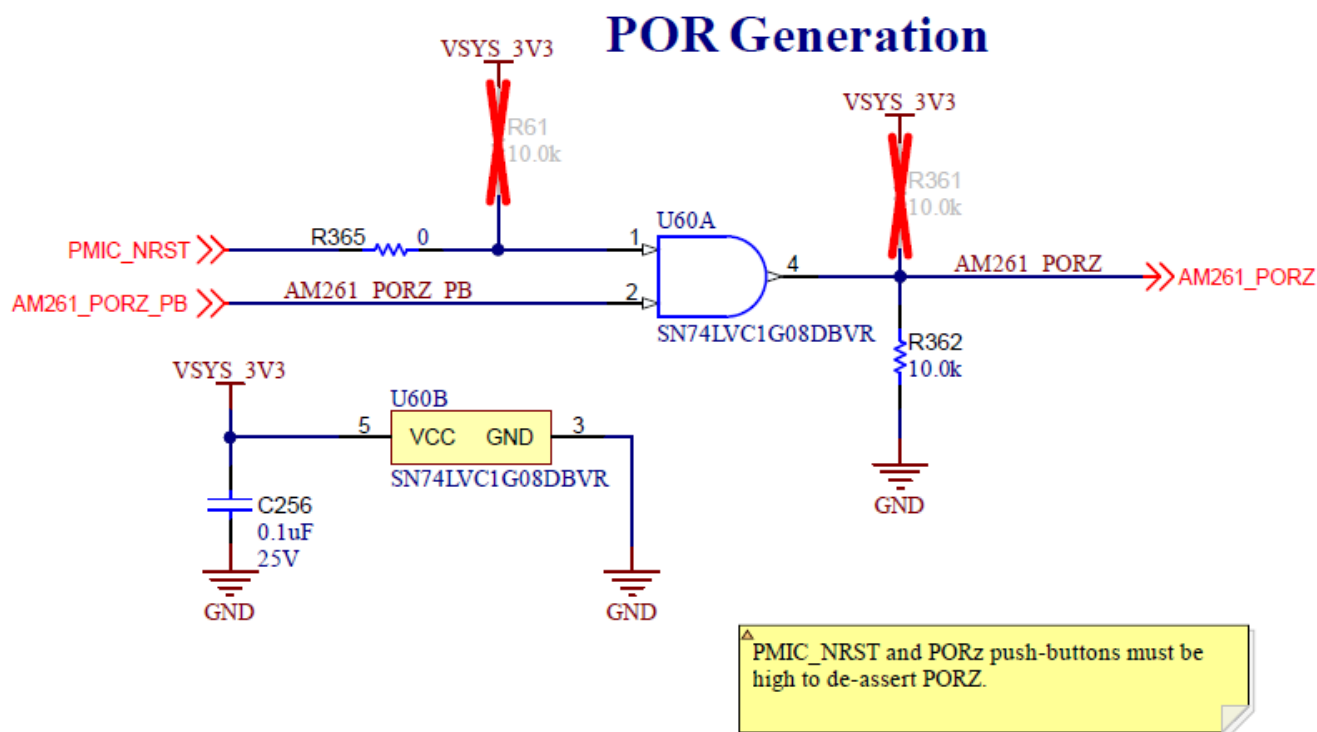


Figure 4-3. Excerpt from AM261x LaunchPad Schematic - PORz Generation

## WARMRST<sub>n</sub>

The schematic diagram illustrates the reset and safety circuit for the T2080. The pins are connected as follows:


- CLKOUT0** is connected to **CLOCKOUT0** (18).
- EXT\_REFCLK0** is connected to **HSEC\_EQEP1\_INDEX** (26).
- SAFETY\_ERRORn** is connected to **SAFETY\_ERRORn** (26).
- PORZ** is connected to **PORZ** (12,13,14,17,21,26).
- VSYS\_MON** is connected to **VSYS\_MON** (TP44, TP29).
- WARMRSTn** is connected to **WARMRESETn** (9,22).
- RESERVED0** is connected to **RESETz** (17).

The circuit is connected to the **DGND** and **DGND** pins. The components are labeled as follows:

- R1493** (0Ω) is connected to **DGND**.
- R325** (10K) is connected to **DGND**.
- R127** (0Ω) is connected to **RESETz** (17).

WARMRSTn can also be configured as a software reset. Additional software reset sources are available on the AM26x devices. For more information on reset functionality, see the *Reset* chapter in the device specific AM26x Technical Reference Manual.

Because of the default open-drain configuration of this pin, if both the reset status output mode and the software reset input mode is needed in a design, open-drain buffers are recommended to drive the optional reset input status. In the case of the AM263x Control Card, a SN74LVC1G07 open-drain buffer is used to optionally drive the push-button WARMRSTn without conflicting with the reset status output which is used to reset the Ethernet PHY onboard during initial board power-on.

 

**Figure 4-5. Excerpt From AM263x Control Card Schematic – WARMRSTn Push-Button Open-Drain Driver**



## 5 Bootstrapping

The sense-on-power (SOP) signals are used to latch in the selected boot mode into the AM26x device. During the PORz rising edge (low to high logic transition) the SOP[3:0] signals are sampled. The resulting 4 bits are used to branch the boot ROM into the selected boot mode. Not all combinations are supported. For a full description of the SOP pin states and supported boot modes, see the device-specific AM26x Technical Reference Manual.


### 5.1 SOP Signal Implementation

Each SOP bootmode selection signal is multiplexed with a subset of OSPI/QSPI and SPI peripheral functional mode signals. For all signal descriptions, see the *Signal Description* tables in the device-specific AM26x Data Sheet. The SOP signal descriptions are excerpted in Figure 5-1. The SoC pin number differs depending on device package type.

**Table 5-1. SOP and Functional Mode Signal Mapping**


SOP Mode Signal	Primary Pinmux Signal	AM26x ZCZ Pin	AM261x ZFG Pin	AM261x ZNC Pin	AM261x ZEJ Pin
SOP[0]	OSPI0/QSPI0_D0	N1	R2	N2	M2
SOP[1]	OSPI0/QSPI_D1	N4	R1	N1	N1
SOP[2]	SPI0_CLK	A11	A13	A12	A12
SOP[3]	SPI0_D0	C10	B12	B12	A10

Because of this SOP/functional-mode multiplexing additional care must be taken in schematic and layout to make sure that the SOP mode selection resistors, jumpers or switch paths are routed in such a way that the SOP mode branches do not present inductive PCB trace stubs to the functional mode signal paths. Failing to take care of this can result in non-functional OSPI/QSPI or SPI.

 


**Figure 5-1. Excerpt From AM263x Launchpad Schematic – SOP[3:0] Functional and SOP Paths**

In the AM263x and AM263Px EVM designs, this SOP mode isolation is accomplished by including a 10KΩ resistor in the SOP signal path. The resistor is placed such that one pad is as close to the AM263x BGA pad and in-line with the functional mode path. This creates a layout where the additional stub length necessary to breakout the SOP path results in minimal impact to the functional mode operation of the signals, as shown in Figure 5-2 and Figure 5-3.

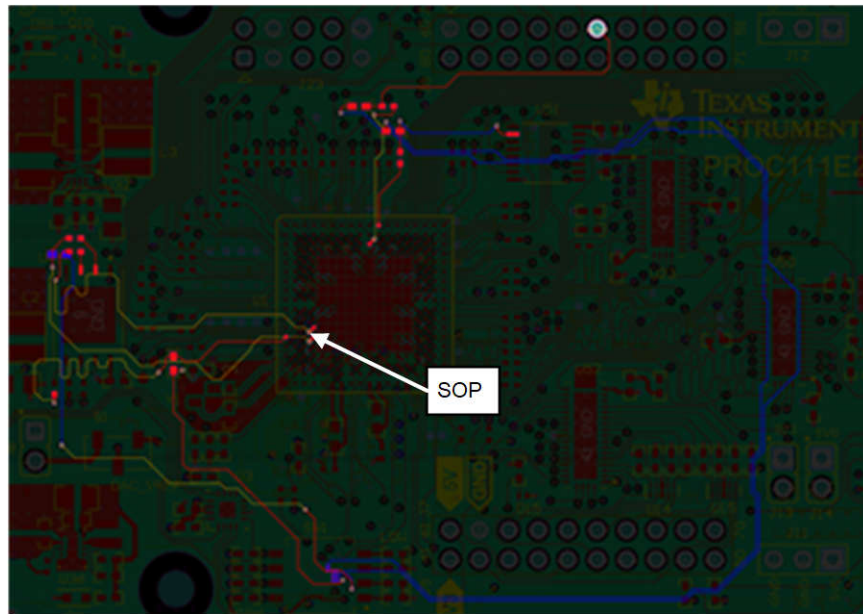

**Figure 5-2. Excerpt From AM263x Launchpad Layout – All SOP[3:0] Functional and SOP Paths**

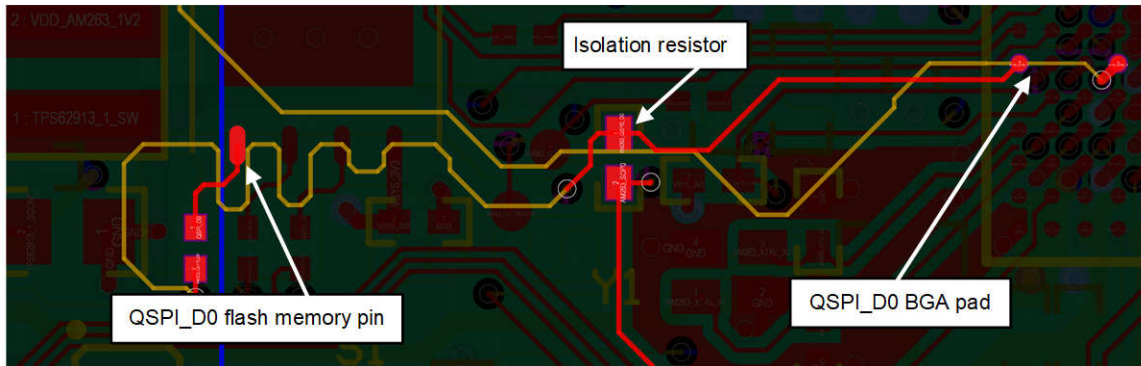

**Figure 5-3. Excerpt From AM263x Launchpad Layout – Highlighting SOP0/QSPI\_D0 Path and SOP Isolation Resistor**

### AM261x ZFG, ZEJ, ZNC Package SOP Isolation

On the AM261x ZFG/ZEJ/ZNC package devices, additional isolation is required to prevent driving the SOP pins before boot is complete, as the functional mode signals shared with the SOP nets are capable of driving the SOP[3:0] states strong enough to disrupt the boot mode setting. This is accomplished on the AM261x LaunchPad by implementing a mux with SOP pin functional mode signals as the inputs, and the nets shared with the SOP signals as the outputs. The Output Enable pin on the mux is controlled by an RC delay circuit driven by the device PORz signal. The RC delay circuit holds the mux enable signal low long enough for the SOP[3:0] pins to be driven and the device boot mode to be latched, thus preventing any voltage applied to the functional mode pins from driving the SOP nets. This scheme is detailed in the following figures:

## AM261x SOP[3:0]

 


Figure 5-4. LP-AM261 SOP Isolation Resistors

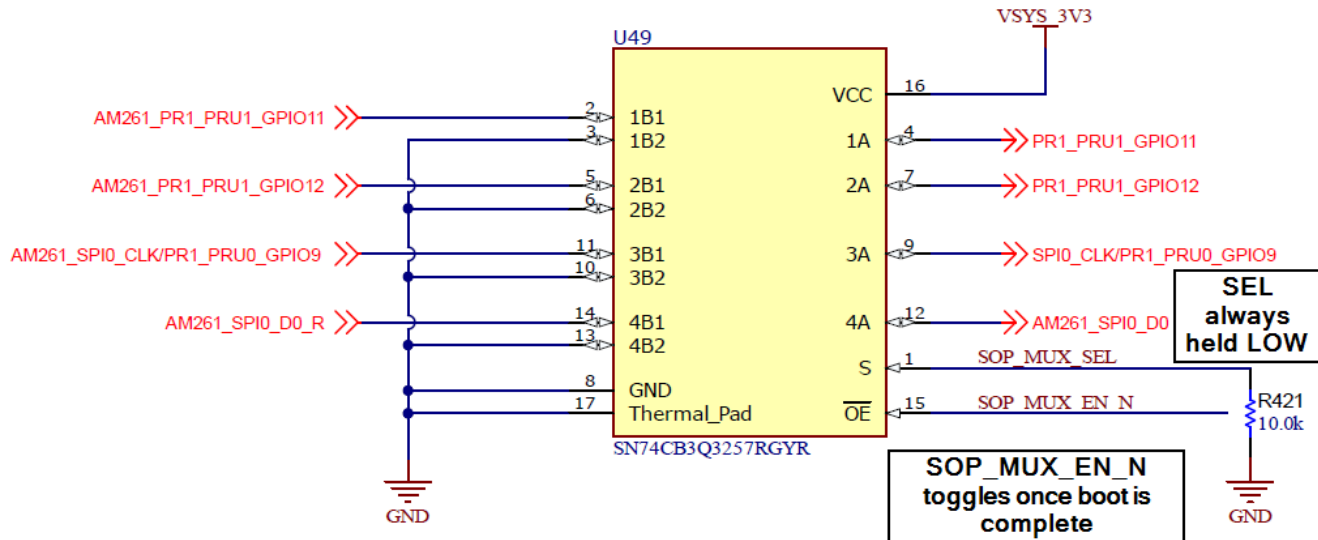


Figure 5-5. LP-AM261 SOP Isolation Mux

### PORz SOP Driver RC Delay

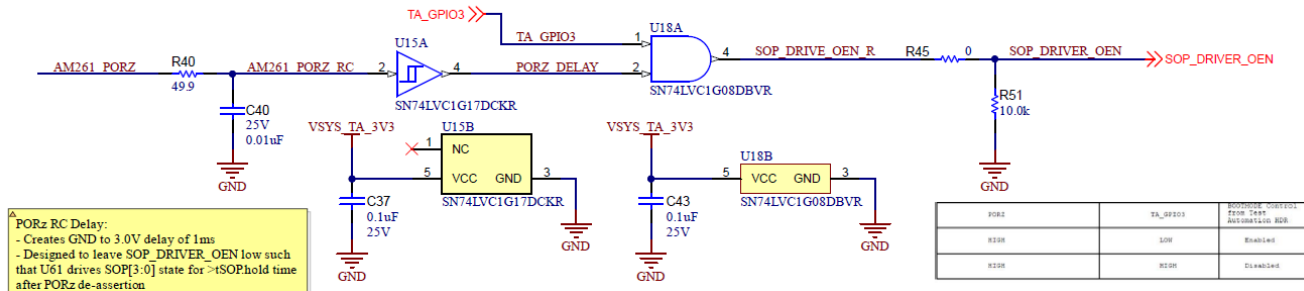


Figure 5-6. LP-AM261 PORz SOP Driver RC Delay

## SOP State Driver

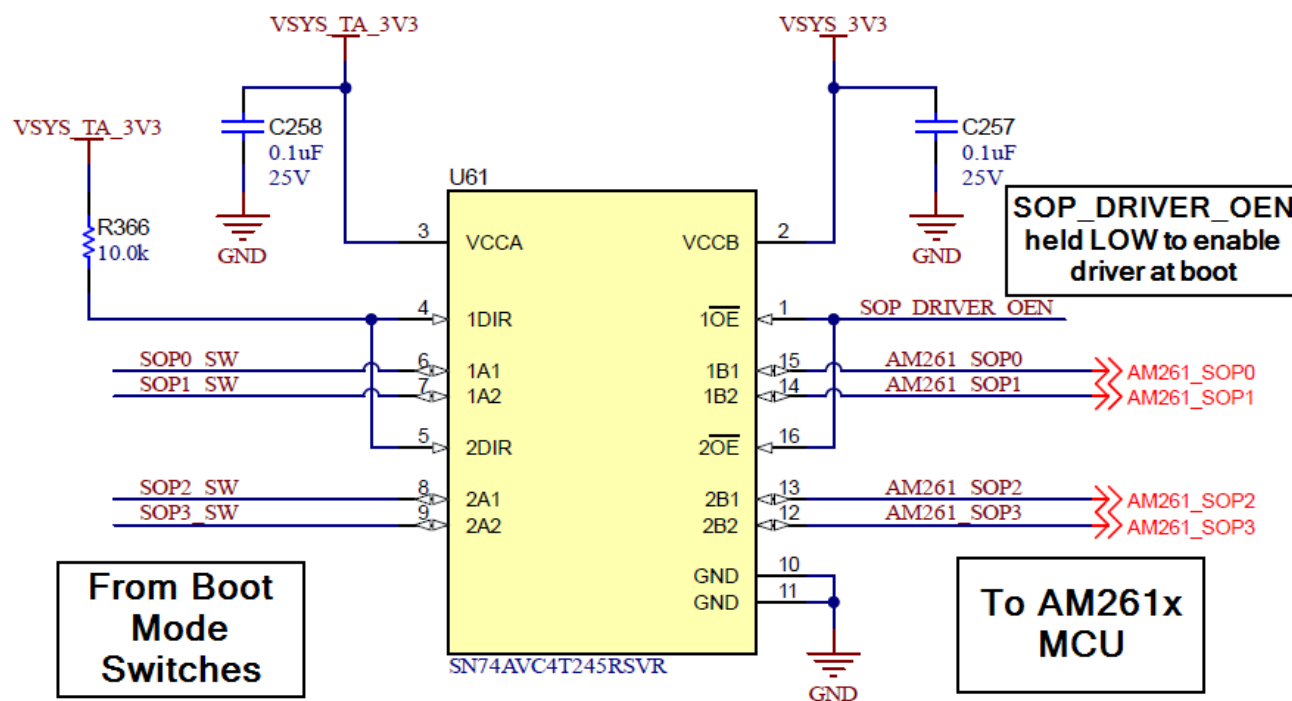


Figure 5-7. LP-AM261 SOP State Driver


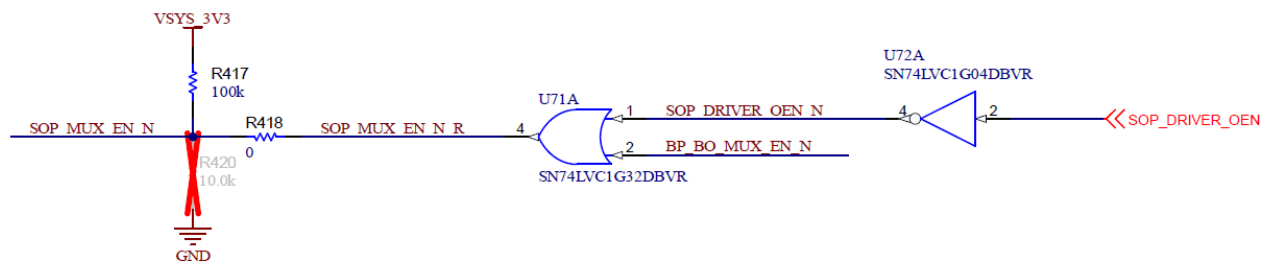


Figure 5-8. LP-AM261 SOP Isolation Mux Output Enable Generation

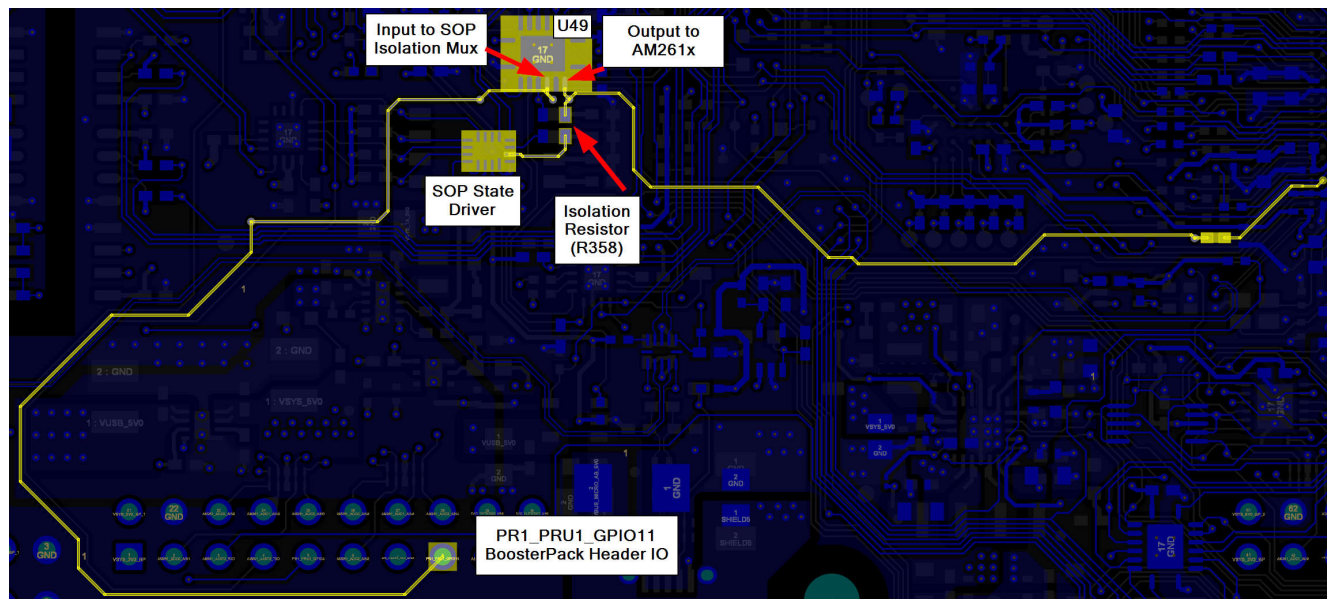


**Figure 5-9. LP-AM261 SOP Isolation - Layout**

The LP-AM261 implementation is likely more complex than necessary for a typical AM261x system due to the wide range of functions the EVM is required to support. For a simpler implementation, tying the delayed PORz signal to the isolation mux enable is sufficient. The key requirement is that there must be sufficient time for the SOP signals to latch the boot mode before any applied voltage is exposed to the shared functional signals.

## 6 OSPI and QSPI Memory Implementation

The OSPI Flash memory interface is the primary bootloader memory location for the AM263Px and AM261x MCUs, and the QSPI Flash memory interface is the primary bootloader memory location for the AM263x MCU. For a full description of boot ROM execution, including OSPI and QSPI boot information, see the device specific AM26x Technical Reference Manual. **The correct OSPI and QSPI pins configured by the AM26x boot ROM are connected to the flash memory device if the intention is to boot from the flash..** Refer to [Section 6.1](#) for additional details


The excerpt from [Figure 6-1](#) shows the implementation of the QSPI NOR flash interface from the LP-AM263 design.

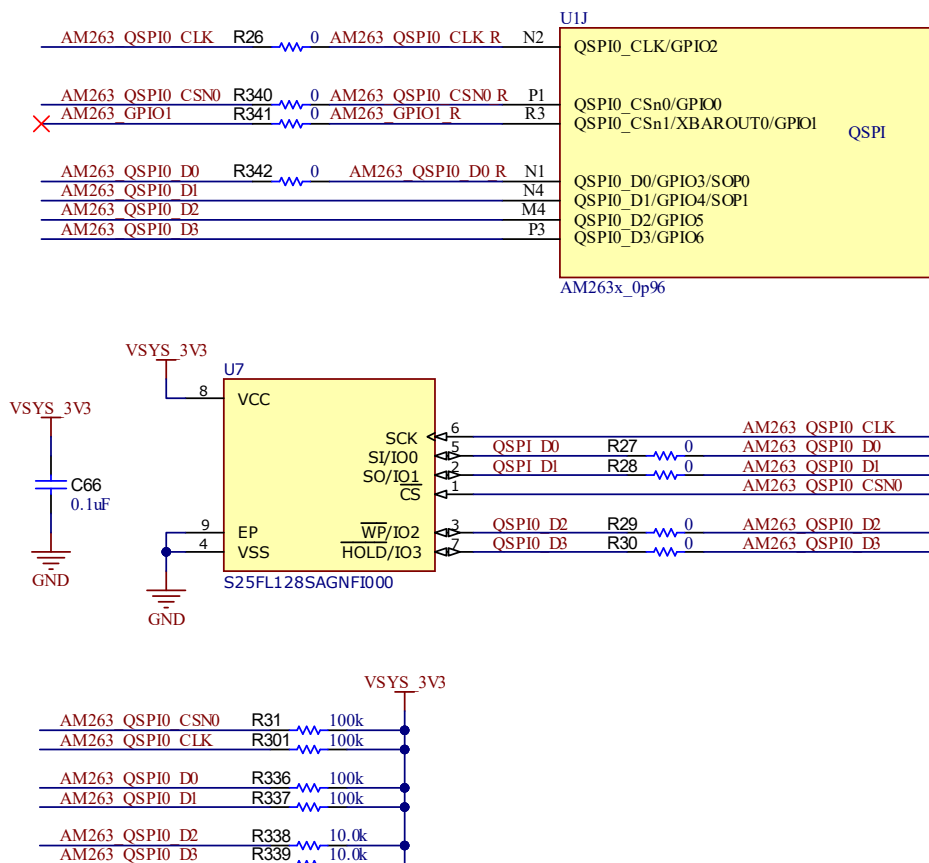

**Figure 6-1. Example AM263x QSPI Controller and NOR Flash Memory Schematic**

The excerpt from [Figure 6-2](#) shows the implementation of the OSPI NOR flash interface on the TMDSCNCD263P AM263Px controlCARD design.



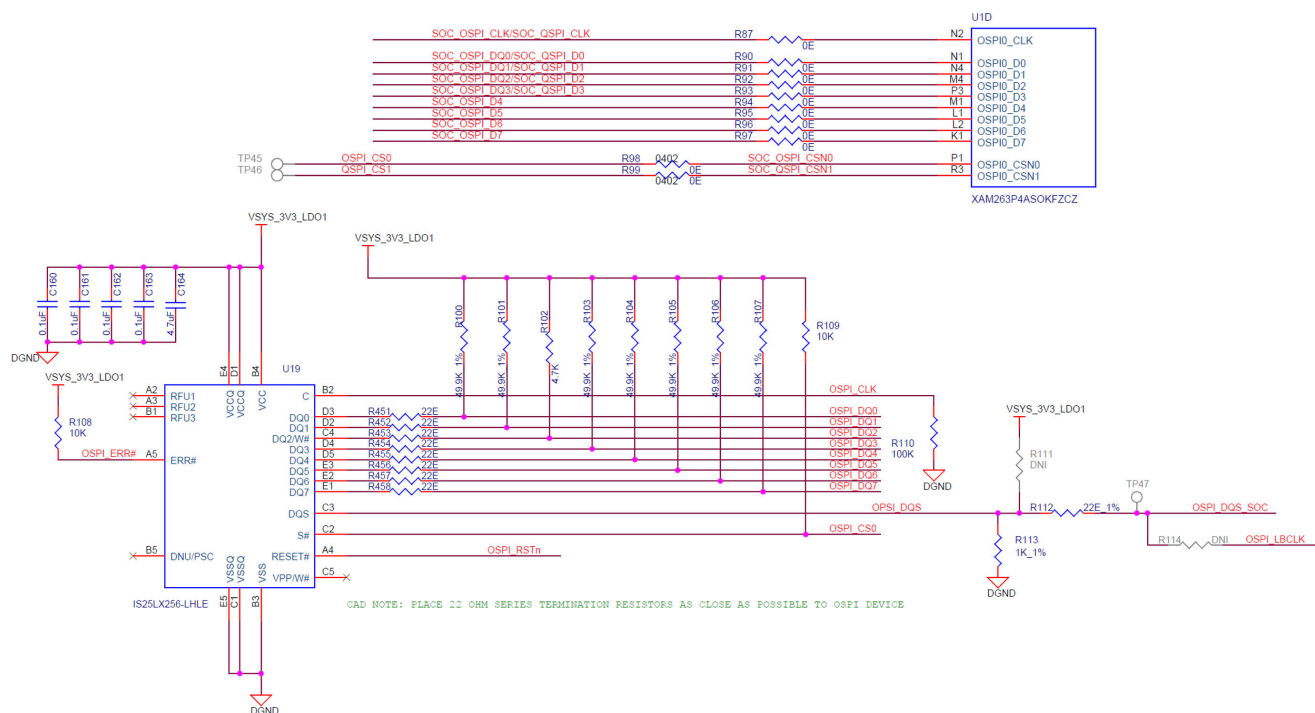

**Figure 6-2. Example AM263Px OSPI Controller and NOR Flash Memory Schematic**

## Series Termination Resistors

To control OSPI and QSPI bus transition overshoot and undershoot, include 22Ω series termination resistors close to the OSPI and QSPI memory pins. The OSPI\_D[7:1] and QSPI\_D[3:1] bits of the interface are used as a read interface and series termination resistors are used at the memory side of the bus. OSPI and QSPI\_D0 can benefit from termination resistors at both the MCU side and the OSPI and QSPI memory side of the bus when used as both a single-mode write and part of single-mode and octal and quad-mode reads. However, placement of additional termination on both sides of this bus can be difficult to achieve from a PCB floor-planning perspective. The termination scheme presented here must be used as a minimum recommendation.

## Power - AM261x ZFG, ZEJ, ZNC

AM263x, AM263Px, and AM261x ZCZ package devices are only capable of 3.3V-IO flash.

AM261x ZFG, ZEJ, ZNC are capable of operating flash in the 3.3V and 1.8V-IO domains. The flash IO level is set by supplying the corresponding power nets with the proper IO voltage - 3.3V or 1.8V:

**Table 6-1. AM261x ZFG, ZEJ, ZNC Flash Power Nets**

Power Rail	Device Power Net	Corresponding OSPI Peripheral
VDDSHV_D	FLASH0	OSPI0
VDDSHV_E	FLASH1	OSPI1

For example, if the OSPI device connected to OSPI0 operates at 1.8V logic, then connect a 1.8V to the VDDSHV\_D pins on the AM261x device. If OSPI1 operates at 3.3V logic, then connect a 3.3V supply to the VDDSHV\_E pins on the AM261x device.

## Pull Resistors - QSPI

Pull resistors are also necessary on the QSPI clock, chip-select, reset and data lines. Different OSPI/QSPI memories can have different pull-up/down requirements depending on the specific memory and application requirements. These pull resistor recommendations are based on the implementation of the S25FL128x memory

used on the LP-AM263 design. To confirm all pin memory configuration details, see the device-specific QSPI Flash memory data sheet. Include the following pull resistors on the QSPI signals:


- QSPI\_CLK, QSPI\_CS[1:0], and QSPI\_D[1:0] - include 100k $\Omega$  pull-up to VDDS33 IO supply.
- QSPI\_D[2] - 10k $\Omega$  pull-up to VDDS33 IO supply. This disables write-protect mode on the S25FL128 flash memories.
- QSPI\_D[3] - 10k $\Omega$  pull-up to VDDS33 IO supply. This disables hold mode on the S25FL128 flash memories.

### Pull Resistors - OSPI

Different OSPI memories have different pull-up and pull-down requirements depending on the specific memory and application requirements. These pull resistor recommendations are based on the implementation of the IS25LX256x memory used on the TMDSCNCD263P design. To confirm all pin memory configuration details, see the device specific OSPI Flash memory data sheet. Include the following pull resistors on the OSPI signals:

- OSPI\_CLK - include 100k $\Omega$  pull-down to GND
- OSPI\_CS - 10k $\Omega$  pull-up to IO supply
- OSPI\_DQS - 1k $\Omega$  pull-down to GND
- OSPI\_D[2] - 4.7k $\Omega$  pull-up to IO supply. This disables write-protect mode on the IS25LX256 flash memories
- OSPI\_D[1:0] and OSPI\_D[7:3] - 49.9k $\Omega$  pull-up to IO supply
- OSPI\_RESETh - 10k $\Omega$  pull-up to IO supply


Stronger pull-up resistors are used to disable write-protect and hold modes by default. Weaker pull-up resistors are used to keep the lines at valid logic levels between transactions. Pull resistors must be placed close to the OSPI and QSPI memory pins to prevent any additional routing stubs from being formed.

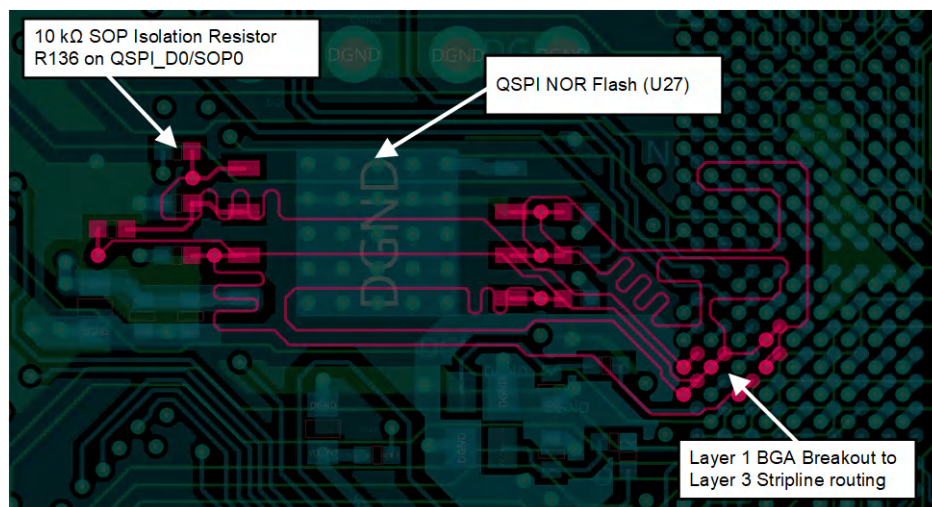

**Figure 6-3. Excerpt From LP-AM263 Launchpad Layout – Highlighting SOP0/QSPI\_D0 Path and SOP Isolation Resistor**


Additional routing guidelines for the QSPI memory interface are provided in [Figure 6-4](#) and [Table 6-2](#). These must be used as maximum routing delay and skew match limits. The QSPI memory must be placed close to the AM26x BGA footprint as possible. This allows for routing that maximizes the delay margins and skew margins and minimizes transmission-line effects.



 

**Figure 6-4. AM26x QSPI - Routing Rules Diagram**

Additional routing guidelines for the OSPI memory interface are provided in [Figure 6-5](#) and [Table 6-3](#). These are used as maximum routing delay and skew match limits. The OSPI memory must be placed close to the AM263Px and AM261x BGA footprint as possible. This allows for routing that maximizes the delay margins and skew margins and minimizes transmission-line effects.

 

**Figure 6-5. AM263Px. AM261x OSPI - Routing Rules Diagram**

**Table 6-2. AM26x QSPI – Recommended Routing Rules**

Spec No.	Specification	Value	Unit
1	QSPI_CLK, QSPI_CS0, QSPI_D[3:0] maximum delay	450	ps
2	QSPI_CLK to QSPI_D[3:0] maximum skew	50	ps
3	Approximate maximum routing distances	3214	mils
4	Approximate maximum routing skew	357	mils
5	A series termination resistor (R1 in diagram above) must be placed close to the QSPI_CLK transmit pin of the AM263x, AM263Px, AM261x to control rise-time and reflections of the clock line.	Variable, 0 to 40	$\Omega$
6	A series termination resistor (R2 in diagram above) must be placed close to the QSPI data pins of the attached memory to control rise-time and reflections of the data lines.	Variable, 0 to 40	$\Omega$

**Table 6-3. AM263Px, AM261x OSPI – Recommended Routing Rules**

Spec No.	Specification	Value	Unit
1	OSPI_CLK, OSPI_CS0, OSPI_D[7:0] maximum delay <sup>(1)</sup>	450	ps
2	OSPI_CLK to OSPI_D[7:0] and OSPI_CS <sub>n</sub> maximum skew	60	ps
3	OSPI_CLK to OSPI_DQS maximum skew	30	ps
4	Approximate maximum routing distances <sup>(1)</sup>	3214	mils
5	OSPI_CLK to OSPI_D[7:0] and OSPI_CS <sub>n</sub> approximate maximum routing skew	429	mils
6	OSPI_CLK to OSPI_DQS approximate maximum routing skew	214	mils
7	A series termination resistor (R1 in diagram above) must be placed close to the OSPI_CLK transmit pin of the AM263Px to control rise-time and reflections of the clock line.	Variable, 0 to 40	$\Omega$
8	Series termination resistor must be placed close to the OSPI data pins of the attached memory and the AM263Px device to control rise-time and reflections of the data lines.	Variable, 0 to 40	$\Omega$

- (1) This routing limit is applicable only in Fixed Timing modes in Internal PHY Loopback, Internal Pad Loopback, or External Board Loopback clock topologies. This does not apply when using DQS Clocking topology.

#### Note

Approximate routing distances are computed assuming a typical 140ps/inch propagation delay in 50 $\Omega$  FR4 Microstrip or Stripline transmission lines. A 2D field solver or appropriate closed-form approximate impedance model must be used to find more exact propagation delay for your specific stackup and routing.

## 6.1 ROM OSPI and QSPI Boot Requirements

The following sections detail the ROM Boot Requirements for booting from a QSPI or OSPI memory device on an AM26x MCU.

### 6.1.1 AM263x QSPI Boot Pin Requirements

The following pins are configured in the device boot ROM to enable boot from the QSPI flash device. These pins must be used in the connection between the AM263x MCU and QSPI flash.

**Table 6-4. AM263x QSPI Pins Configured in Boot ROM**

Package Name	Function Name	GPIO #	PinMux Mode #
QSPI0_CSn0	QSPI0_CSn0	0	0
QSPI0_CLK0	QSPI0_CLK0	2	0
QSPI0_D0	QSPI0_D0	3	0
QSPI0_D1	QSPI0_D1	4	0
QSPI0_D2	QSPI0_D2	5	0
QSPI0_D3	QSPI0_D3	6	0
QSPI_CLKLB	QSPI_CLKLB	145	0

## Reset

When using a QSPI\SPI flash device greater than 128Mb, a flash device package with a RESET signal must be used. This is due to the ROM only using a 3 byte addressing mode (address is 24 bits). To address the full memory address range, software typically switches to 4 byte addressing mode. If a reset to the processor occurs (for example, due to a warm reset), then the ROM executes expecting 3 byte addressing mode, but the flash is left in 4 byte addressing mode. For the flash device to return to 3-byte addressing mode, the flash device must be reset using this signal. This typically can be achieved by using the RESET signal on the flash memory device. ROM code does not issue a software reset command.

For more information, refer to the *QSPI Boot* in the *Initialization* section of the [AM263x Technical Reference Manual](#).

### 6.1.2 AM263Px OSPI and QSPI Boot Pin Requirements


The following pins are configured in the device boot ROM to enable boot from the OSPI (or QSPI) flash device. These pins must be used in the connection between the AM263Px MCU and flash device.

**Table 6-5. AM263Px OSPI Pins Configured in Boot ROM**

Package Name	Function Name	GPIO #	PinMux Mode #
QSPI0_CSn0	QSPI0_CSn0	0	0
QSPI0_CLK0	QSPI0_CLK0	2	0
QSPI0_D0	QSPI0_D0	3	0
QSPI0_D1	QSPI0_D1	4	0
QSPI0_D2	QSPI0_D2	5	0
QSPI0_D3	QSPI0_D3	6	0
MCAN0_RX	OSPI0_D4	7	2
MCAN0_TX	OSPI0_D5	8	2
MCAN1_RX	OSPI0_D6	9	2
MCAN1_TX	OSPI0_D7	10	2

## AM263Px OSPI Reset

The AM263Px can reset an OSPI flash device using the dedicated OSPI0\_RESET\_OUT mux mode on GPIO20, GPIO66, or GPIO64. On the AM263Px controlCARD, the on-board OSPI flash reset signal is generated from the output of an AND gate with PORz and OSPI0\_RESET\_OUT0 as inputs. This method allows the flash device to be reset when the AM263Px device is power cycled, or through a software reset command.

 

**Figure 6-6. AM263Px OSPI Reset Scheme**

For the AM263Px SIP (Silicon-In-Package) device, the boot ROM configures the internal device pads connected to the on-die OSPI flash for boot.

**Table 6-6. AM263Px-SIP Package OSPI Pins Configured in Boot ROM**

Package Name	Function Name	GPIO #	PinMux Mode #
QSPIO_CS <sub>n</sub> 0 <sup>(1)</sup>	QSPIO_CS <sub>n</sub> 0	65	6
QSPIO_CLK0 <sup>(1)</sup>	QSPIO_CLK0	9	6
QSPIO_D0 <sup>(1)</sup>	QSPIO_D0	0	6
QSPIO_D1 <sup>(1)</sup>	QSPIO_D1	66	6
QSPIO_D2 <sup>(2)</sup>	QSPIO_D2	8	6
QSPIO_D3 <sup>(1)</sup>	QSPIO_D3	69	6
MCAN0_RX <sup>(1)</sup>	OSPIO_D4	6	6
MCAN0_TX <sup>(1)</sup>	OSPIO_D5	67	6
MCAN1_RX <sup>(1)</sup>	OSPIO_D6	5	6
MCAN1_TX <sup>(1)</sup>	OSPIO_D7	68	6
GPIO7 <sup>(1)</sup>	OSPIO_DQS	7	6
GPIO70 <sup>(1)</sup>	OSPIO_ECC_FAIL	70	6
GPIO64 <sup>(3)</sup>	OSPIO_RESET_OUT0	64	5

(1) Each of these pins must be left unconnected with no PCB trace

(2) This pin must be connected to VDD<sub>S33</sub> through a separate external 4.7kΩ pull resistor placed as close to the device as possible

(3) To reset the on-die OSPI flash module, OSPI\_RESET\_OUT0 must be connected to an open-drain equivalent of PORz.

## AM263Px-SIP OSPI Reset

The AM263Px-SIP OSPI flash reset is generated using an open-drain version of PORz connected to the dedicated OSPI0\_RESET\_OUT0 pin configured by the device boot ROM. One method of implementing this is connecting the AM263Px-SIP PORz signal to the gate of a P-channel MOSFET, and connecting the source to the OSPI0\_RESET\_OUT0 (GPIO64) pin on the AM263Px-SIP MCU, with a 10kΩ pull-up resistor connected to this net. The drain of the P-channel MOSFET is to be connected to GND.

### 6.1.3 AM261x OSPI and QSPI Boot Pin Requirements

The following pins are configured in the device boot ROM to enable boot from the OSPI (or QSPI) flash device. These pins must be used in the connection between the AM261x MCU and flash device.

**Table 6-7. AM261x ZCZ Package OSPI Pins Configured in Boot ROM**

Package Name	Function Name	GPIO #	PinMux Mode #
OSPI0_CSn0	OSPI0_CSn0	0	0
OSPI0_CLK0	OSPI0_CLK0	2	0
OSPI0_D0	OSPI0_D0	3	0
OSPI0_D1	OSPI0_D1	4	0
OSPI0_D2	OSPI0_D2	5	0
OSPI0_D3	OSPI0_D3	6	0
MCAN0_RX	OSPI0_D4	7	2
MCAN0_TX	OSPI0_D5	8	2
MCAN1_RX	OSPI0_D6	9	2
MCAN1_TX	OSPI0_D7	10	2

**Table 6-8. AM261x ZFG, ZEJ, ZNC Package OSPI Pins Configured in Boot ROM**


Package Name	Function Name	GPIO #	PinMux Mode #
EPWM9_B	OSPI0_CSn0	62	6
MCAN1_TX	OSPI0_CLK0	10	5
OSPI0_CLK	OSPI0_D0	2	4
PR1_PRU0_GPIO9	OSPI0_D1	70	6
MCAN0_RX	OSPI0_D2	7	5
PR1_PRU0_GPIO2	OSPI0_D3	69	2
UART1_TXD	OSPI0_D4	76	2
PR1_PRU0_GPIO0	OSPI0_D5	67	2
MCAN0_TX	OSPI0_D6	8	2
PR1_PRU0_GPIO1	OSPI0_D7	68	2

#### Note

For AM261x devices in OSPI boot mode, the Boot ROM configures GPIO61 as the OSPI0\_RESET\_OUT0 signal and drives the pin low to reset an external OSPI device during this boot mode. **However, due to a reset signal management issue in the OSPI controller, this pin does not de-assert after an external OSPI flash device resets, thus holding any external flash device in reset and causing the boot to fail.** Refer to the [AM261x Errata](#) for more details. Workarounds are detailed in the following sections.

### OSPI Reset Implementation 1: PORz, WARMRESETn

Booting from an OSPI flash requires the flash to be reset before loading data to the AM261x device. Directly connecting PORz or WARMRESETn from the AM261x MCU to the flash device makes sure that the flash is reset upon system power-on, as PORz, WARMRESETn are LOW during boot and drive HIGH once power supplies are stable. Make sure that PORz or WARMRESETn are at the correct IO voltage level as the flash device.

 

**Figure 6-7. Resetting OSPI Flash Using PORz or WARMRESETn**

## OSPI Reset Implementation 2: Other GPIO with OSPI0\_RESET\_OUT0 PinMux (Suggested)

This implementation is recommended because there are both hardware and software reset options, and does not require an additional buffer. Any of the AM261x GPIOs listed in [Table 6-9](#) can be used post-boot as reset inputs to the OSPI flash reset logic, per the device data sheet pin mux. Make sure that the voltage levels of the reset logic inputs and output align with the flash device IO voltage. The suggested implementation is shown in [Figure 6-8](#).

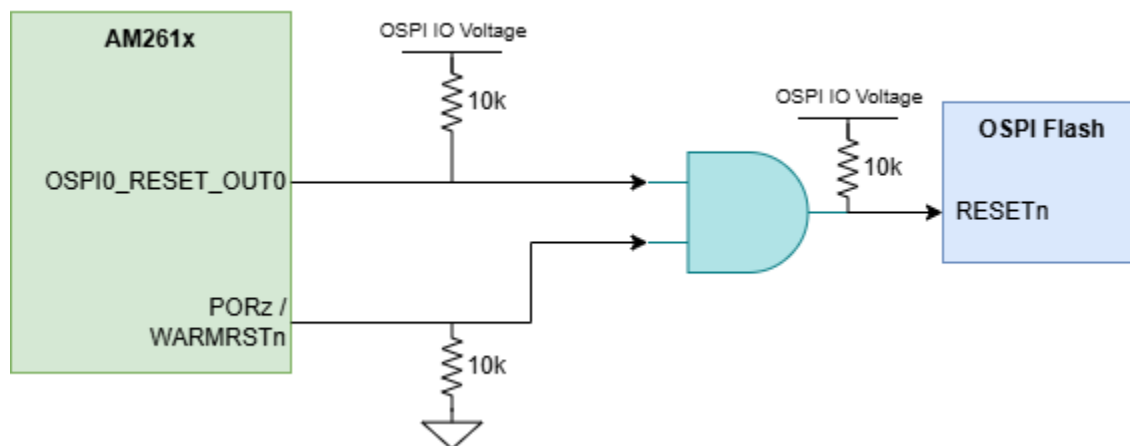


Figure 6-8. Resetting OSPI Flash Using OSPI0\_RESET\_OUT0 and PORz, WARMRESETn

Table 6-9. OSPI0\_RESET\_OUT0 Pin Options

GPIOx	PinMux Mode #
GPIO18 <sup>(1)</sup>	4
GPIO20	1
GPIO54	3
GPIO64 <sup>(2)</sup>	2
GPIO66 <sup>(1)</sup>	0

(1) ZCZ, ZFG, ZEJ packages only

(2) ZCZ, ZFG packages only

## OSPI Reset Implementation 3: Buffered GPIO61

GPIO61 can still be used to reset the OSPI flash by software as OSPI0\_RESET\_OUT0. This signal must be connected to an AND gate with PORz, WARMRESETn as the other input to drive the reset input to the flash device. However, the GPIO61 signal **must be buffered at boot to prevent the LOW signal from propagating to the OSPI reset logic**. This can be done by configuring the buffer output enable pin with a pull-down resistor and driving the output enable using any GPIO on the AM261x device. Make sure that the voltage levels of the reset logic inputs and output align with the flash device IO voltage.

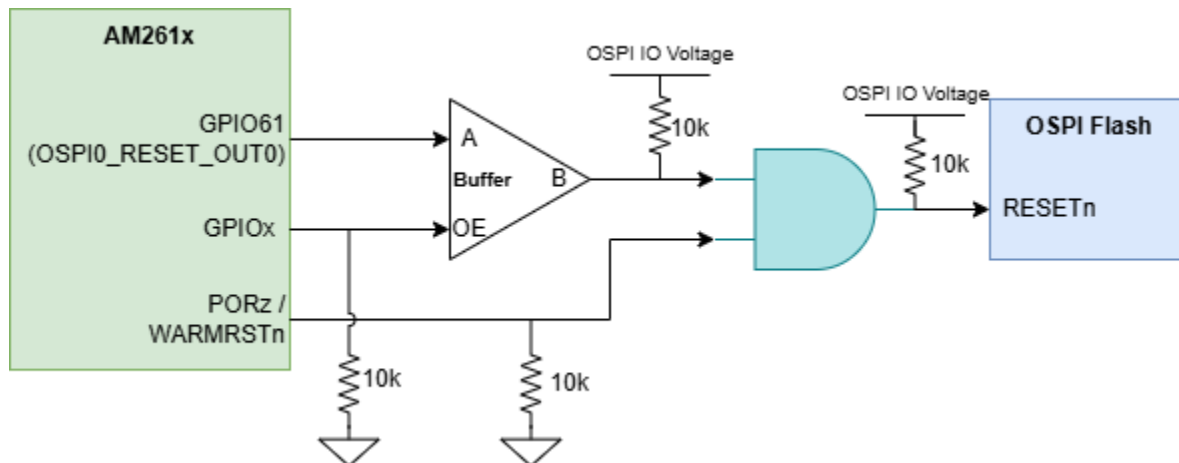


Figure 6-9. Resetting OSPI Flash using Buffered GPIO61 and PORz, WARMRESETn

## 6.2 Additional OSPI and QSPI References

For more information concerning QSPI flash memory compatibility and boot requirements on the AM263x microcontroller, see the [AM263x QSPI Flash Selection Guide](#).

### Note

The S25FL128SAGNFI000 Quad-SPI device from Infineon is utilized on the AM263x controlCard and LaunchPad EVMs.

For more information concerning OSPI flash memory compatibility and boot requirements on the AM263Px microcontroller, see the [AM263P OSPI, QSPI Flash Selection Guide](#).

### Note

The IS25LX256-LHLE Octal-SPI device from ISSI is utilized on the AM263Px controlCard and LaunchPad EVMs and the AM261x controlSOM and LaunchPad EVMs.

For more information concerning OSPI flash memory compatibility and boot requirements on the AM261x microcontroller, see the [AM261x OSPI, QSPI Flash Selection Guide](#).

### Note

The MX25UW6445GXDQ00 Octal-SPI device from Macronix is utilized on the AM261x LaunchPad EVM.

## 7 Debug Interfaces

When designing an AM26x PCB system, route out the debug interfaces of the MCU for connecting to the device cores and checking device health at platform bring-up. The two main debug interfaces on AM26x devices are JTAG, TRACE and UART.

### 7.1 JTAG Emulators and Trace

The AM26x MCUs support multiple different classes of JTAG emulators with or without additional ARM Trace capture capabilities.

For out of box convenience, the LP-AM263, LP-AM263P, LP-AM261, TMDSCNCD263, and TMDSCNCD263P EVM designs implement an onboard XDS110 emulator with JTAG and auxiliary UART-USB bridge implemented with a TI TM4C MCU and high-voltage isolation. However, for actual custom systems, a simpler JTAG or Trace debug header must be implemented. This allows for external JTAG and Trace pods to be attached to the system as needed during development. The header can then be removed entirely or depopulated for full production of the system to save cost.

One popular JTAG and Trace implementation is the MIPI industry standard MIPI-60 shown in [Figure 7-1](#). This is based on the Samtec QSH-030-01-L-D-A. The AM263x controlCARD Docking Station (TMDSHSECDOCK-AM263) and the AM261x controlSOM EVM (AM261-SOM-EVM) feature a MIPI-60 with the full JTAG and 16-bit trace interface of the microcontroller broken out to the header. This implementation is compatible with TI XDS560v2 JTAG or trace pods and other third-party JTAG/Trace pods. Additional TI JTAG debugger connections can be found in the [JTAG Connectors and Pinout](#) document.



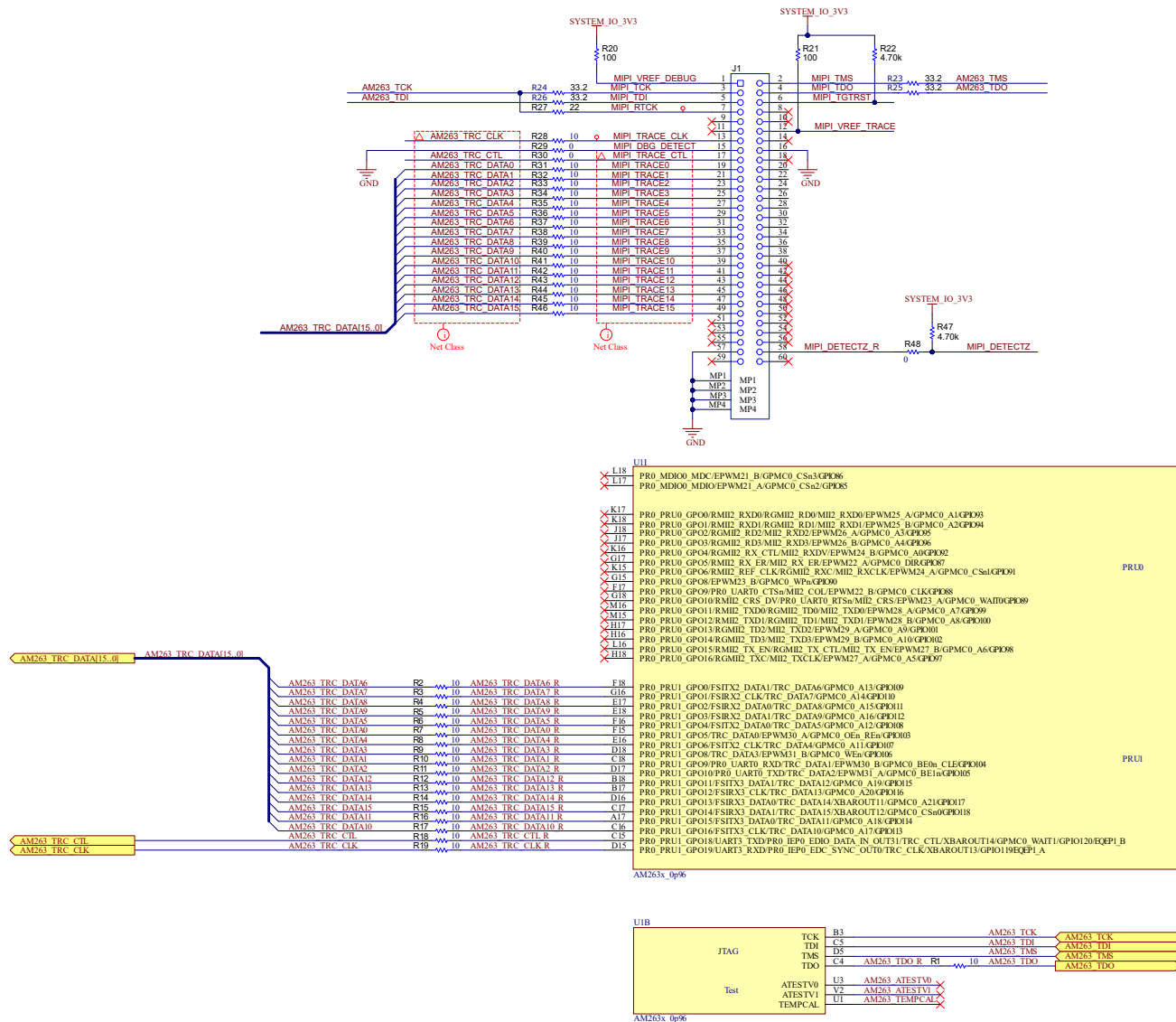


Figure 7-1. Example MIPI-60 JTAG and 16-bit Trace Implementation

## 7.2 UART

On all AM26x devices, UART0 is configured by the device ROM code to 115200 kbaud, 8-n-1 mode, and uses the XMODEM protocol to transfer boot data when the AM26x is placed in UART Boot Mode.

Route out the UART0\_RX and UART0\_TX signals to accessible headers for connecting a UART to USB bridge to access boot data and check AM26x MCU health at system bring-up. This can aid in debugging a prototype system and make sure that the AM26x device is booting properly at power-on.

## 8 USB

The AM261x family of microcontroller devices include an internal USB 2.0 PHY that supports USB Device Mode, USB Host Mode, and USB Dual-Role Mode operation. The internal USB 2.0 PHY is capable of high speed (HS, 480Mbps) and full speed (FS, 12Mbps) operation in both USB 2.0 Host and Device mode, and low speed (LS, 1.5Mbps) operation in host mode only.

The critical component of the internal USB PHY is the bidirectional differential data pins USB0DM (D-) and USB0DP (D+). The USB0\_ID signal is an external net that interfaces with the USB receptacle, indicating which mode the USB2.0 PHY is operating in. On the AM261x EVMs, USB0\_ID is set with a switch, allowing evaluation of the USB 2.0 PHY for both modes.

### USB2.0 Micro\_AB PORT

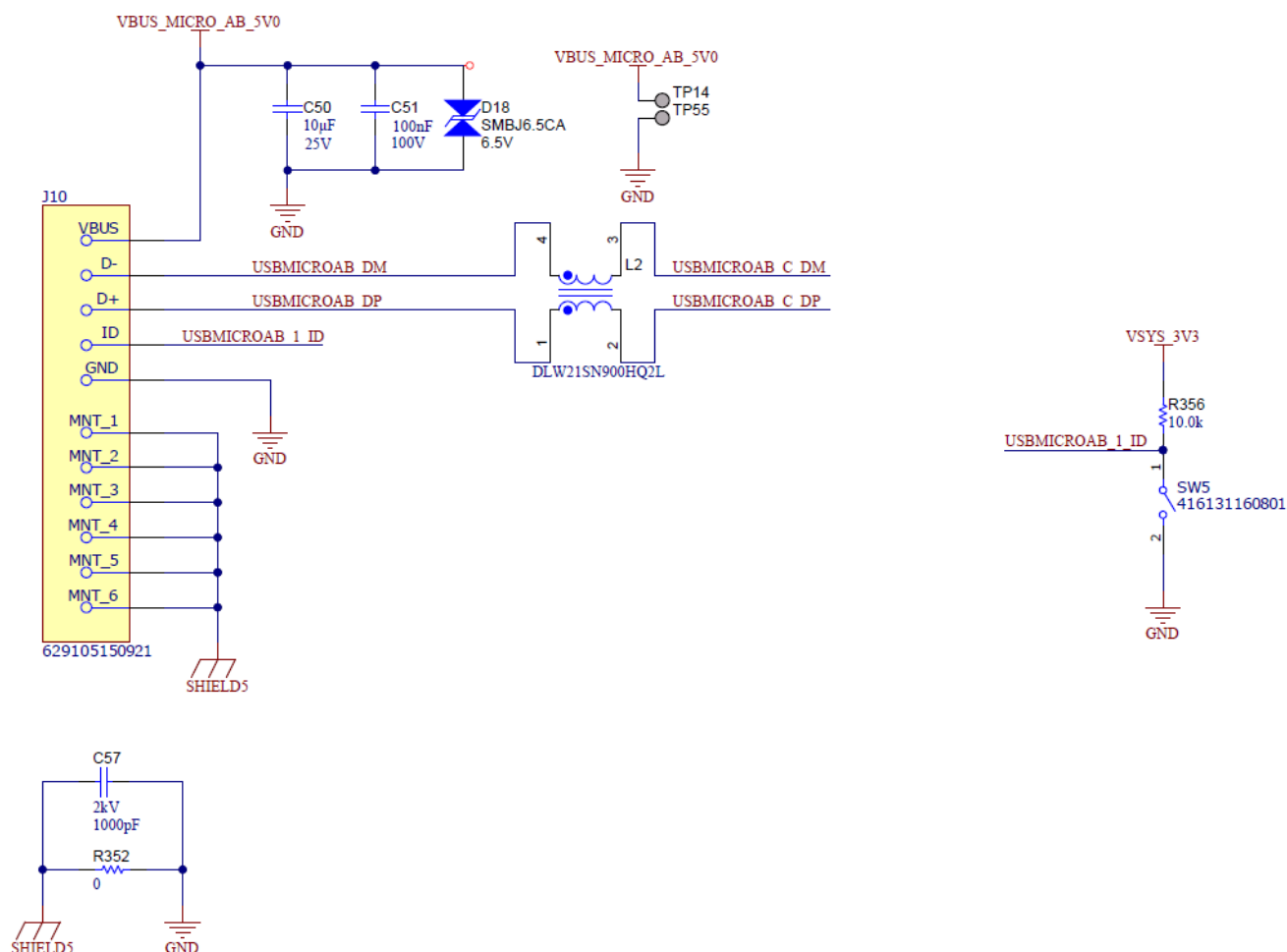


Figure 8-1. USB 2.0 Micro-AB Port Showing Critical Signals - LP-AM261

The following design rules and recommendations need to be followed when routing the USB differential pair for best results:

- Route the USB differential pair on the top layer with trace width and differential spacing tuned to the PCB stack-up for 90Ω differential impedance.
  - This can be difficult to implement a trace geometry that achieves both 90Ω differential impedance and 45Ω single-ended impedance. The most critical parameter to optimize in this design is the 90Ω differential impedance.
  - The trace width and spacing to maintain the required 90Ω differential trace impedance directly at the pins of the microcontroller and directly at the ESD suppressor and USB connector is not possible to achieve. Minimize these deviations as much as possible being sure to maintain symmetry.
- The individual traces within the differential pair needs to be length-matched to within 0.150in (3.81mm).
- Avoid stubs when adding components to D+ and D– signals. Devices such as ESD suppressors must be located directly on the signal traces.
- Maintain symmetry when routing differential pairs. Some PCB layout tools can assist with this kind of routing. Avoid vias if possible. If this is necessary to switch layers, then both signals in the pair pass through a via at the same distance on the trace.
- Total trace length for the USB differential pair is limited to 12 in (30.48 cm).
- Place ESD suppressors as close as possible to the USB connector to minimize any areas of impedance discontinuities. AM261x EVMs utilize the [TPD4E02B04](#) ESD protection diode.

## USB Micro-AB ESD Protection


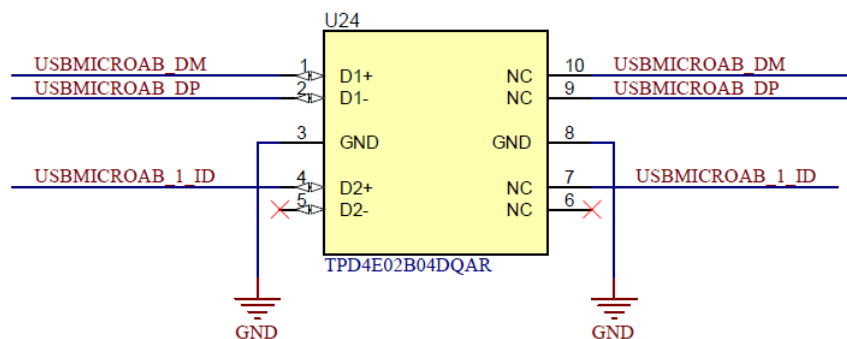


Figure 8-2. USB ESD Suppression - LP-AM261

- For best ESD and EMI performance, create a chassis ground to which the metal shield of the USB connector is connected.
- Depending on the system design, a common mode choke can be helpful to pass EMI testing. A DLW21SN common mode choke by Murata is one recommended device, and is utilized on the AM261x EVMs. If EMI is a concern for the design, then TI recommends that a footprint for the choke be included in the design placed close to the USB connector. [Figure 8-3](#) shows the placement of a DLW21SN choke.
- Additional High Speed USB Platform Design Guidelines including more details on using a common mode choke can be found at [USB.org](http://USB.org).

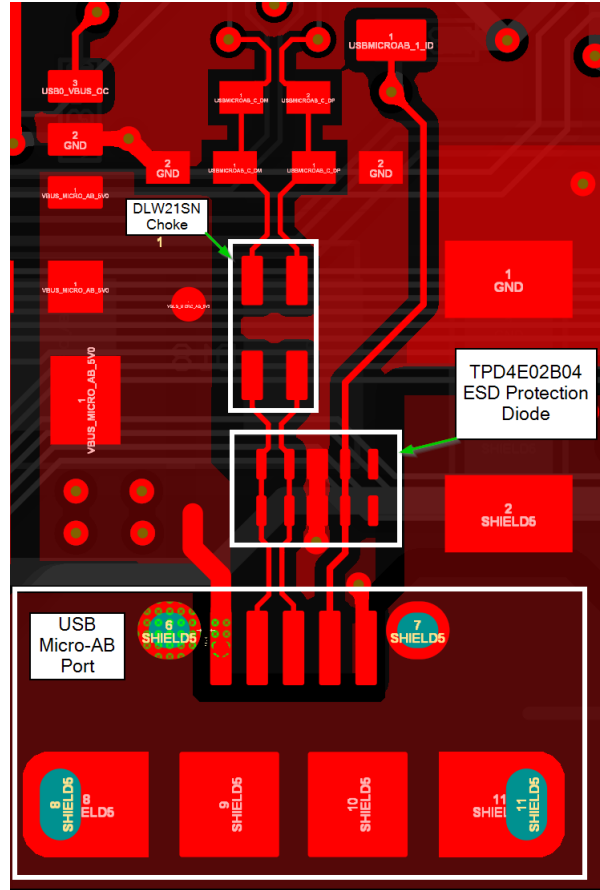

**Figure 8-3. USB Routing Example**

## 8.1 USB Device Mode

For using an AM261x device in USB2.0 Device Mode, the only signal used in addition to USB0\_DM and USB0\_DP is USB0\_VBUS, which is located on pin 1 of USB 2.0 Micro-AB, USB2.0 Type-A, and USB 2.0 Type-B receptacles. In USB device mode, USB0\_VBUS is used to detect when voltage has been applied to or removed from the USB connector, which triggers software to manage the internal USB PHY accordingly.

To indicate Device Mode operation, the USB0\_ID pin on the USB receptacle needs to be left floating or pulled up to a valid logic level using a 10kΩ resistor.

## 8.2 USB Host Mode

For AM261x devices that are used in a host-only configuration, the USB0\_DRVVBUS signal is required. This USB 2.0 PHY signal connects to a power switch, such as the [TPS2051B](#) that is implemented in the AM261x LaunchPad and AM261x controlSOM EVM designs. The power switch controls power to the host's USB connector. Refer to the AM261x data sheet to determine which IO pins the USB0\_DRVVBUS functions are available on.

### USB micro AB Power-Distribution Switch

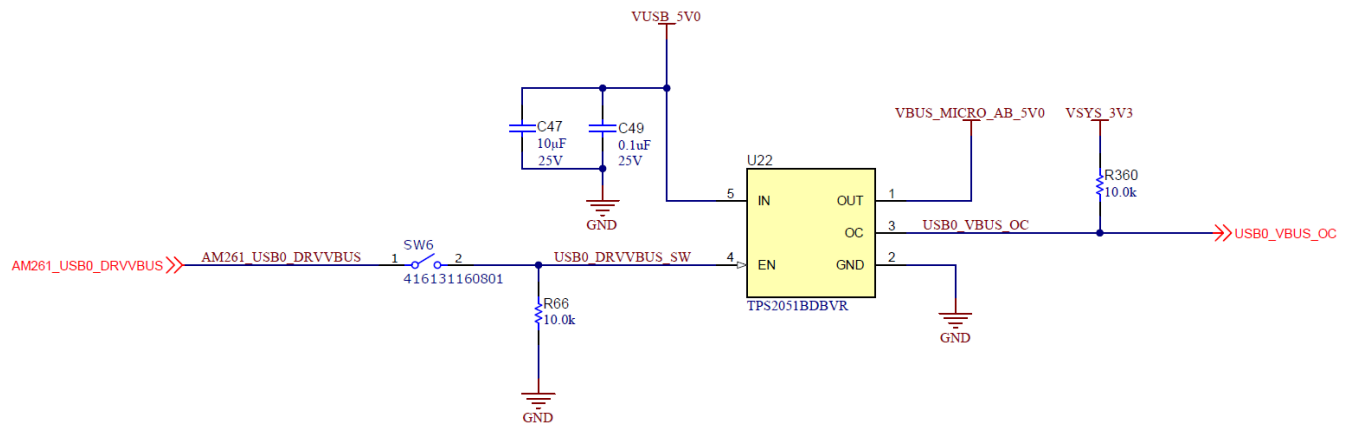


Figure 8-4. USB Host Mode Power Switch - LP-AM261

 


Figure 8-5. TPS2051B Layout Example - LP-AM261

To indicate Host Mode operation, the USB0\_ID pin on the USB receptacle is connected to GND.

## 9 Multiplexed Peripherals

With the large number of multiplexed digital I/O present on the AM26x MCU IOMUX, designers are recommended to make full use of the TI System Configuration tool (SysConfig) to experiment and plan different pin multiplexing scenarios before committing the design to hardware. The resulting SysConfig pin multiplexing configurations can then be used for schematic capture, layout, and software driver creation.

For more details, see <https://www.ti.com/tool/SYSCONFIG>.

## 10 Digital Peripherals

### 10.1 General Digital Peripheral Routing Guidelines

The following general routing recommendations need to be followed throughout an AM26x PCB design. The 45nm LVCMOS process I/O can produce relatively fast edge-rates. Without transmission-line effects planned for, this can result in severe overshoot or undershoot even with relatively short traces on the PCB. These uncontrolled level transitions can damage associated components by presenting attached I/O with over/under-voltage conditions. Additionally, these uncontrolled transitions can radiate excessively which creates cross-talk and EMI compliance problems.

To mitigate these problems:

- Route all digital I/O as controlled impedance transmission-lines (microstrip or stripline).
- Place series termination near each AM26x transmit pin and attached transmit pins of associated IC.
  - The values and performance of these termination resistors need to be validated during wake-up of new PCB hardware.
  - In some cases, these termination resistors are not required, but need to only be removed or eliminated from the design after testing. 0Ω resistors can aid in creating footprints where termination resistors are needed.
- Route with solid ground return planes on adjacent layers.
- Route with ground return rings surrounding constantly switching signals (clocks, EPWM).
- Route with ground return rings surrounding sensitive analog signals (ADC/DAC channels, VREF).

For additional guidance on peripheral routing, refer to [High-speed Interface Layout Guidelines](#).

### 10.2 Trace Length Matching

AM26x microcontrollers are equipped with several peripherals that require strict adherence to trace length matching guidelines. TI highly recommends that any engineer designing a PCB system using AM26x and utilizing the following device peripherals reviews the contents of [High-speed Interface Layout Guidelines](#) and applies these guidelines to the AM26x PCB design.

AM26x digital peripherals that require trace length matching are listed below:

**Table 10-1. AM26x Digital Peripherals - Trace Length Matching**

AM26x Peripheral	Applicable Devices	Notes
USB	AM261x	• See <a href="#">Section 8</a> for more information
QSPI	AM263x, AM263Px, AM261x	• Critical signals are QSPI_D[3:0] and QSPI_CLK
OSPI	AM263Px, AM261x	• Critical signals are OSPI_D[7:0] and OSPI_CLK
MMC	AM263x, AM263Px, AM261x	• Critical signals are MMC0_D[3:0], CLK, and CMD
FSI	AM263x, AM263Px, AM261x	• Lower priority, but helps reduce skew between signals
RGMII Ethernet	AM263x, AM263Px, AM261x	• RX and TX signals are critical • RX signals only need to be matched to other RX signals • TX signals only need to be matched to other TX signals • RX or TX signal groups can be different lengths

## 11 Analog Peripherals

### 11.1 General Analog Peripheral Routing Guidelines

The following general routing recommendations need to be followed throughout the analog portions of an AM26x PCB design. Analog signals are especially sensitive to cross talk and requiring clean signal return paths for maximizing signal integrity.

To mitigate these problems:


- Isolate all analog signals as much as possible with ground isolation between the analog trace and any adjacent trace.
- Route analog signals with solid ground return layers on adjacent layers.
- Avoid routing analog signals near high speed or current signals.
  - When impossible to totally avoid high speed or current signals, cross the traces perpendicularly to avoid as much cross-talk as possible.
- Adding signal amplifier and filter networks can promote signal integrity.

For the SAR ADCs on AM26x, refer to the *Choosing an Acquisition Window Duration* section of the device-specific AM26x Technical Reference Manual and Register Addendum documents for additional guidance.

#### 11.1.1 Resolver ADC Routing Guidelines

The AM263Px Sensor package includes two Resolver to Digital Converter (RDC) peripherals. A resolver is a type of rotary electrical transformer used for measuring degrees of rotation which is typically attached to an electrical motor. A typical resolver consists of a rotary transformer (exciter winding) and two windings separated by 90 degrees on the stator. An excitation sinusoidal signal is applied to the excitation coil of the resolver and the rotation of the motor causes modulated sine and cosine outputs on the sine and cosine sense coils of the resolver. The angle of the modulated sine and cosine signals is directly related to the mechanical angle of the rotor compared to the stator and the speed of the motor rotation.

The AM263Px RDCs generate an excitation signal as a PWM which is routed through an excitation amplifier before being applied to the exciter winding on the motor resolver. The resolver sine and cosine outputs are then routed back into the RDC analog inputs, where the RDC IP converts and interprets the signals to determine motor angle and rotational speed. [Figure 11-1](#) shows an example block diagram of a resolver based design with an AM263P device.

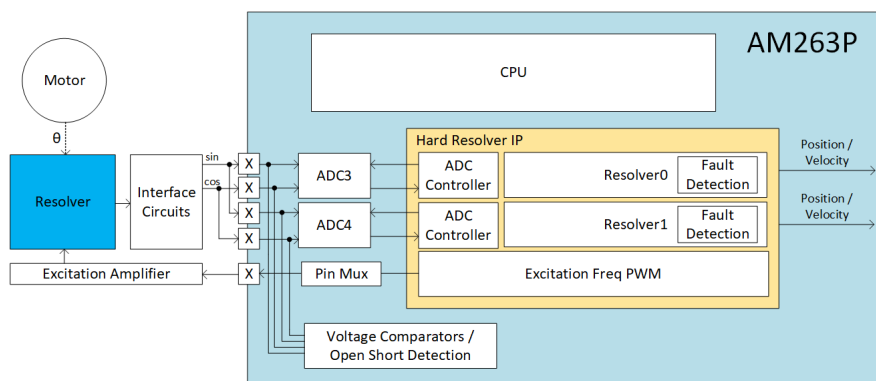

**Figure 11-1. AM263P Resolver ADC System**

The excitation PWM signals from the AM263Px support up to 20KHz and follows the same guidelines for PCB routing as other similar frequency digital signals. For guidance on routing digital signals, see [General Digital Peripheral Routing Guidelines](#).

The Excitation Amplifier is used to convert the excitation PWM signals to sine waves as inputs to the motor resolver. These signals and the sine and cosine signals output from the resolver to the RDC inputs of the AM263Px need to follow the same guidelines for PCB routing as other analog signals. For guidance on routing analog signals, see [General Analog Peripheral Routing Guidelines](#).



## 12 Layer Stackup

The AM263x, AM263Px, and one of the four packages of the AM261x MCUs are packaged in a ZCZ0324A 324 ball, 0.8mm pitch, 18 x 18 full NFBGA array 15mm x 15mm package (referred to as 'ZCZ package' in this document). The larger pitch on this package allows for a low layer count for power and full signal fan-out. In the case of the LP-AM263 EVM, a 6-layer stackup design was able to fully route all power and signal pins across the device for the LaunchPad form-factor of boards. The LP-AM263 LaunchPad stackup below represents the most optimized stackup example for the ZCZ package devices at this time.

Lower layer count stackups for the ZCZ package are likely possible, especially when considering partial signal fan-out designs. However, these have not yet been explored by TI.

Layer Stack Legend		Material	Layer	Thickness	Dielectric Material	Type	Gerber
			Top Overlay			Legend	GTO
		Surface Material	Top Solder	1.00mil	Taiyo PSR 4000 HFX DI-GREEN	Solder Mask	GTS
		Copper Foil 18 microns	Top Layer	2.09mil		Signal	GTL
		Prepreg		3.51mil	Iteq IT180A Prepreg 2113 RC58	Dielectric	
		Copper	GND 1	1.26mil		Signal	G1
		Core		4.00mil	Iteq IT180A 4 mil core 1/1	Dielectric	
		Copper	SIG 1	1.26mil		Signal	G2
		Prepreg		1.75mil	Iteq IT180A Prepreg 106 RC71.5	Dielectric	
		Prepreg		2.66mil	Iteq IT180A Prepreg 1080 RC65	Dielectric	
		Core		28.00mil	Iteq IT180A 28 mil core H/H	Dielectric	
		Prepreg		2.66mil	Iteq IT180A Prepreg 1080 RC65	Dielectric	
		Prepreg		1.75mil	Iteq IT180A Prepreg 106 RC71.5	Dielectric	
		Copper	SIG 2	1.26mil		Signal	G3
		Core		4.00mil	Iteq IT180A 4 mil core 1/1	Dielectric	
		Copper	GND 2	1.26mil		Signal	G4
		Prepreg		3.51mil	Iteq IT180A Prepreg 2113 RC58	Dielectric	
		Copper Foil 18 microns	Bottom Layer	2.09mil		Signal	GBL
		Surface Material	Bottom Solder	1.00mil	Taiyo PSR 4000 HFX DI-GREEN	Solder Mask	GBS
			Bottom Overlay			Legend	GBO
Total thickness: 63.06mil							

Figure 12-1. LP-AM263 Stackup


The other three packages of the AM261x MCU are described in the table below:

Table 12-1. AM261x Package Sizes

Package Name (Type, Ball Count)	Package Dimensions	BGA Pitch	BGA Array
ZNC (NFBGA, 293)	10mm x 10mm	0.5mm	19 x 19
ZEJ (NFBGA, 256)	13mm x 13mm	0.8mm	16 x 16
ZFG (NFBGA, 304)	13.25mm x 13.25mm	0.65mm	20 x 20

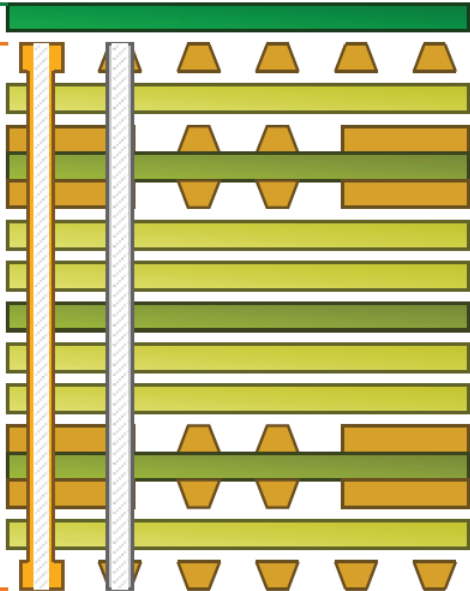In the case of the LP-AM261 EVM, a 6-layer stackup design was able to fully route all power and signal pins across the ZFG package device for the LaunchPad form-factor of boards. The LP-AM261 LaunchPad stackup below represents an optimized, full-system stackup example for the ZFG package at this time:



Layer	Stack up	Description	Type	Processed Thickness
1		Taiyo PSR 4000 HFX DI-GREEN	SolderMask	1.000
		Copper Foil 18 microns	Copper	2.087
		Iteq IT180A Prepreg 2113 RC58	Dielectric	3.511
2				1.260
		Iteq IT180A 4 mil core 1/1	FR4	4.000
3				1.260
		Iteq IT180A Prepreg 106 RC71.5	Dielectric	1.750
4		Iteq IT180A Prepreg 1080 RC65	Dielectric	2.663
		Iteq IT180A 28 mil core H/H	FR4	28.000
5		Iteq IT180A Prepreg 1080 RC65	Dielectric	2.663
		Iteq IT180A Prepreg 106 RC71.5	Dielectric	1.750
6				1.260
		Iteq IT180A 4 mil core 1/1	FR4	4.000
7				1.260
		Iteq IT180A Prepreg 2113 RC58	Dielectric	3.511
8				2.087
		Copper Foil 18 microns	Copper	2.087
9				1.000
		Taiyo PSR 4000 HFX DI-GREEN	SolderMask	1.000

**Figure 12-2. LP-AM261 Stackup**

Lower layer count stackups for the AM261x ZFG and ZNC packages have been explored by TI. Pictured below is an example of a 4-layer stackup for PCB systems utilizing the AM261x ZFG or ZNC package sizes:

#	Name	Material	Type	Weight	Thickness	Dk
	Top Overlay		Overlay			
	Top Solder	Solder Resist	Solder Mask		0.4mil	3.5
1	L1	CF-004	Signal	1oz	1.378mil	
	Dielectric 1	PP-006	Prepreg		7mil	4.1
2	L2		Signal	1oz	1.38mil	
	Dielectric1	FR-4 High Tg	Dielectric		42mil	4.8
3	L3		Signal	1oz	1.38mil	
	Dielectric 2	PP-006	Prepreg		7mil	4.1
4	L4	CF-004	Signal	1oz	1.378mil	
	Bottom Solder	Solder Resist	Solder Mask		0.4mil	3.5
	Bottom Overlay		Overlay			

**Figure 12-3. AM261x ZFG/ZNC PCB System Stackup**

## 12.1 Key Stackup Features

**Table 12-2. Stackup Features by Package Size**

	ZCZ (15mm x15mm, 0.8mm Pitch), ZFG (13.25mm x 13.25mm, 0.65mm Pitch)	ZFG (13.25mm x 13.25mm, 0.65mm Pitch), ZNC (10mm x 10mm, 0.5mm Pitch)
Total Layers	6	4
PCB Thickness	62 mil +/- 10%	62 mil +/- 10%
Optionally Controlled Impedance Routing Layers	4 (L1, L3, L4, L6)	2 (L1, L4)
Signal/Power Layers have Adjacent GND Reference	Yes	Yes
Core Center Layer Thickness	28 mil	42 mil
BGA Fan-out Via Type	Through-hole	Through-hole

### Note

In a 6-layer design, minimal dielectric thickness between L4 power and L5 GND return layers allows for best plane capacitance performance, aiding power integrity and EMI.

**Table 12-3. 6-Layer PCB: Layer Utilization**

Layer Number	Comment
Copper 1 (Top)	Top layer mounting and signal routing
Copper 2	Ground return plane
Copper 3	Embedded microstrip or stripline signal routing and power routing
Copper 4	Embedded microstrip or stripline and power routing
Copper 5	Ground return plane
Copper 6 (Bottom)	Bottom layer mounting and signal routing

**Table 12-4. AM263x, AM263Px, AM261x ZCZ Package, 6-Layer PCB: Controlled Impedance Planning Options**

Layer Number	Reference Layer Number	Structure Name <sup>(1)</sup>	Trace Width (mils)	Trace Separation (mils)	Target Impedance ( $\Omega$ )	Calculated Impedance ( $\Omega$ )	Notes
L1	L2	Coated Microstrip	5.300	0.000	50.000	50.140	
L1	L2	Edge Coupled Coated Microstrip	4.200	5.000	90.000	89.830	L1, USB differential
L1	L2	Edge Coupled Coated Microstrip	4.000	7.700	100.000	99.840	
L1	L2	Edge Coupled Coated Microstrip	4.100	6.800	120.000	120.030	
L3	L3	Offset Stripline	4.750	0.000	50.000	49.960	
L3	L2	Edge Coupled Offset Stripline	4.000	6.000	90.000	90.040	L3, USB differential
L3	L2	Edge Coupled Offset Stripline	3.500	8.100	100.000	99.880	
L3	L2	Edge Coupled Offset Stripline	4.000	12.000	100.000	100.160	
L6	L5	Coated Microstrip	5.300	0.000	50.000	50.140	
L6	L5	Edge Coupled Coated Microstrip	4.200	5.000	90.000	89.830	

**Table 12-4. AM263x, AM263Px, AM261x ZCZ Package, 6-Layer PCB: Controlled Impedance Planning Options (continued)**

Layer Number	Reference Layer Number	Structure Name <sup>(1)</sup>	Trace Width (mils)	Trace Separation (mils)	Target Impedance ( $\Omega$ )	Calculated Impedance ( $\Omega$ )	Notes
L6	L5	Edge Coupled Coated Microstrip	4.000	7.700	100.000	99.840	
L6	L4	Edge Coupled Coated Microstrip	4.100	6.800	120.000	120.030	

**Table 12-5. 4-Layer PCB: Layer Utilization**

Layer Number	Comment
Copper 1 (Top)	Top layer mounting and signal routing
Copper 2	Ground return plane
Copper 3	Power routing
Copper 4 (Bottom)	Bottom layer mounting and signal routing

**Table 12-6. AM261x ZFG Package, 4-Layer PCB: Controlled Impedance Planning Options**

Layer Number	Reference Layer Number	Structure Name <sup>(1)</sup>	Trace Width (mils)	Trace Separation (mils)	Target Impedance ( $\Omega$ )	Calculated Impedance ( $\Omega$ )	Notes
L1	L2	Coated Microstrip	4.000	3.900	50.000	49.640	
L1	L2	Edge Coupled Coated Microstrip	4.200	5.800	90.000	93.700	L1, USB differential
L1	L2	Edge Coupled Coated Microstrip	4.000	7.700	100.000	99.840	
L1	L2	Edge Coupled Coated Microstrip	4.100	6.800	120.000	120.030	
L4	L3	Coated Microstrip	5	8.5	50.000	47.400	
L4	L3	Edge Coupled Coated Microstrip	4.200	5.000	90.000	89.830	
L4	L3	Edge Coupled Coated Microstrip	4.000	7.700	100.000	99.840	
L4	L3	Edge Coupled Coated Microstrip	4.100	6.800	120.000	120.030	

**Table 12-7. AM261x ZNC Package, 4-Layer PCB: Controlled Impedance Planning Options**

Layer Number	Reference Layer Number	Structure Name <sup>(1)</sup>	Trace Width (mils)	Trace Separation (mils)	Target Impedance ( $\Omega$ )	Calculated Impedance ( $\Omega$ )	Notes
L1	L2	Coated Microstrip	3.200	3.300	50.000	52.960	
L1	L2	Edge Coupled Coated Microstrip	4.200	5.800	90.000	93.700	L1, USB differential
L1	L2	Edge Coupled Coated Microstrip	4.000	7.700	100.000	99.840	
L1	L2	Edge Coupled Coated Microstrip	4.100	6.800	120.000	120.030	
L4	L3	Coated Microstrip	3.500	6.650	50.000	49.980	
L4	L3	Edge Coupled Coated Microstrip	4.200	5.000	90.000	89.830	
L4	L3	Edge Coupled Coated Microstrip	4.000	7.700	100.000	99.840	
L4	L3	Edge Coupled Coated Microstrip	4.100	6.800	120.000	120.030	

(1) All impedance calculated using Polar 2D field solver on given copper and dielectric thicknesses, widths and dissipation constants.

## 13 Vias

The AM26x EVMs show different examples of via construction for BGA fan-out and overall board routing. All AM26x EVMs make use of PTH via construction.

**Table 13-1. AM26x EVM Via Types**

EVM	Via Type	Via Diameter (mils)	Via Drill (mils)
AM263x LaunchPad	PTH	18.000	8.000
AM263Px LaunchPad	PTH	18.000	8.000
AM261x LaunchPad	PTH	18.000	8.000
AM263x controlCard	PTH	18.000	8.000
AM263Px controlCard	PTH	18.000	8.000
AM261x controlSOM	PTH	18.000	8.000

## 14 BGA Power Fan-Out and Decoupling Placement

45nm CMOS technology allows for faster core and SRAM clock rates, and faster edge rates for LVCMOS I/O buffers. Therefore, in comparison with previous MCU process nodes, careful power and ground return placement is critical to achieving best power integrity, signal integrity and EMI performance with AM263x, AM263Px, and AM261x designs.

TI recommends that designers follow a similar power distribution layout as implemented in the AM263x, AM263Px, and AM261x EVM PCB designs to achieve good power integrity results across all operating conditions and EMI testing conditions.

The AM263x controlCard EVM represents the most optimized and scrutinized power distribution layout for ZCZ package AM26x devices. The controlCard example is referenced in the ZCZ-specific sections. For non-ZCZ AM261x devices, refer to the ZFG/ZNC-specific sections.

**Table 14-1. BGA Attribute Sections by Device Package**

BGA Attribute	AM263x/AM263Px/AM261x (ZCZ)	AM261x (ZFG)	AM261x (ZNC)
Ground Return	<a href="#">Section 14.1.1</a>	<a href="#">Section 14.1.2</a>	
1.2V Core Digital Power	<a href="#">Section 14.2.1</a>	<a href="#">Section 14.2.2</a>	N/A
3.3V Digital and Analog Power	<a href="#">Section 14.3.1</a>	<a href="#">Section 14.3.2</a>	N/A
1.8V Digital and Analog Power	<a href="#">Section 14.4.1</a>	<a href="#">Section 14.4.2</a>	N/A

## 14.1 Ground Return

This section summarizes the main elements of the ground return routing on AM26x devices.

### 14.1.1 Ground Return - ZCZ Package AM26x Devices


All available ground return BGA must be utilized to create the best possible electrical and thermal connection between the AM263x, AM263Px, or AM261x package and the attached PCB. Maximizing VSS BGA usage is critical from signal integrity, EMI/EMC and thermal perspectives.

Unless a separate top package heat sink is used in the design, the VSS BGA (and VDDCORE to a lesser extent) are the only heat sinking thermal connection for the BGA package. For required, thermal performance, AM26x-ZCZ PCB designs must adhere to following thermal via design requirements.

- A minimum of 49 VSS vias in the center of the BGA must be shorted to PCB ground return planes. However, if possible, and for best thermal performance, then all VSS BGA needs to be connected to PCB ground return planes.
- Solid ground return planes shall be used directly under the BGA on as many layers as possible.
- Solid ground return, or the widest possible traces shall be used on the top or bottom mounting layer for VSS BGA pad connection.
- VSS via drills shall use largest possible drill diameter. This maximizes surface area of the via, providing lowest thermal resistance.
- VSS vias need to be conductively filled, if possible.

All of these thermal via requirements must be balanced against the necessary power and signal fan-out of the design.


The AM26x devices contain both analog and digital ground return pins. Both analog and digital ground return pins need to be shorted to a common set of ground return planes on the PCB for best noise and EMI performance as this creates the lowest possible impedance path for all return currents to follow. TI does not recommend to separate these two return paths as this typically ends up with lower performance return paths for both digital and analog signal paths.

 

**Figure 14-1. AM263x controlCARD Excerpt – Ground Return Vias Under AM263x BGA Layer 1 and Layer**

**2**



 

**Figure 14-2. AM263x controlCARD Excerpt – Ground Return Vias Under AM263x BGA Layer 10**

#### **14.1.2 Ground Return - ZNC and ZFG Package AM261x Devices**

All available ground return BGA must be utilized to create the best possible electrical and thermal connection between the AM261x package and the attached PCB. Maximizing VSS BGA usage is critical from signal integrity, EMI/EMC and thermal perspectives.

Unless a separate top package heat sink is used in the design, the VSS BGA (and VDDCORE to a lesser extent) are the only heat sinking thermal connection for the BGA package. For required thermal performance, AM261x PCB designs must adhere to following thermal via design requirements.

- A minimum of 60 VSS vias (ZNC) or 49 VSS vias (ZFG) in the center of the BGA must be shorted to PCB ground return planes. However, if possible, and for best thermal performance, then all VSS BGA are connected to PCB ground return planes
- Solid ground return planes shall be used directly under the BGA on as many layers as possible.
- Solid ground return, or the widest possible traces shall be used on the top or bottom mounting layer for VSS BGA pad connection.
- VSS by drills use largest possible drill diameter. This maximize surface area of the via, providing lowest thermal resistance.
- VSS vias need to be conductively filled, if possible.

All of these thermal via requirements must be balanced against the necessary power and signal fan-out of the design.

The AM261x devices contain both analog and digital ground return pins. Both analog and digital ground return pins need to be shorted to a common set of ground return planes on the PCB for best noise and EMI performance as this creates the lowest possible impedance path for all return currents to follow. TI does not recommend to separate these two return paths as this typically ends up with lower performance return paths for both digital and analog signal paths.

 


Figure 14-3. AM261x ZFG Routing Study - Ground Return Vias on Layer 1

 


Figure 14-4. AM261x ZNC Routing Study - Ground Return Vias on Layer 1



## 14.2 1.2V Core Digital Power

This section summarizes the main elements of the 1.2V core digital power routing on AM26x devices.


### Note

Industrial-grade AM261x devices (AM261xAO...) require 1.25V


### 14.2.1 1.2V Core Digital Power Key Layout Considerations - ZCZ

For AM26x ZCZ package devices, the 1.2V core digital power routing of the AM263x controlCARD EVM (TMDSCNCD263) is explored - from the 1.2V buck-converter (TPS62913RPUR, U65) through the board power planes and ending at the BGA bulk and per pin decoupling capacitor array.

- AM263x, AM263Px, or AM261x must be co-located with the 1.2V core digital regulator to allow for minimal IR drop from the regulator to the BGA power pins.
- Wide 15 mil traces must be used for all power and ground return via fan-out.
- A dedicated power layer, with tightly coupled ground return reference plane must be used for best transient performance and EMI coupling.
- A wide power plane entry into the center of the BGA 1.2V power pin areas must be used for minimal IR drop and best transient performance.
- Larger packaged, lower-frequency, bulk capacitance must be placed adjacent to the BGA with vias directly to power plane paths.
- Smaller packaged, higher-frequency decoupling capacitance must be placed directly on BGA fan-out vias with as small of a dog-bone to power and ground return vias as possible.

 

**Figure 14-5. AM263x controlCARD Excerpt – 1.2V Core Power Output, Power Plane Vias and BGA Vias**

 

 


Figure 14-8. AM263x controlCARD Excerpt – 1.2V Core Power Decoupling Mounting, Layer 10


#### 14.2.2 1.2V Core Digital Power Key Layout Considerations - ZFG

For AM261x ZFG package devices, the 1.2V core digital power routing of the AM261x LaunchPad EVM (LP-AM261) is explored - from the 1.2V buck output of the PMIC (TPS650366), through the board power planes and ending at the BGA bulk and per pin decoupling capacitor array. A 4-layer PCB layout is also explored at the end of this section.


- AM261x (ZFG) must be co-located with the 1.2V core digital regulator to allow for minimal IR drop from the regulator/PMIC to the BGA power pins.
- Wide 10 mil traces must be used for all power and ground return via fan-out.
- A dedicated power layer, with tightly coupled ground return reference plane must be used for best transient performance and EMI coupling
- A wide power plane entry into the center of the BGA 1.2V power pin areas must be used for minimal IR drop and best transient performance
- Larger packaged, lower-frequency, bulk capacitance must be placed adjacent to the BGA with vias directly to power plane paths
- Smaller packaged, higher-frequency decoupling capacitance must be placed directly on BGA fan-out vias with as small of a dog-bone to power and ground return vias as possible

  The below figures detail the 1.2V core digital power flow from the source to AM261x device on the AM261x LaunchPad EVM (LP-AM261).

 




**Figure 14-9. AM261x LaunchPad Excerpt – 1.2V Core Power Output, Power Plane Vias and BGA Vias**



**Figure 14-10. AM261x LaunchPad Excerpt – 1.2V Core Power Plane, Layer 4**



**Figure 14-11. AM261x LaunchPad Excerpt – 1.2V Core Power Decoupling Mounting, Layer 6**

A 1.2V core digital power flow for a 4-layer PCB is under study for a future revision of this document.


## 14.3 3.3V Digital and Analog Power

This section summarizes the main elements of the 3.3V digital I/O and analog I/O power routing of the AM26x devices.


### 14.3.1 3.3V I/O Power Key Layout Considerations - ZCZ

The 3.3V power system on AM26x ZCZ devices are explored using the AM263x controlCARD EVM (TMDSCNCD263), from the 3.3V buck-converter (TPS62913RPUR, U30) through the board power planes and ending in at the BGA bulk and per pin decoupling capacitor array. A common buck-converter supplies power for all of the AM263x digital I/O, analog I/O and the rest of the controlCard 3.3V loads. This is common in most designs where all 3.3V digital level I/O share a common power supply. Additional filtering for the local AM263x 3.3V analog power net is done through the LC filter of ferrite-bead FL13 and associated capacitors. This is used to create a low-IR drop low-pass filter that attenuates the higher frequency switching harmonics of the TPS62913RPUR regulator.

  - Wide 15 mil traces need to be used for all power and ground return via fan-out.
- 3.3V I/O power tends to be shared across multiple devices in the system, recommend routing with very wide power planes across the PCB to minimize IR drops to all components including AM263x, AM263Px, or AM261x.
- A tightly coupled, adjacent ground return reference plane needs to be used for best transient performance and EMI coupling.
- A wide power plane entry that covers the BGA 3.3V power pin areas needs to be used for minimal IR drop and best transient performance.
- Larger packaged, lower-frequency, bulk capacitance needs to be placed adjacent to MCU BGA with vias directly to power plane paths.
- Smaller packaged, higher-frequency decoupling capacitance needs to be placed directly on BGA fan-out vias with as small of a dog-bone to power and ground return vias as possible.

 


**Figure 14-12. AM263x controlCARD Excerpt – 3.3V Digital and Analog Power Planes on Layer 5 and Layer 6**

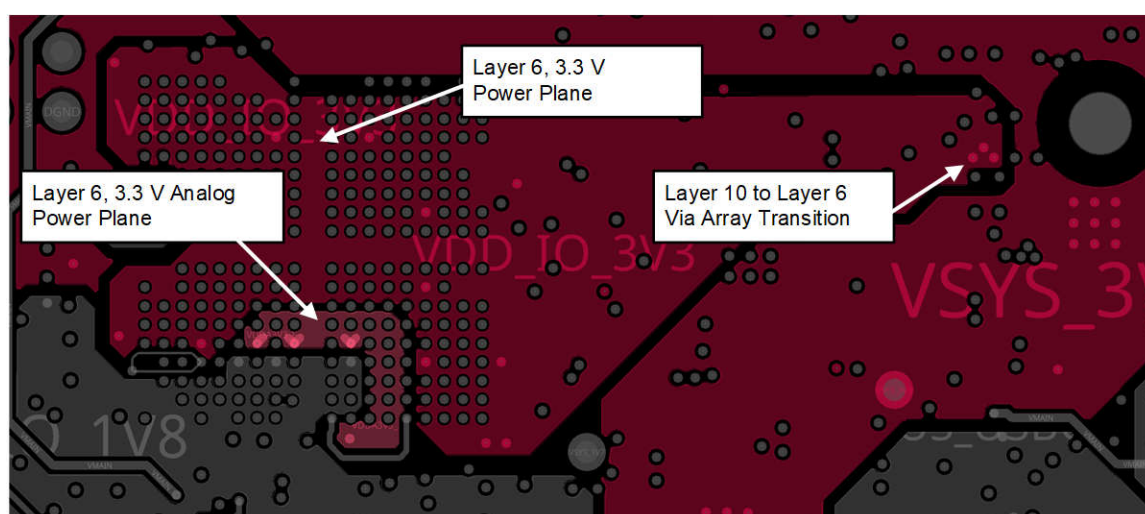


**Figure 14-13. AM263x controlCARD Excerpt – 3.3V Digital I/O and Analog I/O BGA Pinout and Regulator Output**

 




**Figure 14-14. AM263x controlCARD Excerpt – Common 3.3V Plane Transition Vias**



**Figure 14-15. AM263x controlCARD Excerpt – 3.3V Digital and Analog Planes Layer 6**



**Figure 14-16. AM263x controlCARD Excerpt – 3.3V Digital and Analog Power Decoupling Mounting, Layer 10**

### 14.3.2 3.3V I/O Power Key Layout Considerations - ZFG

The 3.3V power system on AM261x ZFG devices are explored using the AM261x LaunchPad EVM (LP-AM261), from the 3.3V buck output of the PMIC (TPS650366) through the board power planes and ending in at the BGA bulk and per pin decoupling capacitor array. The PMIC 3.3V buck output supplies power for all of the AM261x digital I/O, analog I/O, and the rest of the LaunchPad loads. This is common in most designs where all 3.3V digital level I/O share a common power supply. Additional filtering for the local AM261x 3.3V analog power net is done through the LC filter of ferrite-bead FB2 and associated capacitors. This is used to create a low-IR drop low-pass filter that attenuates the higher frequency switching harmonics of the PMIC buck output.

- Wide 10 mil traces need to be used for all power and ground return via fan-out.
- 3.3V I/O power tends to be shared across multiple devices in the system, recommend routing with very wide power planes across the PCB to minimize IR drops to all components (including AM261x SoC).
- A tightly coupled, adjacent ground return reference plane needs to be used for best transient performance and EMI coupling.
- A wide power plane entry that covers the BGA 3.3V power pin areas need to be used for minimal IR drop and best transient performance.
- Larger packaged, lower-frequency, bulk capacitance needs to be placed adjacent to MCU BGA with vias directly to power plane paths.
- Smaller packaged, higher-frequency decoupling capacitance needs to be placed directly on BGA fan-out vias with as small of a dog-bone to power and ground return vias as possible.


 



Figure 14-17. AM261x LaunchPad Excerpt – 3.3V Digital and Analog Power Planes on Layer 3 and Layer

4

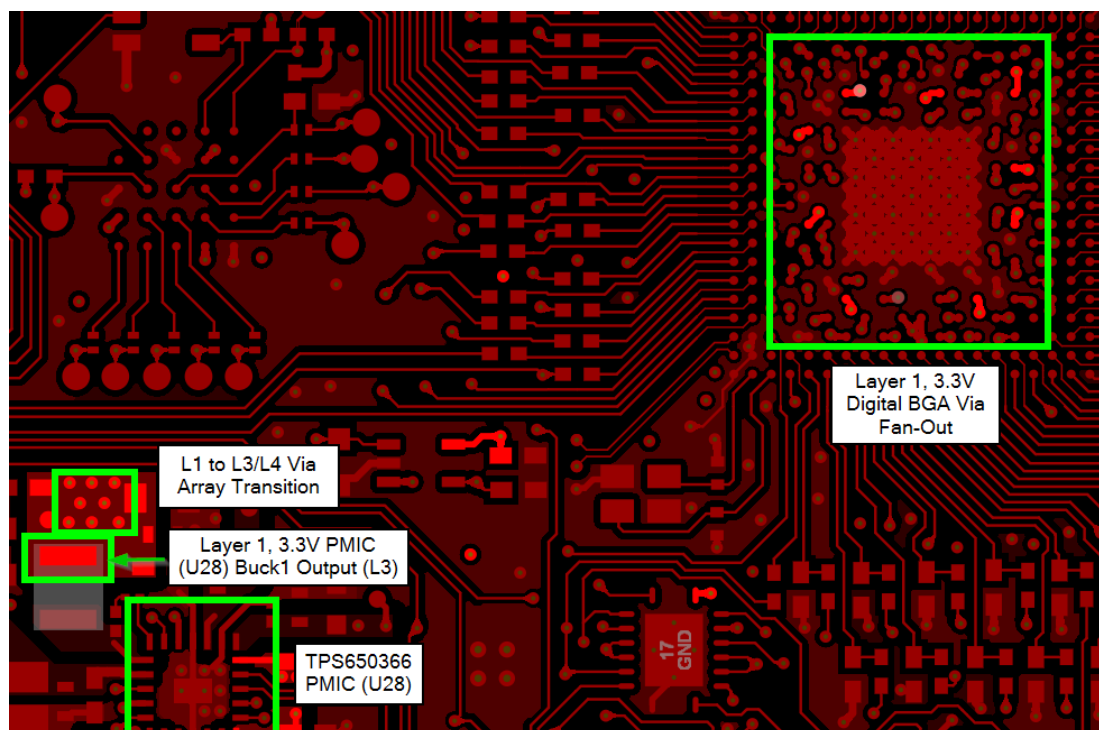



**Figure 14-18. AM261x LaunchPad Excerpt – 3.3V Digital I/O BGA Pinout and PMIC Output**

 

**Figure 14-19. AM261x LaunchPad Excerpt - 3.3V Analog IO BGA Pinout**

 


Figure 14-20. AM261x LaunchPad Excerpt – 3.3V Digital Plane on Layer 3

 


Figure 14-21. AM261x LaunchPad Excerpt – 3.3V Digital Power Decoupling Mounting, Layer 6



A 1.2V core digital power flow for a 4-layer PCB is under study and can be included in a future revision of this document.

#### 14.4 1.8V Digital and Analog Power

This section summarizes the main elements of the 1.8V digital I/O and analog I/O power routing of the AM26x MCU devices. Both 1.8V power nets are generated from an on-chip LDO which are in turn supplied by either the 3.3V digital or 3.3V analog power nets from the PCB.

##### 14.4.1 1.8V Key Layout Considerations - ZCZ

For ZCZ package devices, the AM263x controlCARD EVM is explored as an example. Additional filtering for the local AM263x 1.8V PLL power net is done through the LC filter of ferrite-bead FL12 and associated capacitors. This is used to create an additional low-IR drop low-pass filter that attenuates any high frequency noise present on the 1.8V LDO analog output.

- Wide, minimum 15 mil traces, needs to be used for all power and ground return via fan-out.
- 1.8V digital and analog is generated from on-chip LDO and so is highly localized to the BGA pinout.
- A tightly coupled, adjacent ground return reference plane needs to be used for best transient performance and EMI coupling.
- Smaller power planes or wider traces needs to be used for minimal IR drop and best transient routing across the associated BGA pins.
- Smaller packaged, higher-frequency decoupling capacitance needs to be placed directly on BGA fan-out vias with as small of a dog-bone to power and ground return vias as possible.



 


Figure 14-22. AM263x controlCARD Excerpt – 1.8V Digital Power Via Fan-Out and Plane Routing Layer 6

 


**Figure 14-23. AM263x controlCARD Excerpt – 1.8V Digital Power Decoupling on Layer 10**

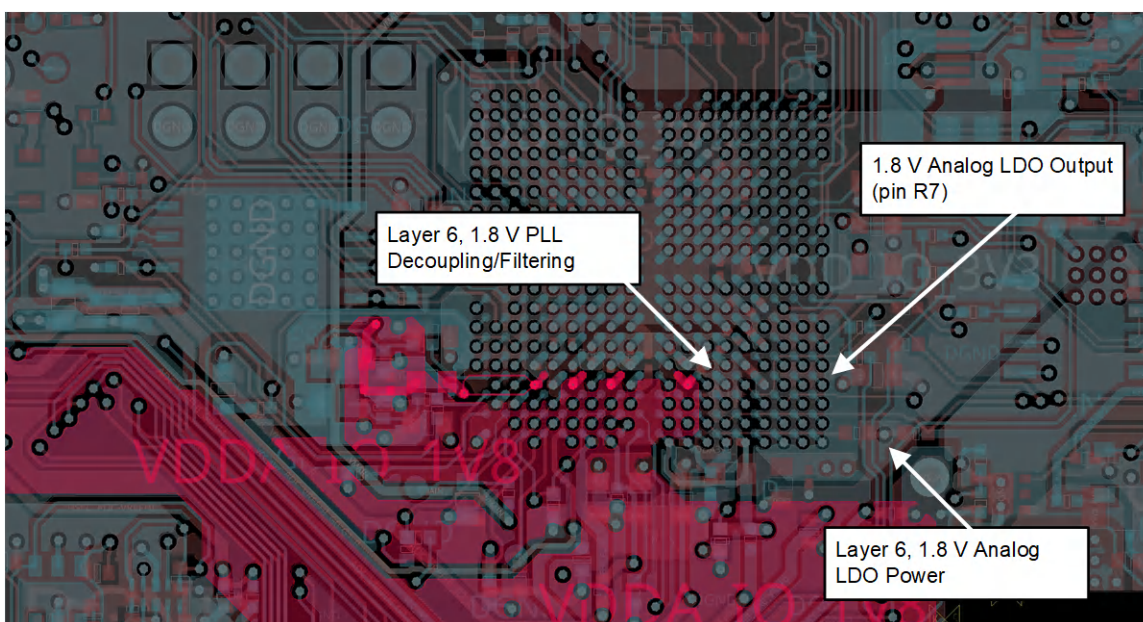

**Figure 14-24. AM263x controlCARD Excerpt – 1.8V Analog Power Via Fan-Out and Plane Routing Layer 6**

#### Note

Figure 2-14 shows an example of an unacceptable routing between the FL12 filter output and the BGA pads. The output of the FL12 filter needs to be routed as a wide trace or small plane, and not smaller traces as was done on this initial revision of the controlCard EVM.

 


**Figure 14-25. AM263x controlCARD Excerpt – 1.8V Analog Power Decoupling on Layer 10**

#### **14.4.2 1.8V Key Layout Considerations - ZFG**


The 1.8V power nets on AM261x ZFG devices are explored using the AM261x LaunchPad EVM (LP-AM261). Additional filtering for the local AM261x 1.8V PLL power net is done through the LC filter of ferrite-bead FB3 and associated capacitors. This is used to create an additional low-IR drop low-pass filter that attenuates any high frequency noise present on the 1.8V LDO analog output.

  - Wide 10 mil traces need to be used for all power and ground return via fan-out.
- 1.8V digital and analog is generated from on-chip LDO, and is highly localized to the BGA pinout.
- A tightly coupled, adjacent ground return reference plane needs to be used for best transient performance and EMI coupling.
- Smaller power planes or wider traces need to be used for minimal IR drop and best transient routing across the associated BGA pins.
- Smaller packaged, higher-frequency decoupling capacitance needs to be placed directly on BGA fan-out vias with as small of a dog-bone to power and ground return vias as possible.

 





**Figure 14-26. AM261x LaunchPad Excerpt – 1.8V Digital Power Via Fan-Out and Plane Routing - Layer 3**



**Figure 14-27. AM261x LaunchPad Excerpt – 1.8V Digital Power Decoupling on Layer 6**



**Figure 14-28. AM261x LaunchPad Excerpt – 1.8V Analog Power Via Fan-Out and Plane Routing - Layer 4**

 

**Figure 14-29. AM261x LaunchPad Excerpt – 1.8V Analog Power Decoupling on Layer 6**

A 1.2V core digital power flow for a 4-layer PCB is under study and can be included in a future revision of this document.

## 15 Summary

The guidelines outlined in this document are essential to follow during the design phase of any AM26x-based PCB system. By strictly adhering to the requirements, an engineer can expect the PCB system to behave properly out of the box, and avoid having to do multiple rounds of prototyping.

Once an AM26x-based custom PCB has completed the fabrication and assembly process, the engineer needs to refer to the [AM26x Custom PCB System Getting Started Guide](#) for initial bring-up and validation of the PCB.

## 16 References

### AM263x

#### Device Documentation

1. Texas Instruments, [AM263x Sitara™ Microcontroller](#), data sheet
2. Texas Instruments, [AM263x Sitara™ Microcontroller Technical Reference Manual](#), technical reference manual
3. Texas Instruments, [AM263x Sitara™ Microcontroller Technical Reference Manual Addendum](#), register addendum

#### EVM Documentation

1. Texas Instruments, [LP-AM263](#), AM263x LaunchPad EVM
2. Texas Instruments, [TMDSCNCD263](#), AM263x controlCARD EVM

#### Software Development

1. Texas Instruments, [MCU-PLUS-SDK-AM263X](#), AM263x MCU software development kit

### AM263Px

#### Device Documentation

1. Texas Instruments, [AM263Px Sitara™ Microcontroller](#), data sheet
2. Texas Instruments, [AM263Px Sitara™ Microcontroller Technical Reference Manual](#), technical reference manual
3. Texas Instruments, [AM263Px Sitara™ Microcontroller Technical Reference Manual Addendum](#), register addendum

#### EVM Documentation

1. Texas Instruments, [LP-AM263P](#), AM263Px LaunchPad EVM
2. Texas Instruments, [TMDSCNCD263P](#), AM263Px controlCard EVM

#### Software Development

1. Texas Instruments, [MCU-PLUS-SDK-AM263PX](#), AM263Px MCU software development kit

### AM261x

#### Device Documentation

1. Texas Instruments, [AM261x Sitara™ Microcontrollers](#), data sheet
2. Texas Instruments, [AM261x Sitara Microcontrollers Technical Reference Manual](#), technical reference manual
3. Texas Instruments, [AM261x Sitara Microcontrollers Register Addendum](#), register addendum

#### EVM Documentation

1. Texas Instruments, [LP-AM261](#), AM261x LaunchPad EVM
2. Texas Instruments, [AM261-SOM-EVM](#), AM261x controlSOM EVM

Software Development

1. Texas Instruments, [MCU-PLUS-SDK-AM261X](#), AM261x MCU software development kit

Software Development Tools

1. Texas Instruments, [System Configuration Tool \(SYSCONFIG\)](#)
2. Texas Instruments, [Code Composer Studio IDE](#)

General HW Design Resources

1. MIPI Alliance, Recommendation for Debug and Trace Connectors, [MIPI Debug & Trace Connector Recommendations](#), white paper
2. Texas Instruments, [JTAG Connectors and Pinout](#), webpage
3. Texas Instruments, [Sitara MCU Thermal Design](#), application note
4. Texas Instruments, [High-speed Interface Layout Guidelines](#), application note

17 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Revision C (January 2025) to Revision D (May 2025)	Page
<ul style="list-style-type: none"> <li>Added AM261x ZFG, ZNC, ZEJ SOP Isolation method. Implementation on LP-AM261 used as an example.....</li> </ul>	37

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2025, Texas Instruments Incorporated