

# Lighting up Automotive Displays with a Transimpedance Configuration

Caroline Fuschino



As the sun sets on commuters driving home for the day, the displays and systems in each car gradually brighten. The manual adjustments required to brighten or dim the display in older vehicles have been replaced by intuitive lighting that adjusts without any action from the driver.

Operational amplifiers (op amps) are a simple way to provide backlighting control throughout the car to give drivers a comfortable viewing experience and save power. Using an op amp instead of a more complex light sensor also enables greater flexibility and customization.


## Designing the Op Amp in a Transimpedance Configuration

Automotive display systems – the [head unit](#), [remote display](#), [cluster](#) or [head-up display \(HUD\)](#) – use the ambient light level (as detected by a circuit) to adjust the backlight brightness according to light intensity or time of day, usually through an analog-to-digital converter (ADC) or a microcontroller (MCU). A transimpedance amplifier circuit, or more specifically a photodiode amplifier circuit, can sense and respond to these changes in ambient light.

The goal of the photodiode amplifier circuit is to transform low-level current from a photodiode into a useful voltage. To do this, the op amp is designed in a transimpedance configuration, as depicted in [Figure 1](#). The photodiode can detect many different light sources, including visible light, infrared and ultraviolet. The photodiode will produce a larger current when exposed to more light energy, increasing the circuit's output voltage.

## Transimpedance in Automotive

For an automotive function, you must apply a small bias voltage to the op amp's non-inverting input so that the output does not saturate at the negative supply rail when there is no input current. Often, a resistor divider from the positive voltage supply will bias the non-inverting input above ground. This reverse bias will cause a reduced photodiode junction capacitance from the zero reverse-biased case, but the circuit will respond more quickly. Reverse bias also improves high-frequency performance. A feedback capacitor is always necessary to maintain the stability of the circuit; you can find methods for proper circuit design in the [photodiode amplifier circuit](#) application note.

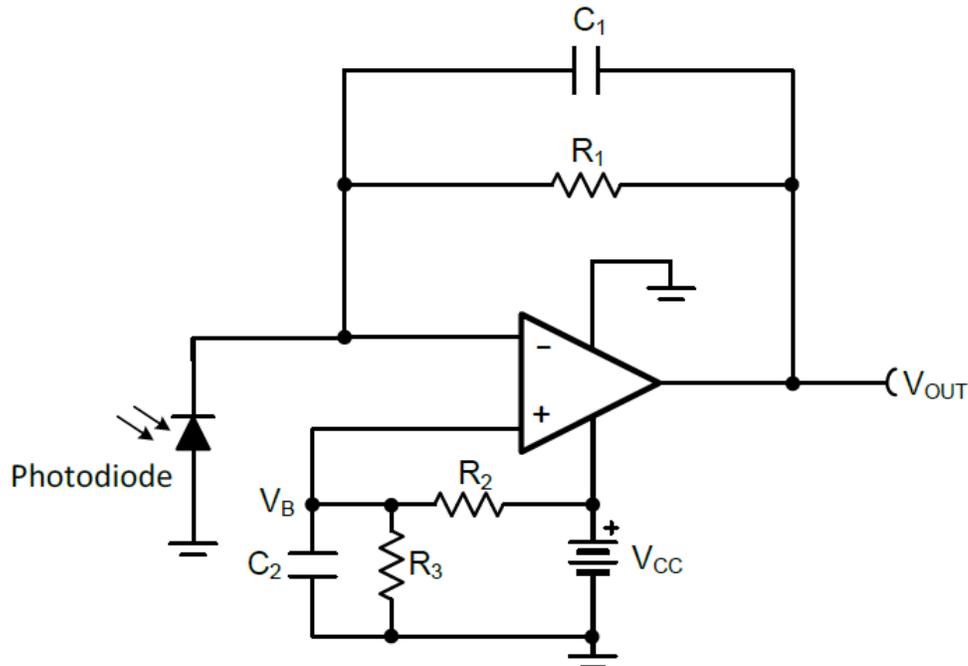

**Figure 1. Transimpedance amplifier configuration with a reverse-offset bias at the noninverting input**

The photodiode amplifier enables you to customize the circuit based on your needs. By strategically choosing any automotive-rated op amp or modifying the components in the circuit, you can control the gain, ensure the correct input bias current or add compensation to fix any unique stability issues. Additionally, there are many automotive-rated op amps available for each specific application. For example, TI's [OPA348-Q1](#) is specifically designed for very low-level photodiode current at 45 $\mu$ A and can operate over an extended bandwidth of 1MHz.

Alternatively, TI's [LM2904-Q1](#) consists of two independent frequency-compensated op amps with a gain-bandwidth product of 0.7MHz. Using op amps provides an economic solution to automatic adjustment: these op amps cost less than \$.25 1,000-unit quantities, while an integrated circuit that performs the same function can cost \$1.14 in 1,000-unit quantities with very little increase in performance.

Photodiode amplifier circuits are a simple and flexible way to automatically measure the backlighting for many automotive systems. TI's library of op amps and resources to aid in proper circuit design enable you to tailor the perfect solution for your backlight control. A transimpedance configuration in an automotive display system will lead to automatic backlight control that is simple, inexpensive and effective.

### Additional Resources

- Calculate the component values using a cookbook for a [photodiode amplifier circuit](#).
- Review the app note, "[Using transimpedance amplifiers for ambient light sensing in automotive displays](#)"
- Read Bonnie Baker's Analog Applications Journal article, "[Automating circuit designs for photodiode amplifiers.](#)"
- Check out the [1MHz, Single-Supply, Photodiode Amplifier Reference Design](#).
- Explore TI's [automotive solutions portal](#) and [op amps](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated