

How Can a Load Switch Extend Your Device's Battery Life?



Alex Triano




Let's say that you're a power electronics engineer and your boss has asked you to extend the battery life of your product. After optimizing the front-end power path ([battery charger](#)) and mid-rail converters ([DC/DCs](#) and [low-dropout regulators \[LDOs\]](#)), you believe there's no room left to squeeze out a few more hours or days of battery life. You're almost ready to report back that it's impossible, but after taking a look in your toolbox, you find the solution: load switches.

One of the many ways that you can use a load switch is to reduce the shutdown current of any load. Do you have a [Bluetooth®](#) or [Wi-Fi®](#) module that consumes over 10 μ A in deep sleep or hibernation mode? Try adding a load switch like the [TPS22916](#) in [Figure 1](#), which can reduce the shutdown current to just 10nA.

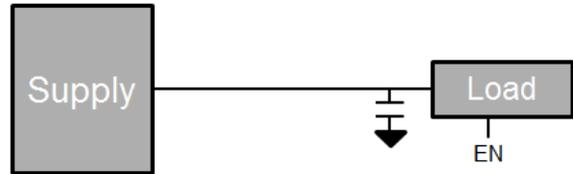
Problem

Load leakage current is high ($10\mu\text{A}$) when load is disabled



Solution

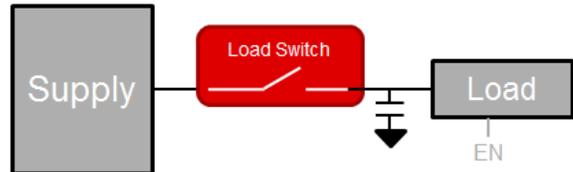Add an electrical disconnect within the power path to reduce leakage current in unused sub-systems



Load switch feature

Ultra-low leakage current (10nA typ) when switch is OFF

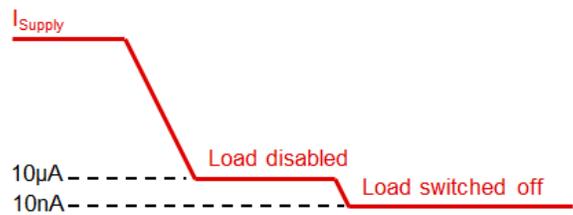


Figure 1. Reduce Shutdown Current by Adding a Low-leakage Load Switch between the Supply and Load.

In some applications, such as wearables, building automation or medical devices, there can be several sensors and wireless transmitters in a single product that load switches can disable. [Figure 2](#) shows the system block diagram of a typical smartwatch and where load switches would be used in the power path.

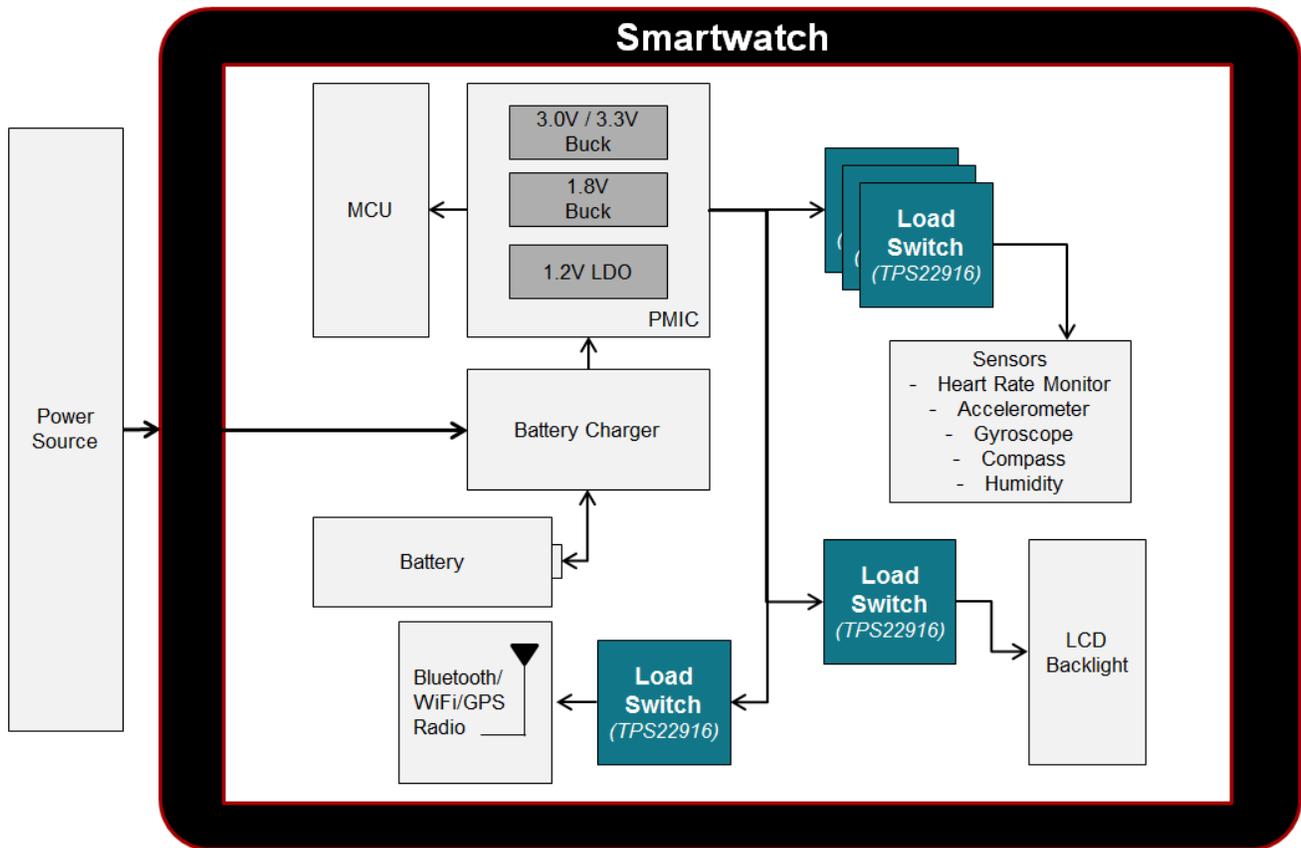


Figure 2. Smartwatch System Block Diagram

Take an example of a smartwatch using a standard 3.7V lithium polymer battery with 65mAh of capacity. In order to last at least five days before charging (a typical work week), you need to leave certain sensors powered (like the step counter), but you can shut down other areas of the board, like the *Bluetooth*® module. If the *Bluetooth*® module draws 10µA when disabled, it is contributing to at least $10\mu\text{A} \times 24 \text{ hours} \times 5 \text{ days} = 1.2\text{mAh}$ of the 65mAh budget. In other words, this one module is contributing at least 1.8% ($1.2\text{mAh}/65\text{mAh}$) to overall battery-life loss. Plus, this very conservative estimate does not take into account minimum/maximum specs over temperature, nor efficiency loss through the DC/DC converters. If you have several modules leaking current, the situation can multiply very quickly.

How do you combat this? Using the [TPS22916](#) will cut that shutdown leakage current to just 10nA. This means that you can continue using your favorite Bluetooth module and it will have virtually no effect (0.0018%) on battery life when disabled, thanks to your new favorite load switch.

To learn more about load switches and the features they can offer, be sure to check out [ti.com/loadswitch](https://www.ti.com/loadswitch).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated