

# How to Use Load Switches and eFuses in Your Set-top Box Design



Aleksandras Kaknevicus

Sitting in front of a TV is easy. Changing the channel is easy. Recording four shows at once while watching one show on your TV and streaming another show to your tablet is excessive – but also easy! It's all thanks to the power of set-top boxes (STBs), such as the one shown in [Figure 1](#).



Figure 1. A Typical STB

STBs take in a cable/satellite signal; translate that signal into video; and then transmit that video to a TV, hard drive or wireless device. Designing these systems can be complicated but designing the power distribution can be easy, especially when you use load switches and eFuses.

## Why Bother Turning Different Loads on and off?

STB designers usually follow standby power requirements so they can improve the system's power efficiency. These requirements limit the amount of power that the STB can draw when it is inactive, so different subsystems need to be off in order to draw a minimal amount of power. Some regions even have specific power requirements, such as Energy Star. [Figure 2](#) shows the common STB subsystems that can be controlled to improve standby power.

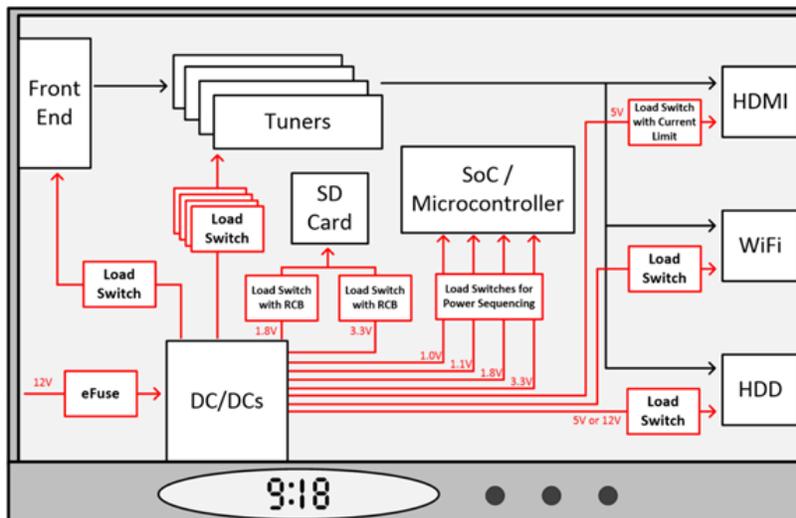


Figure 2. Load Switch and eFuse Applications in STBs

Now let's take a look at some of the subsystems you can switch on and off.

- **Front end/tuner.** This subsystem takes the input signal (cable or satellite) and converts the signal into video. One tuner is responsible for a single video output, so if an STB can record five shows at once, that means that there are five different tuners dedicated to recording. Likewise, there is a tuner for the output video port and for connecting additional devices through Wi-Fi®. Switching the tuners off when they are not being used can reduce shutdown power.
- **Hard drive.** A hard drive that is not recording a show or playing a previously recorded show does not need to be active. This is also the case when the STB is just outputting the cable signal.
- **Wi-Fi.** Wi-Fi connects additional devices to the STB such as tablets or computers, or connects smaller STBs within the same household.


Load switches can control power to each of these subsystems, and both the TPS22918 and TPS22975 can be used depending on the current load. Both are plastic devices that come with an adjustable output rise time suitable for different capacitive loads. The TPS22918 can support loads up to 2A and the TPS22975 can support loads up to 6A.

### What about Using Switches for Additional Features?

Aside from power savings, several other features require a switch:

- **Power sequencing.** The system on chip (SoC) or microcontroller that controls the STB has a specific power-on sequence for its different voltage rails. For optimal performance, devices like the TPS22918 or TPS22975 can turn on each of the rails in order.
- **Input protection.** Voltage and current transients can occur when the 12V adapter is plugged into the STB. Placing the TPS2595 eFuse at the STB input can protect the rest of the system from hot-plug events.
- **SD card.** If an STB uses an SD card, the option exists to power it with 3.3V or 1.8V. Using the TPS22910A and TPS22912C load switches enables you to choose the appropriate rail.
- **HDMI.** The HDMI port is powered with 5V when in use, and the current needs to be limited for user protection. The TPS22945 load switch has a low current limit of 100mA.


All of these applications are modeled in the block diagram in [Figure 3](#).

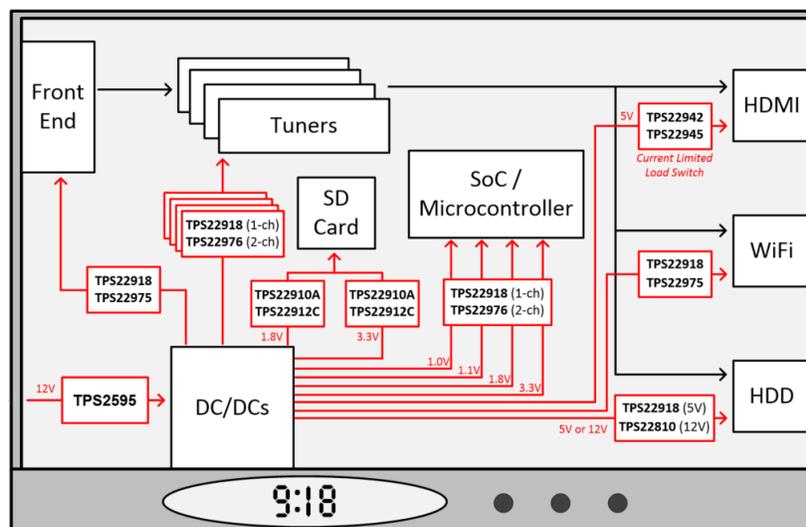

**Figure 3. Recommended Load Switches and eFuses in STBs**

## Where Can You Get Started?

The [Power Switching Reference Design for Set Top Box](#) shows all of the different load switches and eFuses used for each subsystem. With the added DC/DCs, the design helps create a complete solution for STB power delivery.

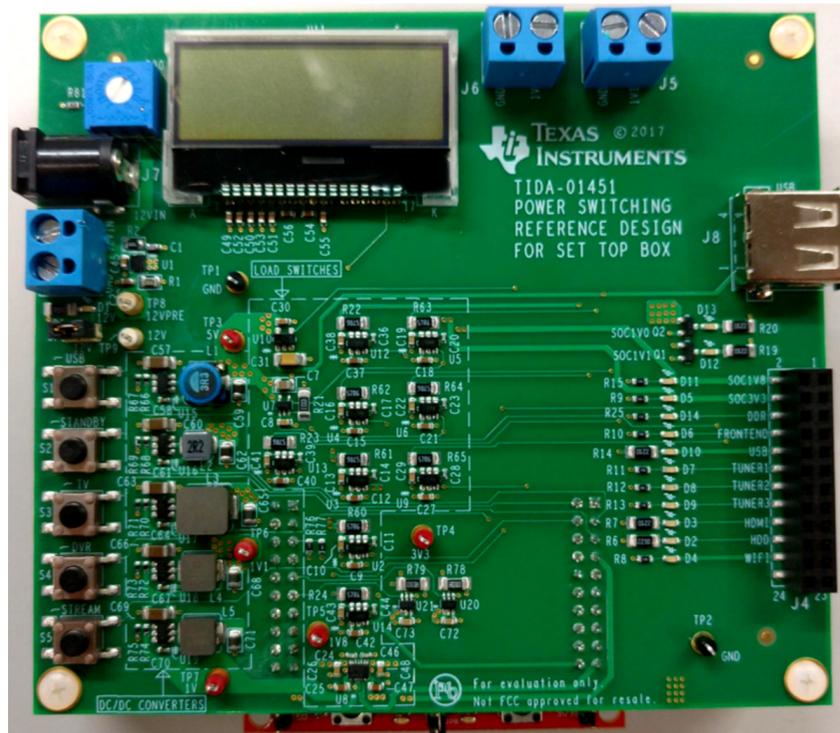

**Figure 4. Power Switching Reference Design for Set Top Box**

With the trend in STB moving to smaller form factors, it's easy to see why designers are looking for more integration in their systems. So keep your STB power design small and easy, and use load switches and eFuses to accomplish your varying power switching needs!

### Additional resources

- Only have a few minutes? Watch some videos:
  - [“Load Switches vs. Discrete MOSFETs”](#) (2:35).
  - [“Load Switches vs. Discrete MOSFETs – Problems with a discrete solution and how a load switch can fix them”](#) (3:22).
  - Learn more about load switches by downloading these application notes:
    - [“Basics of Load Switches.”](#)
    - [“Integrated Load Switches versus Discrete MOSFETs.”](#)
  - Check out the following load switch blog post for more information:
    - [“What is a Load Switch?”](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated