

Discrete SBCs: Versatile and Scalable Solutions for Any Application



John Griffith

A system basis chip, or SBC, is an integrated circuit (IC) that combines many typical building blocks of a system including transceivers, linear regulators and switching regulators. While these integrated devices can offer size and cost savings in a number of applications, they don't work in every case.

For applications where an SBC isn't a good fit, it might be beneficial to build a discrete implementation of these aforementioned building blocks, and that is what I mean by the term "discrete SBC." In this post, I'll describe some scenarios where building discrete SBCs can solve system requirements, and what additional benefits you'll gain by using discrete solutions.

Versatile Power Topologies

Different nodes in an automobile will have widely varying performance requirements during different input transients. For example, gateway modules, which route critical information around a vehicle, will sometimes need to continue normal operation through cold-crank input transients as low as 4.0V. Given this requirement, you'll need some form of boost converter to keep the output voltage rails in regulation through the low-input voltage transient.

An example solution would be to create a two-stage regulator with a wide-input-voltage boost regulator to an intermediate voltage, followed by a wide-input-voltage buck regulator to the desired output voltage. [Figure 1](#) shows a block diagram of this power scheme.

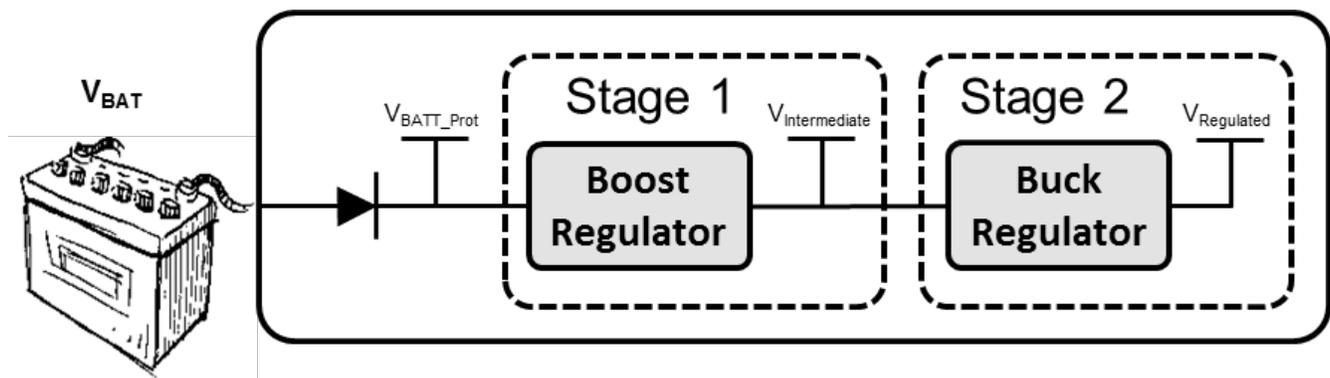


Figure 1. Boost Regulator Followed by Buck Regulator Topology

While this solution requires two regulators, the additional benefits are:

- You can choose the intermediate voltage such that you can regulate multiple output rails from it. Active antenna applications often require regulated voltages from 7V to 12V; Controller Area Network (CAN) transceivers require 5V; and microprocessors typically need 5.0V, 3.3V or 1.8V. By choosing your intermediate voltage above the highest required regulated output voltage, you eliminate the need for a second boost regulator inside the module.
- In applications like eCall, where a module must operate through brownout conditions or a complete battery-disconnect condition for a given amount of time, you can set the intermediate voltage to a higher voltage to store more energy in the output capacitance of the regulator. The total energy stored in the output capacitance, which in this scenario is also acting as the hold-up capacitance during brownout or battery-

disconnect scenarios, is equal to . As you can see, the energy is proportional to the square of the stored voltage, which means that if the intermediate voltage doubles, the total energy stored quadruples, thus making it easier to ride through brownouts or maintain operation longer after battery disconnect.

In my second example, a discrete SBC solution may be beneficial in nodes that need to operate through start-stop transients where battery input voltages can dip down as low or lower than 5.5V. If the module requires both a regulated 5V supply for a CAN transceiver and a 3.3V regulated supply for the microcontroller, a wide-input-voltage buck converter set to 3.3V followed by a small low-input-voltage boost converter can be a competitive solution. [Figure 2](#) shows this topology.

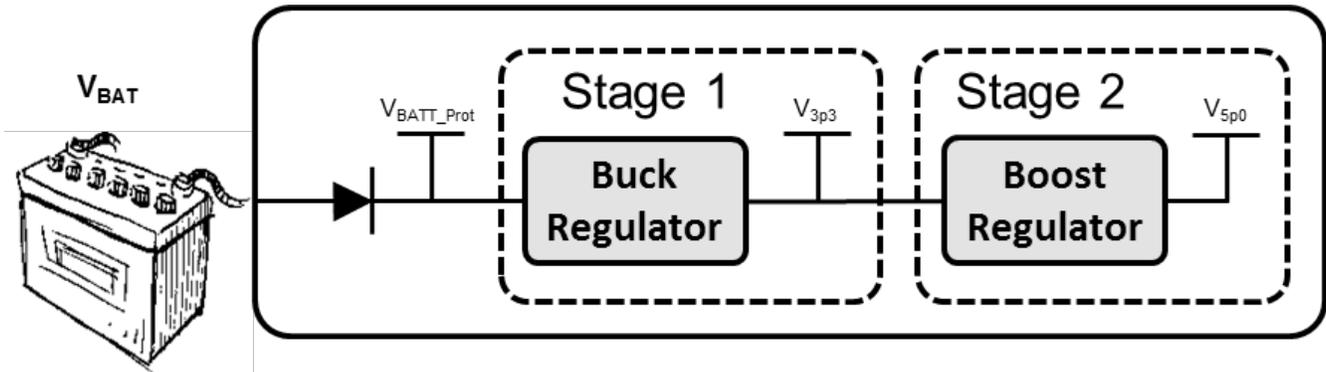


Figure 2. Buck Regulator Followed by Boost Regulator Topology

The additional benefit here is that since the battery's input voltage immediately bucks down to a regulated low voltage, it only requires one wide-input-voltage regulator. Therefore, the 3.3V to 5.0V boost regulator can be a low-input-voltage, low-current device, saving cost.

Scalable Product Families and Controller Products

Discrete families often come with drop in-compatible family members with different current ratings. This makes it easier for you to scale your power supplies for low-, mid- and high-end applications without having to redesign the board.

Some examples of TI families that do this include:

- Buck regulators:
 - [LM53625-Q1](#) and [LM53635-Q1](#) families (2.5A/3.5A).
 - [TPS57040-Q1/57140-Q1/54240-Q1](#) families (0.5A/1.5A/2.5A).
 - Linear regulators (LDOs):
 - [TPS7B63-Q1](#) and [TPS7B68-Q1](#) watchdog LDO families (300mA/500mA).
 - [TPS7B67-Q1](#) and [TLE4275-Q1](#) 450mA LDO families, with and without low power mode.

Devices within each of these families are pin-to-pin equivalent and interchangeable with one another depending on your design's load current or feature requirements. And because both buck and boost regulators have controller products that use external field-effect transistors (FETs) and diodes, you can easily scale these products depending on the load-current requirements of each design variant.

While not all applications have the same requirements as the two examples I've described here, being willing to look at discrete solutions offers superior flexibility and scalability.

As always, log in and leave a comment if you have any questions or topics you would like to hear more about.

Additional Resources

- Download these TI reference designs:
 - [Automotive Pre-Boost, Post-Buck with CAN "Discrete SBC"](#).
 - [Automotive Pre-Buck, Post-Boost with CAN "Discrete SBC"](#).
 - Check out TI's [automotive boost regulator products](#) and [automotive buck regulator products](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated