

Power Tips: How to Upgrade a Legacy Power Bank to USB Type-C™



Yingyang Ou

With more and more portal devices adopting the [USB Type-C™ connector](#), designing a power bank capable of charging these devices is suddenly a big deal. Unfortunately, the USB Type-C connector is a totally new type of USB connector. Understanding the differences between a USB Type-C power bank from legacy USB power banks is critical for successful product migration.

There actually is not much difference between a USB Type-C power bank power stage and a legacy power bank power stage. The key difference is in how the power path connectivity and device attach/detach detection is handled “From” and “To” the Type-C connector.

In a legacy power bank there is always an input charging port (such as Micro USB) and one or more output discharging ports (such as USB Type A). A battery charger inside the power bank connects to the input port. A DC/DC converter, mostly a booster, is located at the output path. [Figure 1](#) shows this block diagram.

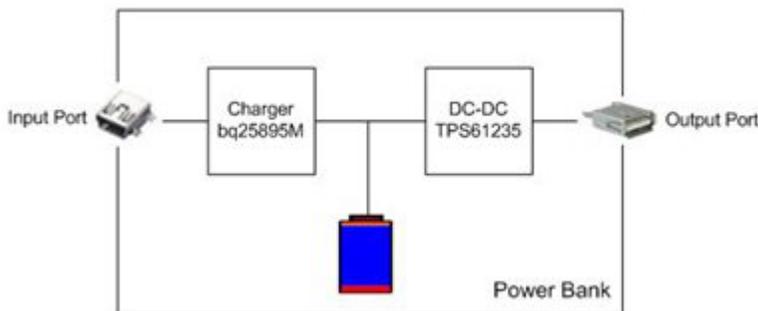


Figure 1. A Legacy Power Bank

Pin Connections

The USB Type-C connector is designed for higher power and higher data transmission speeds and has a nonspecific orientation. Its pin assignment has significantly improved from the USB Type A or USB Type B ports.

[Figure 2](#) gives the pin assignments for a full-featured USB Type-C receptacle. There are 24 pins, including several new pairs. However, power bank being a dataless system, it is not necessary to consider the USB 3.1 pins and SBU pins. However D+/D- pins are needed to support BC1.2 and third party proprietary brick IDs. Use below example for connecting Type-C receptacle pins.

- V_{BUS} and GND: there are four pins defined for each net, respectively. Connect all of the pins in same function to share the current.
- D+/D-: Same definition as USB Type A and USB Type B: these are used to transmit the handshake message between power bank and external device. Two pairs are defined in a USB Type C connector but only one set would be connected to the cable. Connect the two pins in same definition directly.
- CC: this is a new channel configuration (CC) pin used for the discovery, configuration and management of connectors across a USB Type-C cable. Connect it to a USB Type-C controller.

GND	RX2+	RX2-	VBUS	SBU1	D-	D+	CC	VBUS	TX1-	TX1+	GND
GND	TX2+	TX2-	VBUS	V _{CONN}				VBUS	RX1-	RX1+	GND

Figure 2. USB Type-C Receptacle Pin Assignments

Adding V_{BUS} Switches

A USB Type-C port is configurable as dual-role port (DRP). A USB Type-C DRP power bank one can charge or discharge via the same USB Type-C port. This will require the addition of a V_{BUS} switch at the USB Type-C receptacle to separate the charger power path and output DC/DC power path, as shown in Figure 3.

A V_{BUS} switch is typically configured as a back-to-back structure so that it can block the energy flow bidirectionally. When the USB Type-C power bank is connected to an adaptor, the VBUS switch on the charging path can be turned on so that the battery can be charged. If the external device is a cellphone, the VBUS switch on discharging path will be turned on while the VBUS switch on charging path is disabled. Generally, a V_{BUS} switch also has three main purposes:

- It can help block energy from the battery to V_{BUS}. The output DC/DC could be a boost converter, which means that the battery voltage can go to the output through its rectifier diode. Using this V_{BUS} switch can block the voltage applied to V_{BUS} before attachment.
- In a USB Type-C power bank, the valid V_{BUS} voltage and current may vary dynamically. You can turn the V_{BUS} switch off if an overcurrent or overvoltage event occurs at the V_{BUS} to protect the post circuit.
- With a USB Type-C DRP power bank, the DC/DC converters for charging and discharging connect to the same port, which requires separating the bulk capacitors for each converter in order to meet the USB Type-C's requirements for source or sink. The bulk capacitance for a sink is within 1~10uF to limit the input rush current, while the bulk capacitance for a source should be higher than 10uF to keep the VBUS voltage stable.

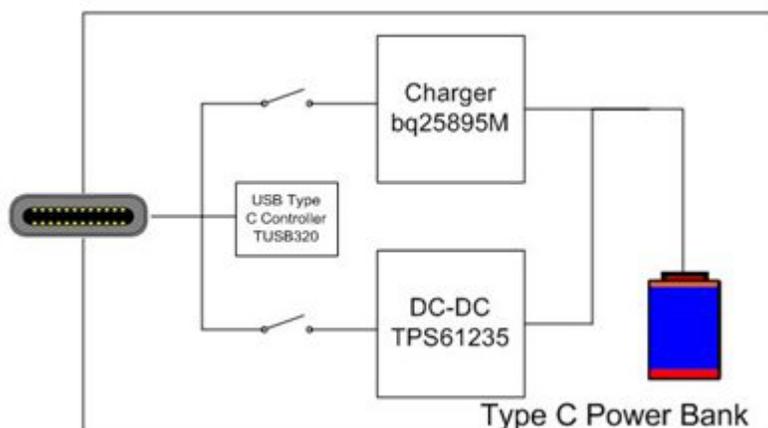


Figure 3. A USB Type-C Power Bank with V_{BUS} Switch

Attachment Event Detection

A traditional power bank can detect the V_{BUS} voltage and current to activate the microcontroller (MCU) once an attach/detach event occurs. With the new USB Type-C port, the traditional detection circuits are out of action. The CC line in a USB Type-C connector takes this responsibility. I recommend a Type-C DRP controller such as TUSB320 to implement port attach/detach events in a type C power bank. The built-in CC detection circuit in TUSB320 connects the CC line to its internal voltage source through a pull-up resistor or a current source when configured to source power. The USB Type-C controller will connect the CC to ground via a pull-down resistor when sinking power. Once there is a connection between two devices, the CC line voltage will change. The internal circuit in both devices will detect this voltage variation and start attachment event detection, as shown in Figure 4.

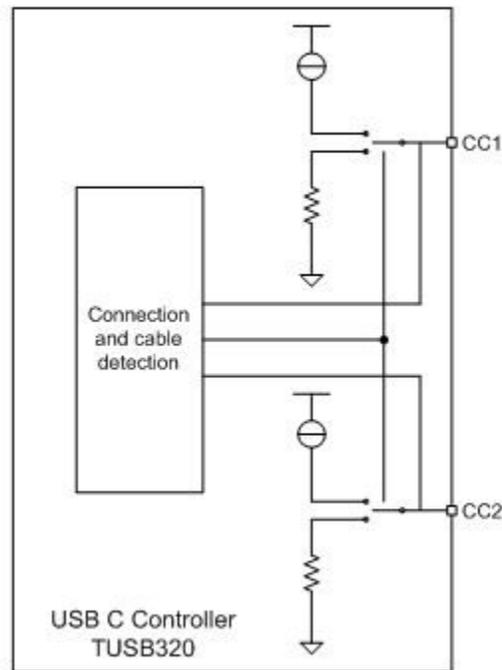


Figure 4. CC Event-detection Circuit

In summary, with a clear understanding of the pin connections, V_{BUS} switches and attachment event detection, you can easily upgrade a legacy power bank to support USB Type-C devices.

Additional Resources

Check out these TI Design reference designs:

- [USB-C DFP+ USB-A Power Bank with Input & Output Fast Charger Reference Design](#)
- [USB-C DFP + 5V2A Power Bank With Input Fast Charger Reference Design](#)
- [USB-C DRP Power Bank With Fast Charger Input Reference Design](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated