

David Xu¹

Automatic meter reading (AMR) systems have become more popular in recent years. This technology saves electricity providers the expense of periodic trips to each physical location to read a meter so that billing is based on real-time consumption rather than on estimations. Because of these advantages, AMR has even become a mandatory requirement to all new generation e-meters in some countries.

Below you'll find a typical block diagram for a [smart e-meter system](#). Data transmission is achieved by a replaceable communication hub with hundreds of microfarad capacitance. The communication hub is plugged in the e-meter, and its power supply comes from the e-meter's internal AC/DC converter. If the communication hub is damaged, it must be replaced, which causes a communication hub hot plug to occur. However, the electricity monitor circuit is required to operate normally even though its power supply comes from the same internal AC/DC converter. In order to meet this requirement, a device with current limit function is necessary to connect the AC/DC converter and communication hub.

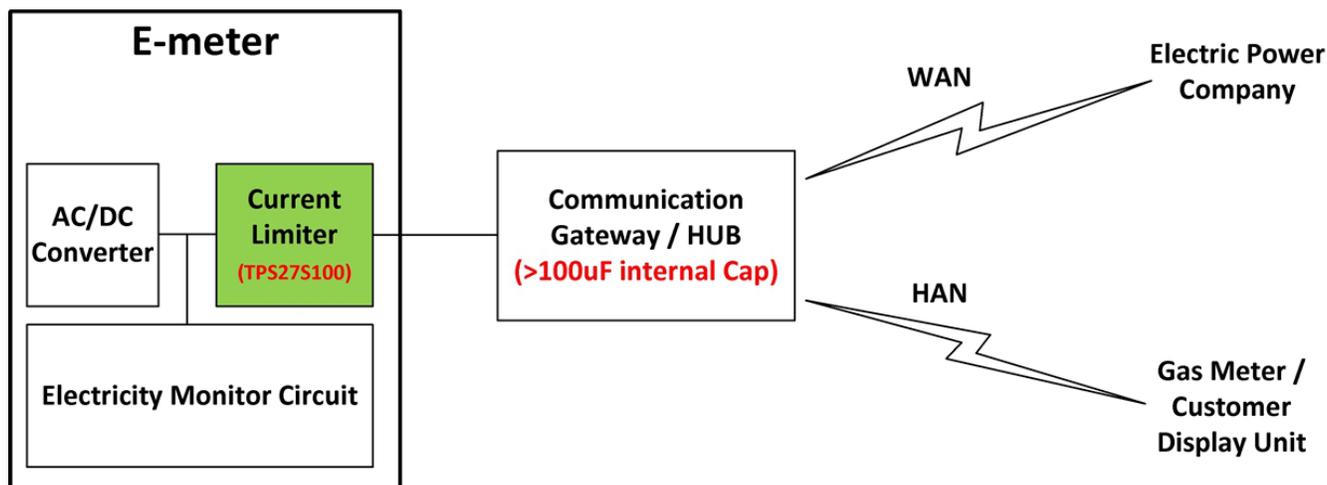


Figure 1. Smart Meter Power Topology

The [TPS27S100](#) is a single-channel 80mΩ R_{ds(on)} smart, high-side switch with full diagnostics and protection. It integrates an accurate adjustable current limit function at 20 percent tolerance across a wide temperature range between -40°C and 125°C. Because the AC/DC converter output voltage is quite stable, a precise power limit is achieved with this accurate adjustable current limit function to help save AC/DC converter power and PCB size.

Take UK smart e-meter standards as an example. The communication hub requires at least 6W power to guarantee its normal operation. To simplify the calculation, the AC/DC output voltage tolerance is neglected. If TPS27S100 is used as the current limiter, the AC/DC converter needs to leave power for the communication hub during the design. However, if a current limiter with 40% current limit accuracy is selected; the AC/DC converter needs to leave power for the communication hub. This example illustrates the current limit accuracy influence to AC/DC converter power margin.

The adjustable current limit accuracy of TPS27S100 is shown below in the two graphs. figure 27 shows the current limit accuracy under 0.5A current limit, and figure 28 shows the current limit accuracy under 1.6A current limit. You see here that the device's actual performance is much better.

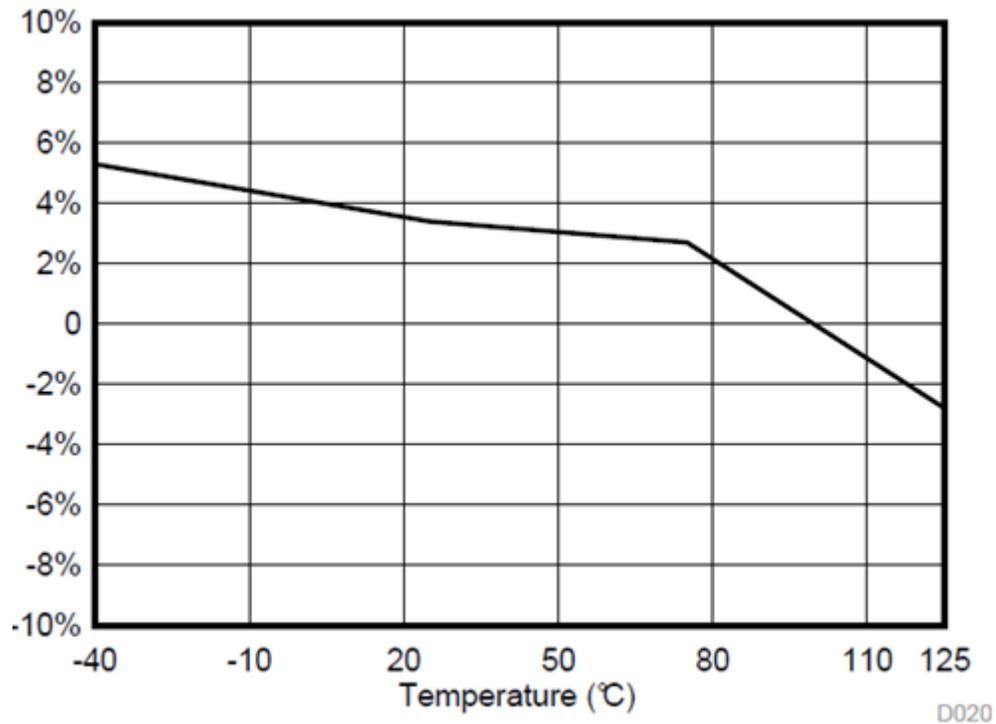


Figure 2. $K_{CL}=0.5A, 13.5V$

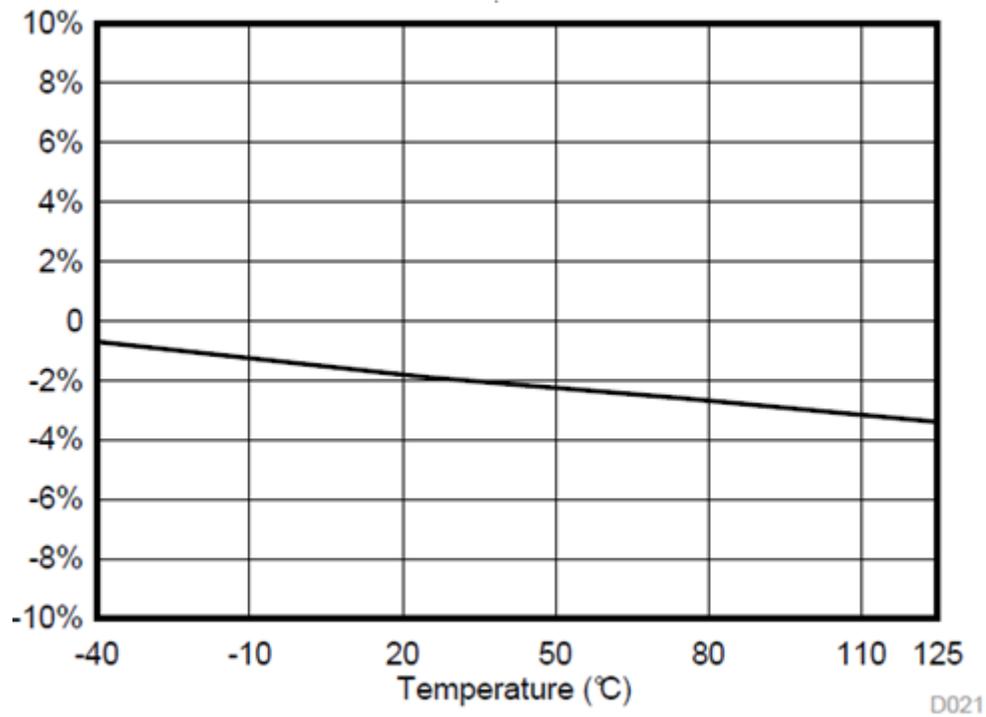


Figure 3. $K_{CL}=1.6A, 13.5V$

In conclusion, a smart e-meter internal AC/DC converter can be designed with lower power capability with a precise current limiter connect behind it. This help to save system cost and size a lot. In the future, the smart e-meter size is going to be smaller, a precise current limiter would be more important in the system.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated