

How to Overcome Minimum On-time Challenges in Switching Power Supplies



David Tseng

In switching power supplies such as a buck converter, the duty cycle controls the output voltage with respect to the input voltage. While a higher switching frequency is great for reducing the solution size by enabling the use of a small inductor, there is a minimum on-time that must be satisfied in order for the switching power supply to function properly. In other words, the high-side FET must be turned on for a certain amount of time within each switching period such that the condition in Equation 1 is met:

$$D \cdot \frac{1}{f_s} > t_{on_min} \quad (1)$$

where D is the duty cycle and f_s is the switching frequency.

Several factors within the circuit necessitate this minimum on-time. For example, one factor is the current spike on the leading edge of the current waveform in the high-side FET. Since the FET has parasitic gate capacitances C_{gs} and C_{gd} , and the current through the high-side FET changes abruptly when it turns on, the capacitances behave similarly to a short in the presence of the changing current. This results in a current spike. In order to prevent this from triggering the current limit, current-limit violations are ignored during blanking time (t_{LEB} in Figure 1). Therefore, the minimum on-time of the switching circuit must be larger than the blanking time – otherwise, the current-limit protection will be turned off for longer than the actual on-time.

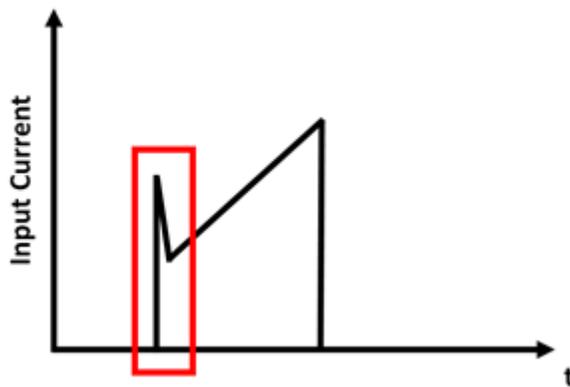


Figure 1. Current Spike on the Leading Edge of the Current Waveform of the High-side FET

Other factors include the rise and fall time of the switch-node voltage and level-shifter delay to set the gate voltage on the high-side FET.

Devices will behave differently when the on-time falls to its minimum, sometimes resulting in problems that may seem unexpected. For example, the switching power supply may start pulse skipping (shown in Figure 2) as a way to compensate for the inability to further decrease the on-time while still maintaining the output voltage. This results in a larger output voltage ripple and unknown harmonics from changes in switching frequencies.

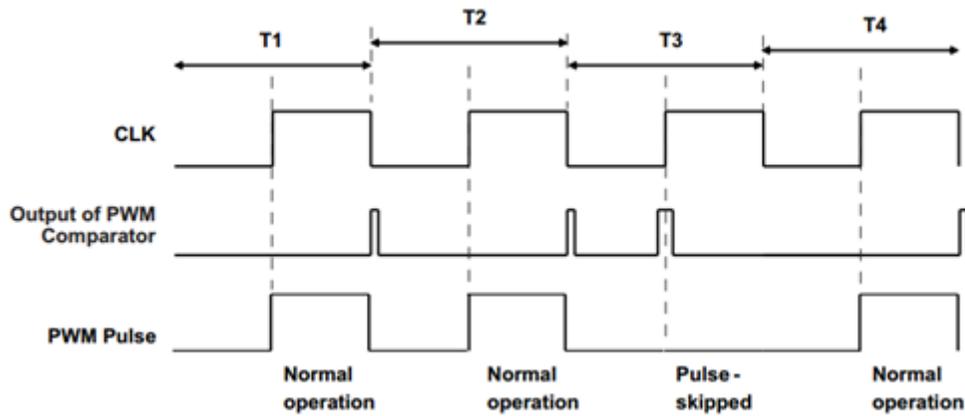


Figure 2. Pulse-skipping Waveform in the TPS61175 Boost Converter

Other devices may instead use frequency foldback to allow the duty cycle to decrease. In this case, the switching frequency drops but the pulses occur regularly – unlike in pulse skipping where entire pulses are dropped. Figure 3 shows an example of this functional mode.

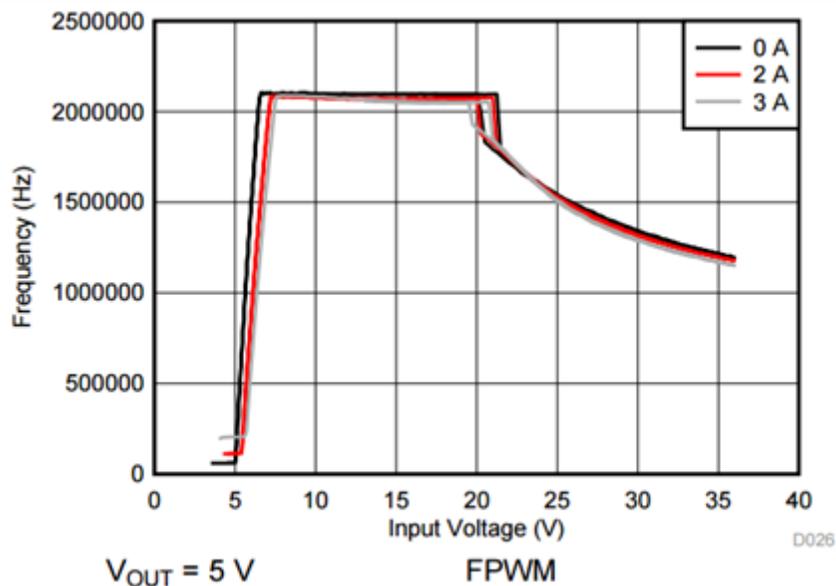


Figure 3. Frequency Foldback in the LM53602 at $v_{OUT} = 5V$

It is critical to note these issues when choosing a device to use for your switching power-supply needs. For example, in automotive applications, frequencies within any circuit must not fall within the AM band. Otherwise, they may interfere with the radio signal and clobber any information that was sent via that frequency band. Any application that involves information transfer on a certain frequency band must pay special attention to the possibility of interference from the regulator. Designs that use devices with a smaller minimum on-time will therefore encounter fewer complications.

One example of a great device with a small minimum on-time is the [LM53602](#) buck converter. Its minimum on-time of 50ns enables a larger range of possible duty cycle and frequency pairings. As long as switching power-supply designers are cognizant of the significance of minimum on-time, their designs will be able to work more effectively in a larger variety of situations.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated