

Chris Glaser



Oops. I attached my field-programmable gate array (FPGA) to the output of my DC/DC converter and now the DC/DC won't start. When I look at the circuit with an oscilloscope, I see [Figure 1](#). The output voltage just doesn't enter regulation. What went wrong?

FPGAs present some unique challenges for their power supplies. For example, FPGA vendors typically require hundreds or even thousands of microfarads (μF) of decoupling capacitance on their input supply to maintain the required regulation of the FPGA's supply voltage among the different frequencies of transients produced by the FPGA, as well as to reduce ripple on the supply voltage. Many FPGAs also require a specific startup time (not too fast and not too slow) and startup monotonicity (with V_{OUT} reaching its set point in a straight line without any downward movements).

In addition to FPGA-related design challenges, more and more FPGA designers must also design the power supply for their FPGA. Being FPGA experts, many of these designers have little experience in power-supply design and so need a very simple power supply – a [power module](#) is an obvious choice.

Power modules achieve simplicity by integrating many or all of the required passive components. Fewer components to select results in a faster and simpler design time. Control-loop compensation is one of the first things to integrate into the power module, but this constrains the design's stable range – and with the large amount of capacitance, an internally compensated power module may not be stable. Consult the device [TPS82084 data sheet](#) and [application report](#) for guidance on stability. The [DCS-Control](#) topology used in many of TI's [TPS82xxx](#) power modules is very stable and supports a wide range of output capacitance.

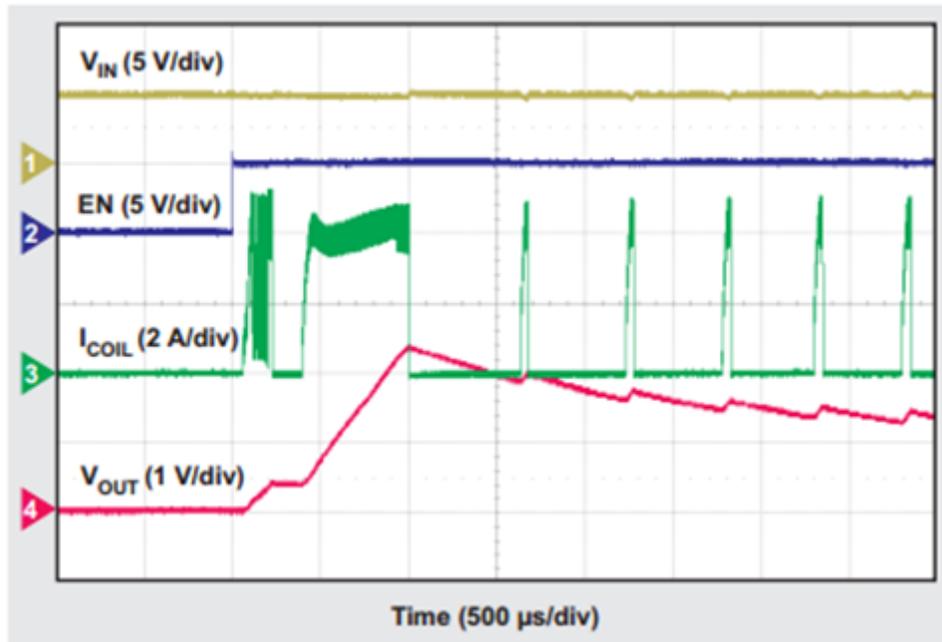


Figure 1. Because of This FPGA's High Startup Load and Very-High Decoupling Capacitance, the DC/DC Converter Cannot Bring Its Output Voltage into Regulation

The very small size of power modules means there are fewer pins to work with. Fewer pins means a simpler device, but also fewer features. Another feature commonly integrated into power modules is soft-start (SS) time. This time is set internally on some power modules, like the [TPS82085](#), but is programmable with a capacitor on other power modules, like the [TPS82130](#). A programmable SS time is generally required for meeting a specific startup time requirement and is very helpful for starting a power module with all of that capacitance connected.

But let's get back to what went wrong. In the waveform shown in [Figure 1](#), the DC/DC converter can't start up when driving the FPGA and its capacitance. This [application note](#) explains the details, but here is a short summary of various ways to fix the issue:

- Delay the startup ramp with a resistor, capacitor, diode (RCD) circuit.
- Switch to a DC/DC converter with a SS pin to program the SS time.
- Use a load switch to decouple the FPGA from the DC/DC.

How Have You Overcome Startup Issues in Your past Designs?

Additional Resources:

- Use the [WEBENCH FPGA Power Architect](#) to start designing today.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated