



- **Forward conduction.** When  $V_{DS,device} > 0$  and  $V_{GS,LV\_Si} \geq V_{GS(th),LV\_Si}$ , the low-voltage silicon FET is on. Regardless of whether the high-voltage GaN HEMT is off or on before entering the forward conduction state, the conduction of the low-voltage silicon FET will force  $V_{GS,HV\_GaN} \approx 0$  and turn on the high-voltage GaN HEMT.
- **Reverse conduction.** When  $V_{DS,device} < 0$  and  $V_{GS,LV\_Si} < V_{GS(th),LV\_Si}$ ,  $V_{GS,HV\_GaN}$  will clamp to the low-voltage silicon FET body-diode forward voltage. Therefore, current will flow through the low-voltage silicon FET body diode and the high-voltage GaN HEMT. When  $V_{DS,device} < 0$  and  $V_{GS,LV\_Si} \geq V_{GS(th),LV\_Si}$ , the low-voltage silicon FET then turns on and  $V_{GS,HV\_GaN}$  is forced to zero. Therefore, current flows through the drain-source channel of both the low-voltage silicon FET and high-voltage GaN HEMT.

Unlike synchronous-drive high-voltage GaN devices, a direct-drive high-voltage GaN device only switches the low-voltage silicon FET on once after its  $V_{DD}$  voltage goes above undervoltage lockout. You can analyze device operation under these two conditions:

- **Without  $V_{DD}$  applied.** When  $V_{DD}$  is not yet applied to the device after applying a positive  $V_{DS,device}$ ,  $V_{GS,HV\_GaN}$  stays at a zero voltage and the  $V_{DS}$  of the low-voltage silicon FET starts to increase. When the  $V_{DS}$  voltage increases to  $V_{GS(th),HV\_GaN}$ , the high-voltage GaN HEMT will turn off and hold the voltage of  $V_{DS,device} + V_{GS(th),HV\_GaN}$ . This operation is similar to the forward-blocking state of a synchronous-drive high-voltage GaN device.
- **With  $V_{DD}$  applied.** After the device powers up by applying  $V_{DD}$ , the gate driver can generate a negative voltage to turn off the high-voltage GaN HEMT directly. Once the gate driver takes control of the high-voltage GaN HEMT, the low-voltage silicon FET can then be on continuously before removing  $V_{DD}$  or detecting any failure.

With a different driving technology, synchronous-drive high-voltage GaN devices and direct-drive high-voltage GaN devices have very different features. Synchronous-drive high-voltage GaN devices can be used as a drop-in replacement for silicon FETs. However, the low-voltage silicon FET is synchronously switched with the high-voltage GaN HEMT. That is, the body diode of the low-voltage FET may conduct current in a steady-state operation. Therefore, the low-voltage silicon FET reverse-recovery charge ( $Q_{rr}$ ) will introduce additional losses and limit the achievable switching frequency with a synchronous-drive high-voltage GaN device.


In contrast to a synchronous-drive high-voltage GaN device, the low-voltage silicon FET in a direct-drive high-voltage GaN device only switches from off to on once and stays on in steady state. This eliminates the reverse-recovery effect due to the low-voltage silicon FET body diode. In addition, the integration of gate driver and startup logic increases the reliability of whole power supply.

TI's 600V LMG3410 GaN device adapts direct-drive technology to achieve zero  $Q_{rr}$  and lower gate charge. Overtemperature protection (OTP) and overcurrent protection (OCP) with a 50nS fast-fault trigger time are also built in. Using TI direct-drive GaN devices in power supplies with a totem-pole switch configuration – like a totem-pole power-factor correction circuit or an inductor-inductor-capacitor (LLC) series resonant half-bridge converter – can eliminate the worry of shoot-through and improper dead-time setting.

Figure 2 shows a shoot-through test on an LLC series resonant half-bridge converter with the TI LMG3410 as input switches. During the test, a high-side switch is forced on, with the low-side switch controlled by a driving signal with gradually increased duty cycles. Once the OCP trips, the LMG3410 quickly disables its driver inside to turn off the switch. This prevents the device from catastrophic failure.

We also tested LMG3410 OTP on the same LLC series resonant half-bridge board with an improper dead-time setting to force the converter into hard-switching operation.

With OCP and OTP built into this zero  $Q_{rr}$  GaN device, you've cleared the most worrisome issues of totem-pole switches. Contact your local TI representative to get a [LMG3410 daughtercard](#) to evaluate how TI direct-drive GaN devices improve system reliability and efficiency.

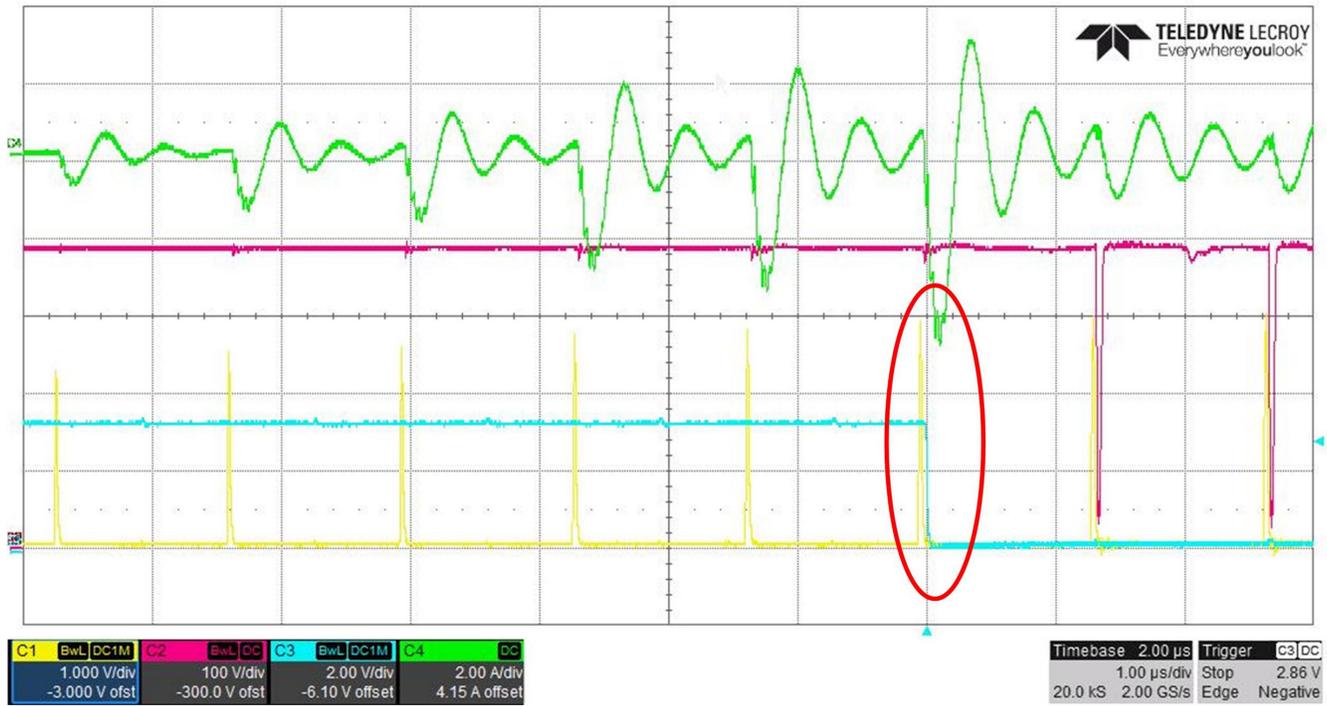

**Figure 2. An TI LMG3410 Shoot-through Test on an LLC Series Resonant Half-bridge Converter:**  
**C1 = Low-side Switch Driving Signal, C2 = Switching-node Voltage, C3 = High-side Switch Driving Signal,**  
**C4 = Primary Inductor Current**

#### Additional Resources

- If you are interested in using TI GaN devices in your power-supply designs, see the [400V – 12V/500W High Frequency Resonant Converter Reference Design Using High Voltage GaN devices \(PMP21842\)](#).
- Read the Power Supply Design Seminar paper, “[GaN FET-Based CCM Totem-Pole Bridgeless PFC.](#)”

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated