

Logic Gates and Switches with Ioff or Powered-off Protection: Empowering You to Power Down



Shreyas Rao

Many modern high-speed systems like enterprise servers or network switches require continuous operation without affecting signal integrity, especially while swapping hardware. One of the essential and basic features for isolation requirements is a partial power-down feature.

As [Figure 1](#) shows, device No. 1 is powered up in the system with 5V, while device No. 2 and No.3 is powered down with $V_{cc} = 0$; all subsequent devices are powered down as well. The bus logic is still active with 5V. The Electrostatic Discharge (ESD) clamp diodes to V_{cc} will become active and start conducting, powering the system back to active. The current through the diode, unless limited by a series resistor, will be heavily forward-biased and hence will conduct tens of milliamps of current, which could lead to device damage. After this event, the reliability of the device when powered back to normal operation is questionable.

 


Figure 1. Device without Powered-off Protection

[Figure 2](#) shows the second device with Powered-off protection (also known as I-off protection) circuitry. The device and the system connected to V_{cc1} are isolated from the active bus lines. The current through the ESD diodes is negligible due to the powered-off protection circuit inside, and the device reliability is intact. Powered-off protection ensures that no excessive current gets drawn into or out of the input, output or input / outputs (I/Os), which are biased to a voltage while the device powers down. The partial power-down mode helps avoid uncertain behavior during power down or power up.

 


Figure 2. Device with Powered-off Protection

The basic Complementary Metal Oxide Semiconductor (CMOS) contains parasitic diodes between N-channel Metal Oxide Semiconductor (NMOS) and P-channel Metal Oxide Semiconductor (PMOS), biased such that there is minimal current leakage. The typical Ioff subcircuit consists of a blocking diode from V_{cc} connected to the

common cathode (also known as the back gate) of the parasitic diodes to prevent current flowing back into Vcc, as shown in [Figure 3](#).

 


Figure 3. Typical Powered-off Protection Circuit

[Figure 4](#) is a setup on the [SN74CB3Q3125](#) device, which acts as a bidirectional switch when enabled and supports powered-off protection. The Vcc is ramping down and a constant current is pushed through the switch. As the Vcc ramps down to about 0.5V, the switch is conducting and lower than 0.5V, the device turns off and the loff circuit takes over.

 


Figure 4. Ioff Setup for Device Turn on

The device families with partial power-down list in the feature section of the datasheet as “loff partial-power-down mode,” and “isolation in powered off mode with $V_+=0$,” among others. In data sheet specs, the loff is a separate row, mentioned along with the test conditions as shown in [Figure 5](#).

1 Features

- Available in the Texas Instruments NanoFree™ Package
- I_{off} Supports Partial-Power-Down Mode Operation

6.4 Electrical Characteristics

over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONS	V_{CC}	MIN	TYP ⁽¹⁾	MAX	UNIT
I_{off}	V_I or $V_O = 5.5$ V	0		±10		μA

Figure 5. Data Sheet Representation and Electrical Specs

TI classifies loff or powered-off protection as Level 1 isolation, which is a primary requirement for hot or live insertion for systems where you need to remove or insert cards in the backplane without compromising the system’s overall signal integrity. The partial power down mode helps reduce energy consumption by turning off a portion of a system and isolating the rest of the subsystem. The partial power-down feature is found in most logic families: ABT, ALVT, AVC, AUC, AUP, CBTLV, CBT-C, GTL, GTLP LV-A, LVC, LVT and VME.

Did you know about the loff or powered-off protection feature and its importance in the applications you are currently using? Please comment if you’ve made a conscious decision to choose a logic device because of its powered-off protection feature rather than another device without one.

The [TMUX1511](#) is pin-out compatible to the [SN74CB3Q3125](#).

Additional Resources

- Read these application reports:
 - [How to Select Little Logic](#)
 - [Logic in Live-Insertion Applications with a Focus on GTLP](#)
 - [Simplifying Design with 1.8-V Logic for Multiplexers and Signal Switches](#)
 - [Selecting the Correct Texas Instruments Signal Switch](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated