

USB Chargers Then and Now: Type-C Meets Energy Efficiency Standards



Kening Gao

While planning to write this post, I typed “type-C” into Google Trends. Interest in the term has been rising since 2015 shown in [Figure 1](#).

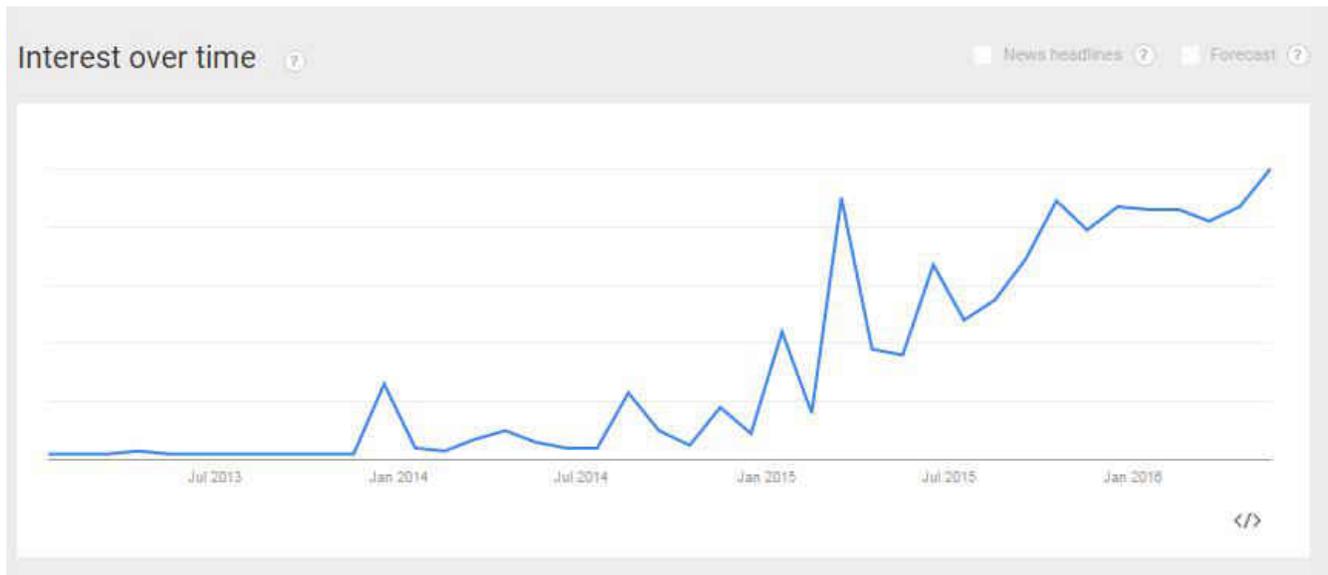


Figure 1. Interest over Time on Google Trends (Keywords: type-C)

USB Type-C devices are getting more and more popular in the real world as well, with many prevalent cell phones and tablets adopting USB Type-C. I expect products with USB Type-C to increase rapidly in the coming years.

Why 15 Watts (5V3A)?

Besides having a flippable plug that works regardless of orientation, USB Type-C delivers more power than any previous USB version. Although USB Type-C can support up to 100W for USB 3.1 and USB Power Delivery, system designers must choose features carefully to keep their overall costs reasonable. The USB Type-C interface also introduces native power capability of 15W, which is six times the standard USB 2.0 charging rate. For most smartphones and tablets, 15W is probably adequate, with a reasonable cost.

Diode Rectification and PSR Are Widely Used for Adapter Current Lower than 2A

In previous power adapters for mobile phones, a normal power level is 5V/2A or below. Primary-side regulation (PSR) is usually used for the AC/DC conversion because of its simplicity and ability to eliminate the optical isolator and programmable reference. A diode rectifier is used at this power level because the load current is not high. Figure 2 shows a simple PSR schematic with diode rectification.

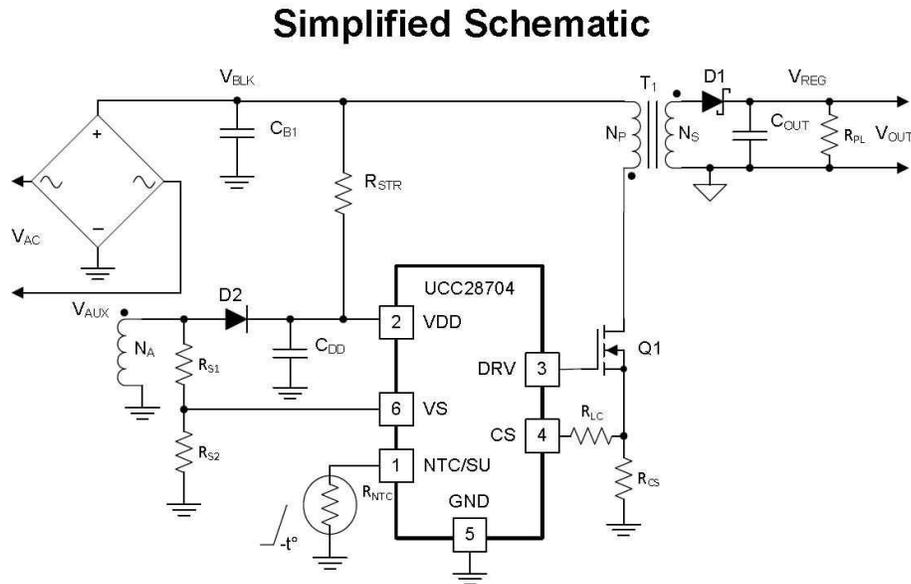


Figure 2. Typical Application Circuit of UCC28704 with Diode Rectification

Synchronous Rectification (SR) Is Preferable to PSR for 5V/3A Adapters with Design Challenges

PSR saves costs because it eliminates the need for secondary-side feedback components and an optical coupler. However designing with PSR + SR is not as easy as using PSR only.

Most PSR controllers will detect the voltage of the auxiliary winding on the knee point when the secondary diode current goes to zero, as the voltage on auxiliary winding is the closest to V_{OUT}/N_A , where N_A is the ratio of the auxiliary winding to the secondary winding.

There is a voltage bump on the auxiliary winding when the body diode conducts at the end of the secondary conduction time if using SR, refer to Figure 3. This bump will affect the PSR-detecting mechanism and cause stability problems, which may manifest as abnormal ripple.

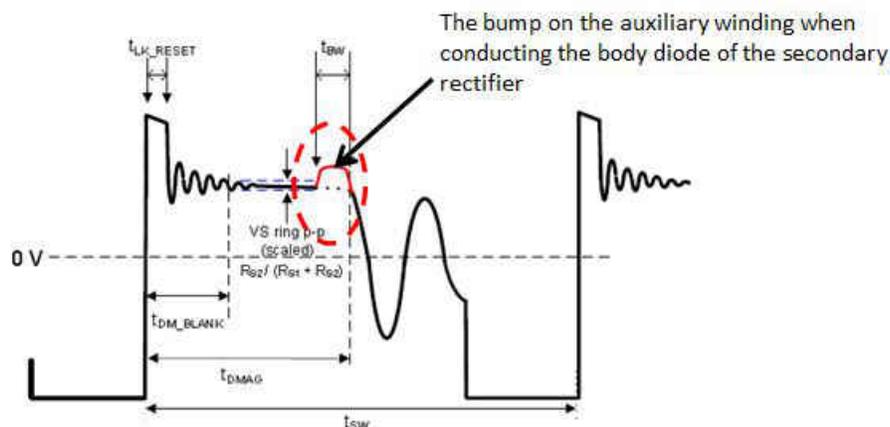


Figure 3. Auxiliary Waveform Details

How to Make PSR+SR Stable

To stabilize PSR + SR, the UCC28704's (PSR controller) data sheet makes it easier to work stably with SR drivers. t_{BW} , t_{DMAG} and working frequency are the parameters to design carefully. Where t_{BW} is the SR bump width, t_{DMAG} is the secondary rectifier conduction time

The critical parameter dictating the maximum switching frequency when using the UCC28704 with SR is determined based on $t_{DMAG(min)}$. The $t_{DMAG(min)}$ needs to be longer than $2.45\mu s$, including the SR bump width (t_{BW}) which is $750ns$. The $750ns$ (t_{BW}) is required for the internal circuit to filter out the SR bump change caused by MOSFET body-diode conduction sensed on the VS pin waveform. The corresponding switching frequency measured at the starting point of constant-current operation should not be greater than $55kHz$.

A 5V/3A Design with the UCC28704 (PSR Controller) and UCC24636 (SR Controller)

Following the guidelines, I made a 5V/3A board as shown in Figure 4. The ripple is below $150mV$, and the efficiency curve is in Figure 5.

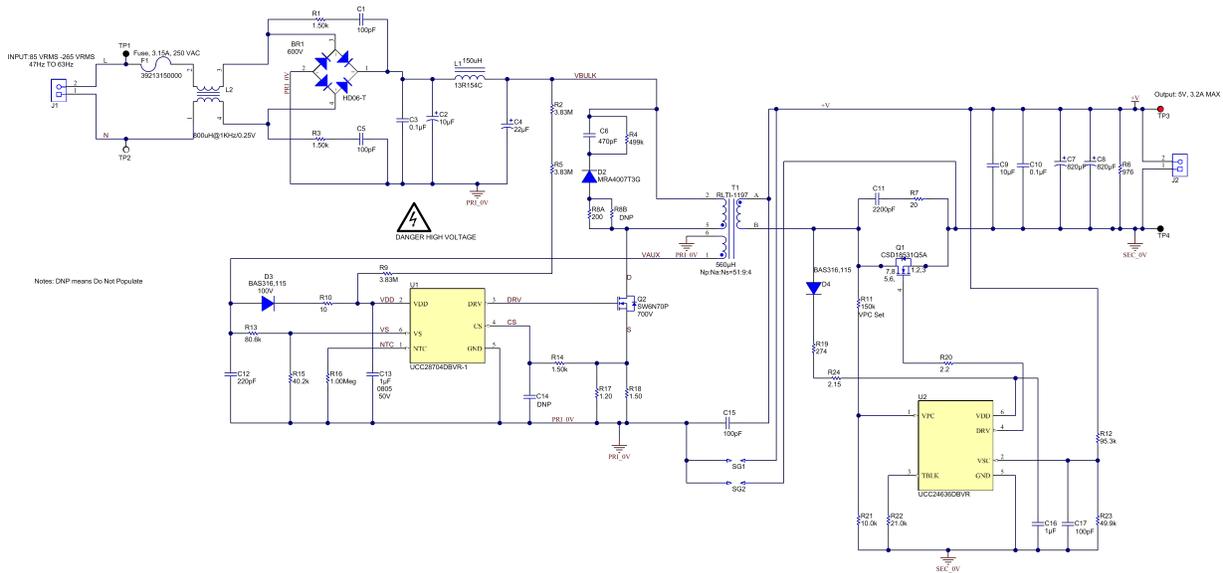


Figure 4. Universal AC Input to 5V/3A Output Reference Design DOE6 and COC V5 Tier 2 Compliant TI Design Schematic

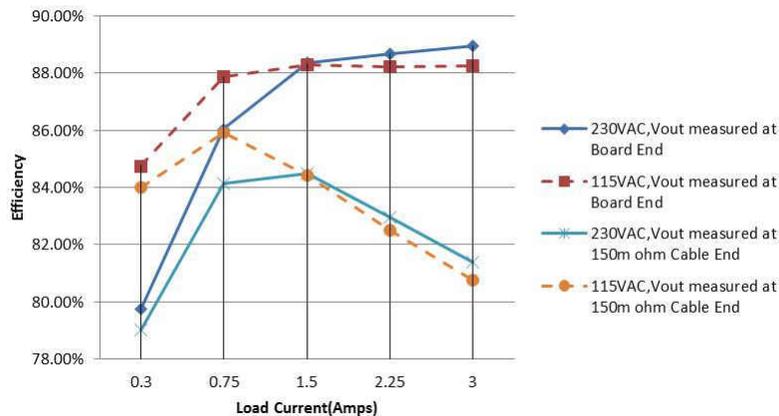


Figure 5. Efficiency Curves

The four-point average efficiency measured at a $150m\Omega$ cable end with $115V_{AC}$ and $230V_{AC}$ inputs are 83.4% and 83.2% . The COC Tier 2 2016 compliance is 81.8% for full load and 72.5% for 10% load.

The board can meet the CoC Tier2 compliance with enough margins even with $150m\Omega$ cable.

Summary

Following the guidelines in the UCC28704 data sheet, you can overcome the limitations and make a PSR + SR design that is low cost, yet has high-enough efficiency for USB Type-C adapters.

Additional Resources

- Learn more how PSR + SR works in the [UCC28704 data sheet](#) and [UCC24636 data sheet](#).
- The [Universal AC Input to 5V/3A Ooutput Reference Design DOE6 and COC V5 Tier 2 Compliant \(PMP15002\)](#) TI Design uses the UCC28704 and UCC24636.
- Read Anwar Sadat's paper, "[Low-cost implementation of USB Type-C.](#)"
- The TI Designs reference design, [Universal AC Input to 5V 2A Output Reference Design Tier 2 2016 Compliant \(PMP11612\)](#), is 5V/2A solution that meets CoC V5 Tier 2.
- Get to know the [USB Type-C DFP Charger 5V3A SSR Control Adapter Reference Design](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated