

USB Type-C Audio: Do I Need to Buy a New Pair of Headphones?



Adam Torma

For a recent trip to New Orleans, I invested in a quality pair of noise cancelling headphones to help me drown out the chatter. I am thrilled with my new purchase but I'm concerned I won't be able to use them when mobile phone developers remove the traditional 3.5mm audio jacks from their phones in exchange for using USB Type-C™ connectors. This change will allow for thinner phones and cost savings due to using one less connector.

The USB 3.1 specification supports both charging and data-transfer capabilities, as well as connections to analog audio headsets, by multiplexing four analog audio signals onto pins on the [USB Type-C connector](#). The analog audio signals are the same as those used by traditional 3.5mm headset jacks. This makes it possible to use existing analog headsets with a 3.5mm-to-USB Type-C adapter if the phone will support analog audio. [Figure 1](#) and [Table 1](#) illustrate the pin mappings of a USB Type-C connector that support analog audio.

A simple solution exists that would enable mobile phone designers to easily remove these 3.5mm audio jacks and remain backwards compatible with the existing analog audio signals.

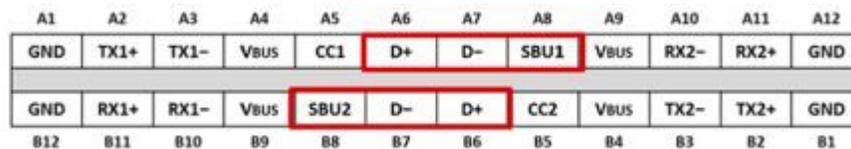


Figure 1. USB Type-C Connector Pinout

Table 1. USB Type-C Connector Analog Audio Pin Assignments

Plug pin	USB name	Analog audio function	Location on 3.5 mm jack	Notes
A6/B6	Dp	Right	Ring 1	Analog audio right channel. A6 and B6 shall be shorted together in the adapter.
A7/B7	Dn	Left	Tip	Analog audio left channel. A7 and B7 shall be shorted together in the adapter.
A8	SBU1	Mic/AGND	Ring 2	Analog audio microphone (OMTP & YD/T) or audio GND (CTIA).
B8	SBU2	AGND/Mic	Sleeve	Audio GND (OMTP & YD/T) or analog audio microphone (CTIA).

The pin mappings in [Table 1](#) look straightforward, but a few challenges will arise when trying to support this type of pinout in your system:

- Analog audio signals have negative voltage swings that can damage the USB physical layer (PHY).
- The USB Type-C connector is reversible.

Analog audio signals traveling through the 3.5mm jack are typically alternating current (AC) signals centered at 0V. The negative voltage portion of the analog audio signal can be damaging to USB PHYs. The best way to resolve this issue is to place a USB and audio switch like the [TS5USBA224](#) on the D+ and D- pins of the USB

Type-C connector. As [Figure 2](#) shows, the device can route the analog audio signals to the codec and the USB signals to the USB PHY when appropriate.

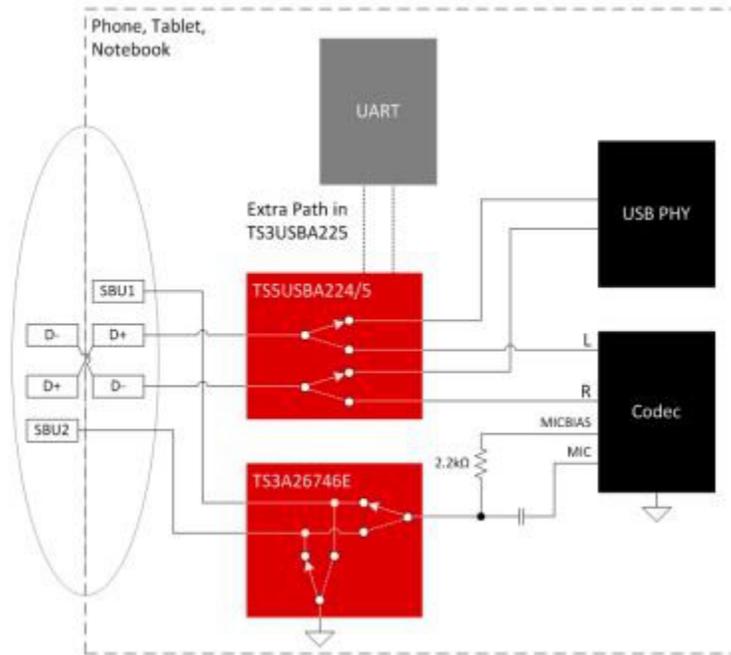


Figure 2. Analog Audio Signal Routing from USB Type-C Connector

The second challenge with supporting the four analog audio signals on a USB Type-C connector is the connector's reversibility. For the left and right signals on the D+ and D- pins, you can easily accommodate this reversibility feature by shorting the D+/D- pins to their respective D+/D- pins on the top and bottom of the USB Type-C receptacle. Handling the microphone and ground signal on the SBU1 and SBU2 is not as simple as shorting the two pins together. You will need a crosspoint switch like the small [TS3A26746E](#) (manual switching) or an audio jack detection crosspoint switch like the [TS3A226AE](#) (automatic switching) to route the microphone and ground signals to the codec appropriately.

It is possible to support the same analog audio signals in a 3.5mm jack by solving many of the challenges that arise in multiplexing analog audio signals onto a USB Type-C connector.

Would you like to see more mobile phones remove their 3.5mm jack, but still be able to use your favorite headphones? Log in to comment or visit the [TI E2E™ Community Signal Switches forum](#).

Additional Resources

- Download the [TS5USBA224](#), [TS3A26746E](#) and [TS3A226AE](#) data sheets.
- Jump-start your design with the [USB Type-C Audio Adapter Accessory Mode Reference Design \(TIDA-00565\)](#).
- See other posts about implementing [USB Type-C](#).
- Learn about TI's complete portfolio of USB Type-C compliant [products and resources](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated