

Power Tips: Power Sharing in USB Type-C Applications



Brian King

The USB Type-C™ Power Delivery (PD) standard makes an allowance for anywhere from 7.5W (5V at 1.5A) to 100W (20V at 5A) per port. In any given system, however, the available input power is limited. In a multiple-port system, how should you allocate power between the various ports?

One obvious power-sharing method is to limit the power on each port so that the total power drawn can never exceed the input power limit. But in this case, any device plugged into the system can never fully utilize the available input power, because the power is divided among the ports.

Another option is to provide one high-power port and severely limit the power to the remaining ports. This gives users the ability to power larger devices and enables faster charging. However, most consumers don't read product labels or instructions. They may not understand why their device charge slower on some ports but not others. This can create a poor user experience, leading to product returns and affecting customer loyalty.

A better approach is to intelligently share the available input power among the ports in a system. The TPS25740A PD source controller has two pins which easily implement port power management in two-port systems.

The UFP pin is an open-drain signal that indicates the status of the output port. The UFP signal is normally high, but goes low whenever a valid load is connected to the output port. The PCTL pin is an input that when pulled low cuts the maximum power advertised from the TPS25740A by a factor of two. Toggling the PCTL pin also forces any connected loads to renegotiate the power contract, which defines the output voltage and maximum power available on the port.

Figure 1 shows an example of a 36W two-port system using port power sharing. Initially, when nothing is plugged into either Type-C output port, both ports advertise that the full 36W is available. When a device is plugged into one of the ports, it can accept the full 36W. Because a valid load has been connected, the UFP pin for that port goes low, pulling down the PCTL pin of the TPS25740A on the opposite port. Thus, the opposite port is now advertising only 18W.

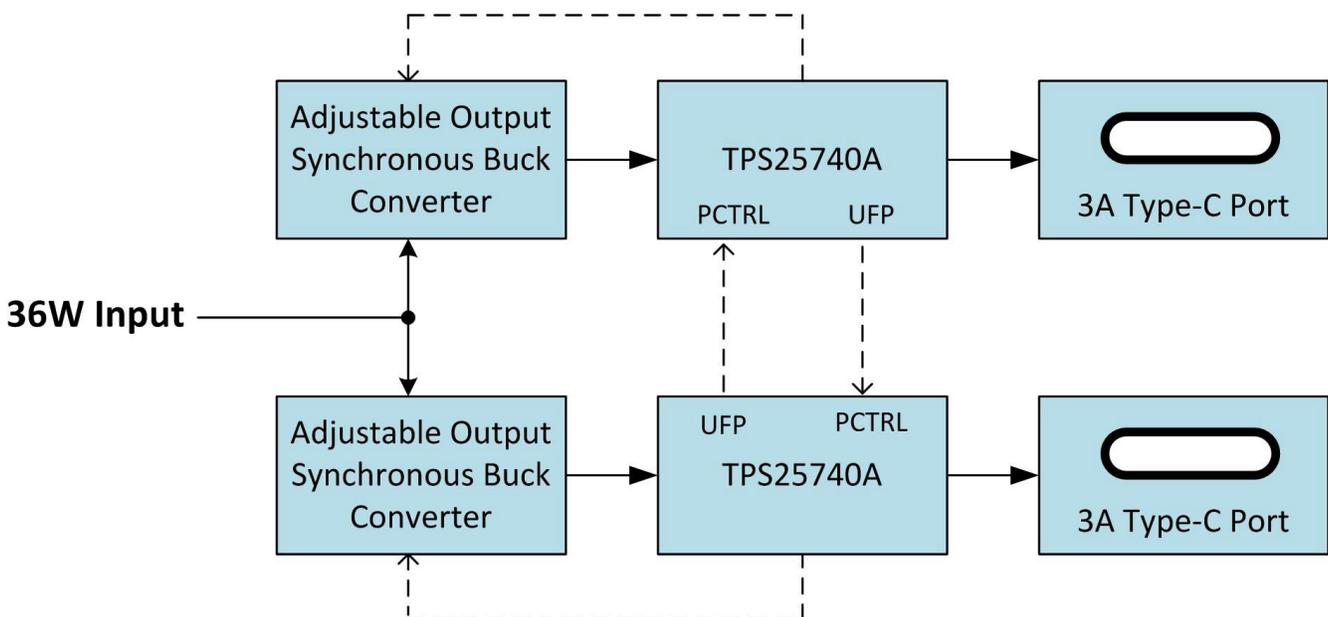


Figure 1. This 36W System with Port Power Management Intelligently Shares Power between Two Ports

Now, if a device is connected to the second port, the UFP pin from that port goes low, forcing the first port to renegotiate the power contract at 18W. When both ports are providing power, they can never exceed 18W each, 36W total.

You can apply similar techniques to systems with more than two ports, but you will usually need a microprocessor given the increased complexity. A microprocessor also allows the system to shift power based on other factors such as temperature.

There are many other things to consider when designing multiple-port systems for USB Type-C PD. Read an article where I discuss a few more details about multiport Type-C systems in my latest [Power Tips post on EE Times](#).

Additional Resources

- Download the [TPS25740A](#) data sheet for additional information about the device and power profiles.
- Get more information on [USB Type-C™ products](#) from TI.

Read Previous [TI Power Tips posts](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated