

Powering Smart Sensor Transmitters in Industrial Applications



Timothy Hegarty

Smart sensor transmitters are widely used in [factory automation](#), process instrumentation and control equipment to measure temperature, pressure, flow, level and many other process variables. [Figure 1](#) is a block diagram of a field transmitter that measures temperature as the primary variable using a resistance temperature detector (RTD), thermistor or thermocouple.

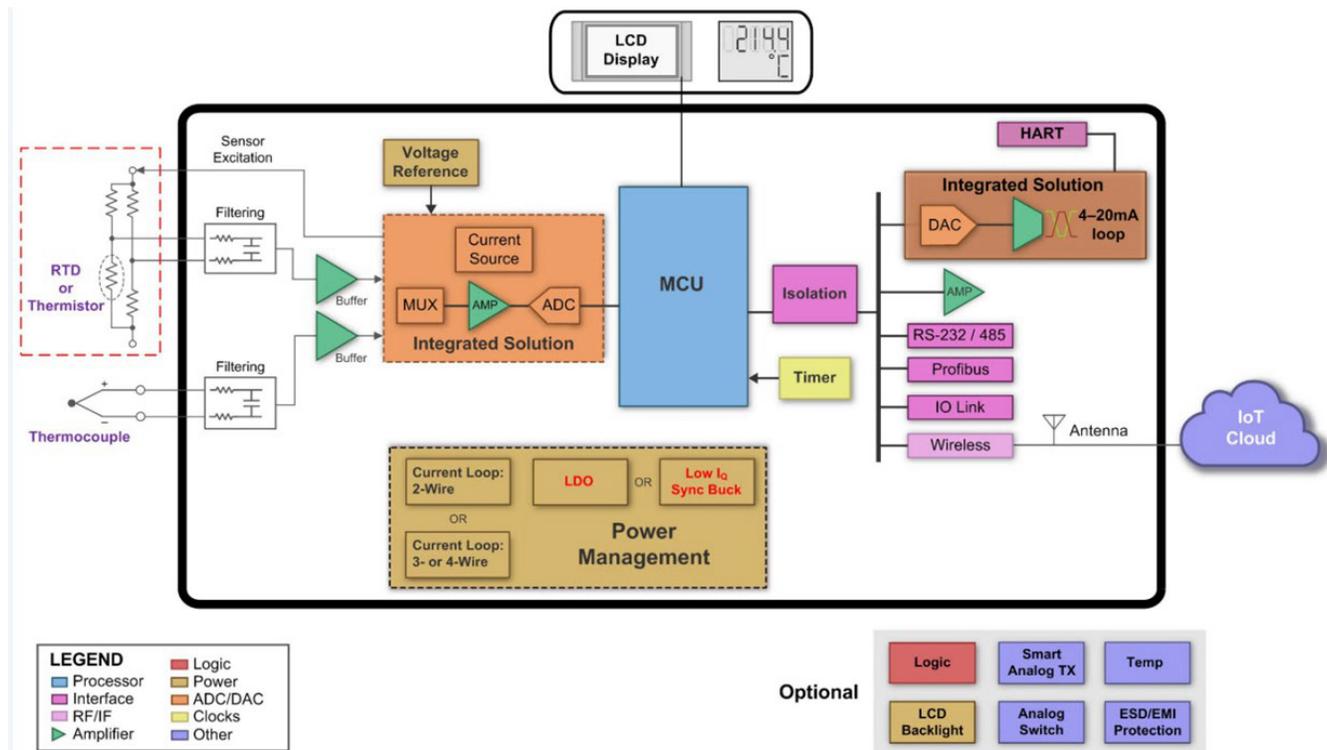


Figure 1. Temperature Transmitter Block Diagram for Process Control Applications

The signal chain includes the sensor analog front end, microcontroller (MCU), and high-precision analog-to-digital and digital-to-analog converters.

Powering Smart Sensors from the 4-20mA Loop

While a basic sensor transmitter circuit's MCU and data converters are usually optimized for low operating current, the added functionality in high-performance smart sensor applications leads to increased current demand. For example, current consumption is greater when the circuit includes features such as isolation, calibration and diagnostics, a liquid crystal display (LCD) interface, or wireless connectivity options such as [Bluetooth® low energy](#) or [wireless HART®](#).

Such intelligent sensor systems may not be able to meet typical underscale current thresholds or the 4mA zero-scale level of the 4-20mA current loop. For example, the default loop currents that demarcate low- and high-error currents for TI's [DAC161S997](#) are 3.375mA and 21.75mA, respectively. The [NAMUR NE43](#) specification has similar current thresholds. Fortunately, a high-efficiency synchronous buck converter provides higher output

current than a low-dropout regulator (LDO) to power sensor electronics, while harvesting less than 3.375mA from the loop.

Wide V_{IN} , Low I_Q Synchronous Buck Converter

For powering sensors, the **LM5165** synchronous buck solution from TI has high-efficiency and ultralow quiescent current ($I_Q = 10.5\mu\text{A}$). Operating from a 20:1 wide input-voltage (V_{IN}) range and capable of sustaining repetitive 65V surges, its output voltage is immune to large and noisy voltage swings at the input. Such transient immunity performance is critical in sensor applications that require high reliability.

Figure 2 shows the converter schematic configured for an output of 5V at 25mA. Adding an input filter with reverse polarity and transient/surge voltage protection helps achieve **electromagnetic compatibility (EMC)**.

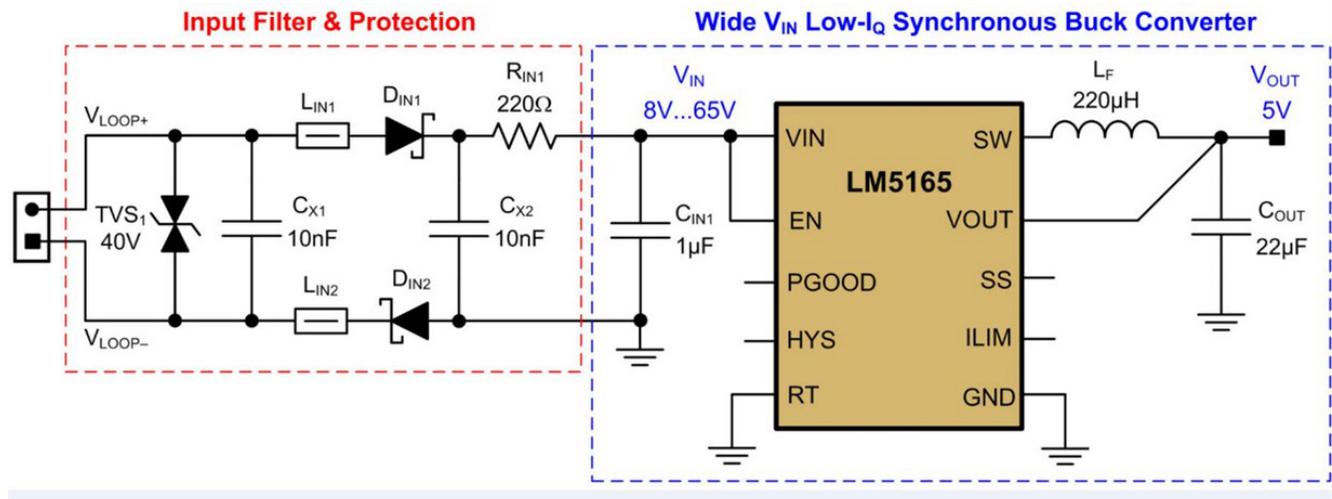


Figure 2. Pulse-frequency Modulation (PFM) Synchronous Buck Converter Schematic, Including an EMC Filter and Protection Circuit

Various features incorporated in the **LM5165** for smart sensor applications include a simple control architecture for optimal solution size, 100% duty cycle capability for low dropout, an open-drain power-good circuit for power-rail sequencing and fault reporting, internally fixed or externally adjustable soft start (SS), and precision enable with customizable hysteresis for programmable-line undervoltage lockout (UVLO). Also, an adjustable cycle-by-cycle current limit optimizes inductor selection and sizing. Figure 3 shows the converter efficiency and power dissipation for a load current from 0.1mA to 30mA.

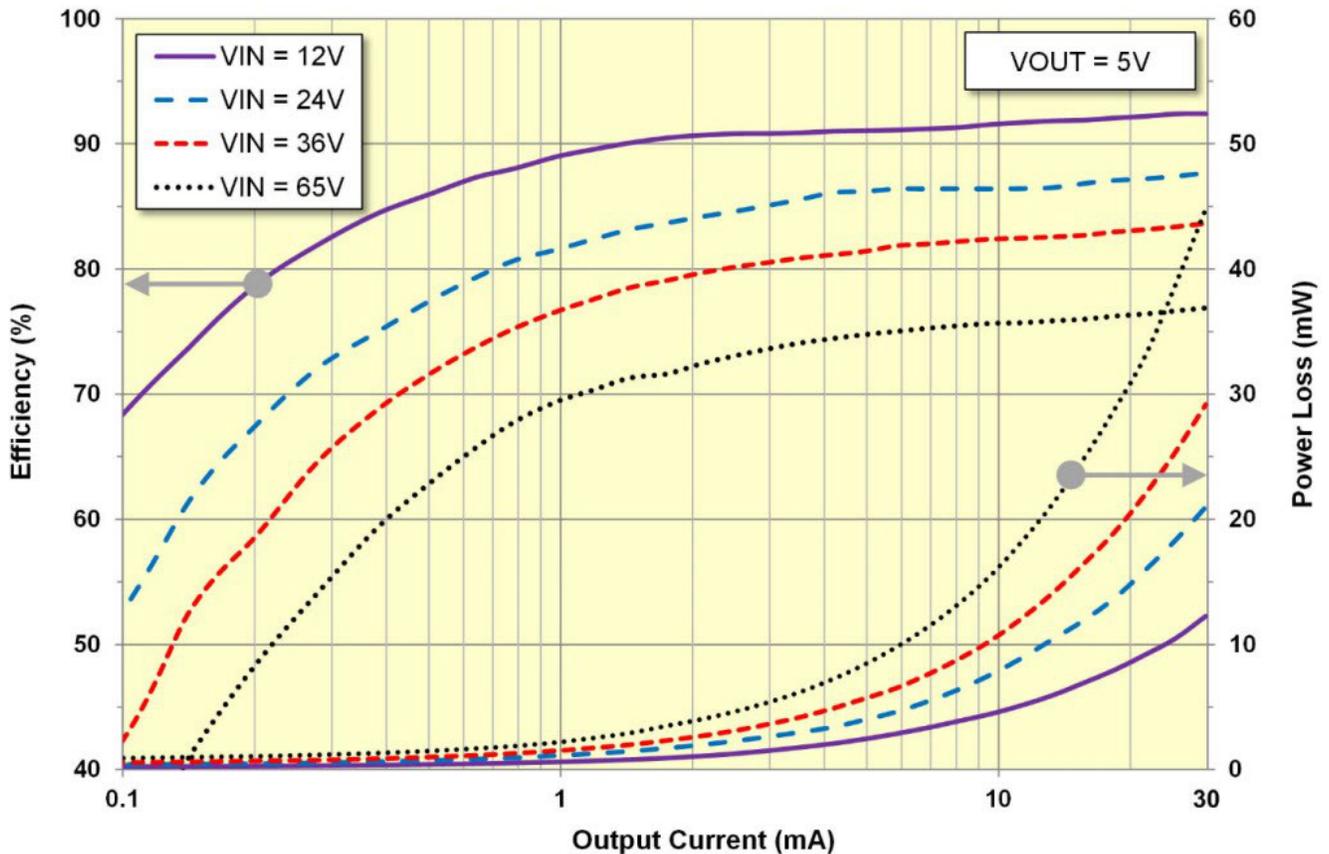


Figure 3. Typical Efficiency of the LM5165 Buck Converter (Output Rated for 5V at 25mA)

Value Proposition of a Wide V_{IN} , Low I_Q Buck Converter

The benefit of a wide V_{IN} buck converter such as the [LM5165](#) lies in its cohesive feature set, which addresses a specific set of power solution needs:

- Synchronous buck design with high efficiency over a wide load current range.
- Enhanced reliability with an operating junction temperature rated to 150°C.
- Wide V_{IN} range with enough margin to survive input-voltage transient disturbances, allowing the use of a higher voltage (and smaller footprint) transient suppressor diode (TVS).
- Small solution size for space-constrained sensor housings.
- Reduced input capacitance to meet requirements for [intrinsically safe](#) (IS) application environments.
- Active slew-rate control of the switch-mode voltage reduces high-frequency conducted and radiated EMI signatures.

To exploit the full potential of modern loop-powered sensor transmitters and retain the simple two-wire architecture, the LM5165 low I_Q synchronous buck converter delivers adequate load current while meeting current loop, solution size, reliability and EMC requirements.

Additional Resources

- Read more about two-wire, 4-20mA [sensor transmitters](#) in TI's Precision Hub blog.
- Order the [PFM](#) and [constant on-time](#) (COT) evaluation modules for the [LM5165](#) synchronous buck converter.
- Use the [LM5165](#) quick-start design tool to expedite a design and examine the converter's efficiency plotted over log and linear scales of output current.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated