

Jennifer Joseph

Automotive electronics and infotainment systems comprise a plethora of electronic components such as microcontrollers, sensors and other peripherals that operate at different voltages. Dropping microcontroller voltages in these electronics achieves higher power efficiencies, but peripherals still require operation at higher voltages. This creates a situation of voltage incompatibility that voltage level-shifters/translators can resolve. TI's automotive portfolio includes [voltage level-shifters/translators](#) that are compliant with Automotive Electronics Council (AEC)-Q100.

Figure 1 illustrates incompatible logic threshold levels between 3.3V microcontrollers and legacy 5V peripherals. To interface at least two devices successfully, requires these conditions:

- The output high voltage (V_{OH}) of the driver must be greater than the input high voltage (V_{IH}) of the receiver.
- The output low voltage (V_{OL}) of the driver must be less than the input low voltage (V_{IL}) of the receiver.
- The output voltage from the driver must not exceed the input/output (I/O) voltage tolerance of the receiver.

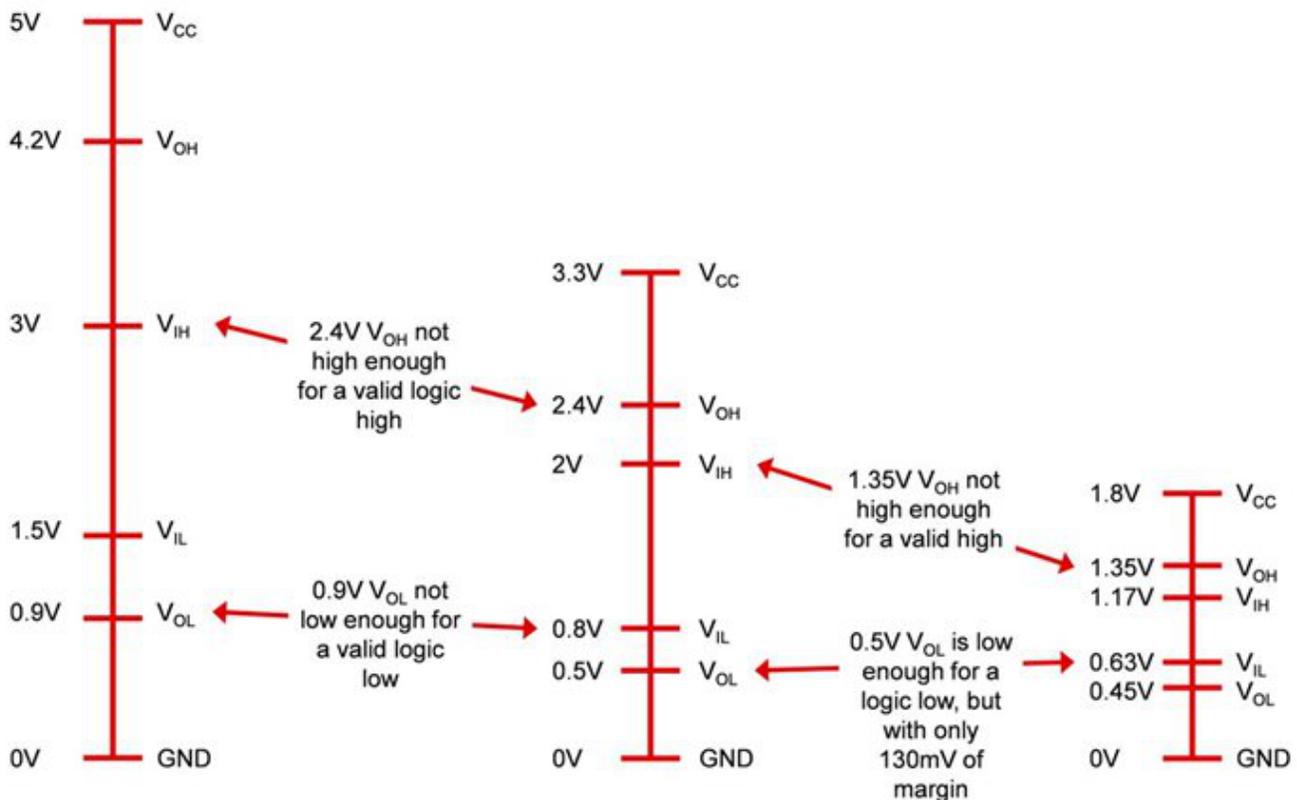


Figure 1. Illustrating Logic-level Incompatibility

In complex infotainment systems, unidirectional voltage-level translators such as the SN74AUP1T34-Q1, allows interfacing from extremely low-voltage processors to 3.3V peripherals. It also provides enough output drive current to fan out to multiple loads. Figure 2 shows an application use case of the SN74AUP1T34-Q1 as a clock fanout buffer. Figure 3 shows the SN74AUP1T34-Q1 measurement data of low jitter (~ 500ps).

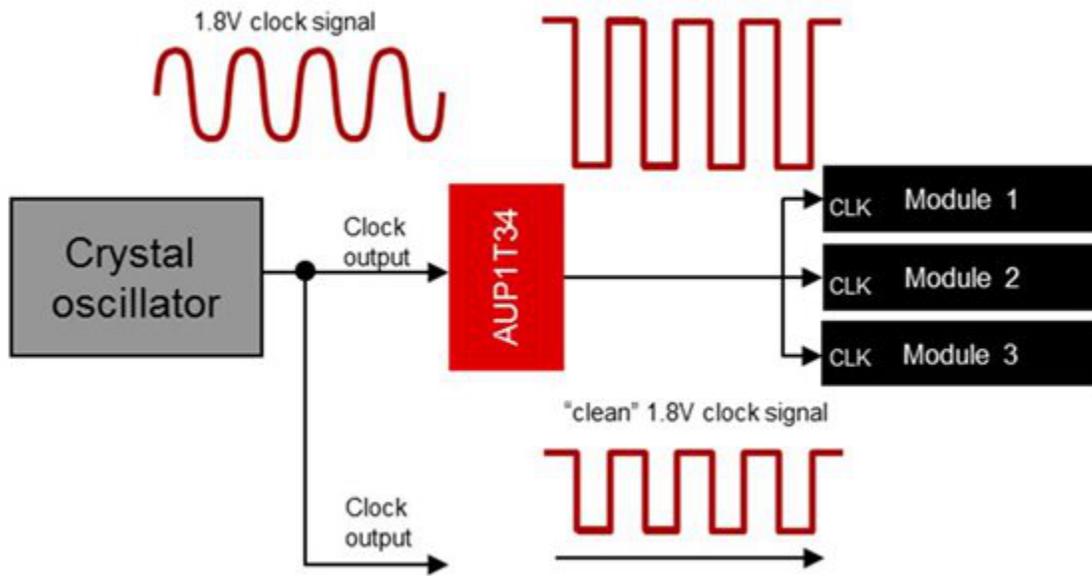


Figure 2. The SN74AUP1T34-Q1 as a Clock Fanout Buffer

V_{cca}: 1.8V, V_{ccb}: 3.3V, C_{load} = 15pF, Decoupling = 1μF, 0.01μF.

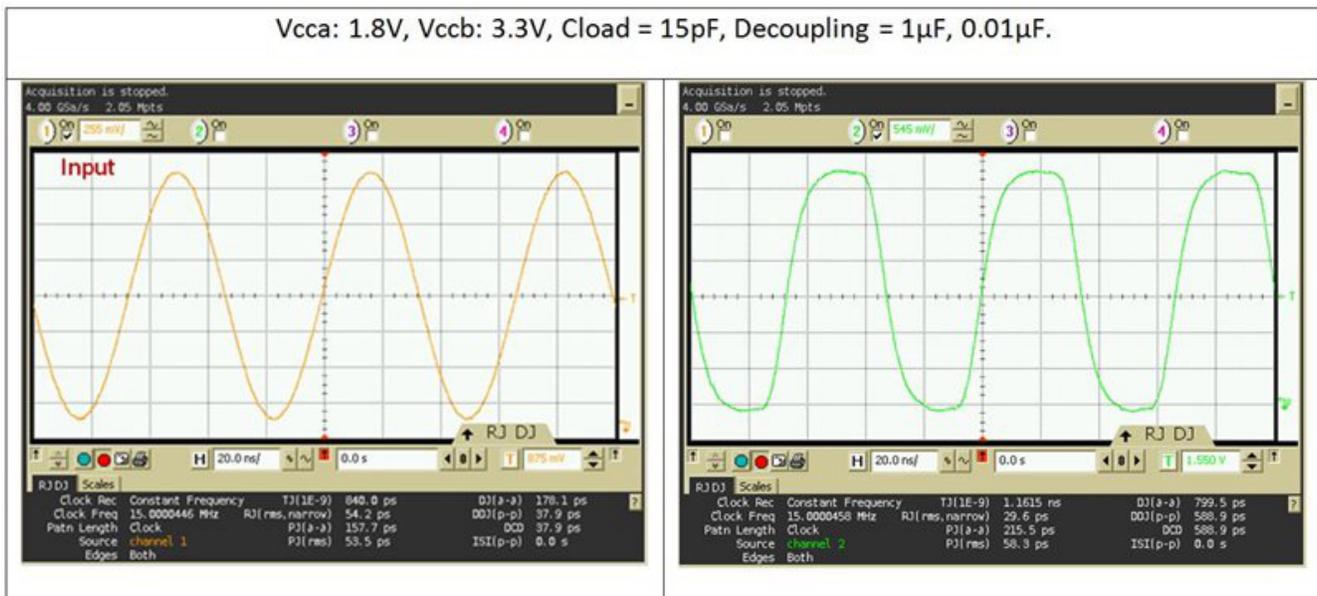


Figure 3. SN74AUP1T34-Q1 Buffers Sine Input to a Square-wave Output

If you do not want to configure the direction of the level shifter, you can use autodirection translators such as the TXS0102-Q1, TXS0104-Q1 and TXB0102-Q1. The TXS0102-Q1 has low leakage and static consumption and saves precious power for other critical devices during start/stop events. Figure 4 shows an application use case of the TXS0102-Q1 for an open-drain signal interface. Figure 5 shows the TXS0102-Q1 measurement data when used as an I²C level shifter.

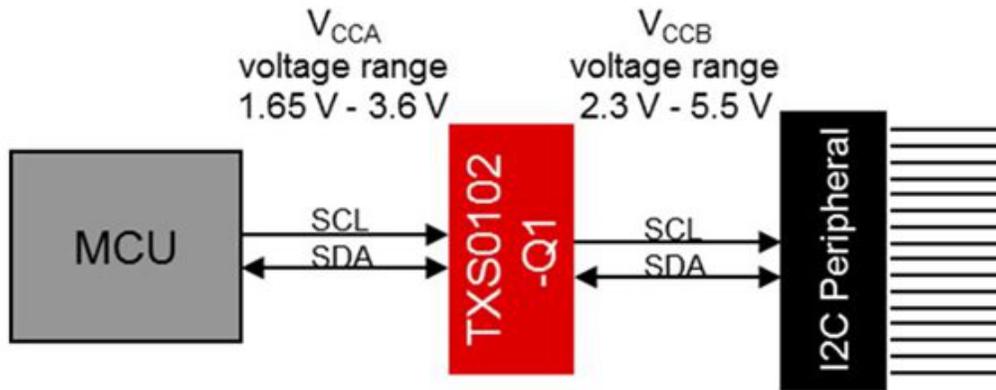


Figure 4. The TXS0102-Q1 as an Open-drain Level Shifter

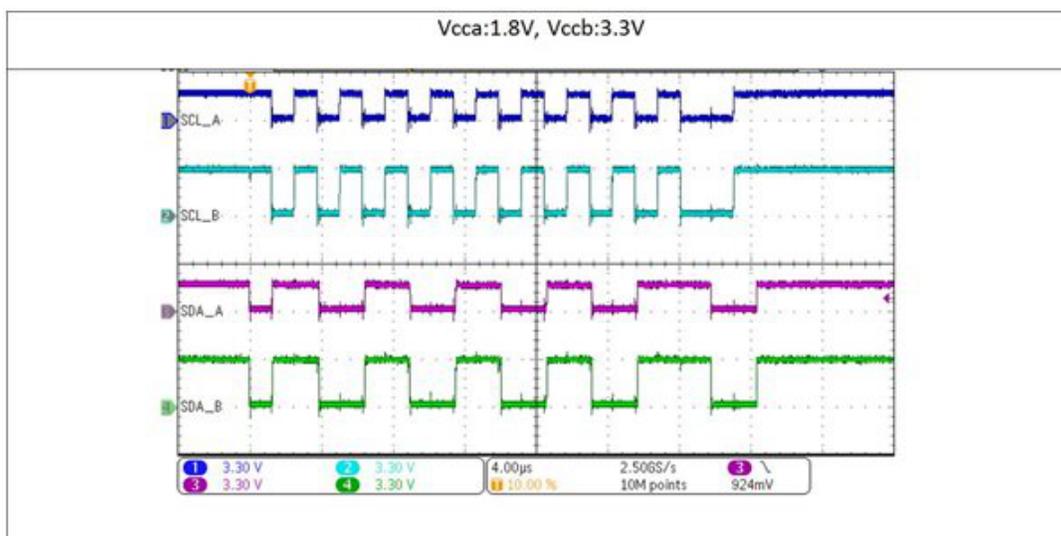


Figure 5. The TXS0102-Q1 I²C Level Shifter for Clock and Data

If you want to control the direction of the level shifter, consider translators such as the [SN74LVCxT245-Q1](#) and [SN74AVCxT245-Q1](#) family for heavily loaded buses where multiple devices are connected to the bus. These devices offer up to 12mA/24mA of current, respectively, and a dedicated DIR pin controls the flow of data.

Since microcontrollers (MCUs) and microprocessors (MPUs) are migrating to more advanced processors with higher processing power for image recognition and greater resolution, cost and power savings are driving the need for lower-voltage operation in infotainment, advanced driver assistance systems (ADAS), telematics and cluster systems. This introduces a need for voltage-level translation that is readily achievable with TI's portfolio of AEC-Q100-compliant voltage level-shifters/translators.

How are you using voltage level-shifters or translators in your automotive applications? Log in to post a comment below.

Additional Resources

- Learn more about [voltage-level translation](#) and the [specific devices](#) discussed in this post.
- Visit the [TI E2E™ Community voltage translation forum](#) to find questions and answers from TI's logic and voltage translation team and fellow engineers.
- Read our blog post, "[Good designs need the right translation.](#)"

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated