

Life was simple when I first became interested in electronics. Components were so big I could solder them without a microscope. Switching converters switched at a whopping 25 kHz, digital circuits all used a 5-V supply voltage and all the computers I came across used the RS-232 serial interface to communicate.

The RS-232 standard specifies that a logic 0 is represented by voltages between 5 V and 25 V, and a logic 1 by voltages between –5 V and –25 V. My problem was that although almost all the components on my boards needed only a 5-V supply, I still had to generate those two extra rails for my RS-232 interface.

Then I came across the [MAX232](#). This device was an inspired product, combining two line drivers, two line receivers, and a positive and negative charge pump. With that bad boy running off a single 5-V supply, I could generate the additional supply voltages I needed and transmit and receive serial data.


Charge pumps are useful little DC/DC converters that use a capacitor to store energy instead of an inductor. They can be found in dedicated charge-pump devices such as the [LM2775/LM2776](#) devices, as auxiliary rails in LCD bias supplies such as the [TPS65150](#), or as external circuits put together from a couple of diodes and a couple of capacitors.

Generally speaking, charge pumps are:

- Simple, often comprising no more than two diodes and two capacitors.
- More forgiving than DC/DC converters.
- Good for output currents in the tens of milliamps range (but not so good for currents much higher than 250 mA).
- Less efficient than inductor-based DC/DC converters, unless they are unregulated and running open-loop.


[Figure 1](#) is a simplified circuit diagram of an unregulated charge pump. The charge pump operates in two phases:

- During the charge phase, switches S1 and S4 are open and switches S2 and S3 are closed. Current flows through S2 and S3 and charges the flying capacitor,  $C_{FLY}$ , up to a voltage of  $V_I$ .
- During the discharge phase, switches S1 and S4 are closed and switches S2 and S3 are open. The negative terminal of  $C_{FLY}$  is now at  $V_I$  and the positive terminal (which is  $V_I$  volts higher) is now at  $2V_I$ . Current flows from  $V_I$  through the flying capacitor  $C_{FLY}$  and switches S1 and S4. Charge is transferred from  $C_{FLY}$  to the output capacitor,  $C_O$ , to generate an output voltage approximately equal to  $2V_I$ .

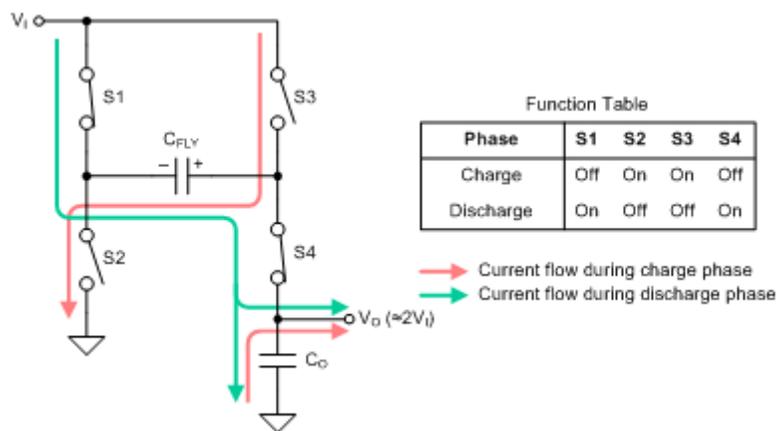

**Figure 1. Simplified Charge-pump Block Diagram (Voltage Doubler)**


You can rearrange the same four components (S1, S2, S3 and S4) to generate a negative output voltage equal to approximately  $-V_I$  (see [Figure 2](#)).

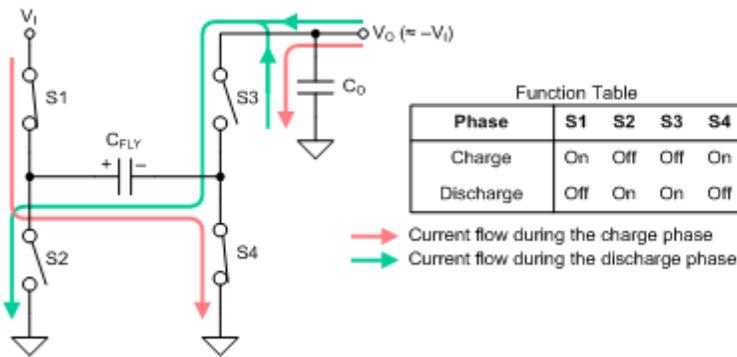

**Figure 2. Simplified Charge-pump Block Diagram (Voltage Inverter)**

The circuit just described works well, but its output voltage is unregulated. Such a simple circuit is sufficient in some applications, but a charge pump with a regulated output is much more useful.

The usual way to regulate the output voltage of a charge pump is to put an adjustable current source,  $I_1$ , in series with switch S1, or S2 in the case of an inverting charge pump (see [Figure 3](#)). The error amplifier, A1, adjusts the value of  $I_1$  until the output voltage is correct. Under steady-state conditions,  $I_1$  is exactly twice the value of  $I_O$ .

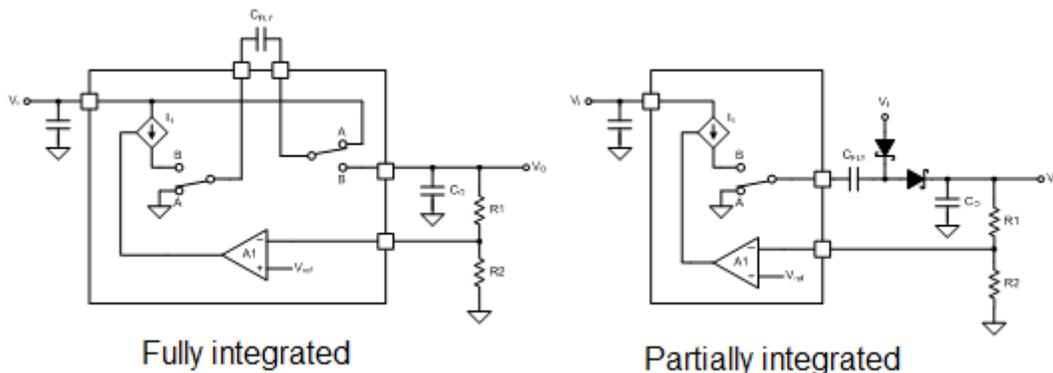

**Figure 3. Different Charge-pump Integration Levels**

Note that a simple, regulated voltage doubler can only regulate its output voltage in the range of  $V_I$  to  $2V_I$ . It cannot generate output voltages lower than  $V_I$ . There are some fancy tricks you can do to make a buck-boost charge pump, but these kinds of devices are more complicated than the one shown in [Figure 3](#).

#### Additional Resources:

- Find help deciding between a [charge pump](#), inductor-based converter or LDO.
- Browse the [charge pump portfolio](#).
- Learn more about “[The Forgotten Converter](#)” in this white paper.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated