

Learn the Inner Workings of a CAN Bus Driver and How to Debug Your System



John Griffith

Welcome to the third post in this [series about the controller area network \(CAN\)](#). In my last post, I focused on what [CAN bus signals look like](#) in terms of voltage levels on the bus pins. In this post, I'll focus on the typical topology of the CAN driver output stage to drive those bus voltages. For anyone that has ever had emissions problems or output differential voltage problems in a CAN network, this blog describes how the driver works and what electrical parameters you can look at in a datasheet to identify a good transceiver. I believe a basic understanding of the CAN driver can also help aid with debugging CAN issues if they arise.

CAN transceivers like the [TCAN332](#) usually have an equivalent two-output structure, as shown in [Figure 1](#). The high-side output structure consists of a series diode and a P-channel transistor, while the low-side output structure consists of a series diode and an N-channel transistor. On the high-side, the series diode blocks current from flowing into V_{CC} net if the CANH bus voltage exceeds V_{CC} during any transients or common-mode disturbances. The series diode on the low-side blocks current from flowing out of ground to the CAN bus if the bus voltage drops below the transceiver's local ground during transients and common-mode disturbances.

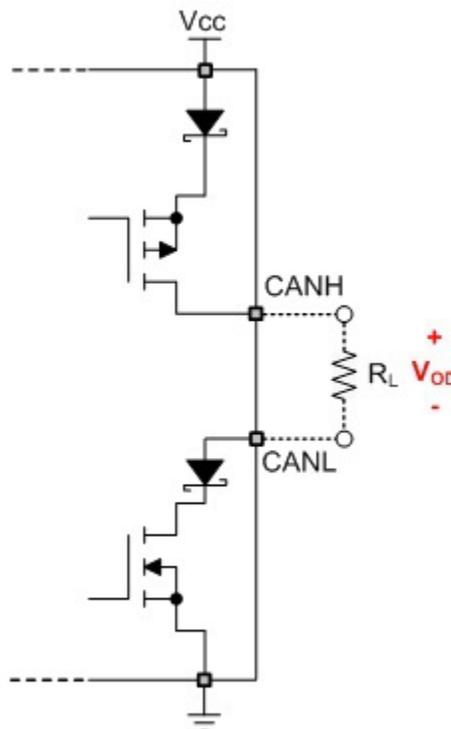


Figure 1. Equivalent Output Schematic of a CAN Transceiver

According to the ISO 11898 CAN standard, the two valid states for a CAN bus are the:

- Dominant state – a minimum 1.5V output differential voltage (V_{OD}) into a 50-65 Ω differential load (TXD = low).
- Recessive state – a maximum 50mV V_{OD} into a 50-65 Ω differential load (TXD = high).

As shown in [Figure 2](#), the driver is recessive when both the high- and low-side transistors are off and in a high impedance state. The driver is dominant when both the high- and low-side transistors are on and in a low impedance state.

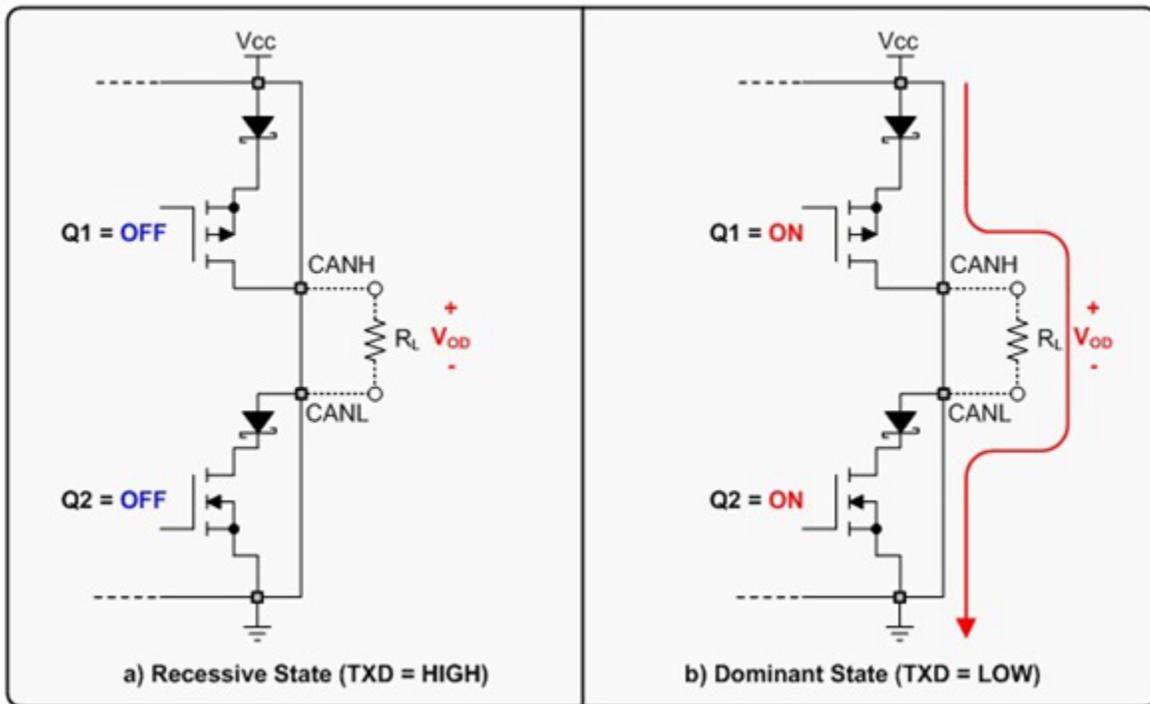


Figure 2. Recessive and Dominant States

Since both transistors are off in the recessive state (see the left side of [Figure 2](#)), negligible current will flow from V_{CC} to ground. The V_{OD} across the load resistance (R_L) is very close to 0V. In the dominant state (the right side of [Figure 2](#)), both transistors are on and in a low impedance state. Therefore, current will flow from V_{CC} to ground through the R_L and create a V_{OD} .

As I said in my [previous blog](#), CANH and CANL are weakly biased to $V_{CC}/2$ in the recessive state. To avoid creating common-mode disturbances when the device switches between recessive and dominant states, it is important to match the drive strength of CANH to V_{CC} and CANL to ground. Looking at [Figure 3](#), you can see that a well-matched drain-to-source on-state resistance ($R_{DS(ON)}$) of the P-channel and N-channel transistors centers the voltage drop across R_L between V_{CC} and GND at $V_{CC}/2$.

If one half of the driver had a considerably lower on-state resistance than the other half, then the bus common-mode voltage would be pulled away from $V_{CC}/2$ for the dominant state and back to $V_{CC}/2$ for the recessive state. This would result in a shift of common-mode for every transition of bus states and therefore higher levels of conducted and radiated emissions.

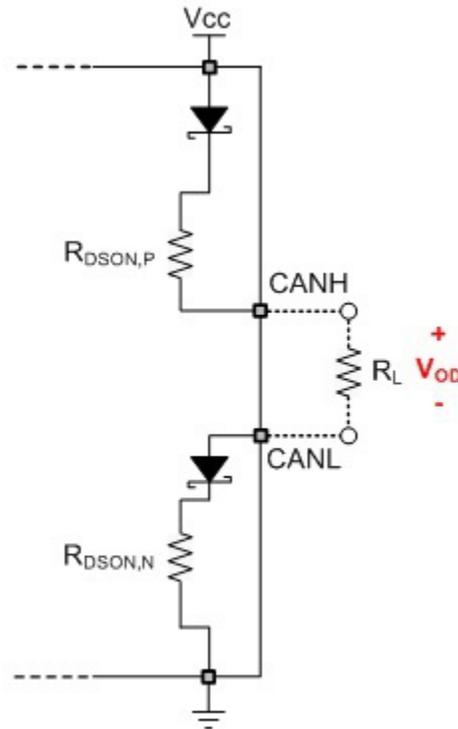


Figure 3. Equivalent Schematic Using $R_{DS(on)}$ Resistor Values

When looking at driver electrical specifications, the two most important things to look for are the guaranteed output voltages for dominant and recessive states with a given load resistance (stronger drivers will guarantee output voltages with a lower resistance) and the driver symmetry between dominant and recessive states.

Now that you know what the output driver of a CAN transceiver looks like, stay tuned for my next post, which will describe a typical input-receiver topology. As always, feel free to post any comments or questions below.

Additional Resources

- Check out the new [CAN bus transceivers page](#) to see our products, support resources and technical documents.
- Explore the [Polarity Correcting Isolated CAN Reference Design](#).
- See all the posts in the [CAN blog series](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated