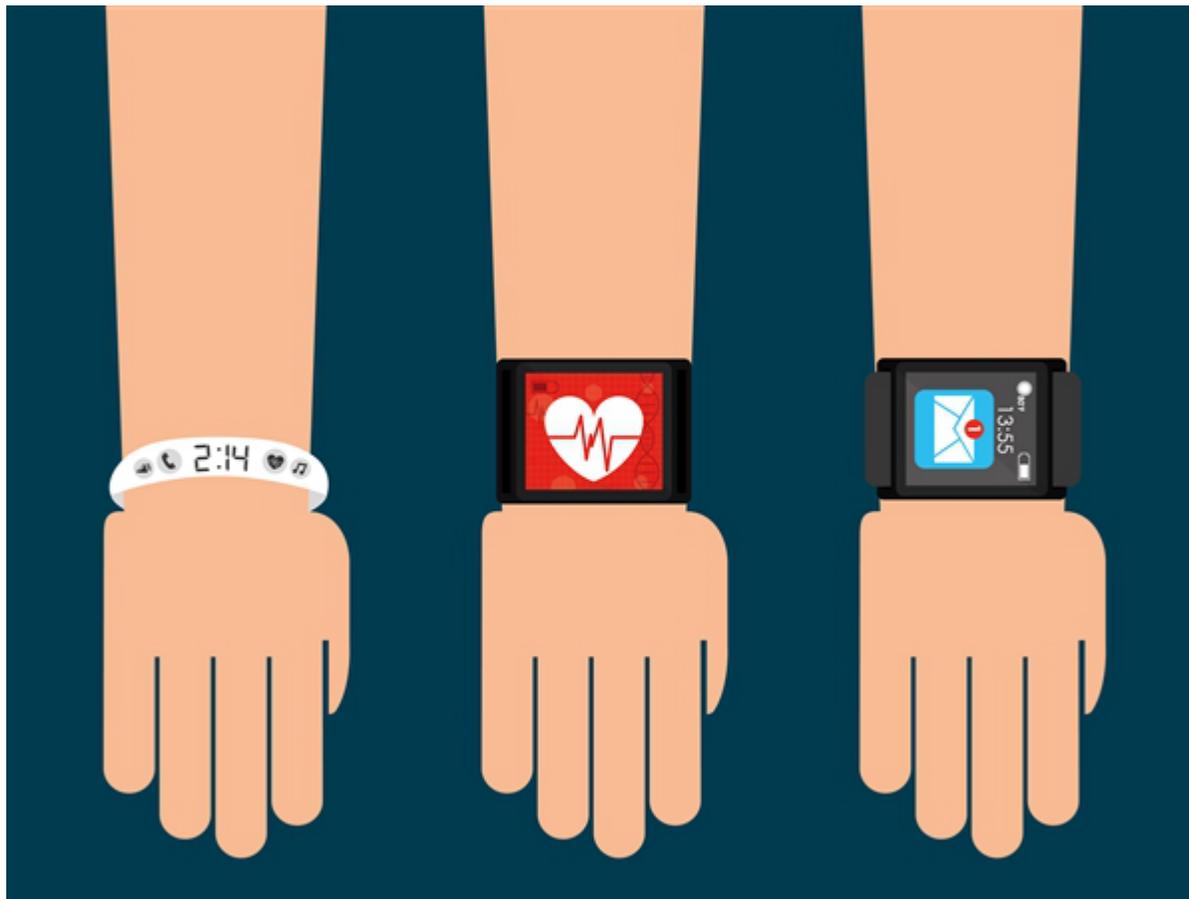


Samantha Watkins



In just five years, wearables have gone from being essentially non-existent to an integral part of daily life. As the popularity of these devices continues to grow, their feature set also becomes more diverse. What started out as a simple way to track your steps has turned into a wrist-worn data center listening to every heart beat and analyzing every e-mail. These complex features mean additional design challenges for engineers.

When it comes to designing a wearable, you must consider many requirements including size, cost, and performance. In this blog, I will focus on two issues that an integrated load switch can address:

- Minimizing leakage current from subsystems and other components.
- Protecting systems from inrush current and other current spikes.

How to Minimize Leakage Current from Subsystems and Other Components

One of the biggest challenges for wearables is their small form factor. This not only makes layout difficult, but presents an even bigger issue as the size of the battery is constrained. In an effort to extend battery life, designers must consider every source of leakage in the system. The highest leakage often comes from subsystems such as the *Bluetooth*® circuitry or the heart rate monitoring signal chain, which are only on during certain modes of operation. Even when disabled, circuitry such as DC/DCs and linear regulators (LDOs)

can exhibit high leakage. By inserting a small-form-factor load switch such as the [TPS22915](#) between the subsystem and the power source, you can significantly reduce the leakage current ([Figure 1](#)).

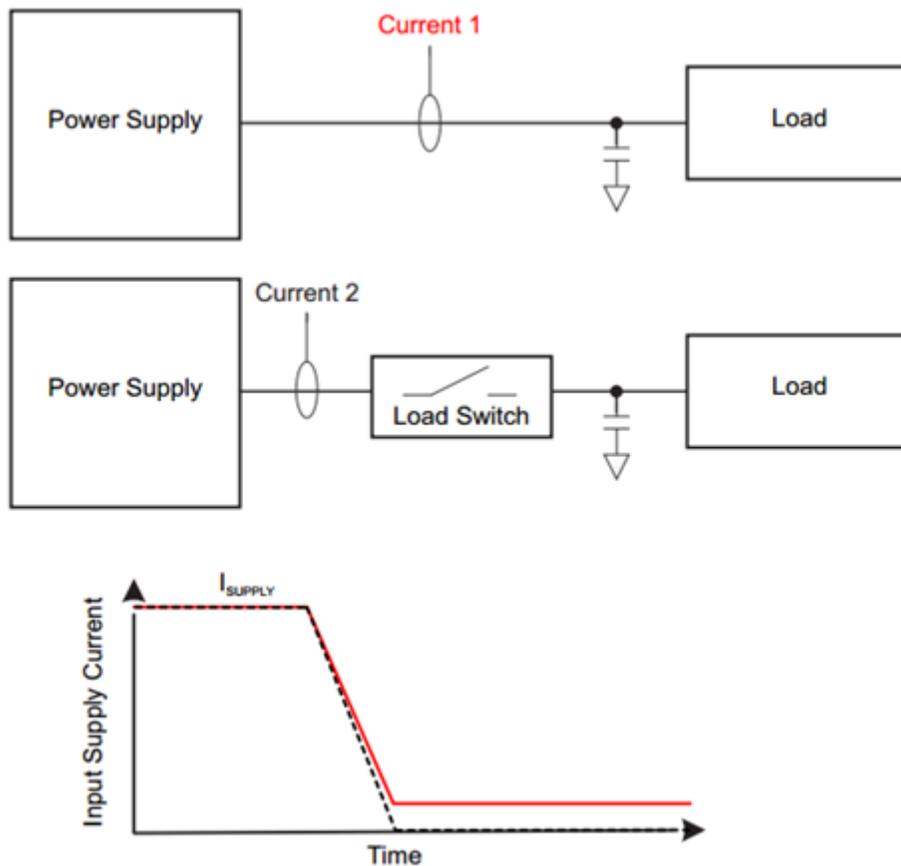


Figure 1. Comparison of Leakage Current with and without a Load Switch

Additionally, the [TPS22915](#) incorporates quick output discharge (QOD), which ties the output to ground when the switch is turned off. This guarantees that the downstream subsystem or additional circuitry is completely off resulting in the lowest possible leakage.

How to Protect Systems from Inrush Current and Other Current Spikes

With customers demanding new features and designers being forced to reduce cost and save board space, it is very easy to put a low priority on protection. However, by using an integrated load switch in your design, you can add protection against inrush current and other current spike events.

Inrush current control is a common problem for wearables. When turning on a subsystem, it is possible for the input rail to sag from a quickly charging load capacitance ([Figure 2](#)). All [TI load switches](#) address this issue by controlling the rise time of the load switch output voltage and limiting the inrush current to ensure that the subsystem sees a controlled current on the input rail ([Figure 3](#)).

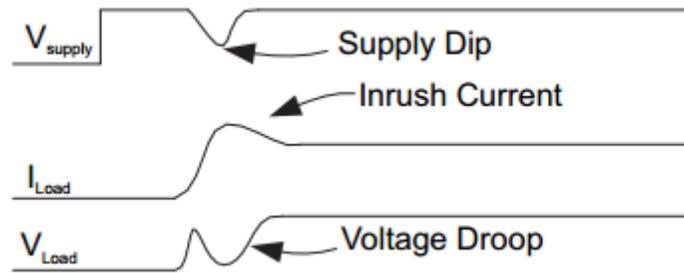


Figure 2. Inrush Current from Turning on a Subsystem

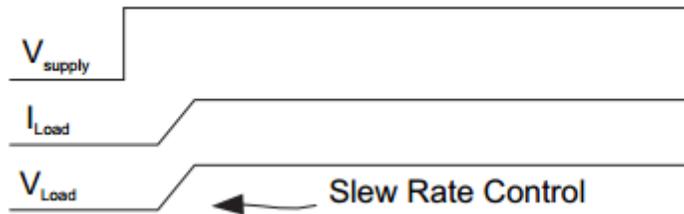


Figure 3. Slew Rate Control Provided by a Load Switch

Additionally, TI load switches such as the [TPS22946](#) incorporate protection features such as current limiting. Current limiting ensures that a constant current is delivered to the system despite any excessive current that would otherwise be pulled by a subsystem or some external circuitry. This is especially critical for devices using USB as a source to recharge the battery.

Adding an integrated load switch to your design can extend your device's battery life by reducing leakage current and can improve reliability by protecting against current spikes. With a TI load switch, you get these benefits with minimum impact to board space or cost. Start integrating a load switch to your design today and check out our additional resources below!

Additional Resources:

- Learn more about [TI's load switch portfolio](#)
- Read the following TI application notes:
 - [“Load Switches: What Are They, Why Do You Need Them and How Do You Choose The Right One?”](#)
 - [“Managing Inrush Current”](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated